
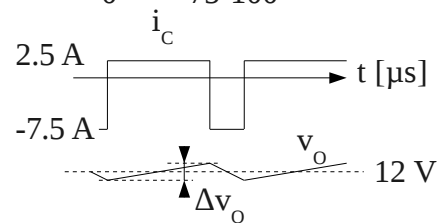
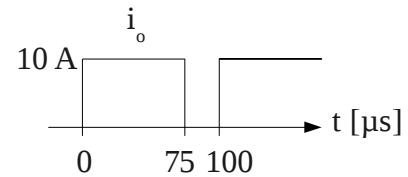


1. a) DPF = cos phi, and cos never becomes larger than 1.
- b) Fill factor = Pmax/(Uopen*Ishort), that is, the maximum output power over the product of no-load voltage times the short-circuit current.
- c) No it is not necessary. The three currents cancels out, and the current through a common ground wire would be zero.
- d) No, the capacitor will only produce reactive power, with zero active power.
- e) The transistor can have a lower forward voltage drop than the diode

2. a) $I_{0avg} = 10 \cdot 75 / 100 = 7.5 \text{ A}$

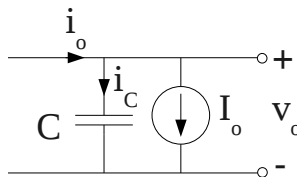
- b) $i_c = i_o - I_o$, alternating
between 2.5 and -7.5 A.



$$i_c(t) = C \frac{dv_c}{dt} = C \frac{dv_o}{dt}$$

$$\Delta v_o = \frac{1}{C} \int_0^{75 \cdot 10^{-6}} 2.5 dt = \frac{75 \cdot 10^{-6} \cdot 2.5}{7500 \cdot 10^{-6}} = 25 \text{ mV}$$

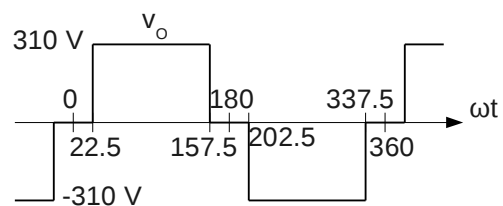3. a) Select $\omega t = 0$ in middle of cancellation time.



$$V_{O,RMS} = \sqrt{\frac{1}{T} \int_0^T v_o^2(t) dt}$$

$$= \sqrt{\frac{1}{360} \int_0^{360} v_o^2(\omega t) d(\omega t)}$$

b)

$$= 310 \sqrt{\frac{1}{360} \left(\int_{22.5}^{157.5} d(\omega t) + \int_{202.5}^{337.5} d(\omega t) \right)}$$

$$= 310 \sqrt{\frac{1}{360} (157.5 - 22.5 + 337.5 - 202.5)}$$

$$= 310 \sqrt{\frac{270}{360}} = 310 \frac{\sqrt{3}}{2} = 268 \text{ V}$$


- c) $f(t)$ with the chosen zero position is half-wave and odd, that is an odd quarter-wave ($f(-t) = -f(t)$, $f(t) = -f(t+1/2T)$). Therefore $a_1 = 0$.

$$b_1 = \frac{4}{\pi} \int_0^{\frac{\pi}{2}} f(t) \sin(\omega t) d(\omega t) = \frac{4}{\pi} \int_0^{\frac{\pi}{2}} 310 \sin(\omega t) d(\omega t) = \frac{4 \cdot 310}{\pi} [-\cos(\omega t)]_{\frac{\pi}{8}}^{\frac{\pi}{2}} =$$

$$= \frac{4 \cdot 310}{\pi} (-\cos(\pi/2) - (-\cos(\pi/8))) = \frac{4 \cdot 310 \cos(\pi/8)}{\pi} = 365 \text{ V}$$

That is, the peak value of the fundamental of the output voltage is 365V.

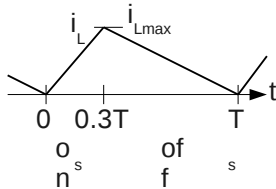4. a) Buck converter voltage output for continuous current gives $V_o = D V_d = 0.3 \cdot 24 = 7.2V$
 b) Boundary between discontinuous and continuous current $\Rightarrow i_L$ goes to zero at $t = T_s = 1/10e3 = 0.1$ ms. Switch on between 0 and $0.3T_s$, off between $0.3T_s$ and T_s .




$$T_s = \frac{1}{f_s} = \frac{1}{10 \cdot 10^3} = 0.1 \text{ ms}$$

$$i_{Lmax} = 0.7 T_s \frac{V_o}{L} = \frac{0.7 V_o}{f_s L} = \frac{0.7 \cdot 7.2}{10 \cdot 10^3 \cdot 0.12 \cdot 10^{-3}} = 4.2 \text{ A}$$

c) $I_o = \frac{i_{Lmax}}{2} = \frac{4.2}{2} = 2.1 \text{ A}$

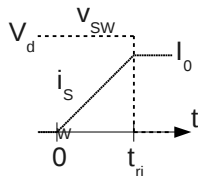
5. a) At turn on without the snubber results in the full voltage V_d being applied over the switch (diode in parallel with I_o conducting) while the current increase from zero to I_o .



$$P_{SWon} = f_{SWon} \cdot V_d \cdot \frac{I_o}{2} \cdot t_{ri} = 10^3 \cdot 300 \cdot \frac{20}{2} \cdot 5 \cdot 10^{-6} = 15 \text{ W}$$

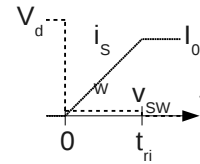- b) 5% of V_d across the switch at turn on leaves 95% of V_d across L. The current increase should still be same as defined by the switch.

$$L = \frac{v_L}{di_L/dt} = \frac{0.95 V_d}{\Delta i_L / t_{ri}} = \frac{0.95 \cdot 300}{20/5 \cdot 10^{-6}} = 71.3 \mu H$$



- c) At turn-off will the diode in parallel with I_o start to conduct when the i_{sw} starts to decrease.

The snubber diode starts to conduct, and the current now flows through R instead of the switch. Assuming the current fall time can be neglected compared to the LR time constant τ_{LR} at time t_{off} :

$$\begin{aligned} v_{sw} &= V_d + R I_o \\ v_{sw} &< 2V_d \\ V_d + R I_o &< 2V_d \\ R I_o &< 2V_d - V_d = V_d \\ R &< \frac{V_d}{I_o} = \frac{300}{20} = 15 \Omega \\ R &< 15 \Omega \end{aligned}$$

