



TSTE19

Power Electronics


Examination (TEN1)

Time:	Saturday 17 December 2011 at 14.00 - 18.00
Place:	TER3
Responsible teacher:	Kent Palmkvist, ISY, 28 13 47, 0705 23 31 59 (kentp@isy.liu.se) Will visit exam location at 15 and 17.
Number of tasks:	5
Number of pages:	4
Allowed aids:	Calculator
Notes:	A pass on the exam requires approximately 30 points. Remember to indicate the steps taken when solving problems.
Exam presentation:	Friday 13 January 2011 13.00-14.00 (Kent Palmkvist's office)

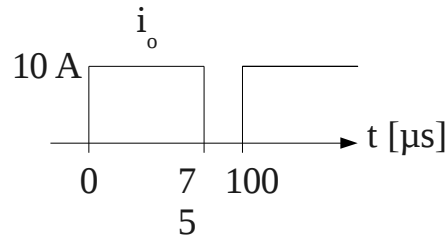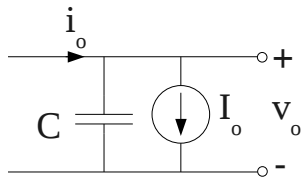1. a) Can the displacement power factor (DPF) be larger than 1? Motivate your answer. (2)
- b) How is the fill factor for a solar cell defined? (2)
- c) Is it necessary to have a common ground wire in a 3-phase system with a linear resistive load? Motivate your answer. (2)
- d) Will an ideal capacitor connected to a 220V 50Hz line outlet voltage get warm due to the current flowing through it? Motivate your answer. (2)
- e) Why is it sometimes better to use a transistor instead of a diode in a full bridge rectifier, even if the behavior (on and off times) is exactly the same. (2)




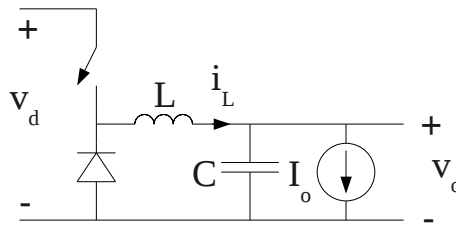2. The output current from a power supply is shown above. The average output voltage V_o is 12V. The capacitor size is 7500 μF . The switching frequency is 10 kHz.
 - a) Calculate the average output current I_o . (4)
 - b) Draw the waveform of the output voltage $v_o(t)$. Indicate timing and voltage values. (6)
3. A full bridge DC->AC inverter is controlled using voltage cancellation with a waveform overlap angle of $\alpha = 45^\circ$. The output fundamental frequency is 50 Hz, and the input voltage is 310V.
 - a) Draw the output voltage waveform of the converter. Indicate voltage levels and phase angles. (6)
 - b) Calculate the output voltage rms value? (6)
 - c) Calculate the amplitude (peak value) of the output voltage fundamental $v_{o1}(t)$. (6)



4. The step-down (buck) converter above is operating at the boundary between discontinuous and continuous current conduction mode. Switching ratio $D = 0.3$. The input voltage is 24V. The inductance L is 0.12 mH. The switching frequency is 10 kHz. The capacitance C is very large.

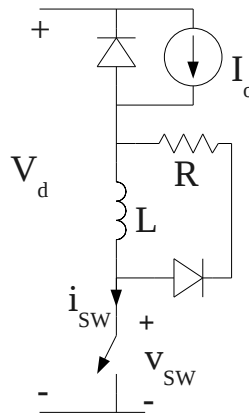- a) What is the output voltage? (6)
- b) Draw the waveform for i_L and indicate when the switch is on and off. (6)
- c) What is the average output current i_L ? (4)



5. The snubber circuit above is designed to reduce the di/dt over the switch at turn-on. The switch have a t_{ri} of 5 μs . The input voltage V_d is 300 V, and the output current I_o is 20 A. The turn-on snubber shall be designed so that the switch voltage at turn on is 5% of the V_d voltage, and that the switch current I_{sw} is equal to I_o after t_{ri} . The switching frequency is 1 kHz. Assume the snubber time constant is much larger than the transistor turn-off time.


- a) How large would the turn-on power dissipation be in the switch if there was no turn-on snubber (that is, $L = 0$)? (4)
- b) Calculate the value of L . (6)
- c) Assume the turn-off switch voltage v_{sw} is not allowed to be larger than twice the value of V_d . What is the largest allowed value of R ? (6)

Formula collection TSTE19 Power Electronics


Fourier series coefficients using symmetry, Table 3.1

Even	$f(-t)=f(t)$	$b_n=0$	$a_n=\frac{2}{\pi} \int_0^{\pi} f(t) \cos(h\omega t) d(\omega t)$
Odd	$f(-t)=-f(t)$	$a_n=0$	$b_n=\frac{2}{\pi} \int_0^{\pi} f(t) \sin(h\omega t) d(\omega t)$
Half-wave	$f(t)=-f(t+\frac{1}{2}T)$	$a_n=b_n=0$ for even h	$a_n=\frac{2}{\pi} \int_0^{\pi} f(t) \cos(h\omega t) d(\omega t)$ for odd h $b_n=\frac{2}{\pi} \int_0^{\pi} f(t) \sin(h\omega t) d(\omega t)$ for odd h
Even quarter-wave	Even and half-wave	$b_n=0$ for all h	$a_n=\frac{4}{\pi} \int_0^{\frac{\pi}{2}} f(t) \cos(h\omega t) d(\omega t)$ for odd h $a_n=0$ for even h
Odd quarter-wave	Odd and half-wave	$a_n=0$ for all h	$b_n=\frac{4}{\pi} \int_0^{\frac{\pi}{2}} f(t) \sin(h\omega t) d(\omega t)$ for odd h $b_n=0$ for even h

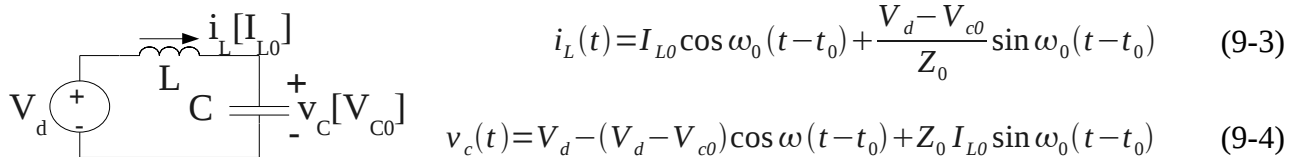Undamped series resonant circuit, equations 9-3, 9-4



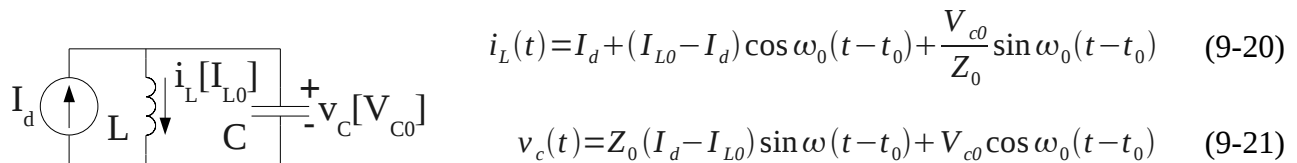Undamped parallel resonant circuit, equations 9-20, 9-21



Integration rules

$$\int_a^b f(ax) dx = \int_A^B f(g(t)) g'(t) dt \quad \text{if } a=g(A) \text{ and } b=g(B)$$

$$\int_a^b \sin(x) dx = [-\cos(x)]_a^b$$

$$\int_a^b \cos(x) dx = [\sin(x)]_a^b$$