


TSTE19

Power Electronics


Examination (TEN1)

Time:	Wednesday 22 August 2012 at 8.00 - 12.00
Place:	TER1
Responsible teacher:	Kent Palmkvist, ISY, 28 13 47, 0705 23 31 59 (kentp@isy.liu.se) Will visit exam location at 9 and 11.
Number of tasks:	6
Number of pages:	4
Allowed aids:	Calculator
Notes:	A pass on the exam requires approximately 30 points. Remember to indicate the steps taken when solving problems.
Exam presentation:	Tuesday 4 September 2012 12.30-13.30 (Kent Palmkvist's office)

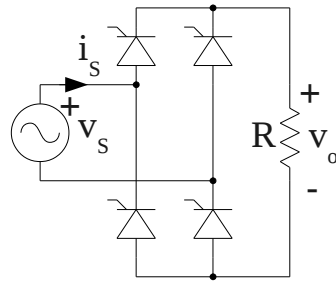
1. a) Is the speed of a synchronous motor dependent on the voltage or frequency of the driving voltage? (2)
- b) Why is a third winding added to the transformer in a practical forward converter? (2)
- c) How does the voltage and current of a diode behave during reverse recovery? (2)
- d) What does the acronym ZVS-CV stand for? (2)
- e) Is the power factor dependent on the voltage amplitude? (2)



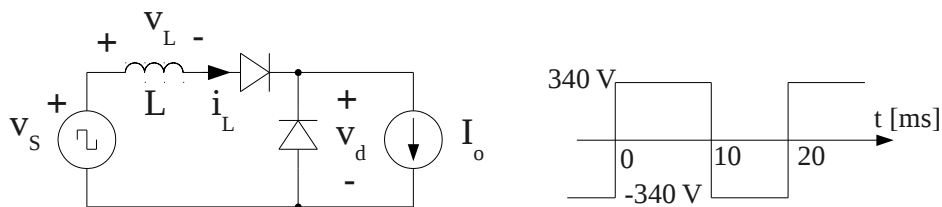
2. The thyristors in the circuit above have a firing angle of 45° . The voltage source v_s is 220V rms. The resistance is 500Ω .
 - a) Draw the voltage v_s and current i_s of the voltage source. Indicate angles, peak voltages and peak currents. (6)
 - b) Calculate the average of the output voltage v_o . (6)



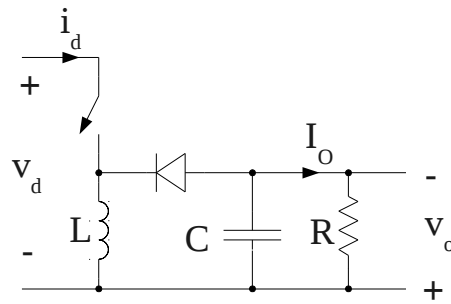3. In the circuit above is v_s a square wave as shown to the right. $L = 136 \text{ mH}$, $I_o = 5 \text{ A}$.
 - a) Draw the inductor voltage v_L and current i_L . (6)
 - b) How long time does it take for the current commutation to complete? (6)
 - c) What is the average output voltage v_d ? (4)
4. A single-phase full-bridge AC-DC converter have a maximum output current rating of 100 A and maximum input voltage rating of 200 V. The diodes have a forward voltage of 0.7 V.
 - a) How much power is dissipated by the diodes? (4)
 - b) What is the minimum output voltage if a 90% efficiency is to be reached when the converter supplies maximum output current? (4)



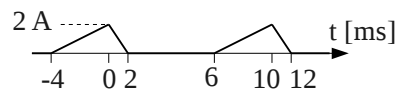5. A 3V negative output voltage (V_o) is generated using the buck-boost converter below. The input voltage V_d is 12V. The converter is running in continuous conduction mode. Assume C is large. $L = 38.4 \mu\text{H}$, $T_s = 20 \mu\text{s}$.
- Calculate the switch ratio D . (6)
 - What is the minimum output current in which the converter still is operating in continuous conduction mode? (6)
 - What is the average of the input current i_d if the output current I_o is 2 A? (4)



6. The simplified view of the current from a full-bridge rectifier is shown above.
- What is the amplitude of the fundamental, 2nd and 3rd harmonics of the current? (8)

Formula collection TSTE19 Power Electronics

Fourier series coefficients using symmetry, Table 3.1

Even	$f(-t) = f(t)$	$b_h = 0$	$a_h = \frac{2}{\pi} \int_0^{\pi} f(t) \cos(h\omega t) d(\omega t)$
Odd	$f(-t) = -f(t)$	$a_h = 0$	$b_h = \frac{2}{\pi} \int_0^{\pi} f(t) \sin(h\omega t) d(\omega t)$
Half-wave	$f(t) = -f(t + \frac{1}{2}T)$	$a_h = b_h = 0$ for even h	$a_h = \frac{2}{\pi} \int_0^{\pi} f(t) \cos(h\omega t) d(\omega t)$ for odd h $b_h = \frac{2}{\pi} \int_0^{\pi} f(t) \sin(h\omega t) d(\omega t)$ for odd h
Even quarter-wave	Even and half-wave	$b_h = 0$ for all h	$a_h = \frac{4}{\pi} \int_0^{\frac{\pi}{2}} f(t) \cos(h\omega t) d(\omega t)$ for odd h $a_h = 0$ for even h
Odd quarter-wave	Odd and half-wave	$a_h = 0$ for all h	$b_h = \frac{4}{\pi} \int_0^{\frac{\pi}{2}} f(t) \sin(h\omega t) d(\omega t)$ for odd h $b_h = 0$ for even h

Undamped series resonant circuit, equations 9-3, 9-4

$$i_L(t) = I_{L0} \cos \omega_0(t-t_0) + \frac{V_d - V_{C0}}{Z_0} \sin \omega_0(t-t_0) \quad (9-3)$$

$$v_C(t) = V_d - (V_d - V_{C0}) \cos \omega(t-t_0) + Z_0 I_{L0} \sin \omega_0(t-t_0) \quad (9-4)$$

Undamped parallel resonant circuit, equations 9-20, 9-21

$$i_L(t) = I_d + (I_{L0} - I_d) \cos \omega_0(t-t_0) + \frac{V_{C0}}{Z_0} \sin \omega_0(t-t_0) \quad (9-20)$$

$$v_C(t) = Z_0 (I_d - I_{L0}) \sin \omega(t-t_0) + V_{C0} \cos \omega_0(t-t_0) \quad (9-21)$$

Integration rules

$$\int_a^b f(x) dx = \int_A^B f(g(t)) g'(t) dt \quad \text{if } a = g(A), \quad b = g(B), \quad \text{and } g \text{ is monotone in } [A, B]$$

$$\int_a^b \sin(x) dx = [-\cos(x)]_a^b$$

$$\int_a^b \cos(x) dx = [\sin(x)]_a^b$$