

TSTE19

Power Electronics


Examination (TEN1)

Time:	Monday 25 March 2013 at 8.00 - 12.00
Place:	U3
Responsible teacher:	Kent Palmkvist, ISY, 28 13 47, 0705 23 31 59 (kentp@isy.liu.se) Will visit exam location at 9 and 11.
Number of tasks:	5
Number of pages:	4 (including this one)
Allowed aids:	Calculator
Notes:	A pass on the exam requires approximately 30 points. Remember to indicate the steps taken when solving problems. Answers may be given in Swedish and/or English.
Exam presentation:	Monday 8 April 2013 12.30-13.30 (Kent Palmkvist's office)

1. a) What will be the output waveform shape of a PWM based DC-AC inverter if the controlling sinusoidal waveform is driving the inverter with maximum overmodulation? (2)
- b) Is the speed of the induction motor dependent on the amplitude or frequency of the input voltage? (2)
- c) Does a power bipolar transistor have a larger or smaller current amplification factor B compared to a small signal bipolar transistor? (2)
- d) Can the switch mode DC-AC inverter feed energy back into the voltage source? (2)
- e) What does the acronym IGBT mean? (2)


2. The buck converter shown below is generating an output voltage $V_o = 3$ V. The inductor $L = 18$ μ H, switching frequency $f_s = 50$ kHz, C is large, switching ratio $D = 0.1$, and the input voltage $V_d = 12$ V.

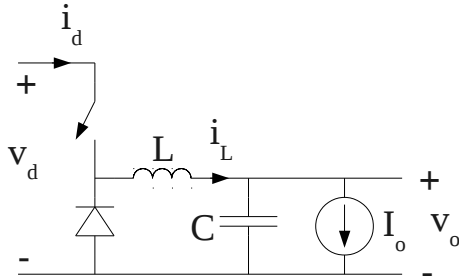
- a) What is the output current I_o ? (6)
- b) What is the average input current I_d ? (4)
- c) At what switching ratio D will the converter switch from discontinuous mode to continuous mode? (4)




3. Assume the inductor current i_L shown below is the inductor current of the buck converter above (at a different D , V_o and I_o setting compared to task 2). Assume the maximum ripple voltage is defined as 0.1 V, $T_s = 20$ μ s, and that $i_{Lmax} = 6$ A.

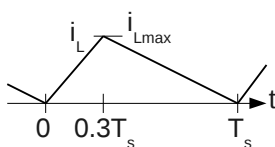- a) Draw the output voltage ripple on V_o . (4)
- b) What minimum size of C to keep the ripple within limits? (6)
- c) What will be the additional ripple voltage contributed by capacitors ESR if it is 0.1 Ω ? (4)



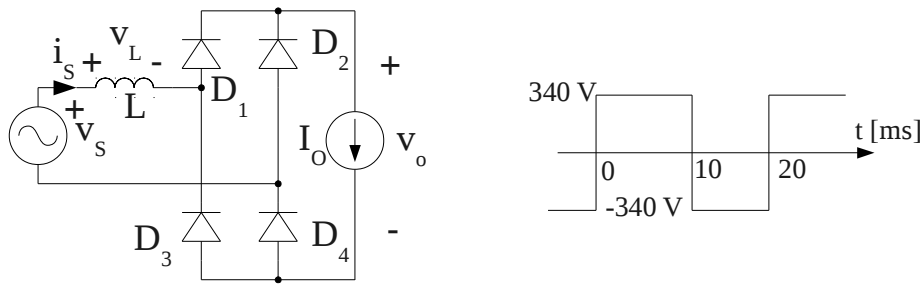

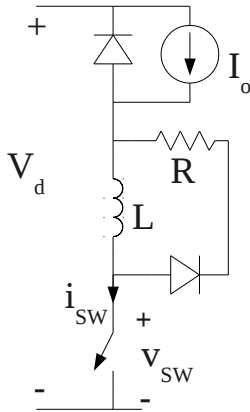4. The full-bridge rectifier shown above to the left have the source voltage v_s shown above to the right. The inductor $L = 34 \text{ mH}$ and the output current $I_o = 10 \text{ A}$.
- Draw the current i_s and voltages v_L and v_o waveforms. Indicate also when each diode is conducting or not conducting. (6)
 - Calculate the average output voltage V_o . (6)
 - What is the source displacement power factor (DPF)? (4)




5. The snubber circuit above is designed to reduce the di/dt over the switch at turn-on. The switch have a t_{ri} of $4 \mu\text{s}$. The input voltage V_d is 200 V , and the output current I_o is 10 A . The turn-on snubber shall be designed so that the switch voltage at turn on is 5% of the V_d voltage, and that the switch current I_{sw} is equal to I_o after t_{ri} . The switching frequency is 1 kHz . Assume the snubber time constant is much larger than the transistor turn-off time.
- Draw the waveform of the switch current i_{sw} and voltage v_{sw} when turning on the switch turns on and when the switch turns off. (4)
 - Calculate the value of L . (6)
 - Assume the turn-off switch voltage v_{sw} is not allowed to be larger than twice the value of V_d . What is the largest allowed value of R ? (6)

Formula collection TSTE19 Power Electronics

Fourier series coefficients using symmetry, Table 3.1

Even	$f(-t) = f(t)$	$b_h = 0$	$a_h = \frac{2}{\pi} \int_0^{\pi} f(t) \cos(h\omega t) d(\omega t)$
Odd	$f(-t) = -f(t)$	$a_h = 0$	$b_h = \frac{2}{\pi} \int_0^{\pi} f(t) \sin(h\omega t) d(\omega t)$
Half-wave	$f(t) = -f(t + \frac{1}{2}T)$	$a_h = b_h = 0$ for even h	
			$a_h = \frac{2}{\pi} \int_0^{\pi} f(t) \cos(h\omega t) d(\omega t)$ for odd h
			$b_h = \frac{2}{\pi} \int_0^{\pi} f(t) \sin(h\omega t) d(\omega t)$ for odd h
Even quarter-wave	Even and half-wave	$b_h = 0$ for all h	
			$a_h = \frac{4}{\pi} \int_0^{\frac{\pi}{2}} f(t) \cos(h\omega t) d(\omega t)$ for odd h
			$a_h = 0$ for even h
Odd quarter-wave	Odd and half-wave	$a_h = 0$ for all h	
			$b_h = \frac{4}{\pi} \int_0^{\frac{\pi}{2}} f(t) \sin(h\omega t) d(\omega t)$ for odd h
			$b_h = 0$ for even h

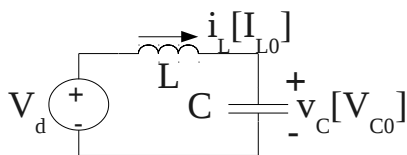
Undamped series resonant circuit, equations 9-3, 9-4



$$i_L(t) = I_{L0} \cos \omega_0(t - t_0) + \frac{V_d - V_{C0}}{Z_0} \sin \omega_0(t - t_0) \quad (9-3)$$

$$v_C(t) = V_d - (V_d - V_{C0}) \cos \omega(t - t_0) + Z_0 I_{L0} \sin \omega_0(t - t_0) \quad (9-4)$$

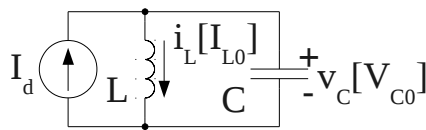Undamped parallel resonant circuit, equations 9-20, 9-21



$$i_L(t) = I_d + (I_{L0} - I_d) \cos \omega_0(t - t_0) + \frac{V_{C0}}{Z_0} \sin \omega_0(t - t_0) \quad (9-20)$$

$$v_C(t) = Z_0 (I_d - I_{L0}) \sin \omega(t - t_0) + V_{C0} \cos \omega_0(t - t_0) \quad (9-21)$$

Integration rules

$$\int_a^b f(x) dx = \int_A^B f(g(t)) g'(t) dt \quad \text{if } a = g(A), \quad b = g(B), \quad \text{and } g \text{ is monotone in } [A, B]$$

$$\int_a^b \sin(x) dx = [-\cos(x)]_a^b$$

$$\int_a^b \cos(x) dx = [\sin(x)]_a^b$$