

TSTE19
Power Electronics
Examination (TEN1)

Time: Wednesday 13th January 2016 at 8:00 – 12:00

Place: U4/U6

Responsible teacher: Tomas Jonsson

Will visit the exam location at 8:45 and 10.

Number of tasks: 6

Number of pages: 8

Allowed aids: Calculator

Total points: 70

Notes: A pass on the exam requires approx. 30 points.

Describe your calculations clearly and detailed, explaining your methods, assumptions and equations used.

Question 1

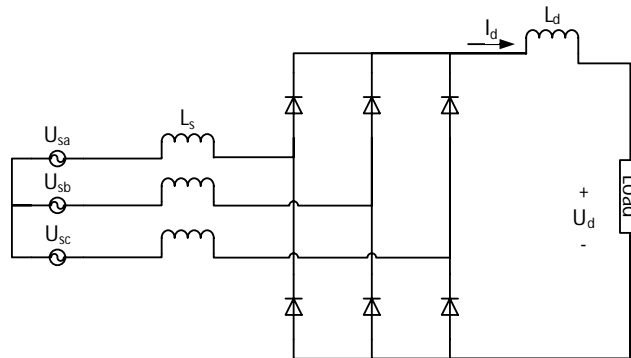


Figure 1

- A three phase diode rectifier according to Figure 1 has inductance, L_s , on the ac-side and L_d on the dc-side. Which inductance shall be large in order to obtain continuous current through the dc-load. (2)
- List the three most important parameters that defines the commutation of current between two diodes in a rectifier as of Figure 1. Give a short motivation why. (3)
- In a DC/DC converter, inductance is commonly used for energy transfer between low and high-voltage sides. If the average voltage across the inductance is greater than zero during a time interval, what can you say about the shape of the inductor current during this interval? (2)

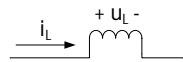


Figure 2

- What device parameters are required to determine the conduction losses of a MOSFET if the drain current is known? (2)
- List three types of semiconductors with turn-off capability. (3)

Question 2

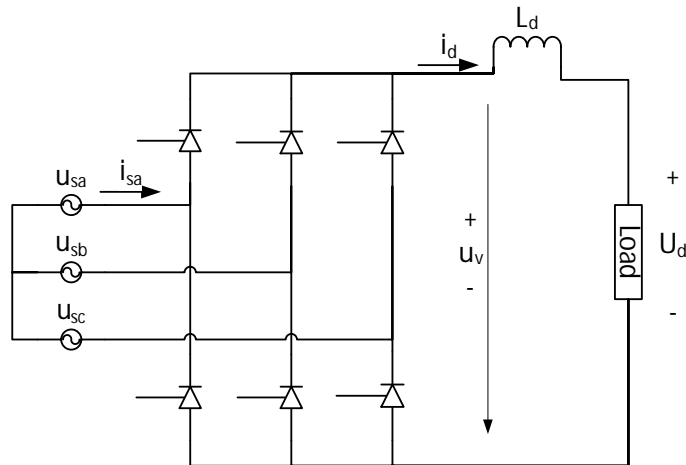


Figure 3

A three phase thyristor rectifier as shown by Figure 3 is connected to a three phase voltage source with the phase-phase voltage $U_s=410$ Vrms. The commutation inductance can be neglected.

- Draw the waveform of the converter dc-side voltage u_v (before the inductor L_d) for a firing angle $\alpha=30$ deg. (2)
- Draw the waveform of the source current, i_{sa} , in one phase. (2)
- Determine the displacement power factor. (2)
- Calculate the dc-load voltage, U_d , and dc-power considering a resistive load of 25 ohm. (5)
- Calculate the fundamental frequency source rms current (i_{sa}). Assume zero losses of the thyristor converter. (3)

Question 3

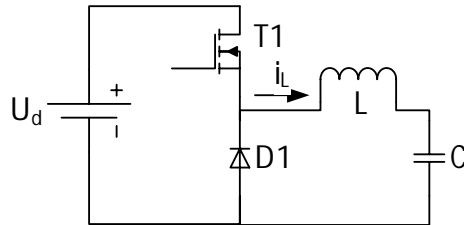


Figure 4

In the buck converter in Figure 4, the current i_L is continuous with an average of 5 A, and with a negligible ripple magnitude. The MOSFET T1 is operated with a switching frequency $f_{sw} = 120$ kHz and a duty cycle in order to keep the capacitor voltage at 10 V for an input voltage $U_d = 24$ V.

- Determine the duty cycle of the MOSFET T1. (2)
- Calculate the conduction losses in the MOSFET T1 if the on-state resistance $R_{ds(on)} = 0.05$ ohm. (3)
- Calculate the turn-on losses in the MOSFET T1 if the rise time of the drain current is 40 ns. Current rises linearly and voltage is constant. (3)
- Calculate the turn-off losses in the MOSFET T1 if the fall time of the drain current is 60 ns. Current falls linearly and voltage is constant. (3)
- Determine the maximum allowed thermal resistance of the heatsink (R_{thHA}) for the MOSFET T1 in order to keep the heatsink temperature, $T_H \leq 60$ °C and the junction temperature, $T_J \leq 100$ °C. The MOSFET has a thermal resistance $R_{thJH} = 45.0$ °C/W. The ambient temperature, $T_A = 25$ °C. Note: T_H or T_J will equal the given limits, the other shall be lower. (5)

Question 4

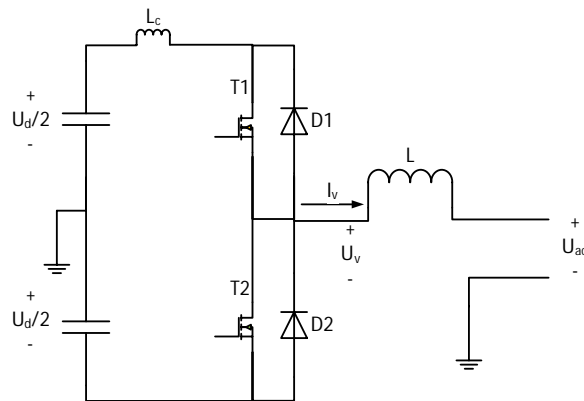


Figure 5

A half-bridge voltage source converter is connected between a dc-source and an ac-load as shown by Figure 5. The control of the switched output voltage is done through pulse width modulation (PWM) with a switching frequency $f_{sw}=950$ Hz, in order to obtain a 50 Hz voltage component with a defined magnitude.

- What is the minimum required dc-side voltage, U_d , required if the magnitude of the 50 Hz voltage component shall be 24V rms when the amplitude modulation ratio, $ma=0.9$. (5)
- Calculate the current ripple in the output current, I_v , during the time interval shown in Figure 6. The time is defined based on the switching frequency cycle, $T_{sw}=1/f_{sw}$. During this time interval $U_{ac} = 0.4 \cdot U_d$, for the value of U_d calculated in a). The inductance $L=3$ mH. The initial current $I_v(t=0)=0$. (5)

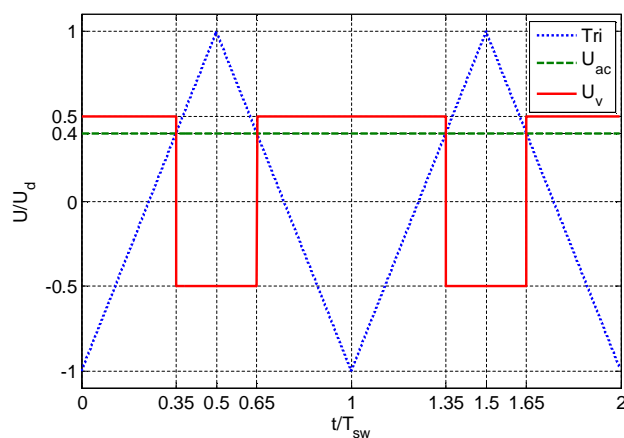


Figure 6

Question 5

The half-bridge converter in Figure 5 has a parasitic inductance, L_c , between the dc-source and the half-bridge. Figure 7 the switching waveform of the current through the MOSFET switch T1. The current $I_V=12$ A flows through L out of the converter.

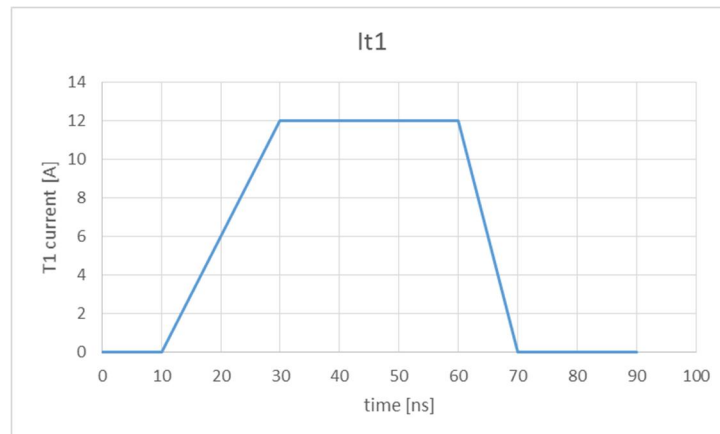


Figure 7

- a) Draw the waveform of the voltage across MOSFET T1, related to the current given in Figure 7 and considering the inductance $L_c=40$ nH. The dc-voltage $U_d=110$ V. (4)
- b) What is the peak voltage across the MOSFET? (4)

Question 6

A parallel capacitive snubber shall be designed for limitation of the peak voltage across the MOSFET switches of a half-bridge converter. The snubber, as shown by Figure 8, consists of a diode D_s , which will charge the snubber capacitor C_s during over-voltage but prevent discharge when the MOSFET turns on. The dc-side voltage $U_d=110$ V. The design shall be based on the switching conditions related to a load current $I_v = 12$ A.

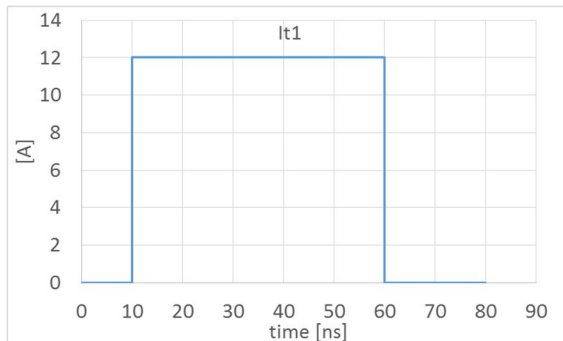
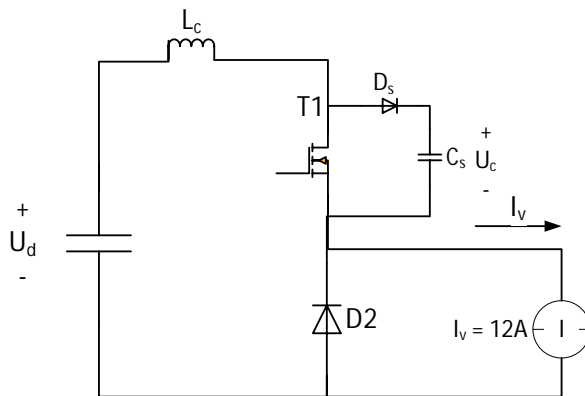


Figure 8

- Draw the waveforms of the current and voltage related to T1, D2 and C_s . Assume the T1 current turn-off to be instantaneous as shown above. The snubber capacitor is initially charged to $U_c = U_d$ at the instant of T1 turn-off. (4)
- Calculate the required snubber capacitance in order to limit the over voltage to 20% when T1 is turned off. (6)

Formula collection TSTE19 Power Electronics

Fourier series coefficients using symmetry,

Even	$f(-t) = f(t)$	$b_h = 0$	$a_h = \frac{2}{\pi} \int_0^{\pi} f(t) \cos(h\omega t) d(\omega t)$
Odd	$f(-t) = -f(t)$	$a_h = 0$	$b_h = \frac{2}{\pi} \int_0^{\pi} f(t) \sin(h\omega t) d(\omega t)$
Half-wave	$f(t) = -f(t + \frac{1}{2}T)$	$a_h = b_h = 0$ for even h	
		$a_h = \frac{2}{\pi} \int_0^{\pi} f(t) \cos(h\omega t) d(\omega t)$ for odd h	
		$b_h = \frac{2}{\pi} \int_0^{\pi} f(t) \sin(h\omega t) d(\omega t)$ for odd h	
Even quart-wave	Even and half-wave	$b_h = 0$ for all h	
		$a_h = \frac{4}{\pi} \int_0^{\frac{\pi}{2}} f(t) \cos(h\omega t) d(\omega t)$ for odd h , $a_h = 0$ for even h	
Odd quarter-wave	Odd and half-wave	$a_h = 0$ for all h	
		$b_h = \frac{4}{\pi} \int_0^{\frac{\pi}{2}} f(t) \sin(h\omega t) d(\omega t)$ for odd h , $b_h = 0$ for even h	

Undamped resonant circuits

Even	$f(-t) = f(t)$	$b_h = 0$	$a_h = \frac{2}{\pi} \int_0^{\pi} f(t) \cos(h\omega t) d(\omega t)$
Odd	$f(-t) = -f(t)$	$a_h = 0$	$b_h = \frac{2}{\pi} \int_0^{\pi} f(t) \sin(h\omega t) d(\omega t)$
Half-wave	$f(t) = -f(t + \frac{1}{2}T)$	$a_h = b_h = 0$ for even h	
		$a_h = \frac{2}{\pi} \int_0^{\pi} f(t) \cos(h\omega t) d(\omega t)$ for odd h	
		$b_h = \frac{2}{\pi} \int_0^{\pi} f(t) \sin(h\omega t) d(\omega t)$ for odd h	
Even quart-wave	Even and half-wave	$b_h = 0$ for all h	
		$a_h = \frac{4}{\pi} \int_0^{\frac{\pi}{2}} f(t) \cos(h\omega t) d(\omega t)$ for odd h , $a_h = 0$ for even h	
Odd quarter-wave	Odd and half-wave	$a_h = 0$ for all h	
		$b_h = \frac{4}{\pi} \int_0^{\frac{\pi}{2}} f(t) \sin(h\omega t) d(\omega t)$ for odd h , $b_h = 0$ for even h	

Integration rules

$$\int_a^b f(x) dx = \int_A^B f(g(t)) g'(t) dt \text{ if } a = g(A), b = g(B) \text{ and } g \text{ is monotone in } [A, B]$$

$$\int_a^b \sin(x) dx = [-\cos(x)]_a^b$$

$$\int_a^b \cos(x) dx = [\sin(x)]_a^b$$