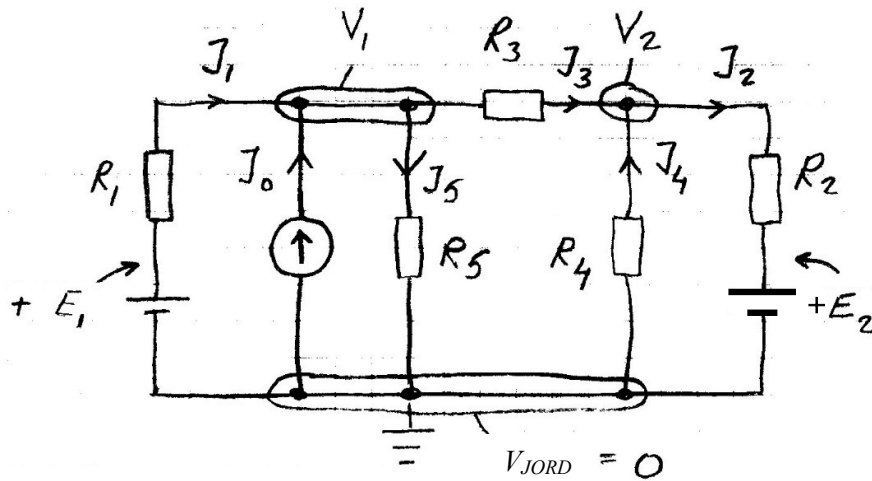


1.



$$J_1 + J_0 - J_5 - J_3 = 0 \dots (1)$$

$$J_3 + J_4 - J_2 = 0 \dots (2)$$

$$\frac{E_1 - V_1}{R_1} + J_0 - \frac{V_1 - 0}{R_5} - \frac{V_1 - V_2}{R_3} = 0 \dots (1)$$

$$\frac{V_1 - V_2}{R_3} + \frac{0 - V_2}{R_4} - \frac{V_2 - E_2}{R_2} = 0 \dots (2)$$

$$\Rightarrow V_1 = +6,75 \text{ V} \quad V_2 = +6,75 \text{ V}$$

$$J_3 = \frac{V_1 - V_2}{R_3} \Rightarrow \underline{\underline{J_3 = 0}}$$

2.

$$\begin{aligned} Z_1 &= R_1 + j\omega L = 65 + j2000\pi = \\ &= \sqrt{65^2 + (2000\pi)^2} e^{j \arctan \frac{2000\pi}{65}} = \\ &\approx 6284 \cdot e^{j89,4^\circ} \Omega \end{aligned}$$

$$\begin{aligned} Z_2 &= R_2 + \frac{1}{j\omega C} = 100 - j \frac{10^6}{2000\pi} = \\ &\approx \sqrt{100^2 + (-159)^2} \cdot e^{j \arctan \frac{-159}{100}} = \\ &\approx 188 \cdot e^{-j57,9^\circ} \Omega \end{aligned}$$

$$\begin{aligned} Z &= \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{6284 \cdot e^{j89,4^\circ} \cdot 188 \cdot e^{-j57,9^\circ}}{65 + j2000\pi + 100 - j159} = \\ &\approx \frac{1,18 \cdot 10^6 \cdot e^{j31,5^\circ}}{165 + j6124} \approx \frac{1,18 \cdot 10^6 \cdot e^{j31,5^\circ}}{6126 \cdot e^{j88,5^\circ}} = \\ &\approx 193 \cdot e^{-j57^\circ} \Omega \end{aligned}$$

$$I = \frac{U}{|Z|} \quad \text{DÄR} \quad U = \frac{\hat{U}}{\sqrt{2}} = 500V$$

$$I = \frac{500}{193} \approx \underline{2,6 A}$$

$$P = U \cdot I \cdot \cos \varphi \rightarrow$$

$$P = 500 \cdot 2,6 \cdot \cos(-57^\circ) \approx \underline{0,71 kW}$$

$$\left(\arg(Z) = \arg\left(\frac{U}{I}\right) = \arg(U) - \arg(I) = \varphi \Rightarrow \varphi = -57^\circ \right)$$

3a)

$$R = \frac{U_C - U_Z}{I_R} \quad \text{DAR} \quad I_R = I_Z + I_L$$

$$\Rightarrow R_{\max} = \frac{10 - 5,1}{0,100 + 0,500} \approx \underline{8,2 \Omega}$$

$$P_{Z_{\max}} = U_Z \cdot I_{Z_{\max}}$$

$$\Rightarrow I_{Z_{\max}} = \frac{5,1}{5,1} = 1,0 \text{ A}$$


$$R_{\min} = \frac{10 - 5,1}{1,0 + 0} = \underline{4,9 \Omega}$$

b)


$$\frac{N_1}{N_2} = \frac{\hat{U}_1}{\hat{U}_2} = \frac{\hat{U}_1}{U_C + 2 \cdot U_{\text{diode}}}$$

$$\frac{N_1}{N_2} = \frac{230\sqrt{2}}{10 + 2 \cdot 0,70} \approx 29$$

c)

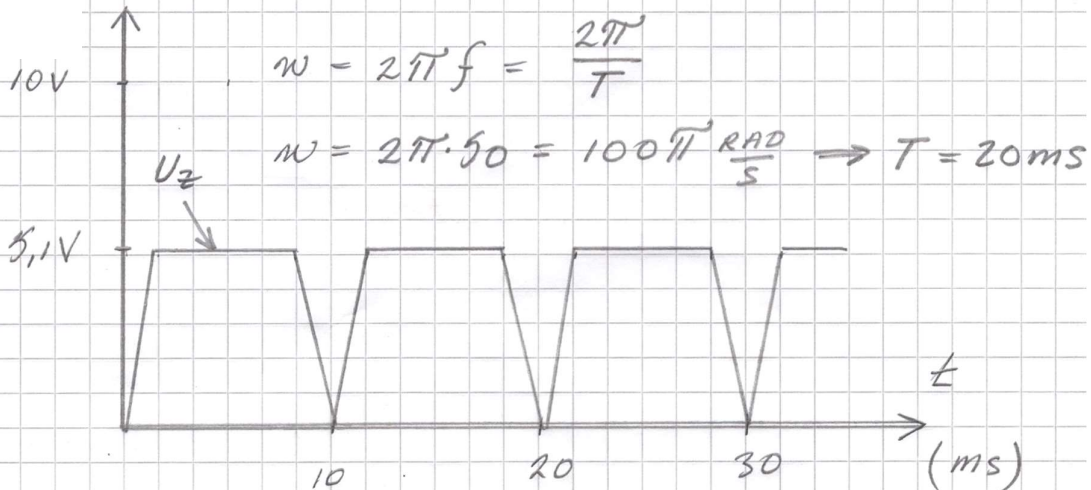

4a) LKSTRÖMSSCHEMA

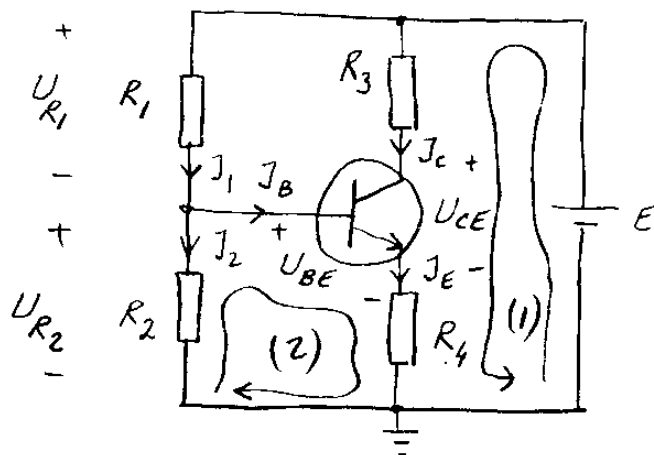

$$+ E - R_3 J_C - U_{CE} - R_4 J_E = 0 \quad \dots (1)$$

$$+ U_{R2} - U_{BE} - R_4 J_E = 0 \quad \dots (2)$$

$$J_B = \frac{J_C}{h_{FE}} \Rightarrow J_B = 17,5 \mu A$$

$$J_E = J_B + J_C \Rightarrow J_E \approx 1,42 \text{ mA}$$

$$(1) \Rightarrow +12 - R_3 \cdot 0,0014 - 6,0 - 1000 \cdot 0,00142 = 0$$

$$\Rightarrow \underline{\underline{R_3 \approx 3,3 \text{ k}\Omega}}$$

$$(2) \Rightarrow U_{R2} - 0,70 - 1000 \cdot 0,00142 = 0$$

$$\Rightarrow U_{R2} \approx 2,12 \text{ V}$$


$$\Rightarrow U_{R1} \approx 12 - 2,12 = 9,88 \text{ V}$$

$$I_2 = \frac{U_{R2}}{R_2} \approx 141,2 \mu A$$

$$I_1 = I_2 + I_B \approx 158,7 \mu A$$

$$R_1 = \frac{U_{R1}}{I_1} \approx \underline{\underline{62 \text{ k}\Omega}}$$

b)

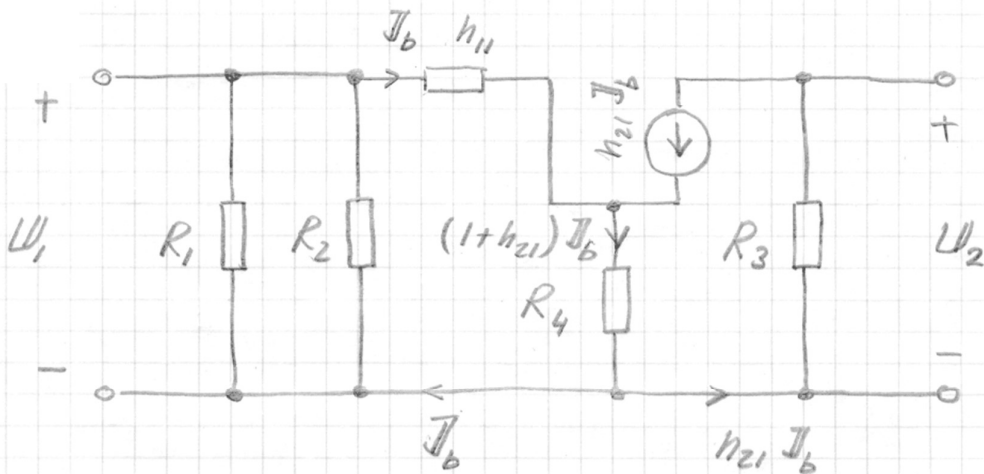

$$U_2 = -h_{21} I_b R_3$$

$$U_1 = h_{11} I_b + (1+h_{21}) I_b R_4$$

$$\frac{U_2}{U_1} = \frac{-h_{21} R_3}{h_{11} + (1+h_{21}) R_4} \approx -3,2$$

$$\begin{aligned} \Rightarrow U_2 &= -3,2 \cdot U_1 = 3,2 \cdot e^{j180^\circ} \cdot 20 \cdot e^{j0^\circ} \text{ mV} = \\ &= 64 \cdot e^{j180^\circ} \text{ mV} \end{aligned}$$

$$\Rightarrow \underline{\underline{u_2(t) = 64 \sin(1000t + 180^\circ) \text{ mV}}}$$

c) AVKOPPLINGSKONDENSATOR "ÖVER" R_4
(R_4 KORTSLUTEN) $\Rightarrow$

$$U_2 = -h_{21} I_b R_3$$

$$U_1 = h_{11} I_b$$

$$\frac{U_2}{U_1} = - \frac{h_{21} R_3}{h_{11}} \approx -165$$


$$\Rightarrow U_2 = -165 \cdot U_1 =$$

$$= 165 \cdot e^{j180^\circ} \cdot 20 \cdot e^{j0^\circ} \text{ mV} = 3,3 \cdot e^{j180^\circ} \text{ V}$$

$$\Rightarrow \underline{u_2(t) = 3,3 \sin(1000t + 180^\circ) \text{ V}}$$


5.

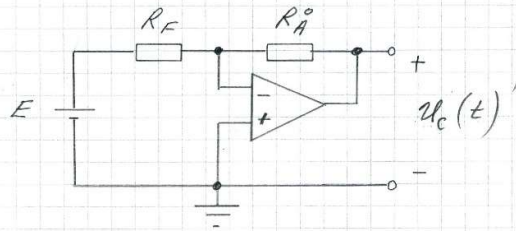5. NOLLSTÄLL $u_F(t)$. BERÄKNA
BIDRAGET FRÅN E :



$$\frac{u_c(t)'}{E} = - \frac{R_A}{R_F} \rightarrow u_c(t)' = -4,0 \text{ V}$$

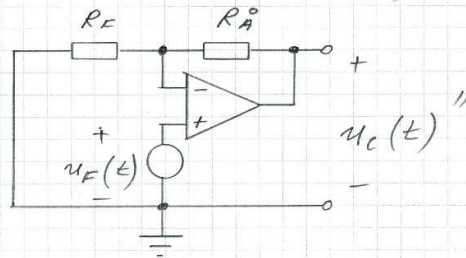NOLLSTÄLL E . BERÄKNA
BIDRAGET FRÅN $u_F(t)$:



$$\frac{u_c(t)''}{u_F(t)} = \frac{R_A + R_F}{R_F}$$


$$\Rightarrow u_c(t)'' = 0,30 \sin(1000t) \text{ V}$$

$$u_c(t) = u_c(t)' + u_c(t)'' \rightarrow$$

$$u_c(t) = -4,0 + 0,30 \sin(1000t) \text{ V}$$

$$\omega = 1000 \frac{\text{RAD}}{\text{S}}$$
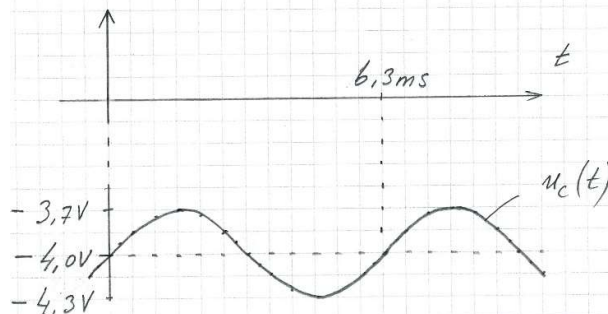
$$\omega = \frac{2\pi}{T} \Rightarrow T \approx 6,3 \text{ ms}$$



6.

Q	J	K	Q^+	Q_A	Q_B	Q_C	J_A	K_A	J_B	K_B	J_C	K_C	Q_A^+	Q_B^+	Q_C^+
0	0	-	0	0	0	0	0	-	0	-	1	-	0	0	1
0	1	-	1	0	0	1	0	-	1	-	-	0	0	1	1
1	-	1	0	0	1	0	0	-	-	1	1	-	0	0	1
1	-	0	1	0	1	1	1	-	-	0	-	0	1	1	1
				1	0	0	-	1	0	-	0	-	0	0	0
				1	0	1	-	0	1	-	-	1	1	1	0
				1	1	0	-	0	-	1	0	-	1	0	0
				1	1	1	-	0	-	0	-	1	1	1	0

VI FAR : $J_A = Q_B \cdot Q_C$ $J_B = Q_C$ $J_C = \bar{Q}_A$
 $K_A = \bar{Q}_B \cdot \bar{Q}_C$ $K_B = \bar{Q}_C$ $K_C = Q_A$

