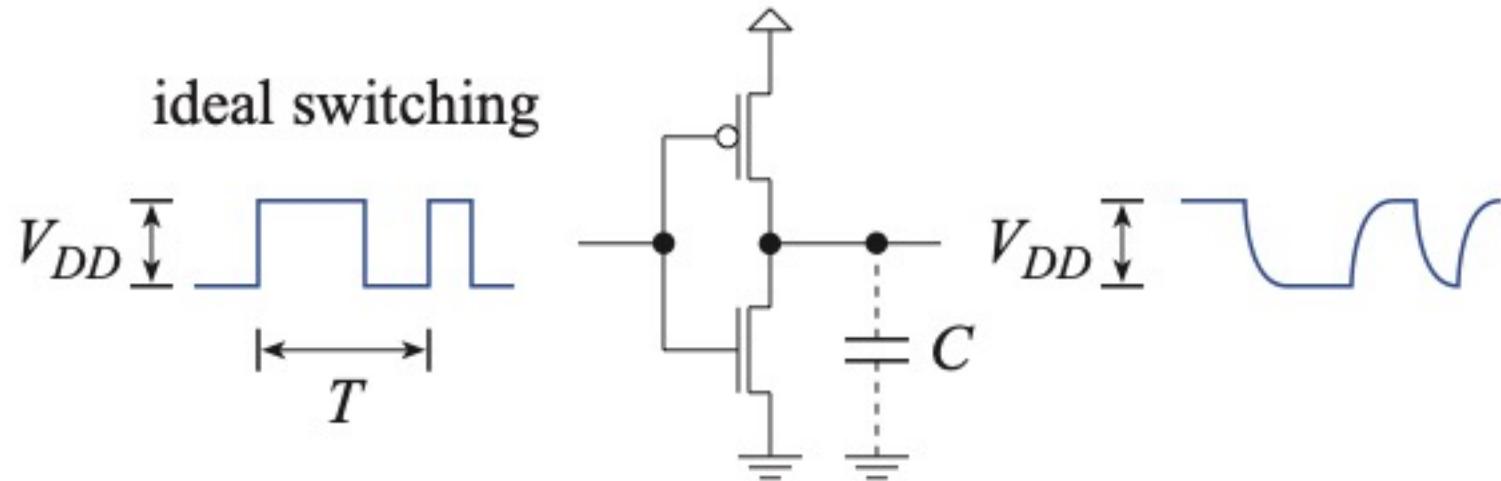


Digital ICs — Lectures

1) Introduction [Ch. 1]	TSEI03/TSTE86
2) Devices [Ch. 3, 4]	TSEI03/TSTE86
3) Interconnect [Ch. 4, 9]	TSTE86
4) Circuits [Ch. 5]	TSEI03/TSTE86
5) Combinational logic [Ch. 6]	TSEI03/TSTE86
6) Sequential circuits [Ch. 7]	TSEI03/TSTE86
7) Synchronization [Ch. 10]	TSTE86
8) Adders [Ch. 11]	TSEI03/TSTE86
9) Multipliers [Ch. 11]	TSTE86
10) Memory [Ch. 12]	TSEI03/TSTE86
11) Manufacturing [Ch. 2]	TSTE86
12) System design [Ch. 8]	TSTE86

Switch Activity




Dynamic power dissipation is

$$P_d = I_{av}V_{DD} = \frac{Q_c}{T}V_{DD} = fCV_{DD} \cdot V_{DD} = af_{clk}CV_{DD}^2$$



where a is the switch activity

Sequential Logic

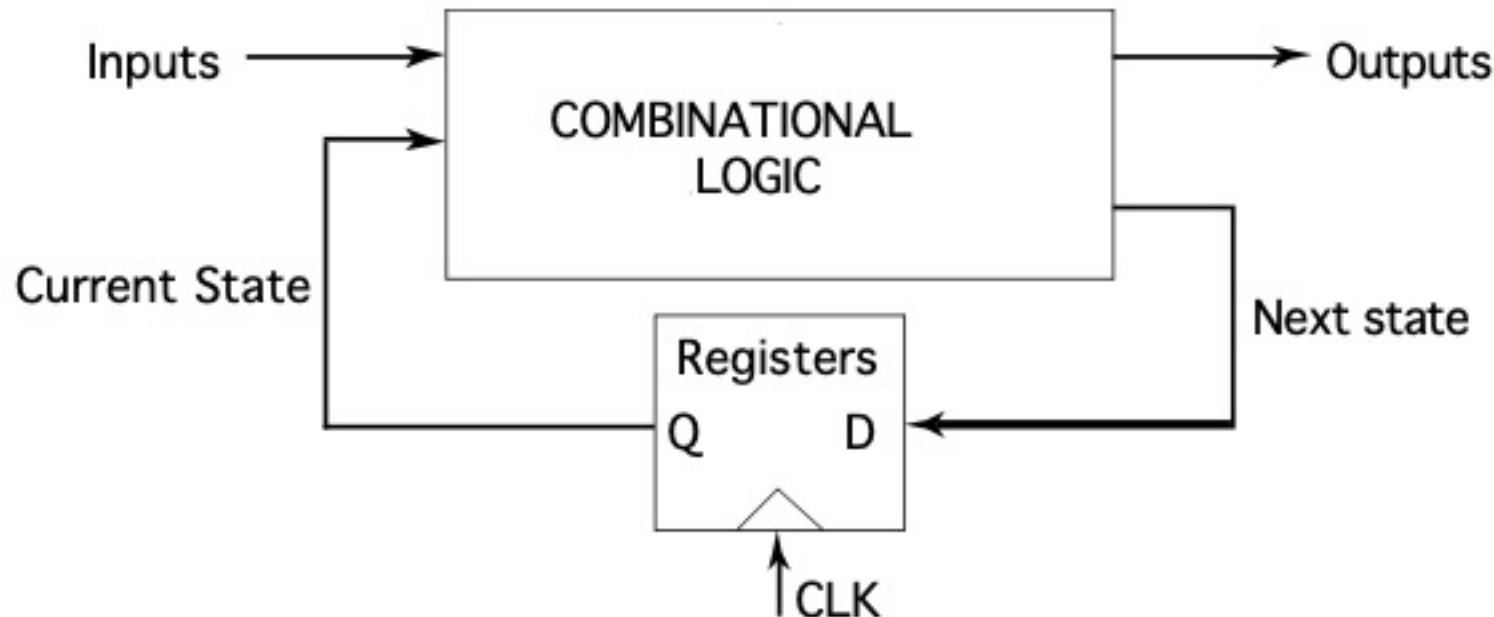

- 2 storage mechanisms
 - positive feedback
 - charge-based

Pipelining

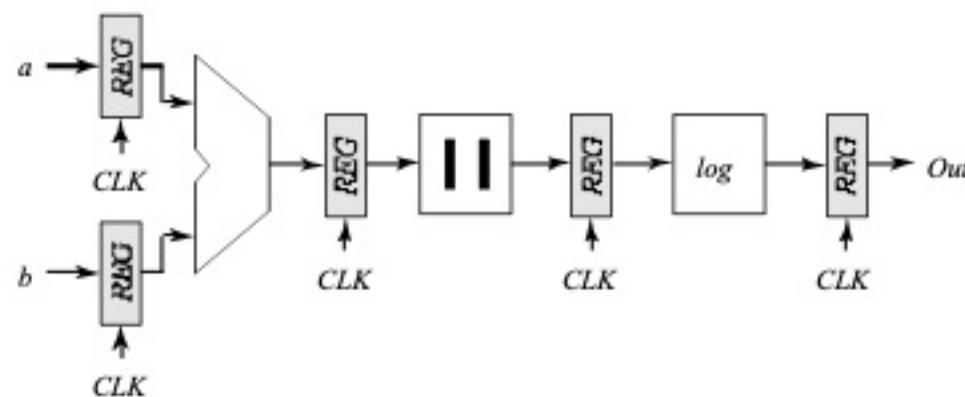
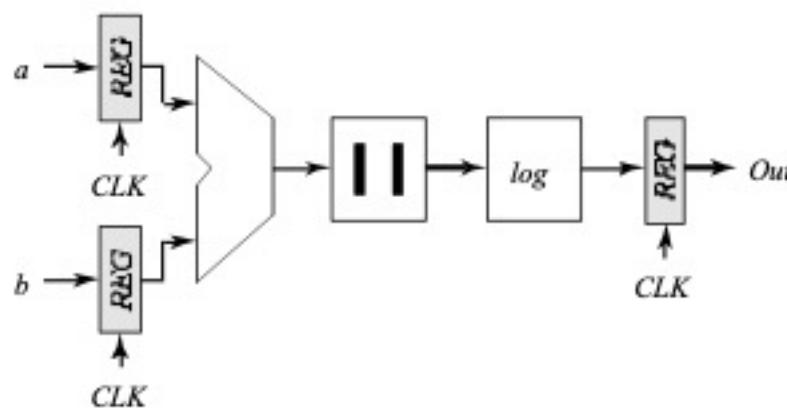


Reference


Clock Period	Adder	Absolute Value	Logarithm
1	$a_1 + b_1$		
2	$a_2 + b_2$	$ a_1 + b_1 $	
3	$a_3 + b_3$	$ a_2 + b_2 $	$\log(a_1 + b_1)$
4	$a_4 + b_4$	$ a_3 + b_3 $	$\log(a_2 + b_2)$
5	$a_5 + b_5$	$ a_4 + b_4 $	$\log(a_3 + b_3)$

Pipelined

Transmission Gate

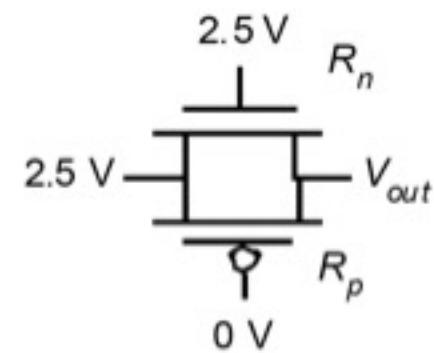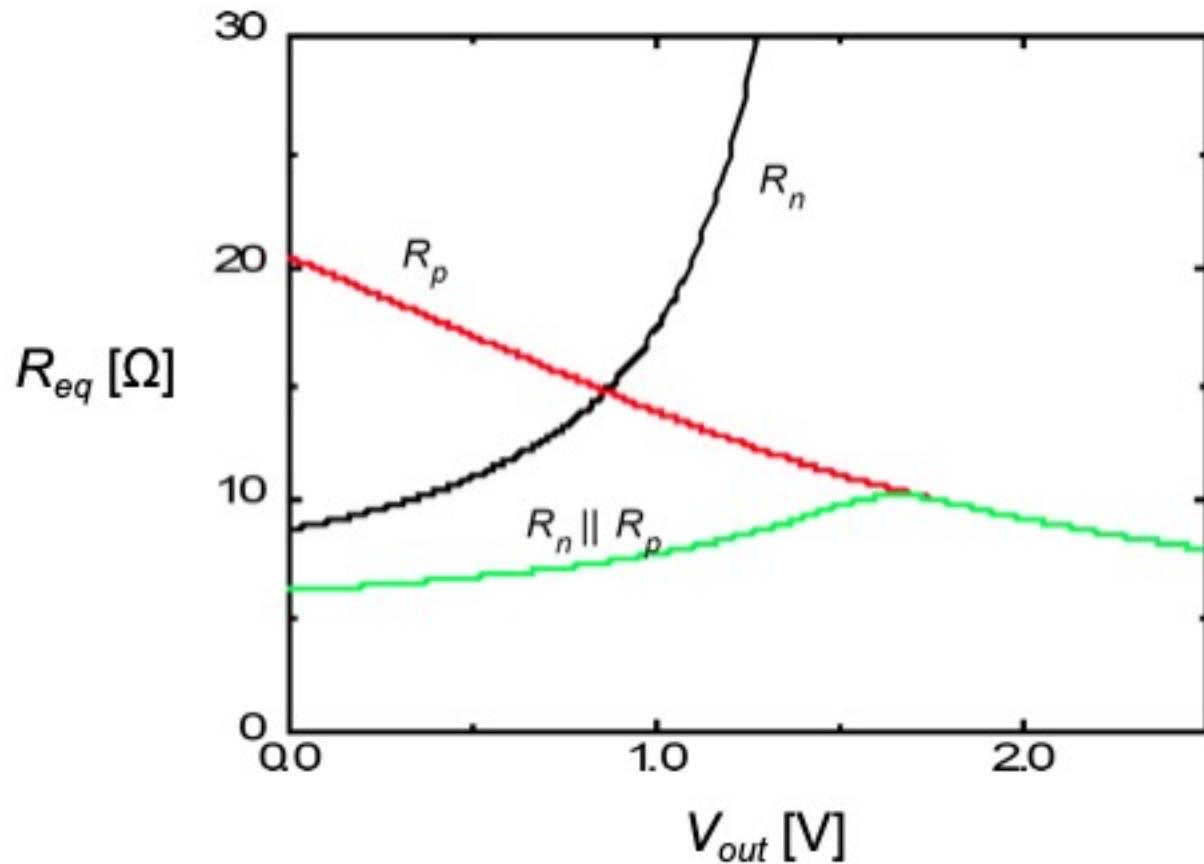


Master-Slave Register


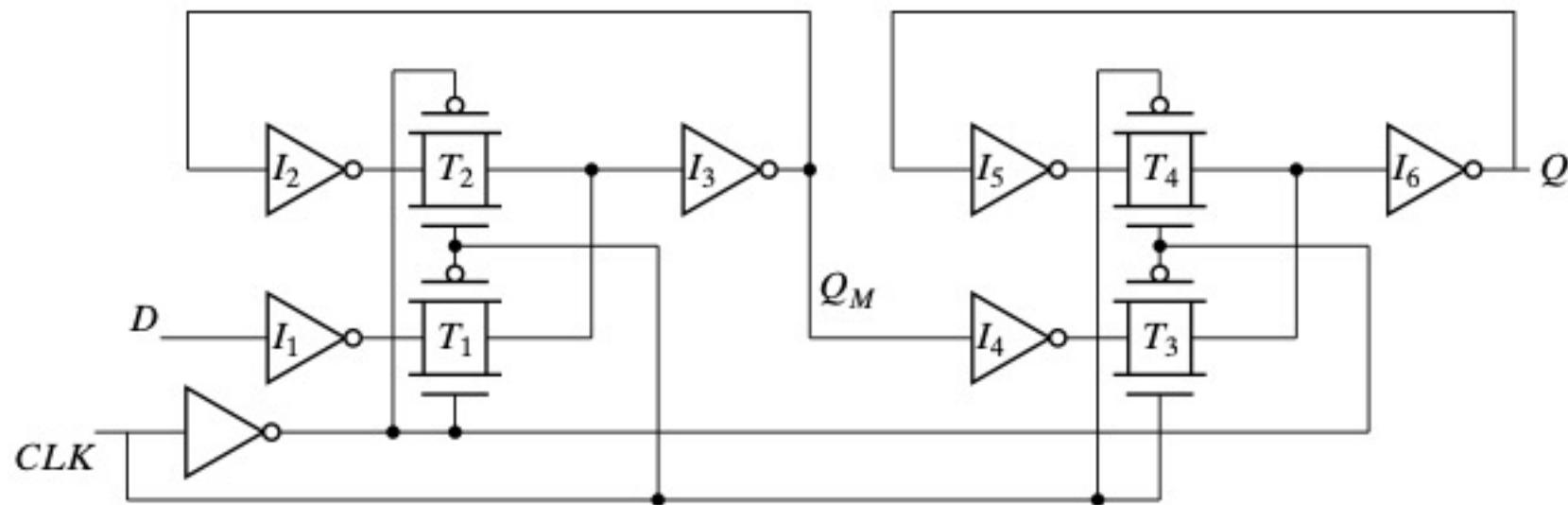


Multiplexer-based latch pair

Positive Feedback

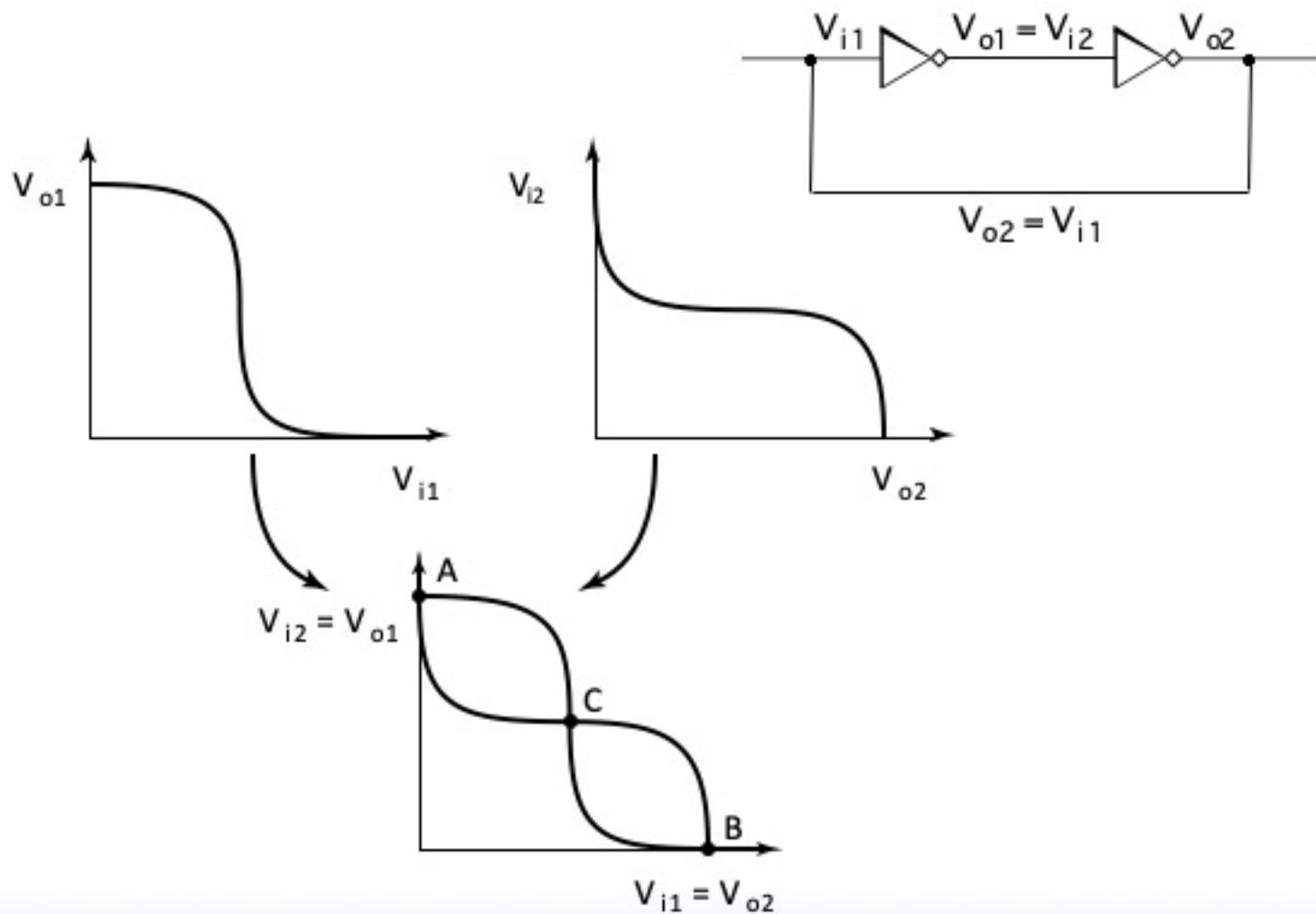


Metastability

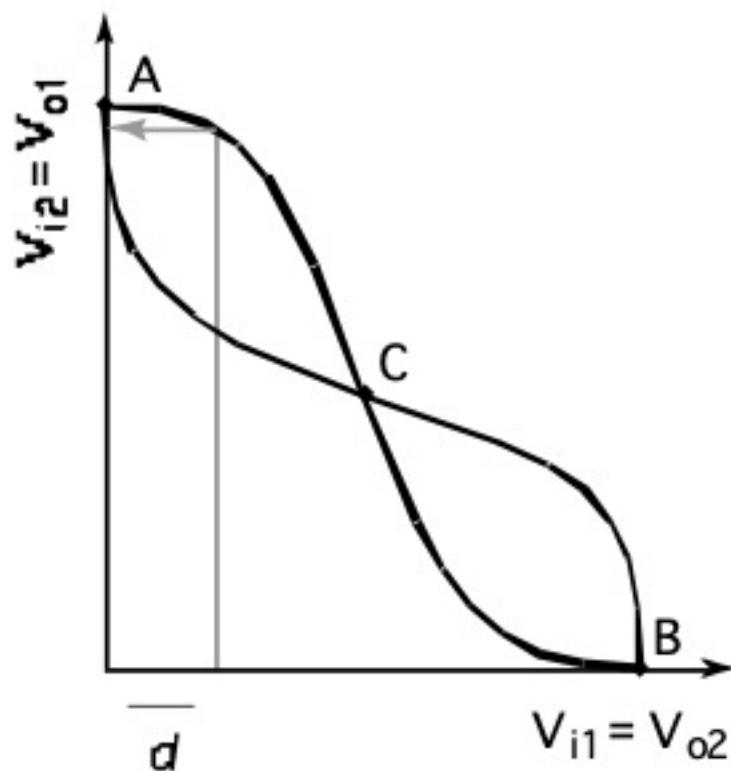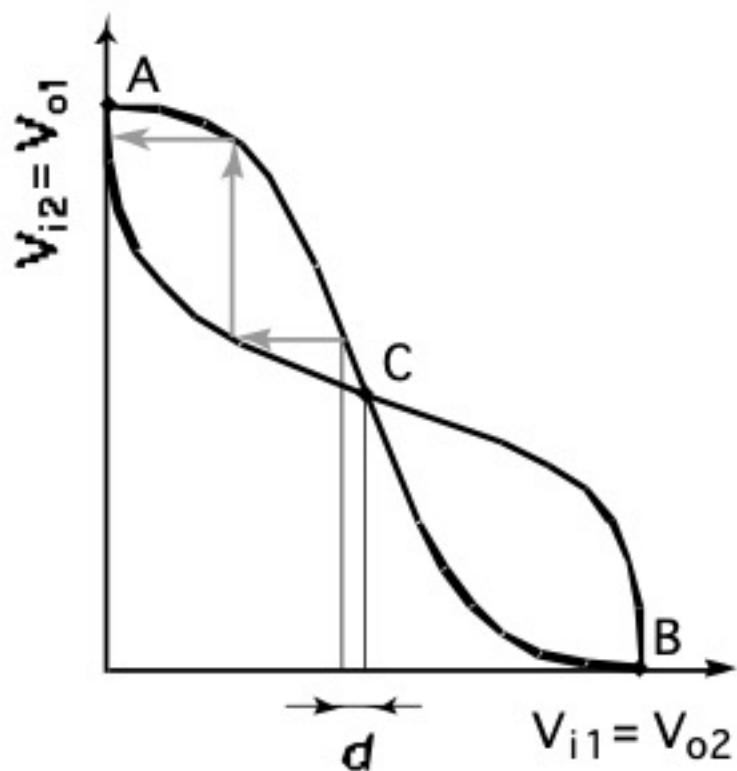


Gain is larger than 1 in the transition region

Setup Time


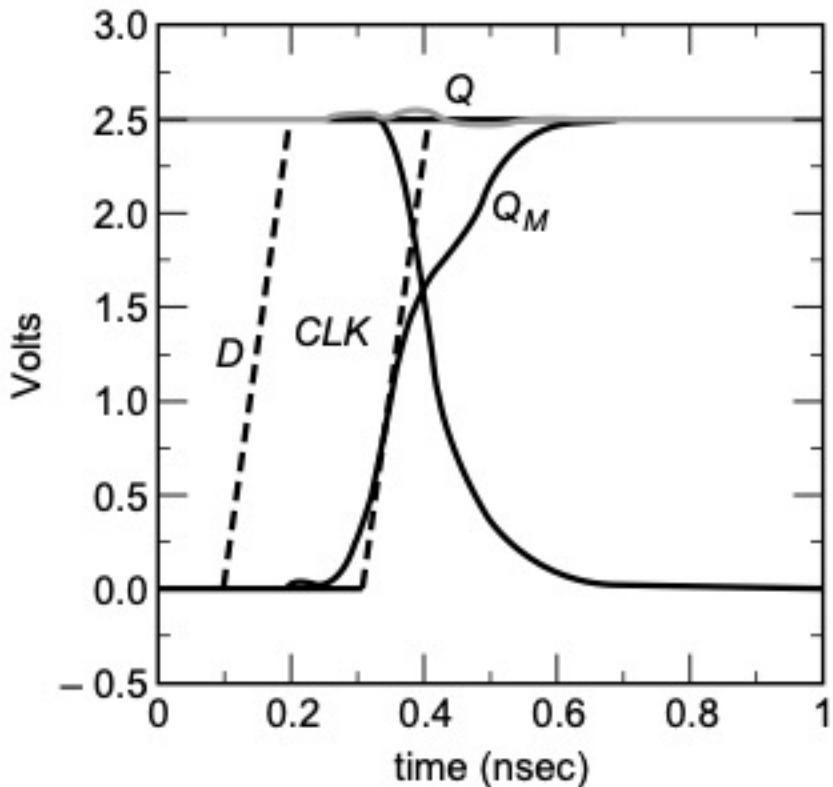


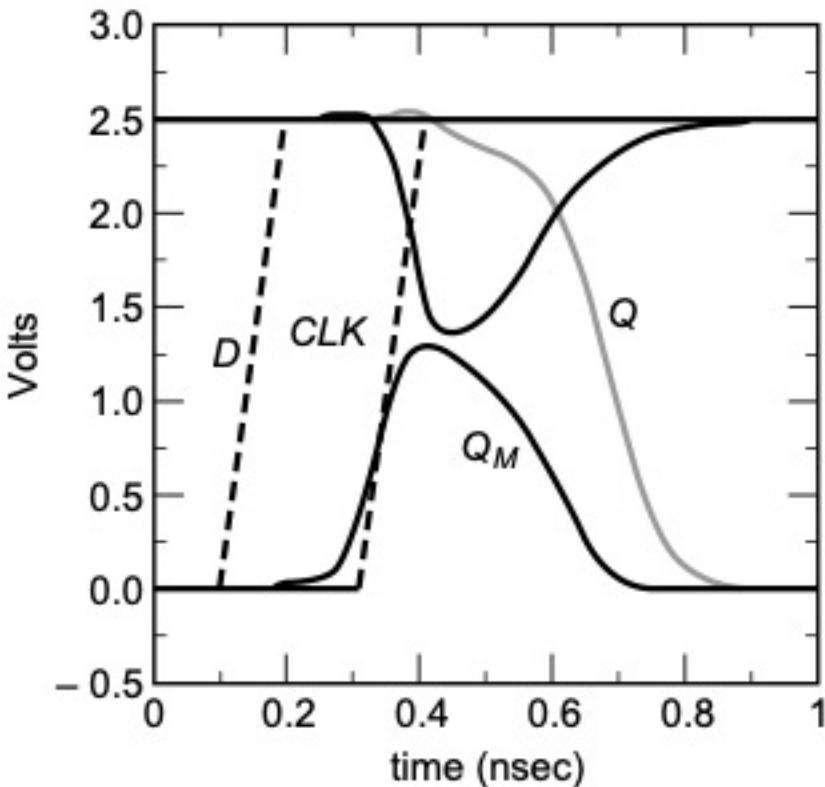(a) $T_{D \rightarrow CLK} = 0.21 \text{ nsec}$




(b) $T_{D \rightarrow CLK} = 0.20 \text{ nsec}$


Setup and Hold Times

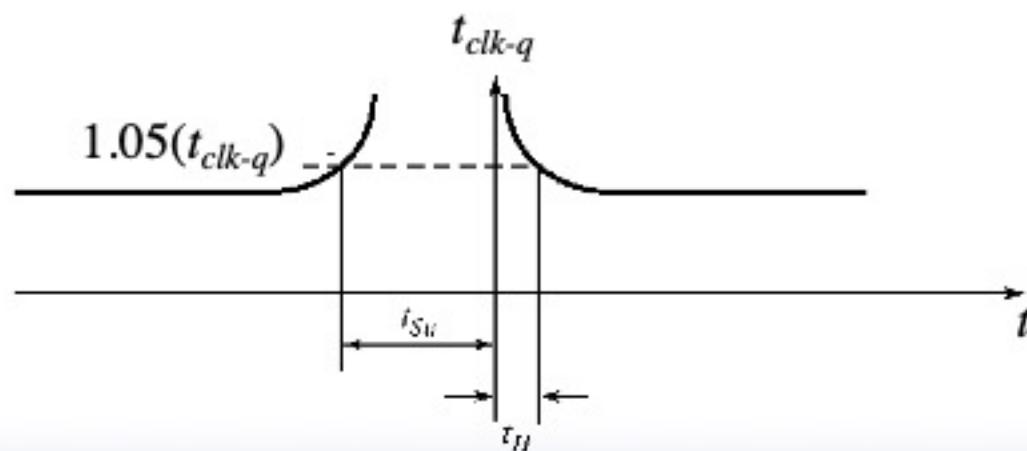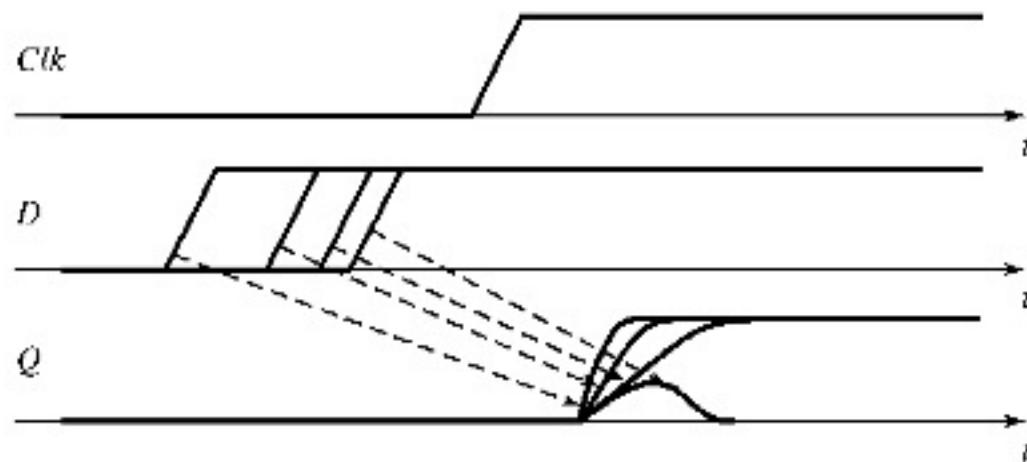


Timing Definitions

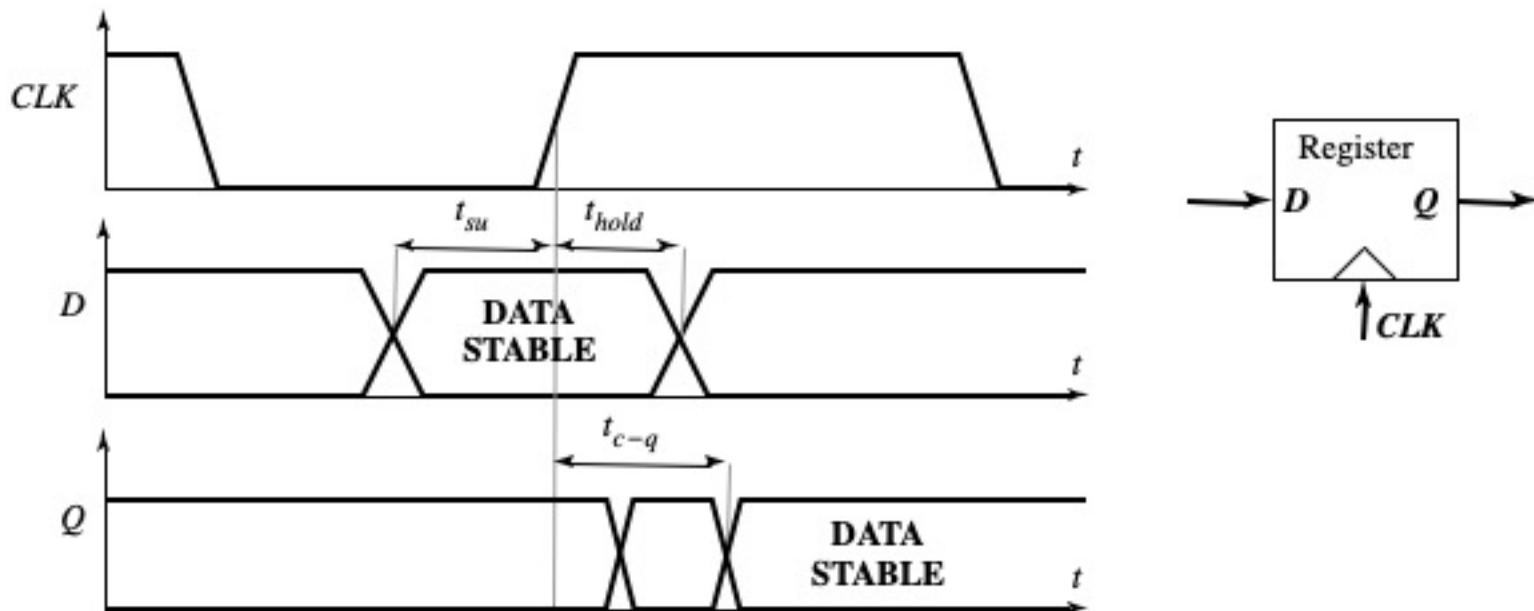

Storage Mechanisms

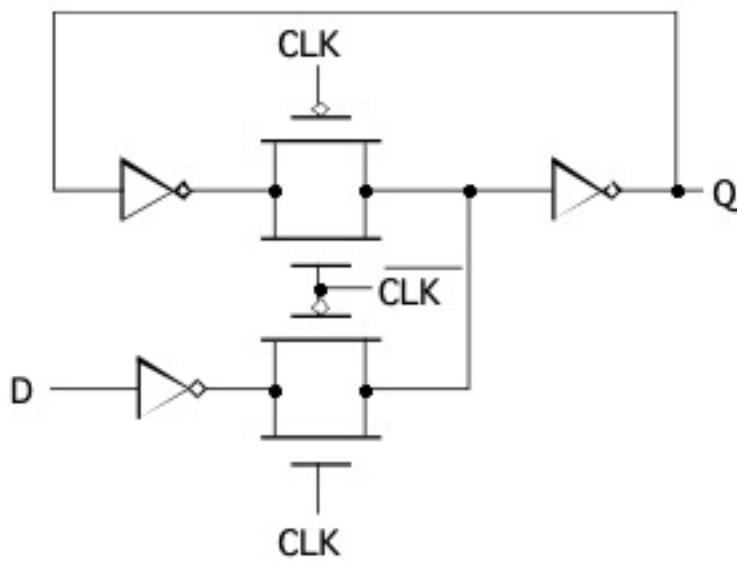


Static latch

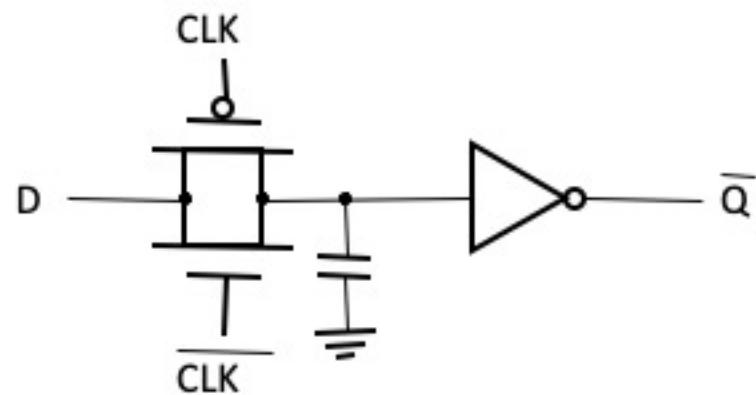


Dynamic latch

Keeper

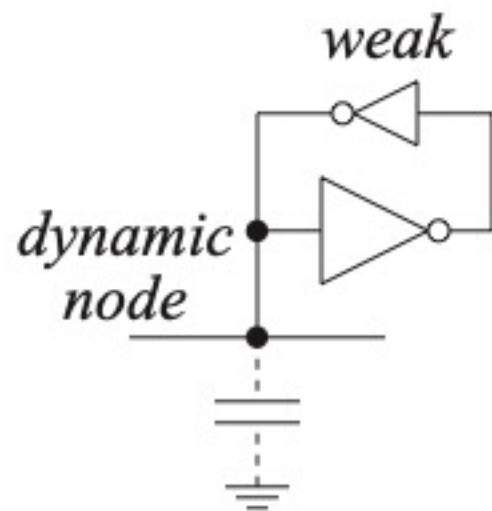


A keeper makes a dynamic circuit static

C²MOS Dynamic Latch

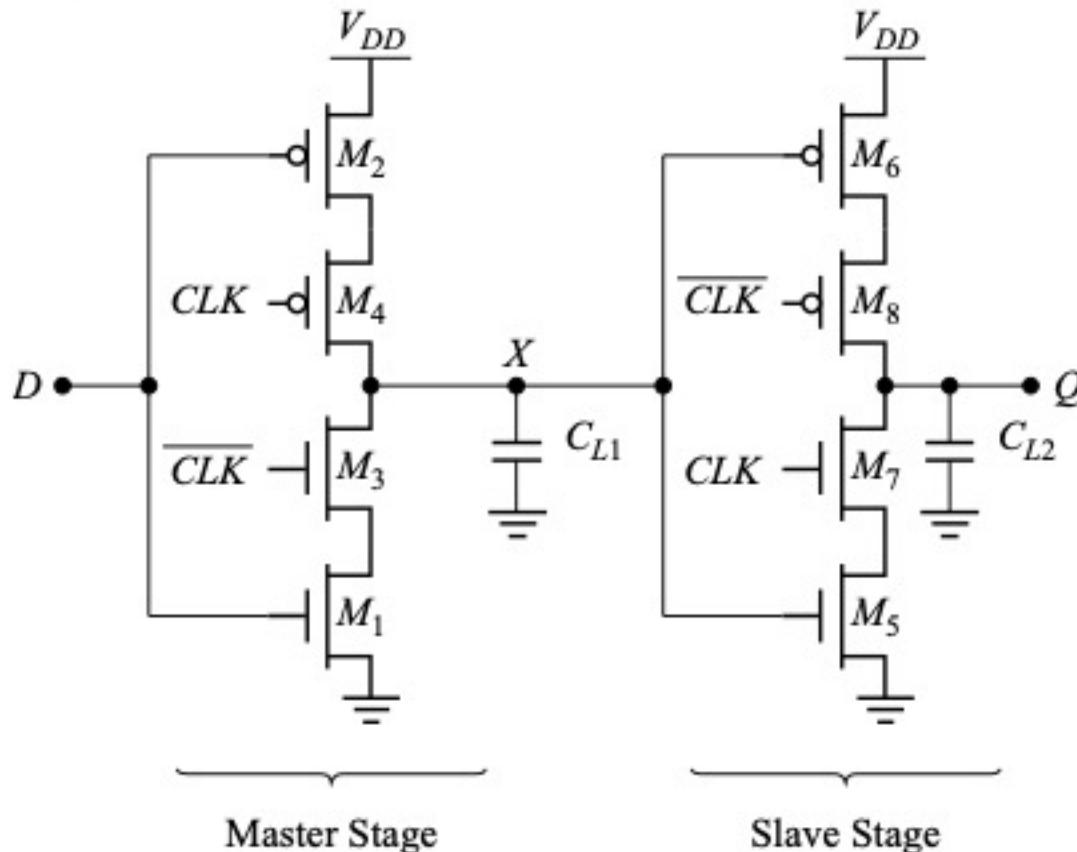

Keepers are often used to make the flip-flop static


TSPC Dynamic Latch

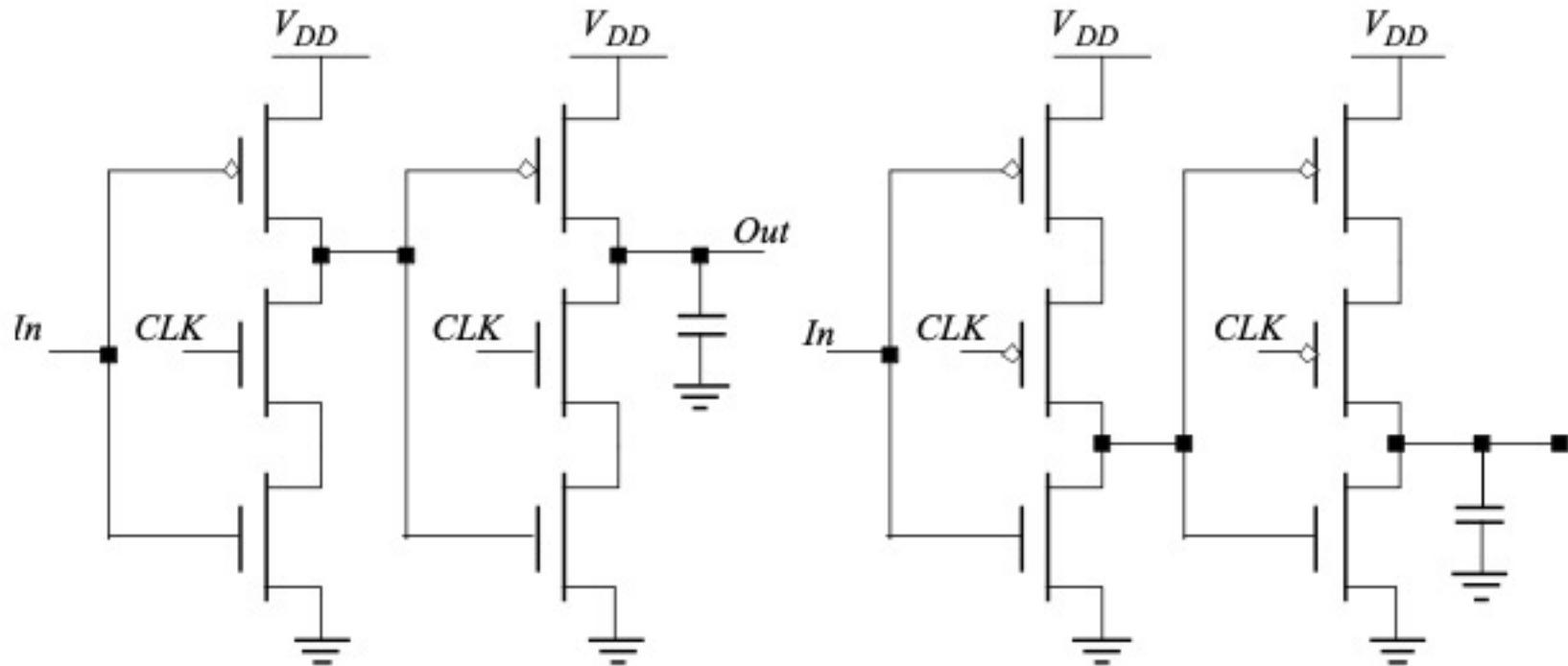


Positive latch
(transparent when $CLK = 1$)

Negative latch
(transparent when $CLK = 0$)

Precharged Logic

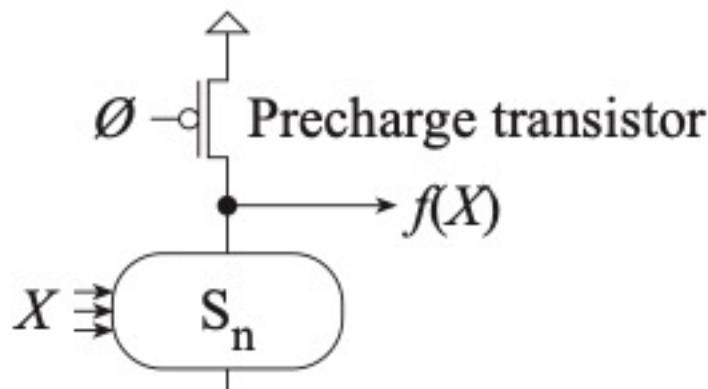


NMOS logic

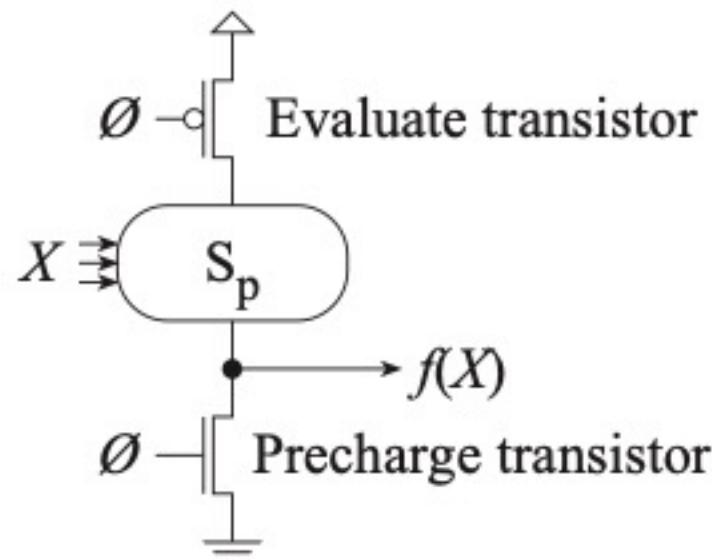


PMOS logic

Operation

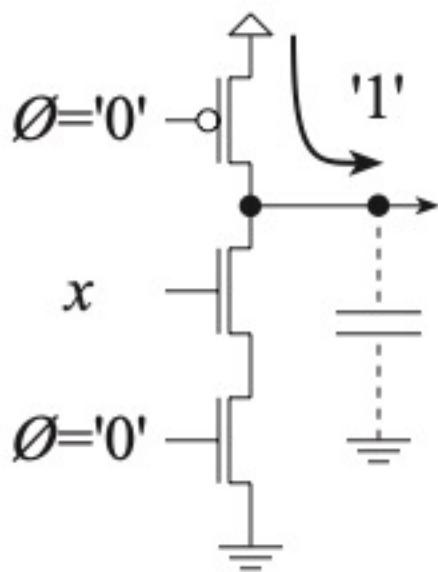


Precharge phase


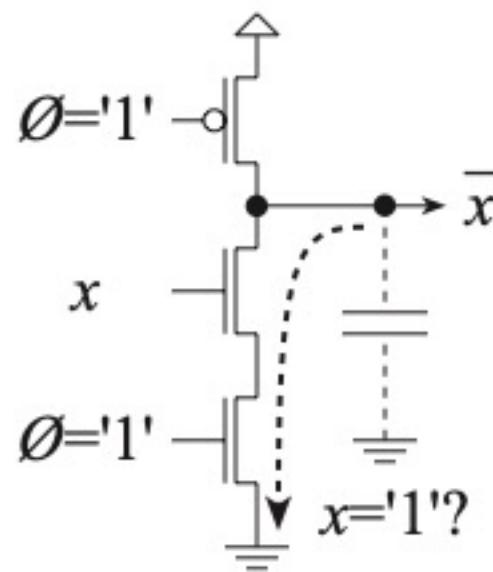


Evaluate phase

Domino Logic

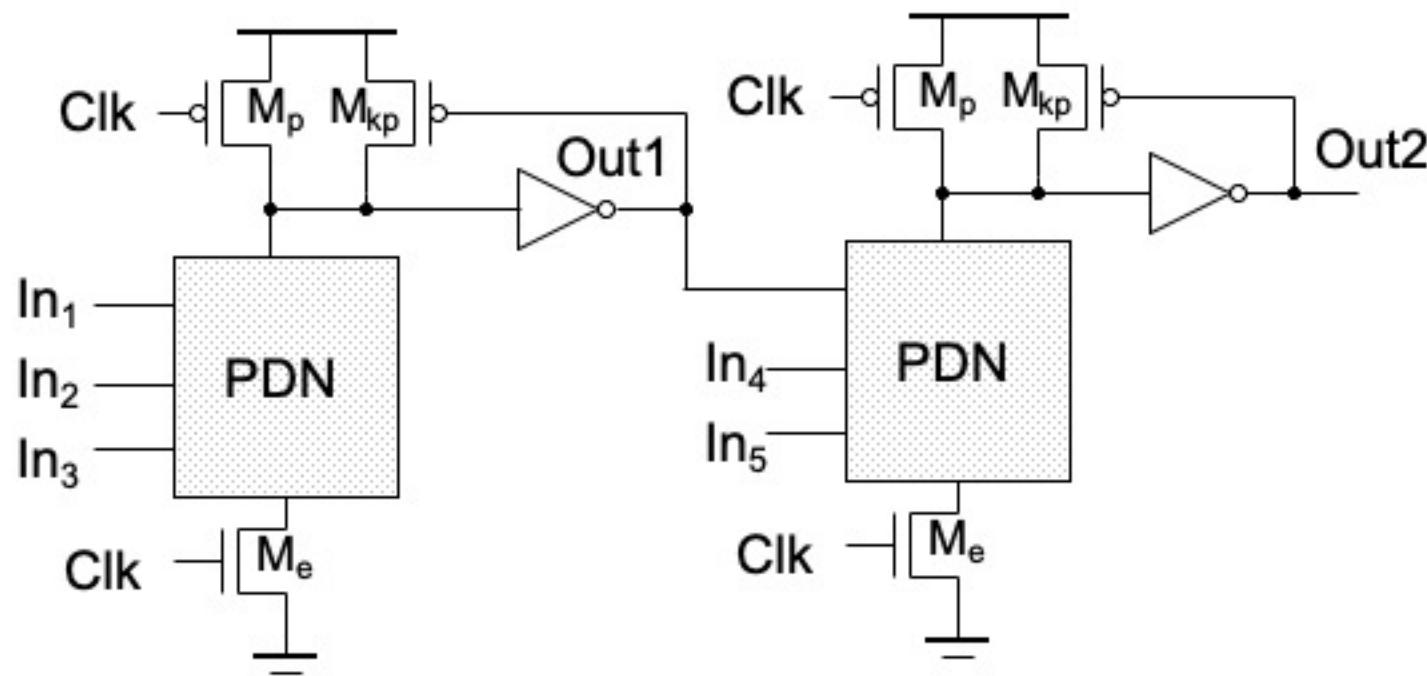


Level Restoring Transistor

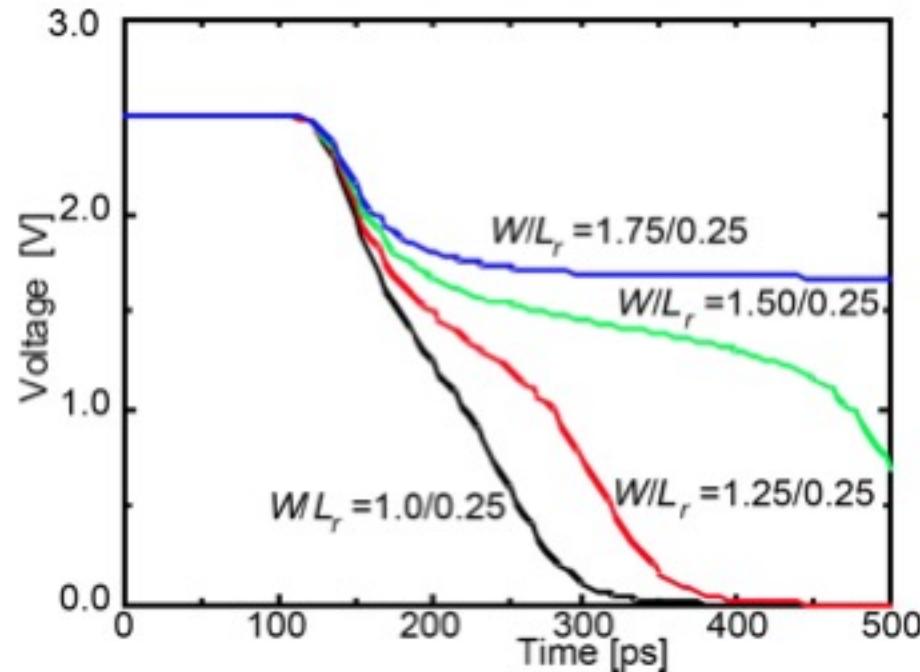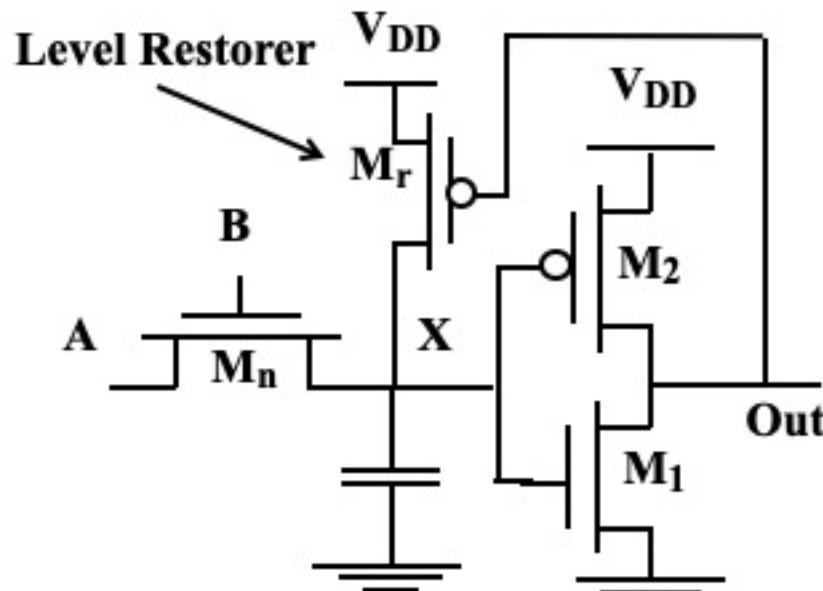


Useful in CPL and Domino logic

Charge Sharing

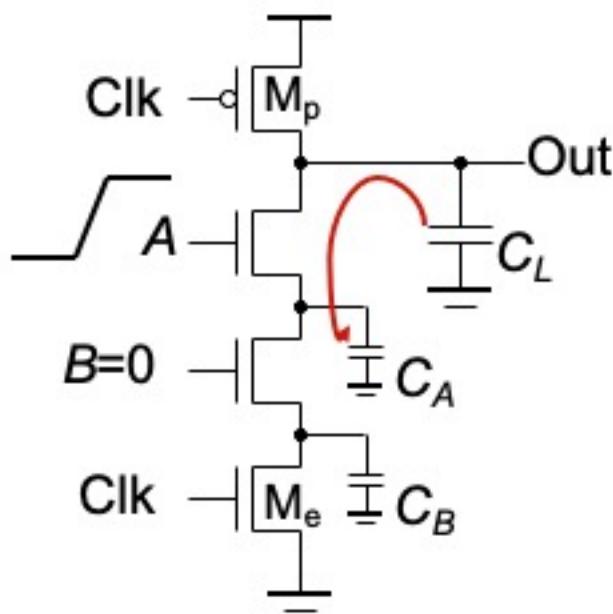


Charge stored originally on C_L is redistributed (shared) over C_L and C_A leading to reduced robustness

Sub-Threshold Conduction

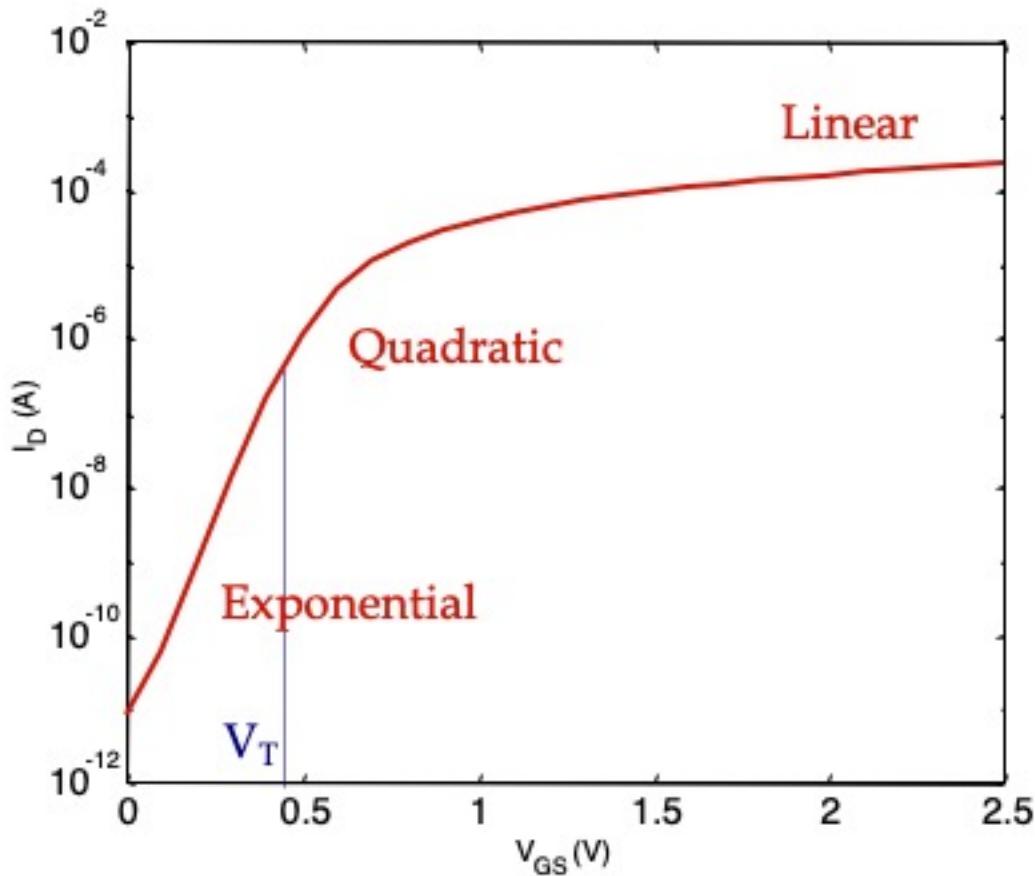


$$I_D = I_0 e^{\frac{qV_{GS}}{nkT}} \left(1 - e^{-\frac{qV_{DS}}{kT}} \right)$$

Charge Leakage

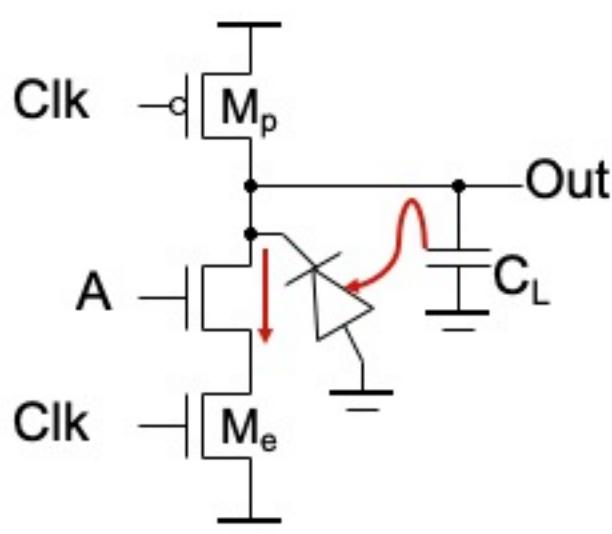

Leakage sources

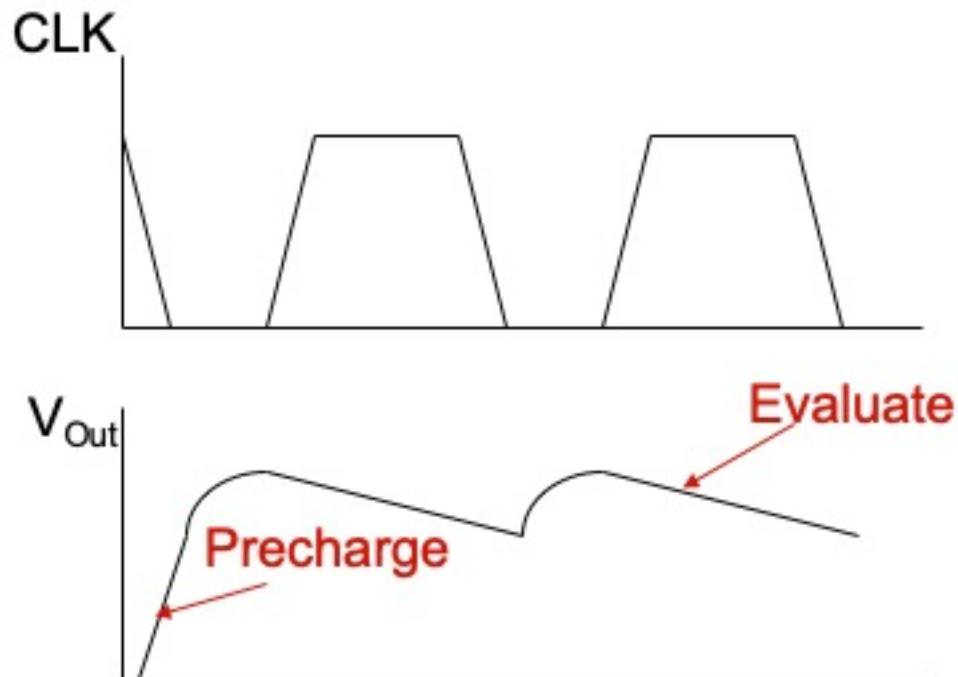

Dominant component is subthreshold current