## TSEI03 Homework 1: Operating modes

The following parameters apply to the MOSFET shown in the circuit in Figure 1.

Threshold voltage for  $V_{SB}=0$   $V_{T0}=0.43~V$ Body-effect coefficient  $\gamma=0.40~V^{1/2}$ Velocity saturation voltage  $V_{DSAT}=0.63~V$ Process transconductance  $k'=115~\mu\text{A/V}^2$ Channel length modulation  $\lambda=0~V^{-1}$ Fermi potential  $\phi=-0.30~V$ 

Plot  $V_{\text{out}}$  vs.  $V_{\text{in}}$  for the circuit with  $V_{\text{in}}$  varying from 0 to 2.5 V in steps of 0.5 V. For each point, determine the operation mode of the MOSFET as well as drain current  $I_D$ . The bulk terminal is connected to ground.

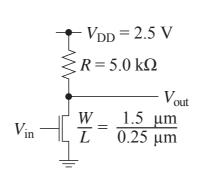


Figure 1. NMOS inverter.