

Tutorial 2: LNA Solutions

Problem 1

It is preferred in current RF designs that the input of LNA be matched to 50Ω . The easiest way is to shunt the gate with a resistor of 50Ω .

- Calculate the gain A_0 , input impedance and noise figure (NF) in absence of gate noise. Assume that $R_{sh} = R_s$ and the resistances R_L and R_{sh} noiseless for NF derivation.
- What are the disadvantages of shunt resistor with reference to gain and NF?

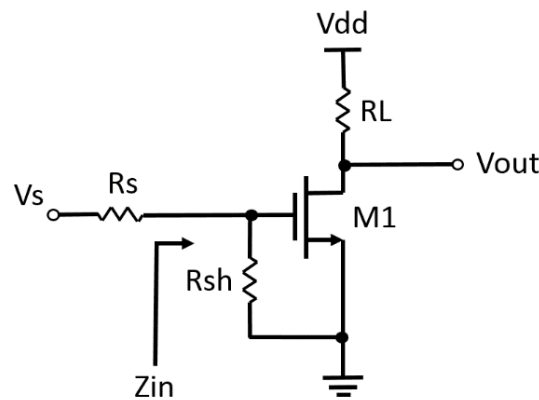


Fig. 1.1. Common-source amplifier with shunt input resistance

Solution:

- For the gain calculation, we make use of the small-signal model shown in Fig. 1.2.

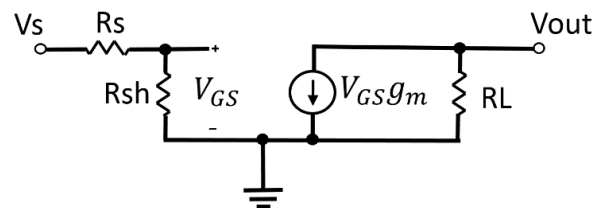


Fig. 1.2. CS small-signal model with shunt input resistance

From Fig. 1.2, we have

$$V_{GS} = V_s \frac{R_{sh}}{R_s + R_{sh}} \quad (1.1)$$

$$V_{out} = -V_{GS} g_m R_L \quad (1.2)$$

Substituting (2.1) into (2.2) and solving for V_{out}/V_s , then expression A_0 can be expressed as

$$\Rightarrow A_0 = \frac{V_{out}}{V_s} = -g_m R_L \left(\frac{R_{sh}}{R_s + R_{sh}} \right) \quad (1.3)$$

To find the input impedance, we make use of a test signal as shown in Fig. 1.3.

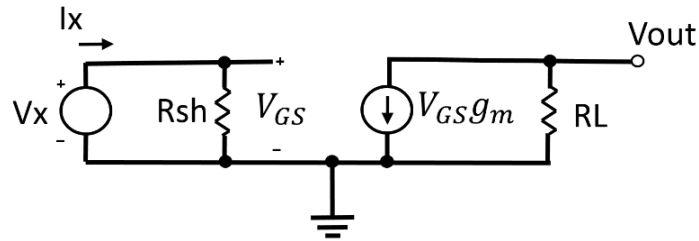


Fig. 1.3. CS small-signal model with test signal

From Fig. 1.2., the input impedance can be expressed as

$$Z_{in} = \frac{V_x}{I_x} = R_{sh} \quad (1.4)$$

Finally, the NF is equal to

$$NF = \frac{\overline{V_{n,out}^2}}{A_0^2} \cdot \frac{1}{4KTR_s} \quad (1.5)$$

The gain A_0 was already calculated, remaining only the total output noise $\overline{V_{n,out}^2}$. For this purpose, we make use of the noise circuit representation shown in Fig. 1.4.

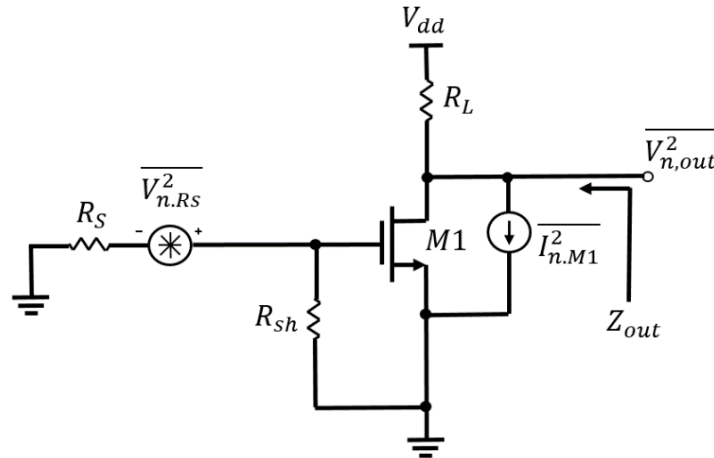


Fig. 1.4. CS noise circuit representation

Notice that R_{sh} and R_L are noiseless. The total output noise can be expressed as

$$\begin{aligned} \overline{V_{n,out}^2} &= \overline{V_{n,R_s}^2} A_0^2 + \overline{I_{n,M1}^2} \cdot |Z_{out}|^2 \\ \Rightarrow \overline{V_{n,out}^2} &= 4KTR_s A_0^2 + 4kT\gamma g_m R_L^2 \end{aligned} \quad (1.6)$$

where Z_{out} is equal to R_L . Substituting (1.6) into (1.5), we obtain for $R_{sh} = R_s$.

$$NF = \frac{4KTR_s A_0^2 + 4kT\gamma g_m R_L^2}{A_0^2 \cdot 4KTR_s}$$

$$\Rightarrow NF = 1 + \frac{\gamma(R_s + R_{sh})^2}{g_m R_s R_{sh}^2} \quad (1.7)$$

Since $R_{sh} = R_s$, NF in (1.7) can be simplified to

$$\Rightarrow NF = 2 + \frac{4\gamma}{g_m R_s} \blacksquare \quad (1.8)$$

b) The utilization of the shunt resistor reduces the voltage gain by a factor $R_{sh}/(R_s + R_{sh})$ for this LNA. Considering input impedance matching, the gain would be reduce by a factor of 2!

From (1.8), notice that there is factor of 2, showing that the NF is higher than 3 dB with the presence of the shunt resistance R_{sh} at the input.

Problem 2

The inductor source degenerate amplifier shown below presents a noiseless resistance of $50\ \Omega$ for input power match.

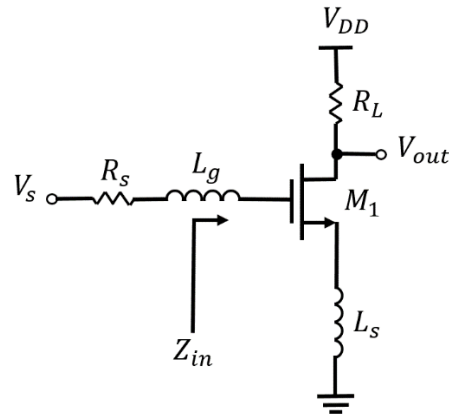


Fig. 2.1. Inductor source degenerated amplifier

- Calculate the input impedance. How we can cancel the imaginary part of the complex input impedance so that the LNA presents $50\ \Omega$ real input resistance at input port. Neglect gate drain, gate-bulk capacitance.
- Calculate the NF. Neglect gate-drain, gate-bulk and gate-source capacitance.
- C_{gd} bridges the input and the output ports. The reverse isolation of this LNA is very poor. Why is reverse isolation important? Suggest a modification to improve the reverse isolation.

Solution:

- The input impedance Z_{in} can be expressed as

$$Z_{in} = \frac{V_x}{I_x} \quad (2.1)$$

where Z_{in} can be found through the small-signal model shown in Fig. 2.2.

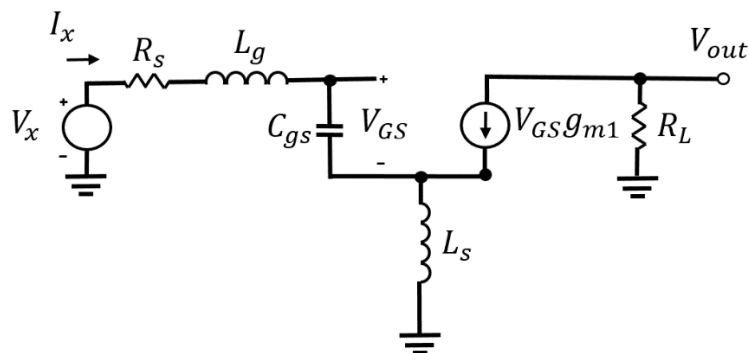


Fig. 2.2 Small-signal model with test signal at the input

From Fig. 2.2, we have,

$$V_x = I_x (Z_{L_g} + Z_{C_{gs}} + Z_{L_s} + Z_{C_{gs}} Z_{L_s} g_{m1}) \quad (2.2)$$

$$\Rightarrow Z_{in} = \frac{V_x}{I_x} = j\omega(L_g + L_s) + \frac{1}{j\omega C_{gs}} + \frac{L_s g_{m1}}{C_{gs}}$$

$$\Rightarrow Z_{in} = \frac{L_s g_{m1}}{C_{gs}} + j \frac{\omega^2 C_{gs} (L_g + L_s) - 1}{C_{gs}} \quad (2.3)$$

From (2.3), notice that the factor $\omega^2 C_{gs} (L_g + L_s)$ has to equal 1 to cancel the imaginary part of Z_{in} . The frequency that satisfies this condition can be expressed as

$$f = \frac{1}{2\pi \sqrt{C_{gs} (L_g + L_s)}} \quad (2.4)$$

On the other hand, since we want to have a 50- Ω input impedance, then

$$\Rightarrow Z_{in} = \frac{L_s g_{m1}}{C_{gs}} = 50 \Omega$$

b) The NF is expressed as

$$NF = \frac{\overline{V_{n,out}^2}}{|A_0|^2} \cdot \frac{1}{4KTR_s} \quad (2.5)$$

The circuit with the noise sources is shown in Fig. 2.3.

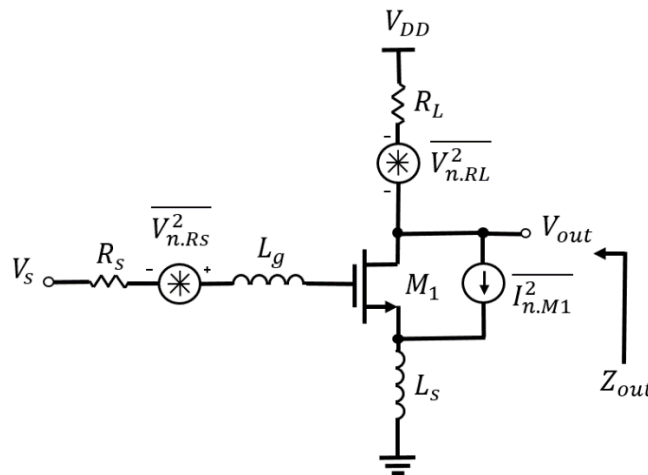


Fig. 2.3. Inductor source degenerated amplifier with noise sources

The total contribution at the output can be expressed as

$$\overline{V_{n,out}^2} = \overline{V_{n,RS}^2} A_0^2 + \overline{V_{n,RL}^2} + \overline{I_{n,M1}^2} |Z_{out}|^2 \quad (2.6)$$

The output impedance $Z_{out} = V_x/I_x$ can be found through the small-signal model show in Fig 2.4.

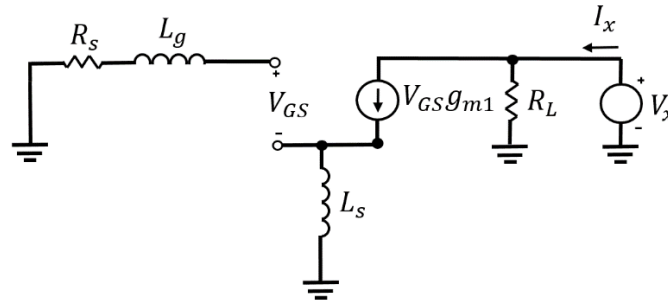


Fig. 2.4. Small-signal model with test signal at the output

From Fig. 2.4, Z_{out} is equal to

$$\Rightarrow Z_{out} = \frac{V_x}{I_x} = R_L \quad (2.7)$$

On the other hand, finding the expression for the gain A_0 . Using the small-signal model from Fig. 2.5. Notice that the parasitic capacitances are neglected.

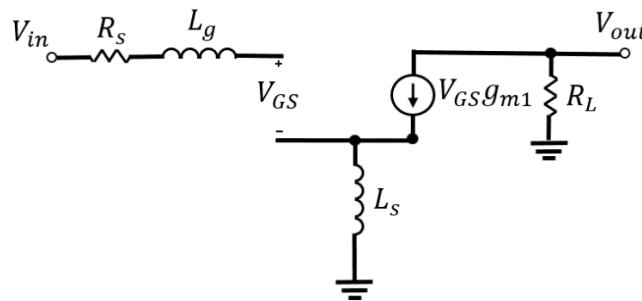


Fig. 2.5. Small-signal model

From Fig. 2.5 we have

$$\begin{aligned} V_{in} &= V_{GS}(1 + Z_{L_s}g_{m1}) \\ \Rightarrow V_{GS} &= \frac{V_{in}}{(1 + Z_{L_s}g_{m1})} \end{aligned} \quad (2.8)$$

On the other hand, V_{GS} is equal to

$$V_{GS} = \frac{-V_{out}}{g_{m1}R_L} \quad (2.9)$$

Substituting (2.9) into (2.8) and solving for A_0

$$A_0 = \frac{V_{out}}{V_{in}} = \frac{-g_{m1}R_L}{1 + Z_{L_s}g_{m1}} \quad (2.10)$$

Finally, substituting (2.6) and (2.10) into (2.5) with Z_{out} equal to R_L , the NF is expressed as

$$\begin{aligned}
 NF &= \frac{\overline{V_{n,R_S}^2} \left| \frac{g_{m1} R_L}{1 + Z_{L_S} g_{m1}} \right|^2 + \overline{V_{n,R_L}^2} + \overline{I_{n,M1}^2} |Z_{out}|^2}{4KTR_S \left| \frac{g_{m1} R_L}{1 + Z_{L_S} g_{m1}} \right|^2} \\
 \Rightarrow NF &= \frac{4KTR_S \left| \frac{g_{m1} R_L}{1 + Z_{L_S} g_{m1}} \right|^2 + 4KTR_L + 4KT\gamma g_{m1} R_L^2}{4KTR_S \left| \frac{g_{m1} R_L}{1 + Z_{L_S} g_{m1}} \right|^2} \\
 \Rightarrow NF &= 1 + \frac{R_L}{R_S \left| \frac{g_{m1} R_L}{1 + Z_{L_S} g_{m1}} \right|^2} + \frac{\gamma g_{m1} R_L^2}{R_S \left| \frac{g_{m1} R_L}{1 + Z_{L_S} g_{m1}} \right|^2} \quad (2.11)
 \end{aligned}$$

c) The reverse isolation is important to avoid leakage from the output to the input port that can lead to instability issues in the circuit as well as out-of-band power emission, causing interference in other frequency bands. A modification in the circuit that improves the reverse isolation is shown in Fig. 2.6.

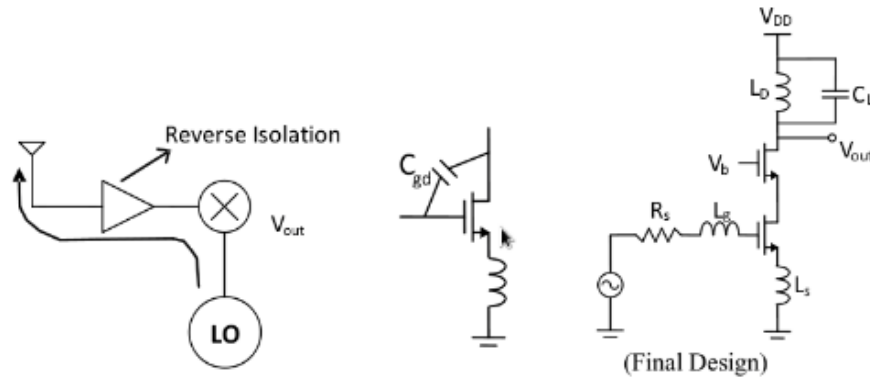


Fig. 2.6. Circuit modification to improve reverse isolation

Problem 3

A common-source low noise amplifier (LNA) with feedback is shown in the figure below. R_S is the input source resistance. Assume that the transistors are long-channel devices and $\lambda = 0$.

- Determine the input impedance R_{in} of the LNA.
- Calculate the voltage gain, $A_0 = V_{out}/V_{in}$ of the LNA after matching if $R_F = 10R_S$.
- Derive an expression for the output noise of the LNA contributed by R_S after matching. Assume $R_F \gg R_S$.

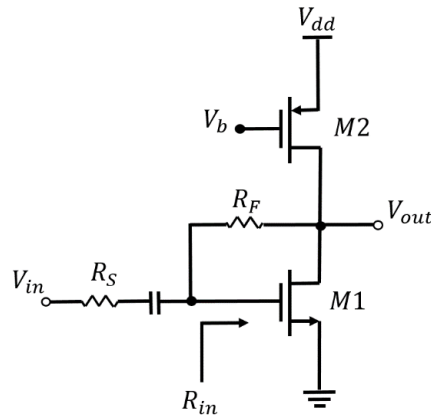


Fig. 3.1 CS stage with resistive feedback

Solution:

- The input resistance can be found from the small-signal circuit shown in Fig 3.2.

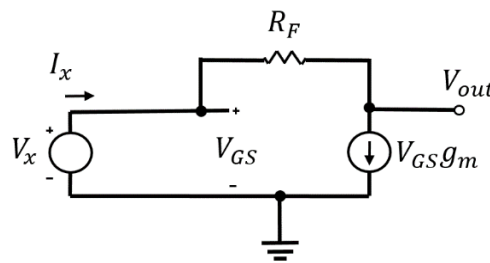


Fig. 3.2. Small-signal model test signal at the input

From Fig 3.2., we have

$$I_x = V_{GS}g_{m1} \quad (3.1)$$

$$V_x = V_{GS} \quad (3.2)$$

Substituting (3.1) into (3.2) and solving for V_x/I_x , we have

$$R_{in} = \frac{V_x}{I_x} = \frac{1}{g_{m1}} \quad (3.3)$$

b) To find the voltage gain $A_0 = V_{out}/V_{in}$, we use the small-signal model shown in Fig 3.3.

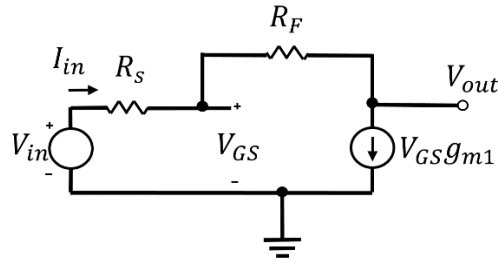


Fig. 3.3. Small-signal model

From Fig 3.3., we have

$$V_{in} - I_{in}(R_S + R_F) = V_{out} \quad (3.4)$$

$$I_{in} = g_{m1}V_{GS} \quad (3.5)$$

$$V_{GS} = V_{in} - I_{in}R_S \quad (3.6)$$

Substituting (3.6) into (3.5) and solving for I_{in} , we have

$$\begin{aligned} I_{in} &= g_{m1}(V_{in} - R_S I_{in}) \\ \Rightarrow I_{in} &= \frac{g_{m1}V_{in}}{(1 + g_{m1}R_S)} \end{aligned} \quad (3.7)$$

Now, substituting (3.7) into (3.4) and solving for V_{out}/V_{in} , we have

$$\begin{aligned} V_{in} - \frac{V_{in}g_{m1}(R_S + R_F)}{(1 + g_{m1}R_S)} &= V_{out} \\ \Rightarrow V_{in} \left[1 - \frac{V_{in}g_{m1}(R_S + R_F)}{(1 + g_{m1}R_S)} \right] &= V_{out} \\ \Rightarrow \frac{V_{out}}{V_{in}} &= \frac{(1 + g_{m1}R_S) - g_{m1}(R_S + R_F)}{(1 + g_{m1}R_S)} \end{aligned} \quad (3.8)$$

Due to matching, we have that $R_S = \frac{1}{g_{m1}}$. Besides, $R_F = 10R_S$. So, substituting for R_S and R_F in (3.8) and simplifying, the gain becomes

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{(1 + 1) - g_{m1}(11R_S)}{(1 + 1)} = \frac{2 - 11}{2} = -\frac{9}{2}$$

c) The output noise contribution from the resistance R_S corresponds to the product between the noise generated by the resistance and A_0^2 . This can be expressed as follows

$$\overline{V_{n,out,R_S}^2} = \overline{V_{n,R_S}^2} A_0^2 \quad (3.9)$$

From (3.8), after some simplification we have for

$$\Rightarrow A_0 = \frac{1}{2} \left[1 - \frac{R_F}{R_S} \right] \quad (3.10)$$

Then, $\overline{V_{n,out,R_S}^2}$ can be expressed as

$$\overline{V_{n,out,R_S}^2} = KTR_S \left[1 - \frac{R_F}{R_S} \right]^2 \approx KTR_S \left[-\frac{R_F}{R_S} \right]^2 = \frac{KTR_F^2}{R_S} \blacksquare \quad (3.11)$$

Problem 4

In the common-source stage shown below, determine

- Input impedance, R_{in} .
- Closed-loop gain.
- Noise Figure

Assume that the channel-length modulation is NOT neglected and matching at the input.

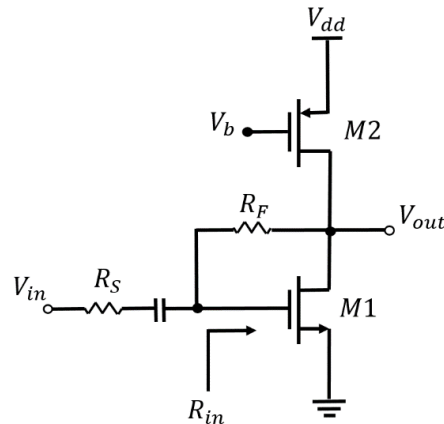


Fig. 4.1 CS stage with resistive feedback

Solution:

- Using the small-signal model with test signal connected at the input as shown in Fig. 4.2 to find R_{in} , we have

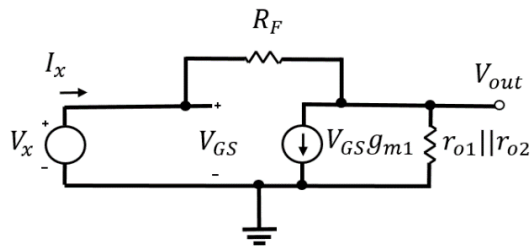


Fig. 4.2. CS small-signal model with resistive feedback and test signal at the input

The input impedance is expressed as follows

$$R_{in} = \frac{V_x}{I_x} \quad (4.1)$$

From Fig. 4.2, we can derive the following equations

$$V_x - V_{out} = I_x R_F \quad (4.2)$$

$$\frac{V_{out}}{r_{o1} || r_{o2}} + V_x g_m = I_x \quad (4.3)$$

Solving for V_{out} in (4.2) and substituting in (4.3), we have

$$\begin{aligned}
 V_x - (I_x - V_x g_m) r_{o1} || r_{o2} &= I_x R_F \\
 \Rightarrow V_x (1 + g_m r_{o1} || r_{o2}) &= I_x (R_F + r_{o1} || r_{o2}) \\
 \Rightarrow R_{in} = \frac{V_x}{I_x} &= \frac{(R_F + r_{o1} || r_{o2})}{(1 + g_m r_{o1} || r_{o2})} \blacksquare
 \end{aligned} \tag{4.4}$$

b) The closed-loop gain can be found through the small-signal model shown in Fig. 4.3.

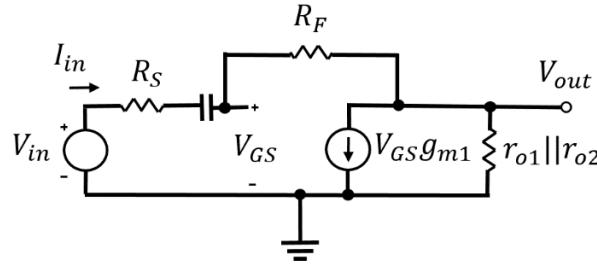


Fig. 4.3. Small-signal model

From Fig. 4.3, we have

$$I_{in} - g_{m1} V_{GS} - \frac{V_{out}}{r_{o1} || r_{o2}} = 0 \tag{4.5}$$

$$V_{GS} = V_{in} - I_{in} R_S \tag{4.6}$$

$$I_{in} = \frac{V_{in} - V_{out}}{R_S + R_F} \tag{4.7}$$

Substituting (4.7) into (4.6), we have

$$V_{GS} = V_{in} - R_S \frac{(V_{in} - V_{out})}{R_S + R_F} \tag{4.8}$$

Now, substituting (4.7) and (4.8) into (4.5) and solving for V_{out}/V_{in} ,

$$\begin{aligned}
 \frac{V_{in} - V_{out}}{R_S + R_F} - g_{m1} \left[V_{in} - R_S \frac{(V_{in} - V_{out})}{R_S + R_F} \right] - \frac{V_{out}}{r_{o1} || r_{o2}} &= 0 \\
 \Rightarrow \frac{V_{in}}{(R_S + R_F)} - g_{m1} V_{in} + \frac{g_{m1} R_S V_{in}}{(R_S + R_F)} &= \frac{V_{out}}{(R_S + R_F)} + \frac{g_{m1} R_S V_{out}}{(R_S + R_F)} + \frac{V_{out}}{r_{o1} || r_{o2}} \\
 \Rightarrow V_{in} [1 + g_{m1} R_S - g_{m1} (R_S + R_F)] &= V_{out} \left[\frac{(r_{o1} || r_{o2}) + g_{m1} R_S (r_{o1} || r_{o2}) + (R_S + R_F)}{(r_{o1} || r_{o2})} \right] \\
 \Rightarrow \frac{V_{out}}{V_{in}} &= \frac{[1 + g_{m1} R_S - g_{m1} (R_S + R_F)] (r_{o1} || r_{o2})}{(r_{o1} || r_{o2}) + g_{m1} R_S (r_{o1} || r_{o2}) + (R_S + R_F)}
 \end{aligned} \tag{4.9}$$

Considering matching impedance at the input, then (4.9) can be simplified to

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{\left[1 + \frac{R_F}{R_S}\right] (r_{o1} || r_{o2})}{\left[2(r_{o1} || r_{o2}) + (R_S + R_F)\right]} \quad (4.10)$$

c) The NF is expressed as

$$NF = \frac{\overline{V_{n,out}^2}}{A_0^2} \cdot \frac{1}{4KTR_S} \quad (4.11)$$

The circuit with the noise sources is shown in Fig. 4.4.

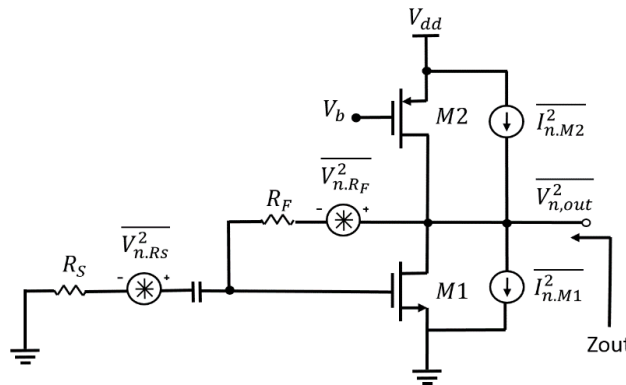


Fig. 4.4. CS circuit with noise sources

The total contribution at the output can be expressed as

$$\overline{V_{n,out}^2} = \overline{V_{n,R_S}^2} A_0^2 + \overline{V_{n,R_F}^2} + \left(\overline{I_{n,M1}^2} + \overline{I_{n,M2}^2} \right) |Z_{out}|^2 \quad (4.12)$$

The output impedance, Z_{out} , has to be found. For this purpose, using the small-signal model with the test signal connected at the output as shown in Fig. 4.5.

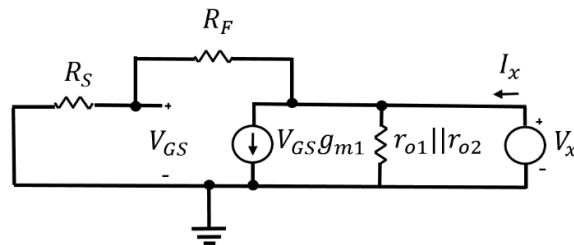


Fig. 4.5. Small-signal model with output test signal

From Fig. 4.5, we have

$$I_x = \frac{V_x}{r_{o1} || r_{o2}} + V_{GS} g_{m1} + \frac{V_x}{(R_S + R_F)} \quad (4.13)$$

$$V_{GS} = V_x \frac{R_S}{(R_S + R_F)} \quad (4.14)$$

Substituting (4.14) into (4.13) and solving for V_x/I_x ,

$$Z_{out} = \frac{V_x}{I_x} = \left[\frac{1}{(r_{o1} || r_{o2})} + \frac{(g_{m1}R_s + 1)}{(R_s + R_F)} \right]^{-1}$$

Simplifying through the input matching

$$\Rightarrow Z_{out} = \left[\frac{(r_{o1} || r_{o2})(R_s + R_F)}{(R_s + R_F) + 2(r_{o1} || r_{o2})} \right] \quad (4.15)$$

Elaborating more for (4.12), we have

$$\overline{V_{n,out}^2} = 4KTR_s A_0^2 + 4KTR_F + 4kT\gamma(g_{m1} + g_{m2}) \left[\frac{(r_{o1} || r_{o2})(R_s + R_F)}{(R_s + R_F) + (r_{o1} || r_{o2})(g_{m1}R_s + 1)} \right]^2 \quad (4.16)$$

Substituting (4.10) and (4.16) into (4.11) and after some simplification, we have

$$\begin{aligned} NF &= 1 + \frac{R_F}{\left[\frac{(1 + R_F/R_s)(r_{o1} || r_{o2})}{[2(r_{o1} || r_{o2}) + (R_s + R_F)]} \right]^2 R_s} + \frac{\gamma(g_{m1} + g_{m2})}{R_s} \left[\frac{(R_s + R_F)}{(1 + R_F/R_s)} \right]^2 \\ \Rightarrow NF &= 1 + \frac{R_F}{\left(\frac{R_F}{R_s} \right)^2 \left[\frac{(R_s/R_F + 1)(r_{o1} || r_{o2})}{[2(r_{o1} || r_{o2}) + (R_s + R_F)]} \right]^2 R_s} + \frac{\gamma(g_{m1} + g_{m2})}{R_s} R_s^2 \\ \Rightarrow NF &= 1 + \frac{R_s/R_F}{\left[\frac{(R_s/R_F + 1)(r_{o1} || r_{o2})}{[2(r_{o1} || r_{o2}) + (R_s + R_F)]} \right]^2} + \gamma(g_{m1} + g_{m2})R_s \quad \blacksquare \quad (4.17) \end{aligned}$$