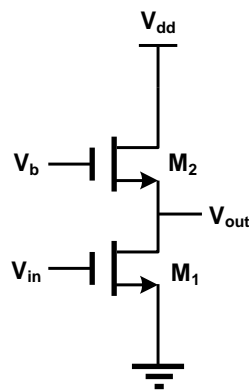


Tutorial 6: Repetition Solutions

Problem 1. Noise


A cascode amplifier stage is shown in figure below. Assume that both transistors are long-channel devices and V_b is the bias voltage for M_2 . Furthermore, assume that $g_{m1} \neq g_{m2}$ and $\lambda \neq 0$. Determine the input-referred noise voltage. Consider only the thermal noise sources and ignore the gate noise of the transistors.



A cascode stage.


Problem 2. LNA

For the common-gate LNA shown below, matched to 50 Ohm, compute the noise figure at the output resonance frequency.

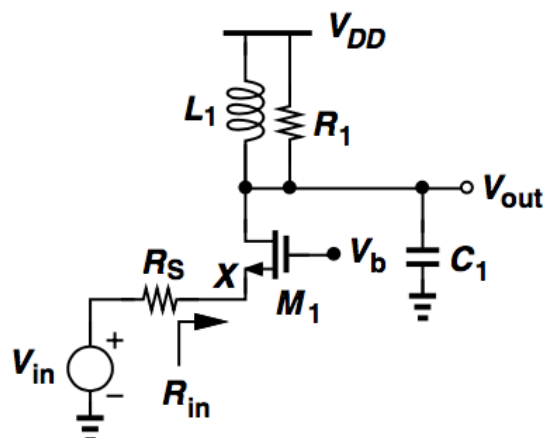

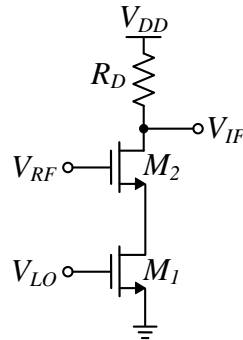Problem 3. Mixer

The circuit shown below is a dual-gate mixer used in traditional microwave design. Assume abrupt edges and a 50 % duty cycle for the LO and neglect channel-length modulation and body effect. Also assume M_1 is an ideal switch and has no noise contribution.



- Compute the voltage conversion gain of the circuit.
- Derive the expression for the noise figure of the mixer.

Problem 4. Oscillator

4) A negative-resistance oscillator operating at 2.4 GHz frequency is shown in Fig. 4. The resonant circuit is implemented using inductor $L = 5$ nH with $Q = 10$ and a variable capacitor C . Assume that we can neglect all parasitics associated with the transistors.

- What is the minimum width of two identical transistors M_1 and M_2 to ensure the oscillation? (2 p)
- How much should the variable capacitance C be varied to enable tuning from 2.4 GHz to 2.5 GHz? (1 p)
- For a capacitance corresponding to 2.4 GHz oscillation frequency, if an additional inductor of 5 nH is connected in parallel with the capacitor C , how much will the oscillation frequency change (in percentage)? (2 p)

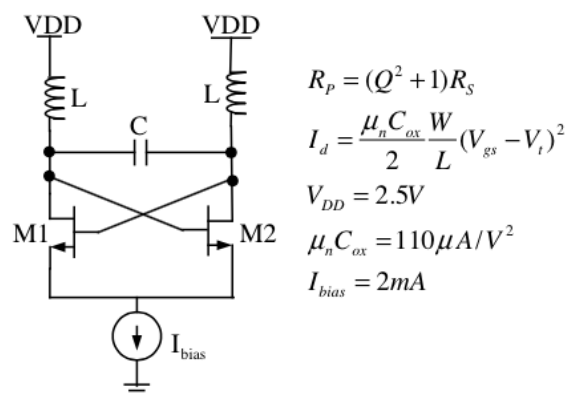



Fig. 4. A negative-resistance oscillator.

Solutions

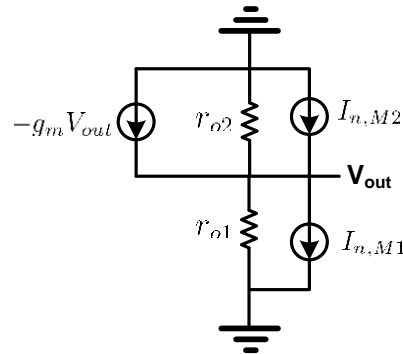Problem 1. Noise

Alt. 1 ($g_{m1} = g_{m2}$)

There are two thermal noise sources as shown below.



Since for long-channel devices:

$$\overline{I_{n,M1}^2} = 4kT\gamma g_m$$

$$\overline{I_{n,M2}^2} = 4kT\gamma g_m$$

Then because of uncorrelation, we can use superposition. Using KCL at the output node for $I_{n,M1}$:

$$(g_m V_{out} + I_{n,M1}) \cdot (r_{o1} \parallel r_{o2}) = V_{out} \rightarrow \overline{V_{out}^2} = \overline{I_{n,M1}^2} \cdot (r_{o1} \parallel r_{o2} \parallel 1/g_m)^2$$


Similarly, we get the effect of $I_{n,M2}$ at the output. Then by superposition:

$$\overline{V_{n,out}^2} = 8kT\gamma g_m (r_{o1} \parallel r_{o2} \parallel 1/g_m)^2$$

To get the input-referred noise voltage we should divide the total output noise by the gain square ($g_m^2 (r_{o1} \parallel r_{o2} \parallel 1/g_m)^2$):

$$\overline{V_{n,in}^2} = \frac{\overline{V_{n,out}^2}}{A_v^2} = \frac{8kT\gamma g_m (r_{o1} \parallel r_{o2} \parallel 1/g_m)^2}{g_m^2 (r_{o1} \parallel r_{o2} \parallel 1/g_m)^2} = \frac{8kT\gamma}{g_m}$$

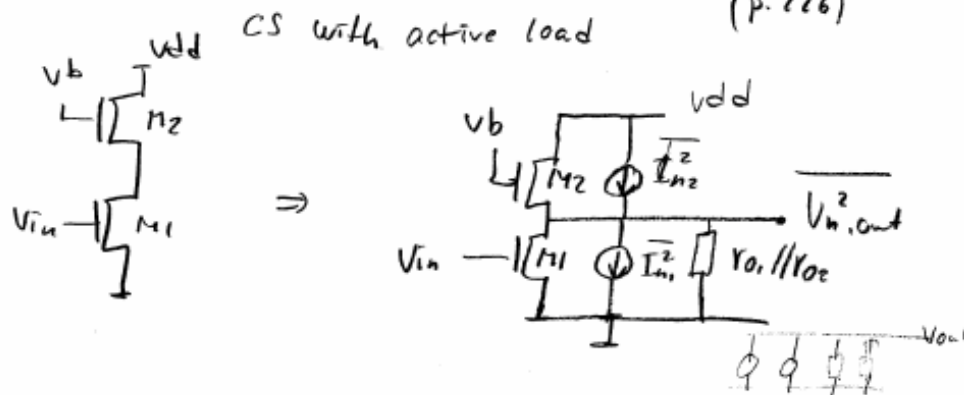Alt 2
 Similar to Example 7.10 in Razavi Analog CMOS:
 (p. 226)



Sources are uncorrelated, can be added.

$$\overline{V_{n,out}^2} = 4kT\gamma (g_{m1} + g_{m2}) (r_{o1} || r_{o2})^2$$

$$(V = i_{noise} \cdot r_o)$$

$$\text{Since } \overline{I_{n1}^2} = 4kT\gamma g_{m1}, \overline{I_{n2}^2} = 4kT\gamma g_{m2}$$

For a CS with current-source load: $A_v = -g_m \cdot R_D$

$$A_v = -g_{m1} (r_{o1} || r_{o2}) \quad (\text{Razavi CMOS p. 58})$$

$$\overline{V_{n,in}^2} = \frac{4kT\gamma (g_{m1} + g_{m2}) \cdot (r_{o1} || r_{o2})^2}{A_v^2} = \frac{4kT\gamma (g_{m1} + g_{m2})}{(-g_{m1} (r_{o1} || r_{o2}))^2} \cdot g_{m1}^2$$

$$= 4kT\gamma \left(\frac{1}{g_{m1}} + \frac{g_{m2}}{g_{m1}^2} \right)$$


$$\text{If } g_{m1} = g_{m2} \Rightarrow$$

$$= 4kT\gamma \cdot \frac{2}{g_m} = \frac{8kT\gamma}{g_m}$$

Problem 2. LNA


Tu6 LNA

Page 1

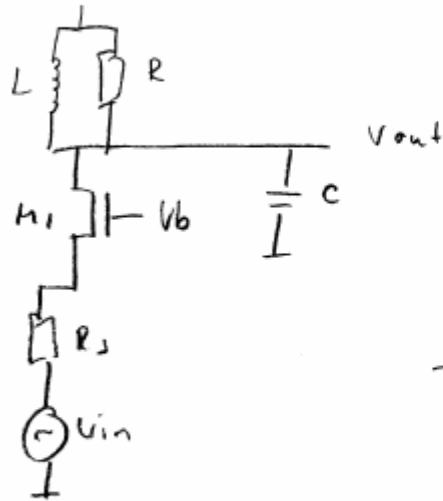


Common-gate LNA

Small-signal transistor model:

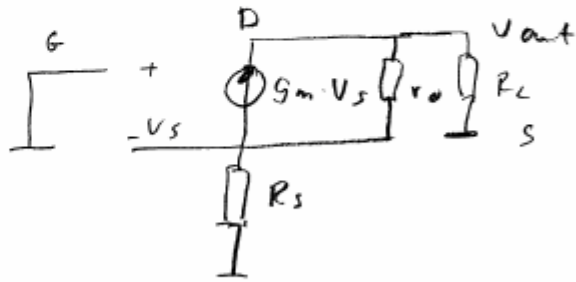

Our circuit

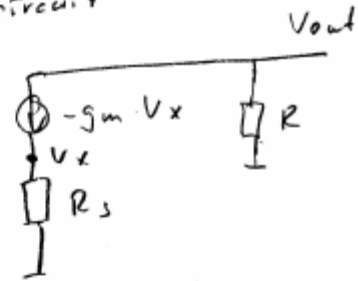

1) voltage gain Av


$$V_{out} = -g_m \cdot V_x \cdot R$$

($V = R \cdot I$)

$$A_v = \frac{V_{out}}{V_x} = g_m \cdot R = \frac{R}{R_s}$$

matching
 $g_m = 1/R_s$
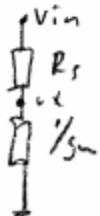
$$V_x = V_{in} \cdot \frac{1/g_m}{R_s + 1/g_m} = V_{in} \cdot \frac{R_s}{2R_s} = \frac{V_{in}}{2}$$



$$A_v = \frac{V_{out}}{V_{in}} = \frac{V_{out}}{2V_x} = \frac{1}{2} \frac{R}{R_s}$$

Noise LNA

Page 2

$$1) R \quad \overline{V_{n,out,R}^2} = 4kTR$$

$$2) R_s \quad \overline{V_{n,out,R_s}^2} = 4kTR_s \cdot A_v^2 = 4kTR_s \left(\frac{R}{2R_s}\right)^2 = \frac{kTR^2}{R_s}$$

$$3) M_1 : \text{gain from } V_g \text{ to } V_{out} = \frac{R_1}{R_s + \frac{1}{g_m}} \quad * \text{ do yourself. (testbook)}$$

$$\text{noise modelled as } \overline{V_{n,m_1}^2} = \frac{4kT\gamma}{g_m} \quad (\text{voltage source})$$


$$\Rightarrow \overline{V_{n,out,m_1}^2} = \frac{4kT\gamma}{g_m} \left(\frac{R_1}{R_s + \frac{1}{g_m}}\right)^2 = \frac{4kT\gamma}{g_m} \left(\frac{g_m R}{g_m R_s + 1}\right)^2$$

$$= \left(R_s = \frac{1}{g_m}\right) \Rightarrow 4kT\gamma \cdot R_s \frac{R^2}{R_s^2} \cdot 4 = kT\gamma \cdot \frac{R^2}{R_s}$$


$$NF = \frac{4kTR + \frac{kTR^2}{R_s} + kT\gamma \frac{R^2}{R_s}}{kTR^2 \frac{1}{R_s}} =$$

$$= 1 + 4 \frac{R_s}{R} + \gamma$$

$$* A_v = \frac{g_m \cdot R_1}{1 + g_m \cdot R_s}$$

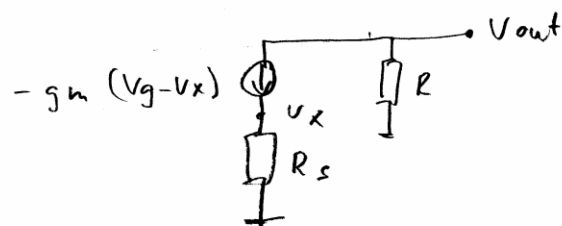

Problem 3. Mixer

a)  L_O See T3; prob 4

$$i_{L_O}(t) = \frac{1}{2} + \frac{2}{\pi} \cos \omega_{L_O} t - \frac{2}{3\pi} \cos 3\omega_{L_O} t + \dots$$

$$i_{RF} = I_{bias} + I_{RF} \cdot \cos \omega_{RF} t$$

$$i_{IF} = i_{L_O} \cdot i_{RF} = \left(\frac{1}{2} + \frac{2}{\pi} \cos \omega_{L_O} - \dots \right) (I_{bias} + I_{RF} \cos \omega_{RF})$$

$$= \left[\begin{array}{l} \text{For IF, we are} \\ \text{only interest in} \\ (\omega_{RF} - \omega_{L_O}) \text{ component} \end{array} \right] \Rightarrow \frac{2 I_{RF}}{\pi} \cos \omega_{L_O} \cdot \cos \omega_{RF}$$

upmix downmix

$$= \frac{2}{\pi} I_{RF} \left(\frac{1}{2} \cos (\omega_{RF} + \omega_{L_O}) + \frac{1}{2} \cos (\omega_{RF} - \omega_{L_O}) \right) \Rightarrow$$

$$i_{IF} = \frac{I_{RF}}{\pi} \cos (\omega_{RF} - \omega_{L_O})$$

$$\text{conv. gain} = \left| \frac{V_{IF}(t)}{V_{RF}(t)} \right| = \left| \frac{R_D \cdot \frac{I_{RF}}{\pi} \cos (\omega_{RF} - \omega_{L_O})}{\frac{1}{g_m} I_{RF} \cos \omega_{RF}} \right| =$$

$$= \boxed{\frac{1}{\pi} g_m \cdot R_D}$$

b) Noise source: R_D, R_S, M_2

$$M_2: \overline{V_{n,out,M_2}^2} = R_D^2 \cdot \overline{i_{n,out,M_2}^2} = R_D^2 \cdot 4kT\delta g_m$$

$$R_D: \overline{V_{n,out,R_D}^2} = 4kTR_D$$

$$R_S: \overline{V_{n,out,R_S}^2} = 4kTR_S \cdot (g_m \cdot R_D)^2$$

$$NF = \frac{SNR_{in}}{SNR_{out}} = \frac{\frac{S_{in}}{N_{in}}}{\frac{S_{out}}{N_{out}}} = \frac{S_{in}}{S_{out}} \cdot \frac{N_{out}}{N_{in}} = \frac{1}{G_c} \cdot \frac{N_{out}}{N_{in}}$$

$$G_c = \frac{1}{\pi} g_m \cdot R_D \quad (\text{from a)})$$


gain for noise
from input to output

$$\Rightarrow NF = \frac{1}{\left(\frac{1}{\pi} g_m \cdot R_D\right)^2} \cdot \frac{4kT\delta g_m R_D^2 + 4kTR_D + 4kTR_S (g_m \cdot R_D)^2}{4kTR_S}$$

$$= \frac{\pi^2 \delta g_m R_D^2 + R_D + R_S g_m^2 R_D^2}{g_m^2 R_D^2 R_S} =$$

$$= \pi^2 \left(1 + \frac{1}{g_m^2 R_D R_S} + \frac{\delta}{g_m R_S} \right)$$

Please note that in the noise calc, gain of 1 is used for the noise \rightarrow output \rightarrow input, while for the signal, the gain = G_c

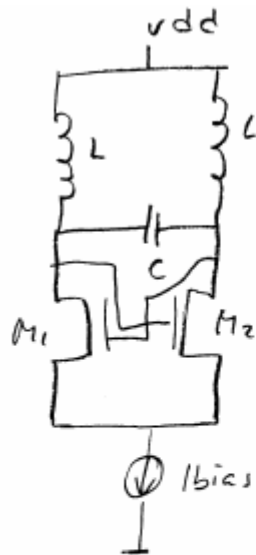Problem 4. Oscillator

$$R_p = (Q^2 + 1) R_s \quad f = 2.4 \text{ GHz}$$

$$L = 5 \text{ nH}$$

$$V_{DD} = 2.5 \text{ V}$$

$$Q = 10$$

$$\mu_n C_{ox} = 110 \mu\text{A/V}^2$$



$$I_{bias} = 2 \text{ mA}$$

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{gs} - V_T)^2$$

$$\Rightarrow g_m \approx \sqrt{2 \mu_n C_{ox} \cdot I_D \cdot \frac{W}{L}}$$

a) $\frac{W}{L}$ min for M_1, M_2 to oscillate?

Given L is L_s (or $\frac{1}{2} L_s$)

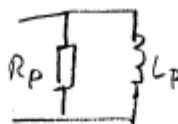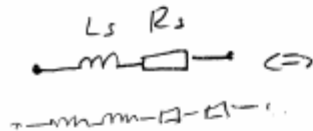

$$\omega_p = \frac{1}{\sqrt{L_p \cdot C}}$$

$$Q = \frac{\omega L_s}{R_s} \Rightarrow R_s = \frac{\omega \cdot L_s}{Q} = \frac{2\pi \cdot f \cdot L}{10} = \frac{2\pi \cdot 2.4 \cdot 10^9 \cdot 5 \cdot 10^{-9}}{10}$$

$$= 7.54 \Omega$$

$$R_p = (Q^2 + 1) \cdot 2 R_s = 1523 \Omega$$

$$\text{Oscillation: } R_{neg} = R_p = \frac{2}{g_m} \Leftrightarrow g_m = 1.31 \frac{\text{mA}}{\text{V}}$$

$$I_D = \frac{I_{bias}}{2}$$

$$g_m^2 = 2 \mu_n C_{ox} \cdot I_D \cdot \frac{W}{L}$$

$$\frac{W}{L} = \frac{g_m^2 \cdot L}{\mu_n C_{ox} \cdot I_{bias}} = 7.84$$

b) For high Q $L_p \approx L_s$ (here $L_p \approx 2L_s$)

Parallel resonance $\omega = \frac{1}{\sqrt{L_p \cdot C}} \approx \frac{1}{\sqrt{2L_s \cdot C}}$


$$C = \frac{1}{\omega^2 2L_s}$$

$$f = 2.4 \text{ GHz} \Rightarrow C = 0.440 \text{ pF}$$

$$2.5 \text{ GHz} \quad C = 0.405 \text{ pF}$$

$$\text{Tuning}^* = \frac{0.440 - 0.405}{\frac{0.440 + 0.405}{2}} = 8.3 \%$$

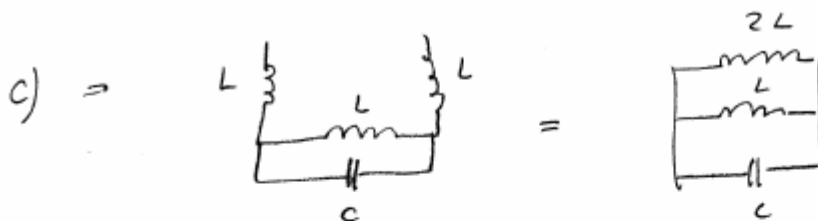* defined here in the middle of the range



$$L_{\text{eq}} = \frac{2L \cdot L}{2L + L} = \frac{2}{3}L = 3.33 \text{ nH}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \left[\begin{array}{l} C = 0.440 \text{ pF} \\ L = 3.33 \text{ nH} \end{array} \right] \Rightarrow f = 4.16 \text{ GHz}$$

$$\text{Change} = \frac{4.16 - 2.4}{2.4} = 73 \%$$