

Answers for Tutorial 1: Single Ended Amplifiers

1. Problem 3.20 in the course book

$$\begin{aligned}
 \text{a) } A_v &= -\frac{g_{m1} \frac{1}{R_F}}{\frac{1}{R_F} + \frac{1}{R_D} + \frac{1}{r_{o1}}} \\
 \text{b) } A_v &= \frac{g_{m1} + \frac{1}{R_1} + \frac{1}{r_{o1}}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{r_{o1}}} \\
 \text{c) } A_v &= -\frac{g_{m1} - g_{m2}}{g_{m2} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}}} \\
 \text{d) } A_v &= \frac{g_{m1}(g_{m2}R_D - 1)}{g_{m2} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}} \left(1 + \frac{R_D}{r_{o1}}\right)} \\
 \text{e) } A_v &= -\frac{g_{m1} \left(g_{m2} + \frac{1}{R_S}\right) r_{o2}}{g_{m1} + \frac{1}{R_S} + \frac{1}{r_{o1}} \left(1 + r_{o2} \left(g_{m2} + \frac{1}{R_S}\right)\right)}
 \end{aligned}$$

2. Problem 3.21(h) in the course book

$$A_v = -\frac{g_{m1}g_{m2}r_{o1}r_{o2}r_{o3}}{(r_{o1} + r_{o3})(1 + g_{m2}r_{o2}) + g_{m2}g_{m3}r_{o1}r_{o2}r_{o3}}$$

3. Problem 3.27 in the course book. Assume $\mu_n C_{ox} = 200 \mu A/V^2$, $V_{t0,n} = 0.5 V$, $|2\Phi_f| = 0.9 V$ and $V_{DD} = 3 V$. Also assume that in part (a) both transistors are in saturation region.

$$\begin{aligned}
 \text{a) } (W/L)_1 &= 20 \text{ and } (W/L)_2 = 5 \\
 \text{b) } (W/L)_1 &= 94.5 \text{ and } (W/L)_2 = 5 \text{ and } V_{in,m} = 1.92 V
 \end{aligned}$$

4. A two-stage single-ended amplifier is shown in Figure 1. Calculate the small-signal voltage gain and the output resistance. Assume $g_m \gg 1/r_{o1}$ and $R_D \ll r_{o2}$. ($\lambda \neq 0$ and $\gamma = 0$).

$$A_V = -g_{m2}R_D \text{ and } R_o = R_D$$

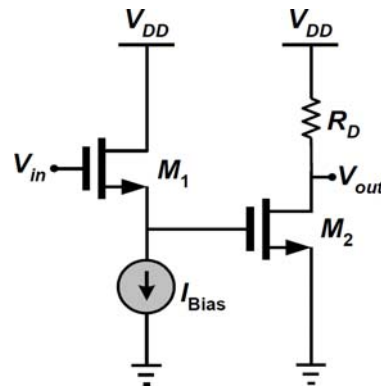


Figure 1 A two-stage amplifier

5. Using the small-signal model, calculate the voltage gain of the cascode stage shown in Figure 2 For both transistors we assume $g_m \gg g_{mb}$ and $r_o \rightarrow \infty$.

$$A_V = -\frac{g_{m1}g_{m2}R_1R_2}{1 + g_{m2}R_1}$$

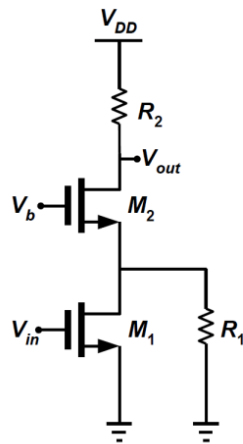


Figure 2 A cascode amplifier stage