

Exercises for Tutorial 2: Differential Amplifiers

1. Problem 4.18 in the course book (Only for Fig. 4.38. Assume $\gamma = 0$. For Fig. 4.38(a) assume $r_o \gg R_1$ and $r_o \gg 1/g_m$. Also in Fig. 4.38(e), assume $\lambda = 0$).

$$\text{a) } A_V = \frac{g_{m1}R_1}{2+g_{m3}R_1}$$

$$\text{b) } A_V = -g_{m1}(r_{o1} \parallel (r_{o3} + R_1 + R_1g_{m3}r_{o3}))$$

$$\text{c) } A_V = -g_{m1}(r_{o1} \parallel r_{o3} \parallel R_1/2)$$

$$\text{d) } A_V = -g_{m1}(r_{o1} \parallel r_{o3} \parallel R_1)$$

$$\text{e) } A_V = -\frac{g_{m1}}{g_{m3}}(1 - g_{m3}R_1)$$

2. Problem 4.22 in the course book.

$$A_{DM-DM} = -\left(g_m + \frac{1}{2R_P}\right)(R_D \parallel 2R_P \parallel 2g_mR_DR_P)$$

$$A_{CM-DM} = \frac{R_D \parallel 2R_P \parallel 2g_mR_DR_P}{R_P}$$

$$CMRR = g_mR_P + 0.5$$

3. Problem 5.3(a) in the course book for $\gamma = 0$. Assume all the transistors in the saturation region and $\mu_n C_{ox} = 4\mu_p C_{ox} = 200 \mu A/V^2$, $V_{tn} = |V_{tp}| = 0.5 V$ and $V_{DD} = 2.5 V$.

$V_P = 0.45 V$, the drain voltage of the PMOS diode-connected transistors are 1.37 V and 1.68 V (from left to right respectively).

4. Calculate the small-signal voltage gain of the cascade differential pair shown in Figure 3. Assume $\gamma = 0$.

$$|A_V| \approx g_{m1} \frac{(g_{m3}g_{m5}r_{o1}r_{o3}r_{o5}r_{o7})}{g_{m3}r_{o3}r_{o1} + g_{m5}r_{o5}r_{o7}}$$

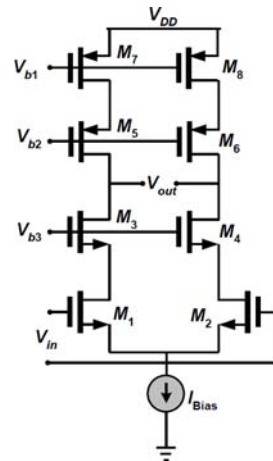


Figure 3 A differential amplifier.

5. Consider the differential amplifier shown in Figure 4. Due to a manufacturing defect, a large parasitic resistance has appeared between the drains of M_1 and M_4 . Assume $\lambda = \gamma = 0$. Calculate the small-signal gain, common-mode gain, and CMRR. Assume that $(W/L)_1 = (W/L)_2$ and $(W/L)_3 = (W/L)_4$.

$$A_0 = \frac{V_{out1} - V_{out2}}{V_{ind}} = \frac{-g_{m1} R_P}{1 + \frac{R_P}{R_D} + \frac{1}{g_{m3} R_D}}$$

$$A_{CM} = 0 \quad \{\lambda = 0, g_{m1} = g_{m2}\}$$

$$CMRR = \infty$$

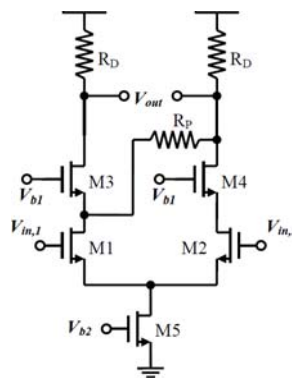


Figure 4 A differential amplifier.

