

## Exercises for Tutorial 3: Frequency Response

- 1) Problem 6.6. in the course book.
- 2) Problem 6.8(e) in the course book.
- 3) Problem 6.9(b) in the course book.
- 4) Problem 6.10(b) in the course book. Assume  $r_{o3} \gg R_2$ .
- 5) Figure 6 shows an amplifier schematic. For simplicity we can ignore all parasitics of  $M_1$  and  $M_2$  and we assume that the dominant pole occurs at the output node. Also, we assume  $g_m \gg 1/r_0$ . Find the product  $|A_0|\omega_{-3dB}$ , where  $A_0$  is the DC gain and  $\omega_{-3dB}$  is the 3 dB cut-off frequency. Assume  $\gamma = 0$ .

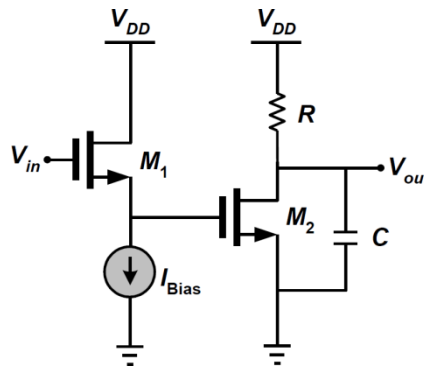


Figure 6 An amplifier schematic.

- 6) Figure 7 shows an amplifier schematic. For simplicity we can ignore all parasitics of  $M_1 - M_4$  and we assume that the dominant pole occurs at the output node. If the input signal has an angular frequency of  $\omega_i = 10^9 \text{ rad/s}$ , determine the AC gain of the amplifier. Assume  $g_{m1} = g_{m3} = 4 \text{ mA/V}$ ,  $g_{m2} = g_{m4} = 1 \text{ mA/V}$ ,  $C = 1 \text{ pF}$ ,  $g_m \gg 1/r_0$  and  $\gamma = 0$ .

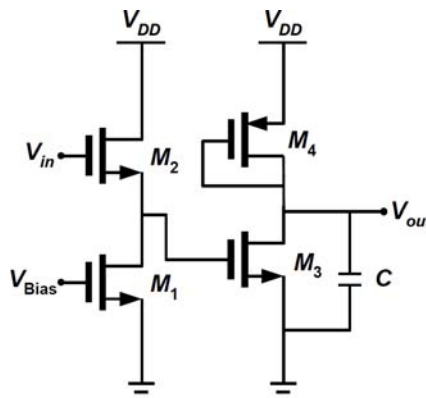


Figure 7 An amplifier schematic.