

Exercises for Tutorial 4: Feedback, Stability, Frequency Compensation

- 1) Problem 10.1 in the course book.
- 2) Problem 10.9 in the course book. In part (b) assume that the gain crossover point is the same as that of part (a). Also assume $\mu_n C_{ox} = 134 \mu A/V^2$, $\lambda_n = 0.1 V^{-1}$ and $\lambda_p = 0.2 V^{-1}$. All transistors are in saturation region.
- 3) Figure 8 shows an amplifier schematic. For simplicity we can ignore all parasitics of M_1 and M_2 . Also, we assume $g_{m1} \gg 1/r_{o1}$ and $\gamma = 0$.
 - a) Determine the transfer function of the amplifier.
 - b) If $g_{m1} = g_{m2} = 1 mA/V$, $R = r_{o2} = 20 k\Omega$ and $C_1 = C_2 = 1 pF$, calculate the phase margin of the circuit.
 - c) Use the assumptions in part (b) to calculate the AC gain, if the input frequency is $f = \frac{1}{2\pi} \times 10^8 Hz$.

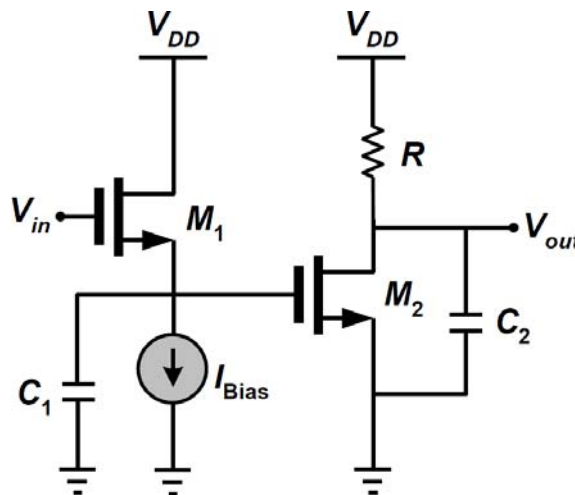


Figure 8 An amplifier schematic.

- 4) Figure 9 shows an amplifier schematic. For simplicity we can ignore all parasitics of M_1 and M_2 . Also we assume $\lambda = 0$.
 - a) Determine the transfer function of the amplifier.
 - b) If the amplifier behaves like a single-pole system, show $g_{m2}R = 1$.
 - c) If $g_{m1} = g_{m2} = 0.32 mA/V$, $R = 5 k\Omega$, $C_1 = 0.2 pF$ and $C_2 = 1 pF$, calculate the phase shift through the amplifier circuit for an input signal with $f = 143.3 MHz$.

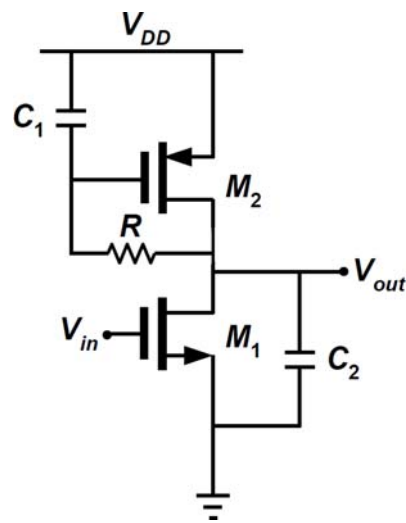


Figure 9 An amplifier schematic.

- 5) An amplifier circuit has two poles at 100 Mrad/s and 500 Mrad/s , with no zeros. Calculate the DC gain of the amplifier to get a phase margin of 90° .
- 6) Figure 10 shows a source-follower circuit. For simplicity we can ignore all parasitics. Also we assume $\lambda = 0$.
 - a) Determine the transfer function of the circuit.
 - b) If $g_{m1} = 1 \text{ mA/V}$, $R = 10 \text{ k}\Omega$, $C_1 = 1 \text{ pF}$ and $C_2 = 0.1 \text{ pF}$, calculate the AC gain and the phase shift through the source-follower circuit for an input frequency of 5 Grad/s .

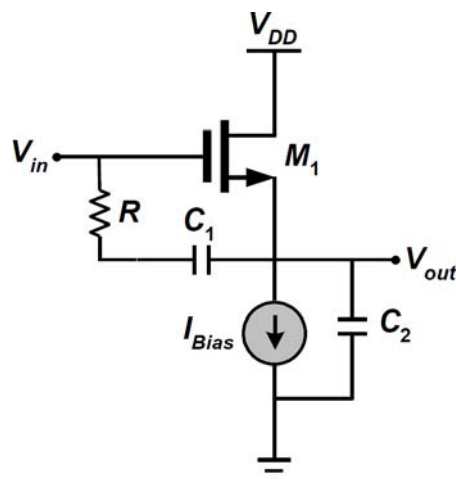


Figure 10 Source follower.