

Exercises for Tutorial 4: Frequency Response and Stability

- 1) Problem 10.1 in the course book.

$$A_0 = 31.3 \text{ dB (Using linear approximation} = 29.9 \text{ dB)}$$

- 2) Problem 10.9 in the course book. In part (b) assume that the gain crossover point is the same as that of part (a). Also assume $\mu_n C_{ox} = 134 \mu\text{A}/\text{V}^2$, $\lambda_n = 0.1 \text{ V}^{-1}$ and $\lambda_p = 0.2 \text{ V}^{-1}$. All transistors are in saturation region.

$$\text{a) PM} = 60.8^\circ \text{ (Using linear approximation} = 56.3^\circ)$$

$$\text{b) } C_{Y\text{max}} = 516 \text{ fF (Using linear approximation} = 434 \text{ fF)}$$

- 3) Figure 8 shows an amplifier schematic. For simplicity we can ignore all parasitics of M_1 and M_2 . Also, we assume $g_{m1} \gg 1/r_{o1}$ and $\gamma = 0$.

- a) Determine the transfer function of the amplifier.

$$H(s) = \frac{g_{m1}}{g_{m1} + sC_1} \frac{-g_{m2}(R \parallel r_{o2})}{1 + s(R \parallel r_{o2})C_2}$$

- b) If $g_{m1} = g_{m2} = 1 \text{ mA}/\text{V}$, $R = r_{o2} = 20 \text{ k}\Omega$ and $C_1 = C_2 = 1 \text{ pF}$, calculate the phase margin of the circuit.

$$\text{PM} = 59.3^\circ$$

- c) Use the assumptions in part (b) to calculate the AC gain, if the input frequency is $f = \frac{1}{2\pi} \times 10^8 \text{ Hz}$.

$$A_{ac} = 7$$

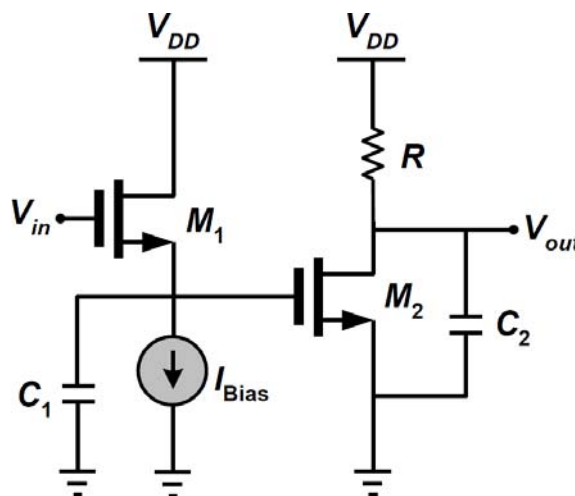


Figure 8 An amplifier schematic.

- 4) Figure 9 shows an amplifier schematic. For simplicity we can ignore all parasitics of M_1 and M_2 . Also we assume $\lambda = 0$.

a) Determine the transfer function of the amplifier.

$$H(s) = -\frac{g_{m1}(1 + sRC_1)}{s^2RC_1C_2 + s(C_1 + C_2) + g_{m2}}$$

b) If the amplifier behaves like a single-pole system, show $g_{m2}R = 1$.

c) If $g_{m1} = g_{m2} = 0.32 \text{ mA/V}$, $R = 5 \text{ k}\Omega$, $C_1 = 0.2 \text{ pF}$ and $C_2 = 1 \text{ pF}$, calculate the phase shift through the amplifier circuit for an input signal with $f = 143.3 \text{ MHz}$.

$$\text{Phase shift} = 72.4^\circ$$

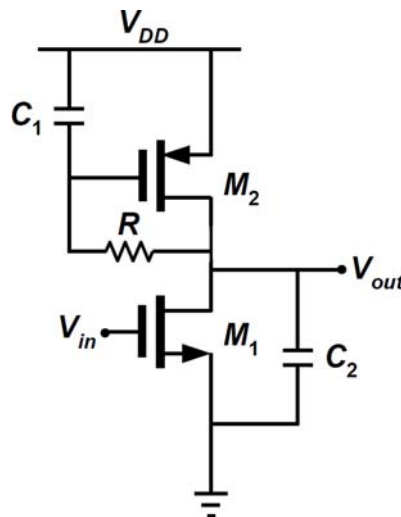


Figure 9 An amplifier schematic.

- 5) An amplifier circuit has two poles at 100 Mrad/s and 500 Mrad/s , with no zeros. Calculate the DC gain of the amplifier to get a phase margin of 90° .

$$A_0 = 2.7$$

6) Figure 10 shows a source-follower circuit. For simplicity we can ignore all parasitics. Also we assume $\lambda = 0$.

a) Determine the transfer function of the circuit.

$$H(s) = \frac{g_{m1} + sC_1(1 + g_{m1}R)}{s^2RC_1C_2 + s(g_{m1}RC_1 + C_1 + C_2) + g_{m1}}$$

b) If $g_{m1} = 1 \text{ mA/V}$, $R = 10 \text{ k}\Omega$, $C_1 = 1 \text{ pF}$ and $C_2 = 0.1 \text{ pF}$, calculate the AC gain and the phase shift through the source-follower circuit for an input frequency of 5 Grad/s .

$$A_{ac} = 0.9$$

$$\text{Phase shift} = 22.3^\circ$$

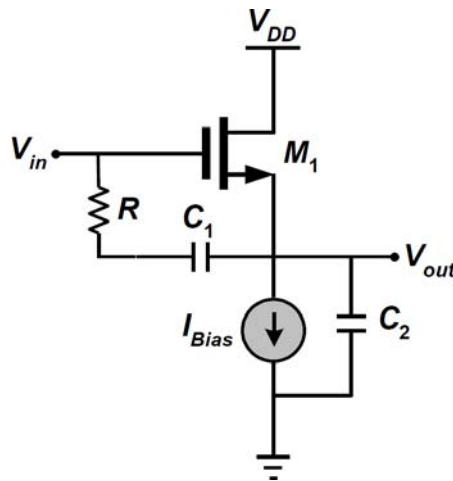


Figure 10 Source follower.