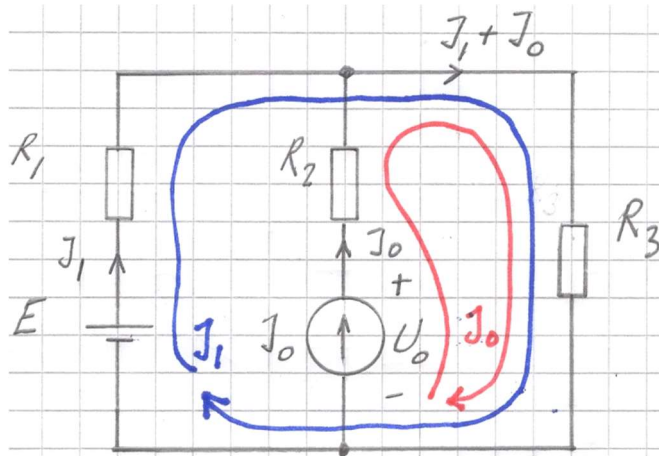


Lösningförslag till tentamen TSFS13 Elektroteknik 2022-10-20

1.




$$+E - R_1 J_1 - R_3 (J_1 + J_0) = 0 \dots (1)$$

$$+U_0 - R_2 J_0 - R_3 (J_1 + J_0) = 0 \dots (2)$$

$$(1) \rightarrow J_1 = 0$$

$$\text{INS I (2)} \rightarrow \underline{U_0 = 20 \text{ V}}$$

2a)

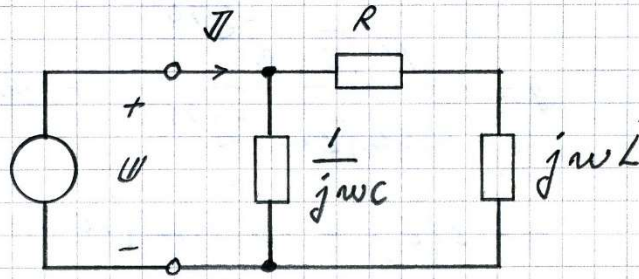

$$I = \frac{U}{Z} \dots (1)$$

$$u(t) = 10\sqrt{2} \cdot \sin(1000t - 90^\circ) \text{ V}$$

$$\rightarrow U = 10\sqrt{2} e^{-j90^\circ} \text{ V}$$

$$Z = \frac{\frac{1}{j\omega C} \cdot (R + j\omega L)}{\frac{1}{j\omega C} + (R + j\omega L)} =$$

$$= \frac{R + j\omega L}{1 + j\omega CR - \omega^2 CL} \rightarrow$$

$$Z = \frac{1000 + j1000}{1 + j - 1} =$$

$$= 1000 - j1000 = 1000\sqrt{2} \cdot e^{-j45^\circ} \Omega$$

INSÄTTNING I (1) \Rightarrow

$$\underline{I} = \frac{10\sqrt{2} \cdot e^{-j90^\circ}}{1000\sqrt{2} \cdot e^{-j45^\circ}} = 0,010 e^{-j45^\circ} \text{ A}$$

$$\Rightarrow \underline{i(t)} = \underline{10 \sin(1000t - 45^\circ) \text{ mA}}$$

b) $S = U \cdot I \dots (2)$

$$P = S \cdot \cos \varphi \dots (3)$$

$$Q = S \cdot \sin \varphi \dots (4)$$

$$\hat{U} = 10\sqrt{2} \text{ V} \Rightarrow U = 10 \text{ V}$$

$$\hat{I} = 10 \text{ mA} \Rightarrow I = \frac{10}{\sqrt{2}} \text{ mA}$$

$$\varphi = \arg U - \arg I \rightarrow$$

$$\varphi = -90^\circ - (-45^\circ) = -45^\circ$$

EFFEKTFAKTOR

$$\cos \varphi = \cos(-45^\circ) \approx \underline{\underline{0,71}}$$

$$(2) \rightarrow S = 10 \cdot \frac{10}{\sqrt{2}} \text{ mVA} \approx \underline{\underline{71 \text{ mVA}}}$$

$$(3) \rightarrow P = 71 \cdot 0,71 \text{ mW} = \underline{\underline{50 \text{ mW}}}$$

$$(4) \rightarrow Q = 71 \cdot (-0,71) \text{ mVAR} = \underline{\underline{-50 \text{ mVAR}}}$$

3a)

$$\frac{N_1}{N_2} = \frac{\hat{U}_1}{\hat{U}_2} = \frac{\hat{U}_1}{U_C + 2 \cdot 0,70}$$

$$\Rightarrow \frac{N_1}{N_2} = \frac{230\sqrt{2}}{15 + 1,4} \approx \underline{\underline{20}}$$

b)

$$U_C - R \cdot J_R - U_Z = 0 \dots (1)$$

$$P_{Z_{MAX}} = U_Z \cdot J_{Z_{MAX}} \dots (2)$$

$$(2) \Rightarrow 2,0 = 12 \cdot J_{Z_{MAX}} \Rightarrow J_{Z_{MAX}} \approx 0,17 \text{ A}$$


"
NÄR LAST SAKNAS BLIR
 J_Z MAXIMAL OCH LIKA
MED J_R .

$$(1) \Rightarrow 15 - R \cdot 0,17 - 12 = 0$$

$$\Rightarrow \underline{\underline{R = 18 \Omega}} \quad (R_{MIN})$$




c)

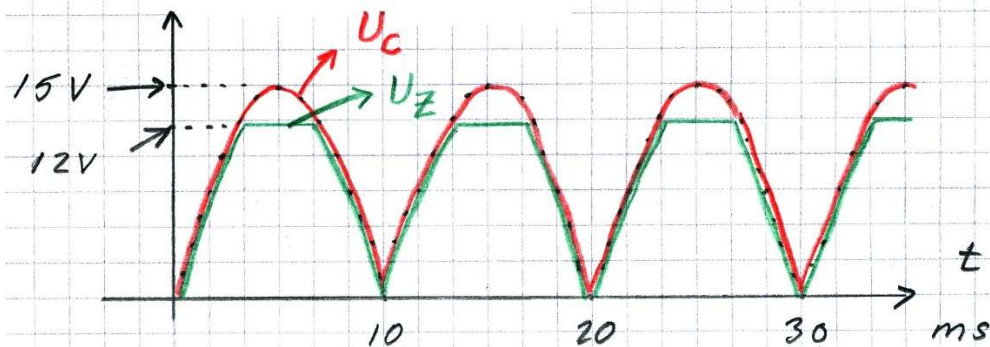TIDSDIAGRAM FÖR U_C OCH U_Z
DÅ GLÄTTNINGSKONDENSATORN
GÅTT SÖNDER.



$$\omega = 100\pi \text{ RAD/S} \quad \omega = \frac{2\pi}{T} \Rightarrow T = 20 \text{ ms}$$


4a)

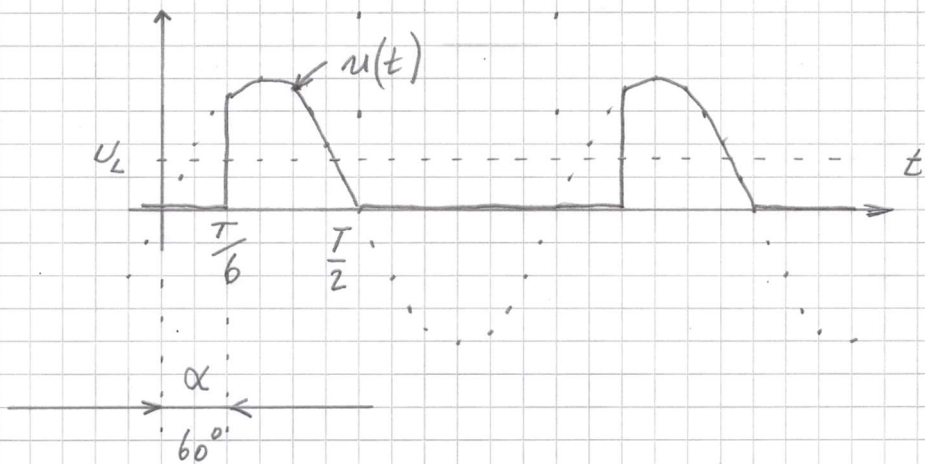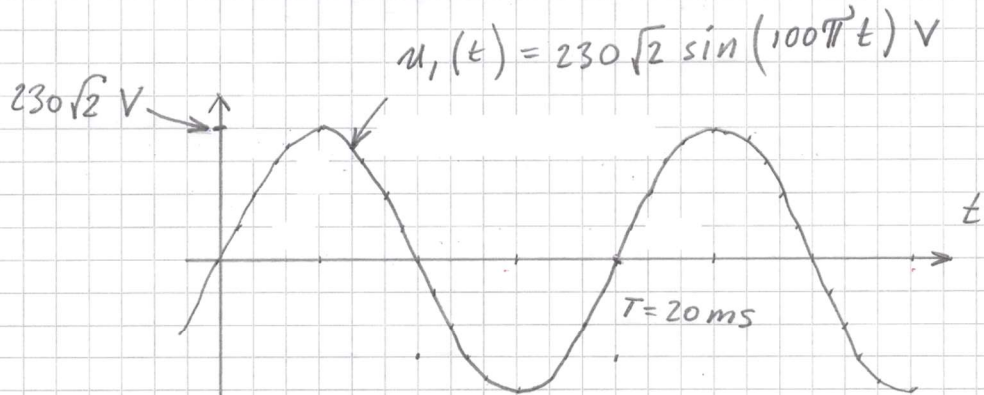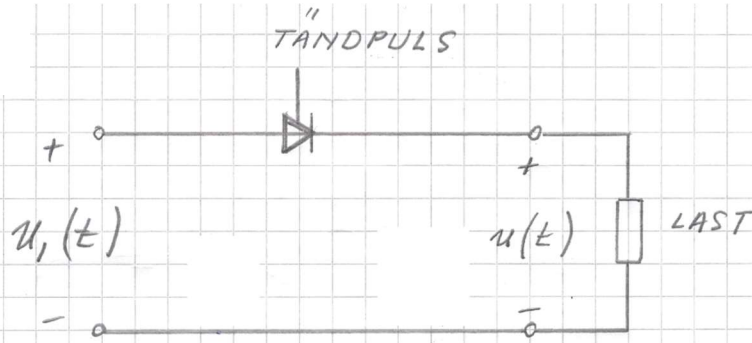

$$U_L = \frac{1}{T} \int_0^T u(t) dt = \frac{1}{T} \int_{\frac{T}{6}}^{\frac{T}{2}} u_1(t) dt = \frac{2\pi}{T} \int_{\frac{\pi}{6}}^{\frac{\pi}{2}} 230\sqrt{2} \sin(100\pi t) dt = 2\pi f$$

$$\begin{aligned}
 &= \frac{\omega}{2\pi} \int_{\frac{\pi}{3\omega}}^{\frac{\pi}{\omega}} 230\sqrt{2} \sin(\underbrace{100\pi t}_{\omega t}) dt = \\
 &= \frac{230\sqrt{2}}{2\pi} \left[\frac{-\cos(\omega t)}{\omega} \right]_{\frac{\pi}{3\omega}}^{\frac{\pi}{\omega}} = \\
 &= \frac{230\sqrt{2}}{2\pi} \left[-\cos(\pi) + \cos\left(\frac{\pi}{3}\right) \right] \approx \underline{78V}
 \end{aligned}$$

4b)

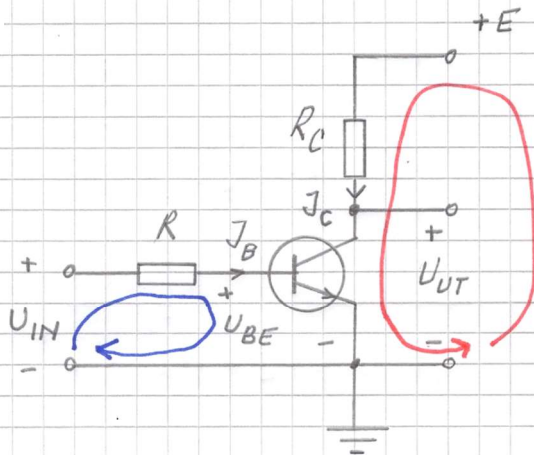

$$+E - R_C J_C - U_{UT} = 0 \dots (1)$$

$$+U_{IN} - R J_B - U_{BE} = 0 \dots (2)$$

$$U_{IN} = 5,0V \Rightarrow U_{UT} = 0 \text{ och } U_{BE} = 0,70V$$

$$(1) \rightarrow J_C = 8,0 \text{ mA}$$

$$h_{FE} = \frac{J_C}{J_B} \rightarrow J_B = 160 \mu A \text{ VÄLT } J_B = 320 \mu A$$

$$\text{INS I (2)} \rightarrow \underline{R \approx 13 \text{ k}\Omega} \text{ (13437,5)}$$

4c) Summatorkoppling med operationsförstärkare

$$u_C(t) = - \frac{R_A}{R_{F1}} (-E) - \frac{R_A}{R_{F2}} \cdot u_F(t)$$

$$4,0 + 4,0 \sin(1000t) = 2E - 5u_F(t)$$


$$\text{ALLTSÅ: } 4,0 = 2E \Rightarrow \underline{E = 2,0 \text{ V}}$$

$$4,0 \sin(1000t) = -5u_F(t)$$

$$\Rightarrow \underline{u_F(t) = -0,80 \sin(1000t) \text{ V}}$$

$$\left(\text{ELLER } u_F(t) = 0,80 \sin(1000t - 180^\circ) \text{ V} \right)$$

5. Separatmagnetiserad likströmsmotor

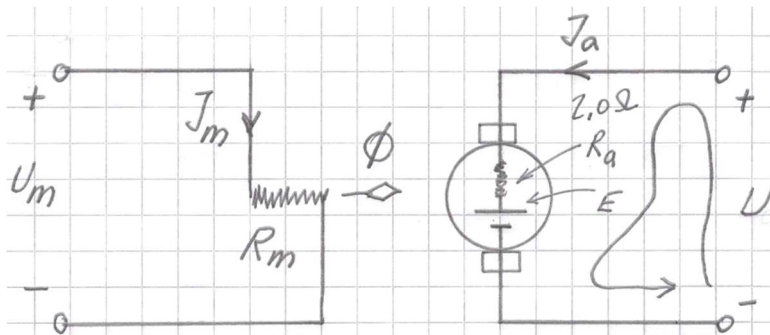

FALL I

$$U_I = 200 \text{ V}$$

$$J_{aI} = 10 \text{ A}$$

$$E_I = ?$$

$$n_I = 1000 \text{ RPM}$$

FALL II

$$U_{II} = 170 \text{ V}$$

$$J_{aII} = ?$$

$$E_{II} = ?$$

$$n_{II} = ?$$

SAMMA MOMENT OCH MAGNETISKT
FLÖDE I DE TVÅ FALLEN.

$$\begin{aligned} a) \quad M &= k_2 \Phi J_{aI} \\ M &= k_2 \Phi J_{aII} \end{aligned} \quad \Rightarrow \quad J_{aII} = J_{aI} = \underline{10 \text{ A}}$$

b) KIRCHHOFFS SPÄNNINGSLAG \Rightarrow

$$+U_I - R_a J_{aI} - E_I = 0 \quad \Rightarrow \quad \underline{E_I = 180 \text{ V}}$$

$$+U_{II} - R_a J_{aII} - E_{II} = 0 \quad \Rightarrow \quad \underline{E_{II} = 150 \text{ V}}$$

$$\frac{E_I}{E_{II}} = \frac{k_1 \Phi n_I}{k_1 \Phi n_{II}} \quad \Rightarrow \quad \underline{n_{II} = 833 \text{ RPM}}$$