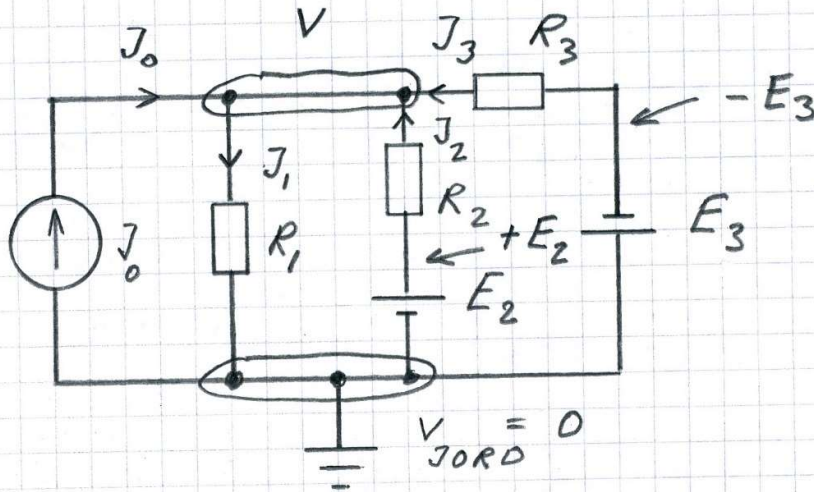


1. NODANALYS :



$$J_1 = \frac{V - 0}{R_1} \dots (1)$$


$$J_0 - J_1 + J_2 + J_3 = 0 \rightarrow$$

$$J_0 - \frac{V - 0}{R_1} + \frac{E_2 - V}{R_2} + \frac{-E_3 - V}{R_3} = 0$$

$$\rightarrow V = + 2,25 \text{ V}$$

$$\text{INS i (1)} \rightarrow \underline{\underline{J_1 = 1,5 \text{ A}}}$$

2.

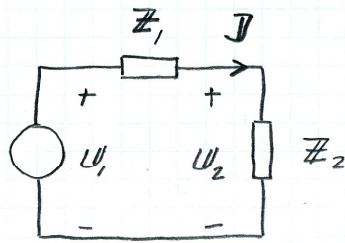

$$u_1(t) = 115\sqrt{2} \sin(120\pi t - 0^\circ) \text{ V} \Rightarrow U_1 = \underbrace{120\sqrt{2}}_{\hat{U}_1} e^{j0^\circ} \text{ V}$$

$$U_2 = 230 \text{ V} \Rightarrow \hat{U}_2 = 230\sqrt{2} \text{ V}$$

$$U_2 = U_1 \cdot \frac{Z_2}{Z_1 + Z_2}$$

$$Z_1 = \frac{1}{j\omega C} = -j \frac{1}{\omega C}$$

$$Z_2 = R + j\omega L$$

$$|U_2| = |U_1| \cdot \frac{|R + j\omega L|}{|-j \frac{1}{\omega C} + R + j\omega L|}$$

$$230\sqrt{2} = 115\sqrt{2} \cdot \frac{\sqrt{20,0^2 + (120\pi \cdot 0,127)^2}}{\sqrt{20,0^2 + \left(120\pi \cdot 0,127 - \frac{1}{120\pi \cdot C}\right)^2}}$$

$$\Rightarrow \underline{\underline{C = 84,6 \mu\text{F}}}$$

$$J = \frac{U_2}{|Z_2|}$$

$$J = \frac{230}{\sqrt{20,0^2 + (120\pi \cdot 0,127)^2}} \approx 4,43 \text{ A}$$

$$P = R \cdot J^2 \Rightarrow \underline{\underline{P = 393 \text{ W}}}$$

$$3a) U_{ut} = U_Z - U_{BE} \Rightarrow \underline{U_{ut} = 5,5 \text{ V}}$$

$$U_{CE} = U_{in} - U_{ut} \Rightarrow \underline{U_{CE} = 6,5 \text{ V}}$$

3b) Spänningsfallet mellan plus- och minusingången på OP:n är noll.

$$\Rightarrow U_{R2} = U_Z$$

$$U_{R2} = U_{ut} \cdot \frac{R_2}{R_1 + R_p + R_2}$$

$$R_p = 0 \Rightarrow$$

$$3,3 = U_{ut} \cdot \frac{2400}{7500 + 0 + 2400} \Rightarrow U_{ut} \approx 14 \text{ V} \\ (13,6 \text{ V})$$



$$R_p = 10 \text{ k}\Omega \Rightarrow$$

$$3,3 = U_{ut} \cdot \frac{2400}{7500 + 10000 + 2400} \Rightarrow U_{ut} \approx 27 \text{ V} \\ (27,4 \text{ V})$$

$$\text{ALLTSÅ } \underline{14 \text{ V} \leq U_{ut} \leq 27 \text{ V}}$$

$$3c) U_{ref} = U_{ut} \cdot \frac{R_1}{R_1 + R_2} \Rightarrow \underline{R_2 \approx 2,1 \text{ k}\Omega} \\ (2089,8 \Omega)$$

4a)

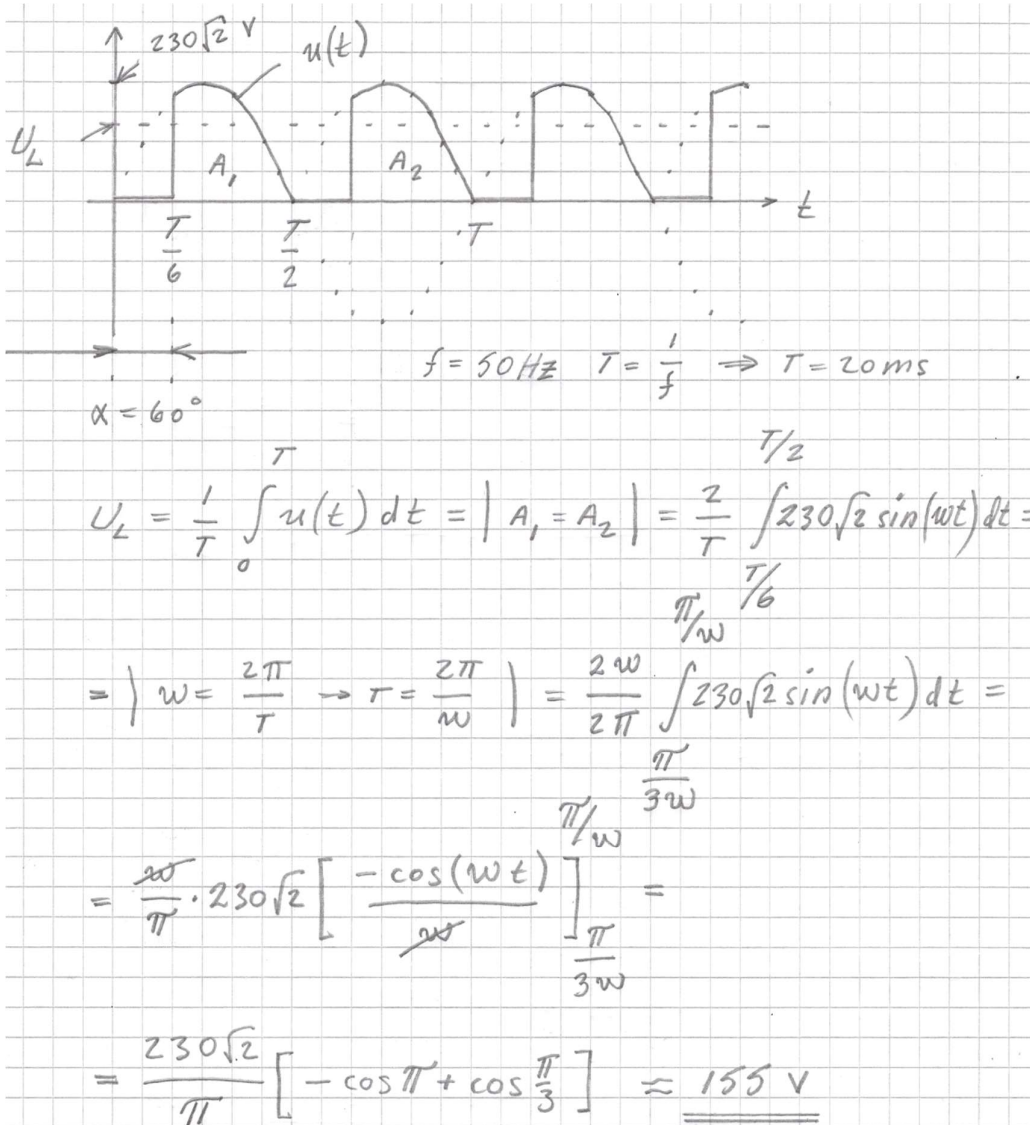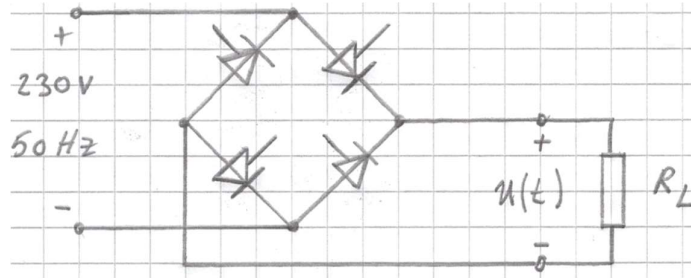

4b)

$$\alpha = \text{MAX} (180^\circ) \Rightarrow U_L = 0$$

$$\alpha = \text{MIN} (0^\circ) \Rightarrow$$

$$U_L = \frac{1}{T} \int_0^T u(t) dt = |A_1 = A_2| = \frac{1}{T} \int_0^{\frac{T}{2}} 230\sqrt{2} \sin(\omega t) dt =$$


$$= \left| \omega = \frac{2\pi}{T} \Rightarrow T = \frac{2\pi}{\omega} \right| = \frac{2\omega}{2\pi} \int_0^{\frac{\pi}{\omega}} 230\sqrt{2} \sin(\omega t) dt =$$

$$= \frac{230\sqrt{2}\omega}{\pi} \left[\frac{-\cos(\omega t)}{\omega} \right]_0^{\frac{\pi}{\omega}} =$$

$$= \frac{230\sqrt{2}}{\pi} \left[-\cos\pi + \cos 0 \right] = 207 \text{ V}$$

$$\text{ALLTSA} \quad \underline{\underline{0 \text{ V} < U_L < 207 \text{ V}}}$$

5.

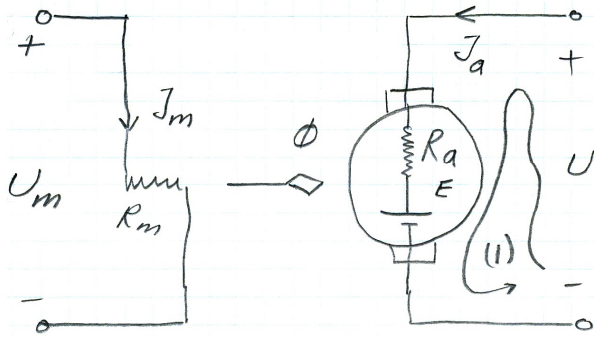

a)

FALL I

FALL II

$$U_I = 250V$$

$$U_{II} = 250V$$

$$U_{mI} = 100V$$

$$U_{mII} = 80V$$

$$\Phi_I = k J_{mI} = k \cdot \frac{U_{mI}}{R_m}$$

$$\Phi_{II} = k J_{mII} = k \cdot \frac{U_{mII}}{R_m}$$

$$\Rightarrow \Phi_{II} = 0,80 \cdot \Phi_I$$

$$M_I = k_2 \cdot \Phi_I \cdot J_{aI}$$

$$M_{II} = k_2 \cdot \Phi_{II} \cdot J_{aII}$$

$$J_{aI} = 20A$$

$$M_{II} = M_I \Rightarrow J_{aII} = 1,25 \cdot J_{aI} = 25A$$

$$n_I = 1000 \text{ RPM}$$

$$n_{II} = ?$$

$$+ U - R_a J_a - E = 0 \dots (1) \quad \text{DAR } E = k_1 \Phi n$$

$$\text{FALL I INS 1 (1)} \Rightarrow$$

$$+ 250 - 0,80 \cdot 20 - k_1 \Phi_I \cdot 1000 = 0 \Rightarrow k_1 \Phi_I = 0,234$$

$$\text{FALL II INS 1 (1)} \Rightarrow$$

$$+ 250 - 0,80 \cdot 25 - 0,234 \cdot 0,80 \cdot n_{II} = 0$$

$$\Rightarrow \underline{\underline{n_{II} = 1229 \text{ RPM}}}$$

$$b) \left. \begin{array}{l} P_2 = EJ_a \\ P_2 = M \cdot \frac{2\pi n}{60} \end{array} \right\} \rightarrow EJ_a = M \cdot \frac{2\pi n}{60} \dots (2)$$

FALL I INS 1 (2) \rightarrow

$$0,234 \cdot 1000 \cdot 20 = M_I \cdot \frac{2\pi \cdot 1000}{60}$$

$$\Rightarrow M_I \approx 45 \text{ Nm}$$

RESULTATET BLIR DETSAMMA

IFALL FALL II INS 1 (2) \rightarrow

$$0,234 \cdot 0,80 \cdot 1229 \cdot 25 = M_{II} \cdot \frac{2\pi \cdot 1229}{60}$$

$$\Rightarrow M_{II} \approx 45 \text{ Nm}$$

ALLTSÅ: DET AKTUELLA

BELASTNINGSMOMENTET ÄR 45 Nm