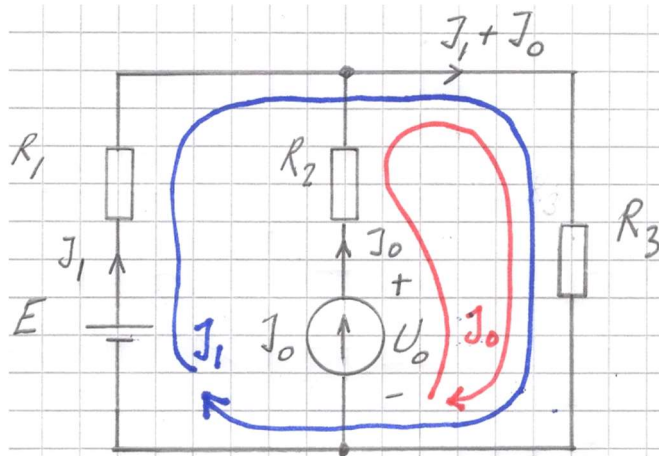


Lösningförslag till tentamen TSFS13 Elektroteknik 2024-01-02

1.




$$+E - R_1 J_1 - R_3 (J_1 + J_0) = 0 \dots (1)$$

$$+U_0 - R_2 J_0 - R_3 (J_1 + J_0) = 0 \dots (2)$$

$$(1) \rightarrow J_1 = 0$$

$$\text{INS I (2)} \rightarrow \underline{U_0 = 20 \text{ V}}$$

2a)

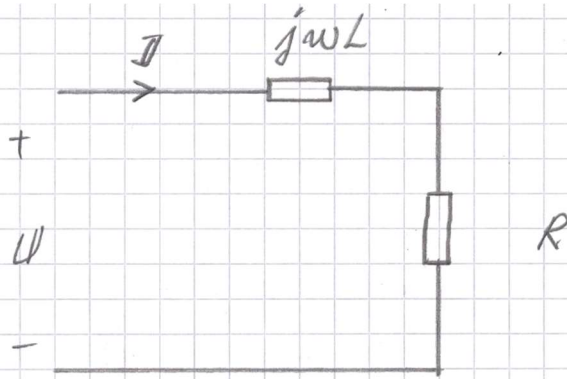

$$u(t) = 230 \sqrt{2} \sin(100\pi t + 0^\circ) \text{ V} \rightarrow U = 230 \sqrt{2} e^{j0^\circ} \text{ V}$$

$$I = \frac{U}{R + j\omega L} \Rightarrow$$

$$I = \frac{230 \sqrt{2} e^{j0^\circ}}{24,0 + j100\pi \cdot 0,0573} =$$

$$= \frac{230 \sqrt{2} e^{j0^\circ}}{\sqrt{24^2 + 18^2} \cdot e^{j \arctan \frac{18}{24}}} = 7,67 \sqrt{2} e^{-j37^\circ} \text{ A}$$

$$\rightarrow \underline{i(t) = 7,67 \sqrt{2} \sin(100\pi t - 37^\circ) \text{ A}}$$

2b)

$$I = \frac{\hat{I}}{\sqrt{2}} = 7,67 \text{ A}$$

$$P = R I^2 \Rightarrow \underline{P = 1,41 \text{ kW}}$$

(Q<sub>L</sub>)

$$Q = X_L I^2 = |X_L| = \omega L = \underline{1,06 \text{ kVAR}}$$

$$S = \sqrt{P^2 + Q^2} \Rightarrow \underline{S = 1,76 \text{ kVA}}$$

ALTERNATIVT SÄTT ATT RÄKNA :

$$P = U \cdot I \cdot \cos \varphi$$

$$(Q_L) Q = U \cdot I \cdot \sin \varphi$$

$$S = U \cdot I$$

$$\varphi = \arg U - \arg I = 37^\circ$$

↑            ↑  
0°        -37°

$$U = \frac{\hat{U}}{\sqrt{2}} = 230 \text{ V}$$

2c)

$$Q = Q_L - Q_C$$

$$Q = 0 \Rightarrow Q_C = Q_L$$

$$Q_C = \frac{U^2}{X_C} = \frac{1}{X_C} = \frac{1}{\omega C} = U^2 \omega C$$

$$1,06 \cdot 10^3 = 230^2 \cdot 100\pi \cdot C \Rightarrow \underline{C = 63,7 \mu\text{F}}$$

2d)

$$Q = 0 \Rightarrow S = P \text{ och } \cos \varphi = 1 \Rightarrow \varphi = 0^\circ$$

$$S = U \cdot I \Rightarrow 1,41 \cdot 10^3 = 230 \cdot I$$

$$\Rightarrow I = 6,13 \text{ A} \quad \hat{I} = 6,13 \sqrt{2} \text{ A}$$

$$\Rightarrow \underline{i(t) = 6,13 \sqrt{2} \sin(100\pi t) \text{ A}}$$

( $\varphi = 0^\circ$  INNEBÄR ATT  $\arg I = \arg U$ )

3a)

$$\frac{N_1}{N_2} = \frac{\hat{U}_1}{\hat{U}_2} \quad \text{DÄR} \quad \hat{U}_2 = U_c + 2 \cdot 0,70 \text{ V}$$

$$\Rightarrow \frac{N_1}{N_2} = \frac{230\sqrt{2}}{15 + 1,4} \approx 20 \quad (19,8)$$

3b)

ÖVRE LÄGET  $\Rightarrow$ 

$$U_2 = U_{ut} \cdot \frac{R_3 + R_4}{R_2 + R_3 + R_4}$$

$$5,6 = 6,6 \cdot \frac{R_3 + R_4}{30000 + R_3 + R_4} \rightarrow$$

$$R_3 + R_4 = 168000 \Omega$$

NEDRE LÄGET  $\Rightarrow$ 

$$U_2 = U_{ut} \cdot \frac{R_4}{R_2 + R_3 + R_4}$$

$$5,6 = 13,2 \cdot \frac{R_4}{30000 + 168000} \rightarrow$$

$$\underline{R_4 = 84 \text{ k}\Omega}$$

$$\rightarrow \underline{R_3 = 84 \text{ k}\Omega}$$

SPÄNNINGEN "ÄR NOLL MELLAN PLUS- OCH MINUSINGÅNGEN PÅ OPERATIONSFÖRSTÄRKAREN."

3c)

$$U_{OP} - U_{BE} = U_{ut} \rightarrow U_{OP} = U_{ut} + U_{BE}$$

↑  
0,70 V

$$U_{ut} = 6,6 \text{ V} \rightarrow U_{OP} = \underline{7,3 \text{ V}}$$

$$U_{ut} = 13,2 \text{ V} \rightarrow U_{OP} = \underline{13,9 \text{ V}}$$

3d)



$I_{R1} = I_Z$  TY STRÖMMEN IN TILL  
OP'NS PLUSINGÅNG ÄR NOLL.

$$R_1 = \frac{U_{R1}}{I_{R1}} = \frac{U_{in} - U_Z}{I_Z}$$

$$R_1 = \frac{15 - 5,6}{0,030} = 313 \Omega$$



VÄLJ  $R_1$  STRAX UNDER 313  $\Omega$

4a)

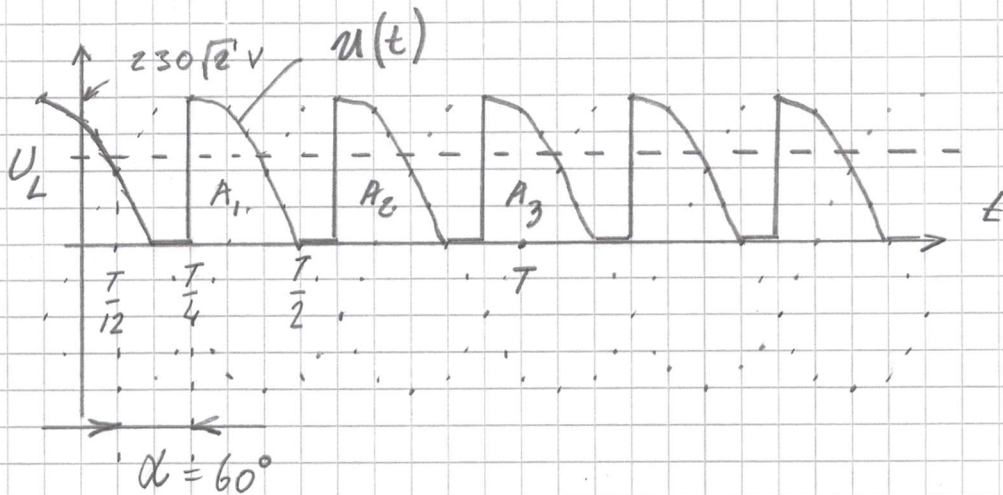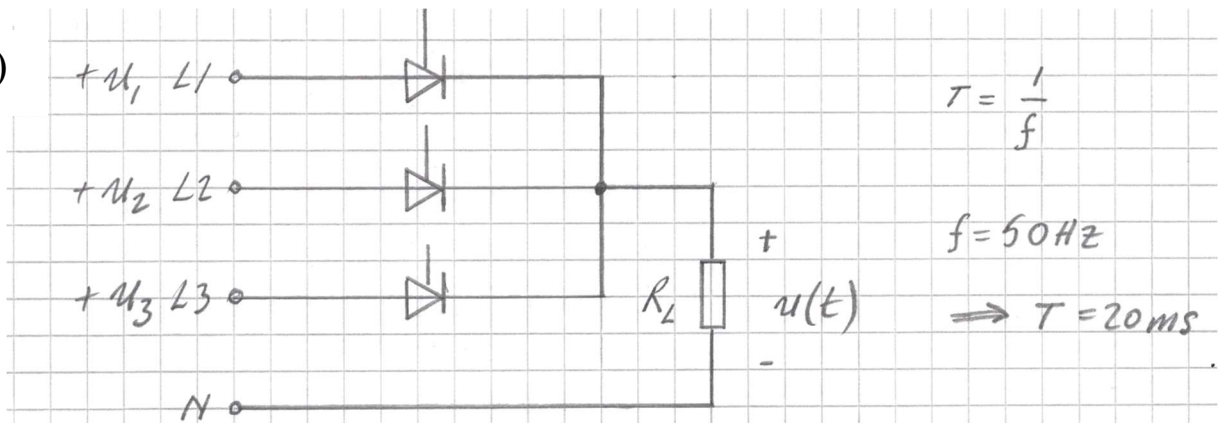

$$\begin{aligned}
 \underline{U_L} &= \frac{1}{T} \int_0^T u(t) dt = \left| A_1 = A_2 = A_3 \right| = \\
 &= \frac{3}{T} \int_{T/4}^{T/2} u(t) dt = \frac{3}{T} \int_{T/4}^{T/2} 230\sqrt{2} \sin(\omega t) dt = \\
 &= \left| T = \frac{2\pi}{\omega} \right| = \frac{3\omega}{2\pi} \cdot 230\sqrt{2} \left[ \frac{-\cos(\omega t)}{\omega} \right]_{\frac{\pi}{2}}^{\pi} = \\
 &= 155,3 \left[ -\cos\pi + \cos\frac{\pi}{2} \right] = \underline{155 \text{ V}} \quad (155,3)
 \end{aligned}$$


4b)

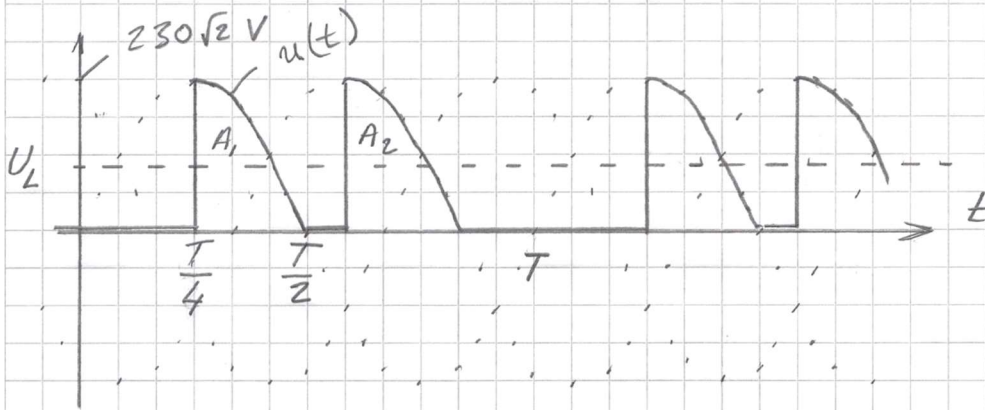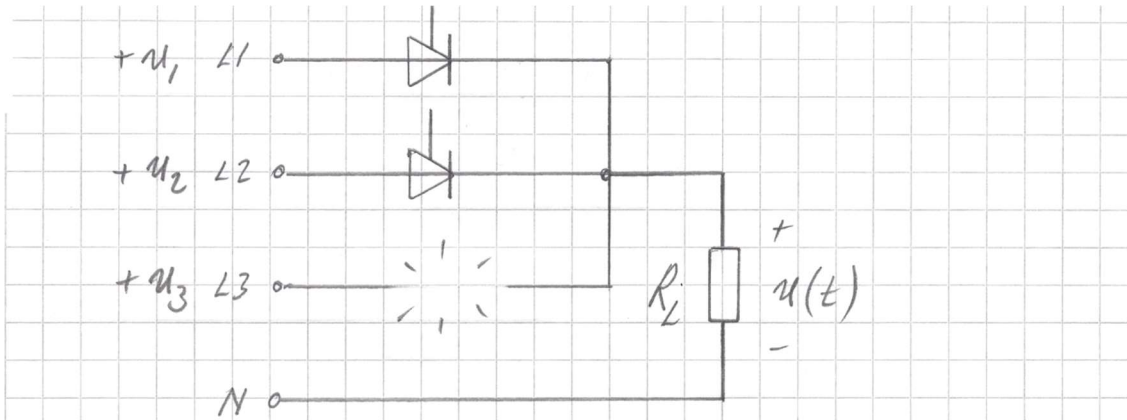

$$\underline{U_L} = \frac{1}{T} \int_0^T u(t) dt = |A_1 = A_2| = \frac{2}{T} \int_{T/4}^{T/2} u(t) dt =$$

$$= \dots \approx \underline{104 \text{ V}} \quad (103,5)$$

## 5. Separatmagnetiserad likströmsmotor

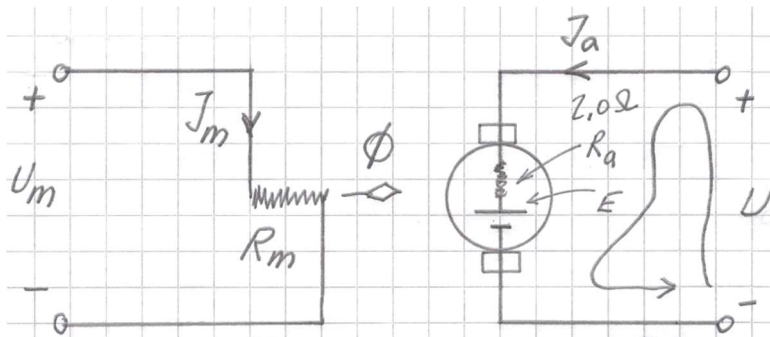

FALL I

$$U_I = 200 \text{ V}$$

$$J_{aI} = 10 \text{ A}$$

$$E_I = ?$$

$$n_I = 1000 \text{ RPM}$$

FALL II

$$U_{II} = 170 \text{ V}$$

$$J_{aII} = ?$$

$$E_{II} = ?$$

$$n_{II} = ?$$

SAMMA MOMENT OCH MAGNETISKT  
"FLÖDE" I DE TVÅ FALLEN.

$$\begin{aligned} a) \quad & M = k_2 \Phi J_{aI} \\ & M = k_2 \Phi J_{aII} \end{aligned} \quad \Rightarrow \quad J_{aII} = J_{aI} = \underline{10 \text{ A}}$$

b) KIRCHHOFFS SPÄNNINGSLAG  $\Rightarrow$

$$+U_I - R_a J_{aI} - E_I = 0 \quad \Rightarrow \quad \underline{E_I = 180 \text{ V}}$$

$$+U_{II} - R_a J_{aII} - E_{II} = 0 \quad \Rightarrow \quad \underline{E_{II} = 150 \text{ V}}$$

$$c) \quad \frac{E_I}{E_{II}} = \frac{k_1 \Phi n_I}{k_1 \Phi n_{II}} \quad \Rightarrow \quad \underline{n_{II} = 833 \text{ RPM}}$$