



Lecture 7, ANIK

Operational amplifiers 2

What did we do last time?



Operational amplifiers

Top-level aspects

Compensation

Phase margin, stability, etc.

What will we do today?



Operational amplifiers continued

Circuit-level aspects

Implementation details

Operational amplifiers, revisited

Operational transconductance amplifier (OTA)

Drive capacitive load, typically on-chip

Operational amplifiers (OP)

Drive resistive load, typically off-chip


Specifications

Differential input, opt. differential output

Infinite gain

Infinite input impedance

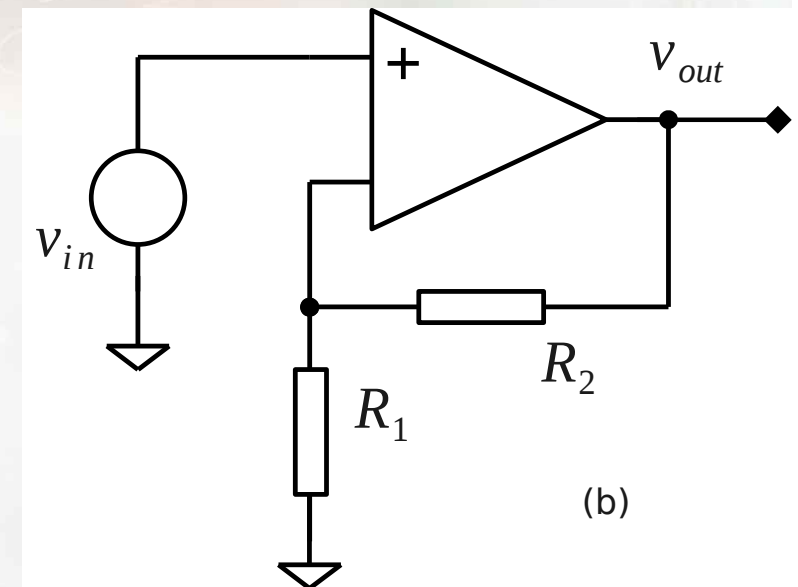Infinite (OTA) / Zero (OP) output impedance



Always used in feedback (otherwise it is a comparator)!

Why do you want controlled feedback?

Gain is now under control!


No variation with g_m/g_{ds} , instead it is given by passive components

"Unlimited" drive capability

Isolation of input and output

Linearization

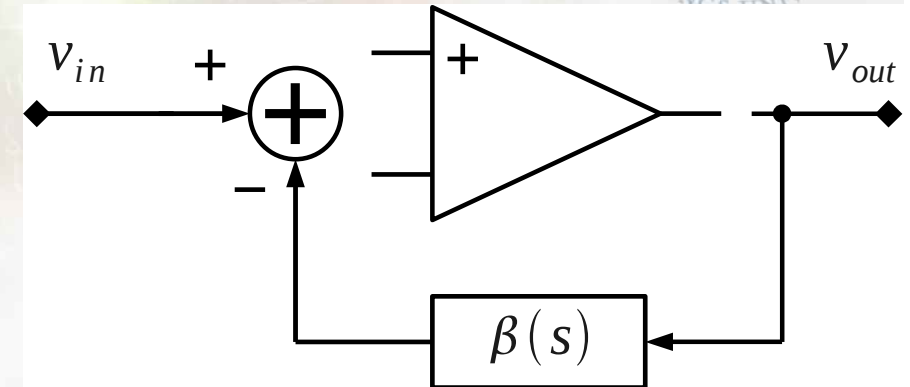Remember, it is a regulation loop. It is designed to track the changes, anything added in the loop will be suppressed.



Operational amplifier architectures



Telescopic

Two-stage

Folded-cascode

Current-mirror

Essentially just cascaded stages

Telescopic OTA




Stack many cascodes on top of each-other and use gain-boosting, etc.

Omitted, since it is not applicable for modern processes.

The swing is eaten up.

Two-stage OP/OTA

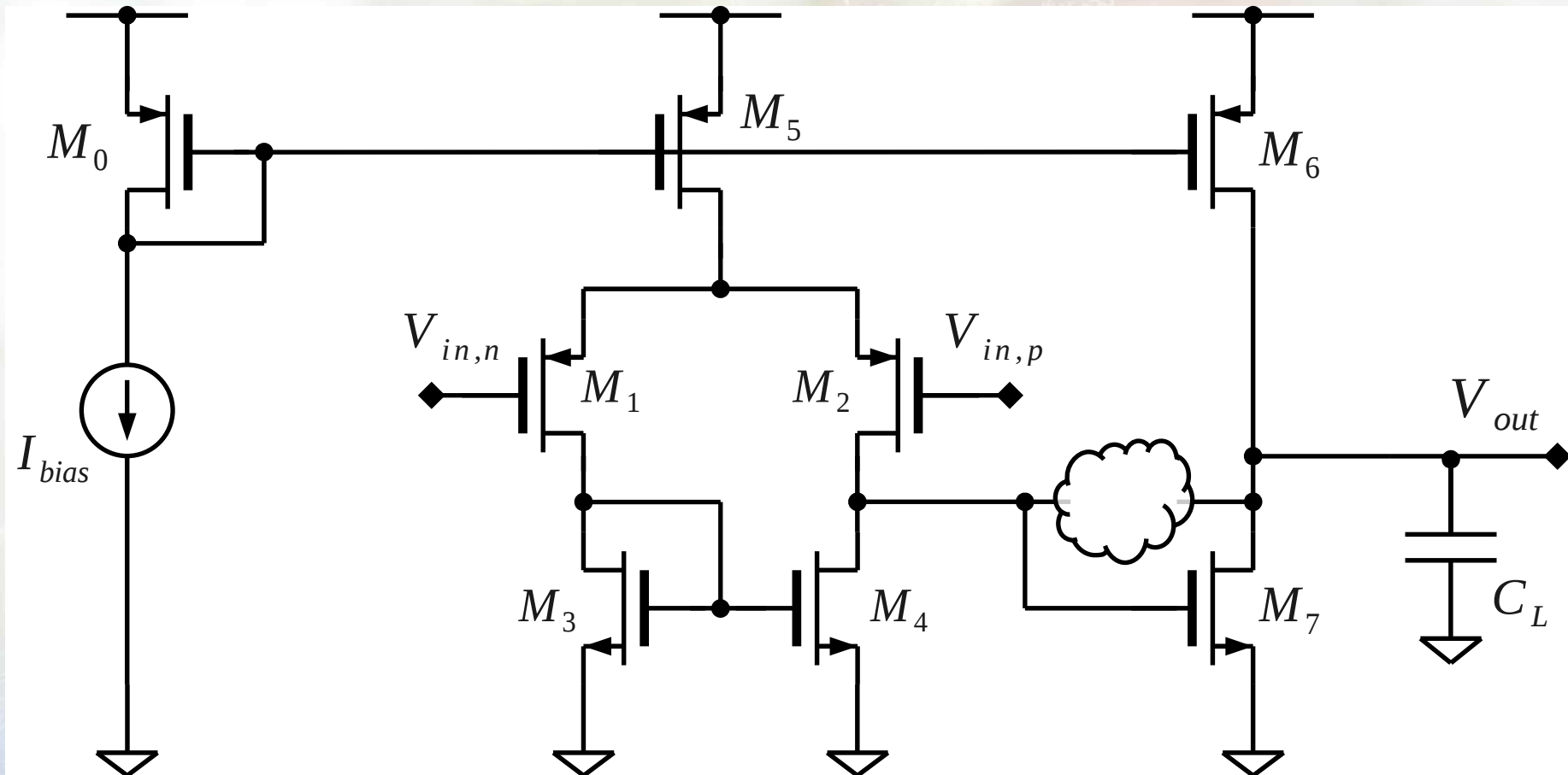

Two-stage OP, how it works




Gain

Transconductance
Impedances


Swing

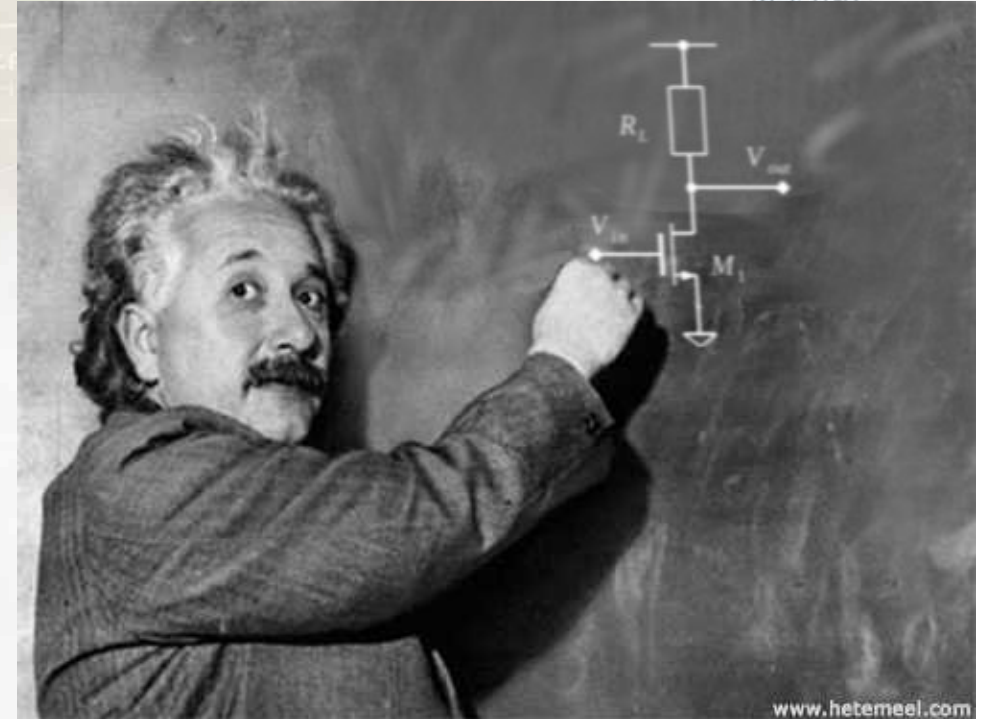Common-mode range
Output range
Input range



www.hetemeel.com

Current-mirror OP/OTA

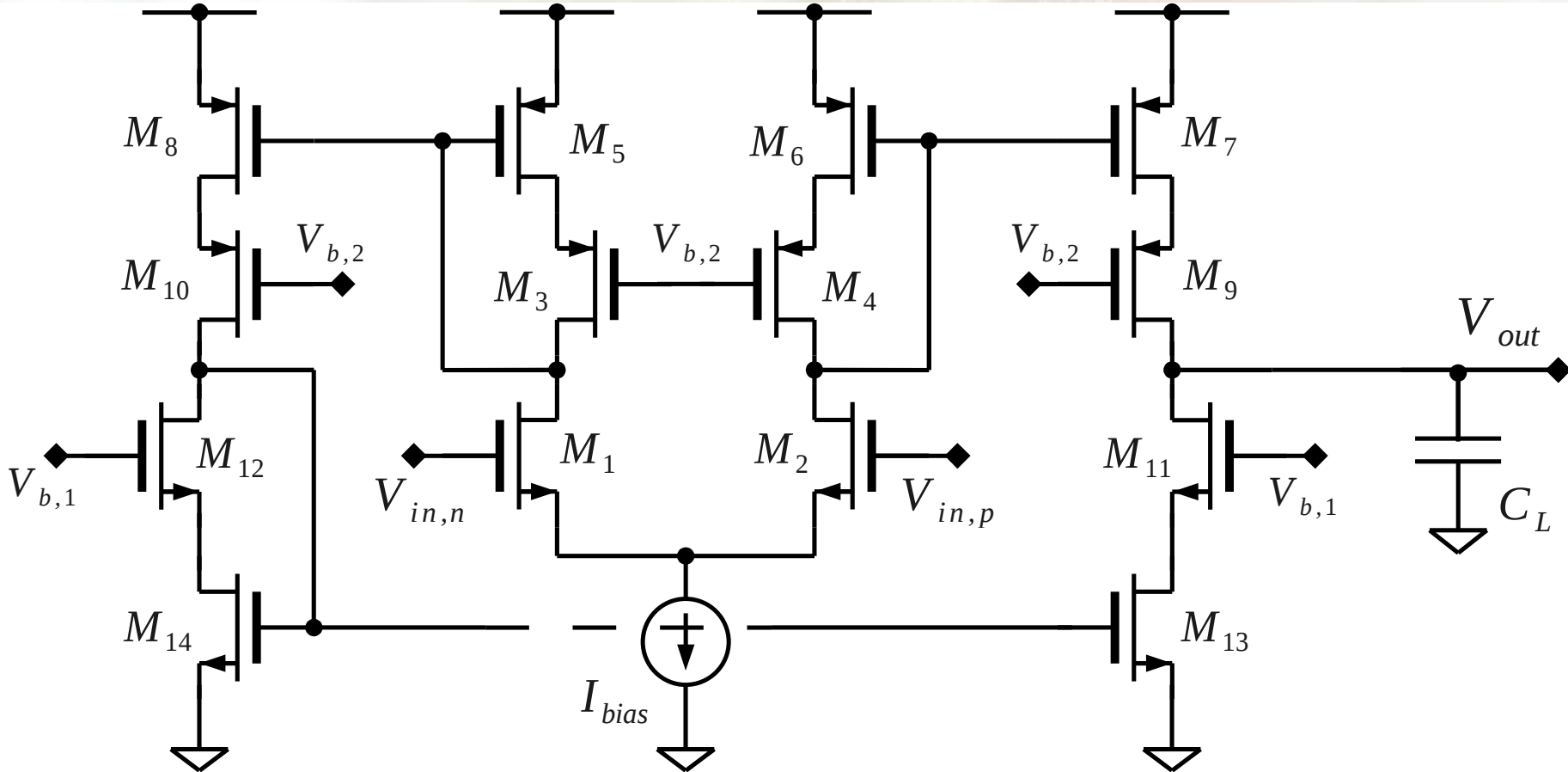

Current-mirror OP/OTA, how it works




Gain

Transconductance
Impedances


Swing

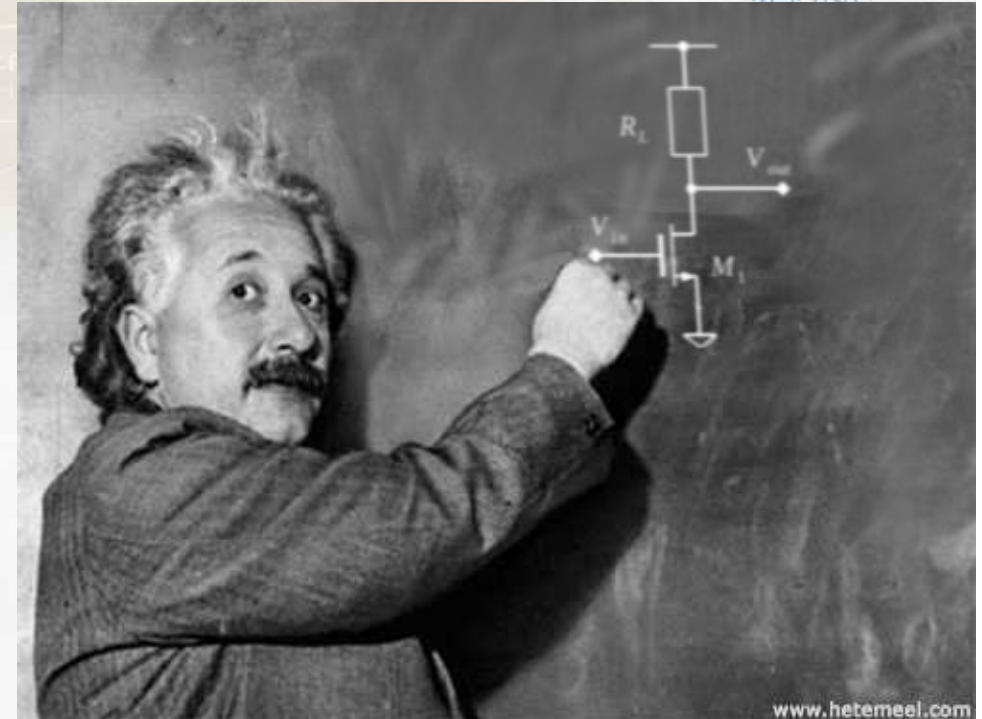Common-mode range
Output range
Input range



www.hetemeel.com



Folded-cascode OP/OTA

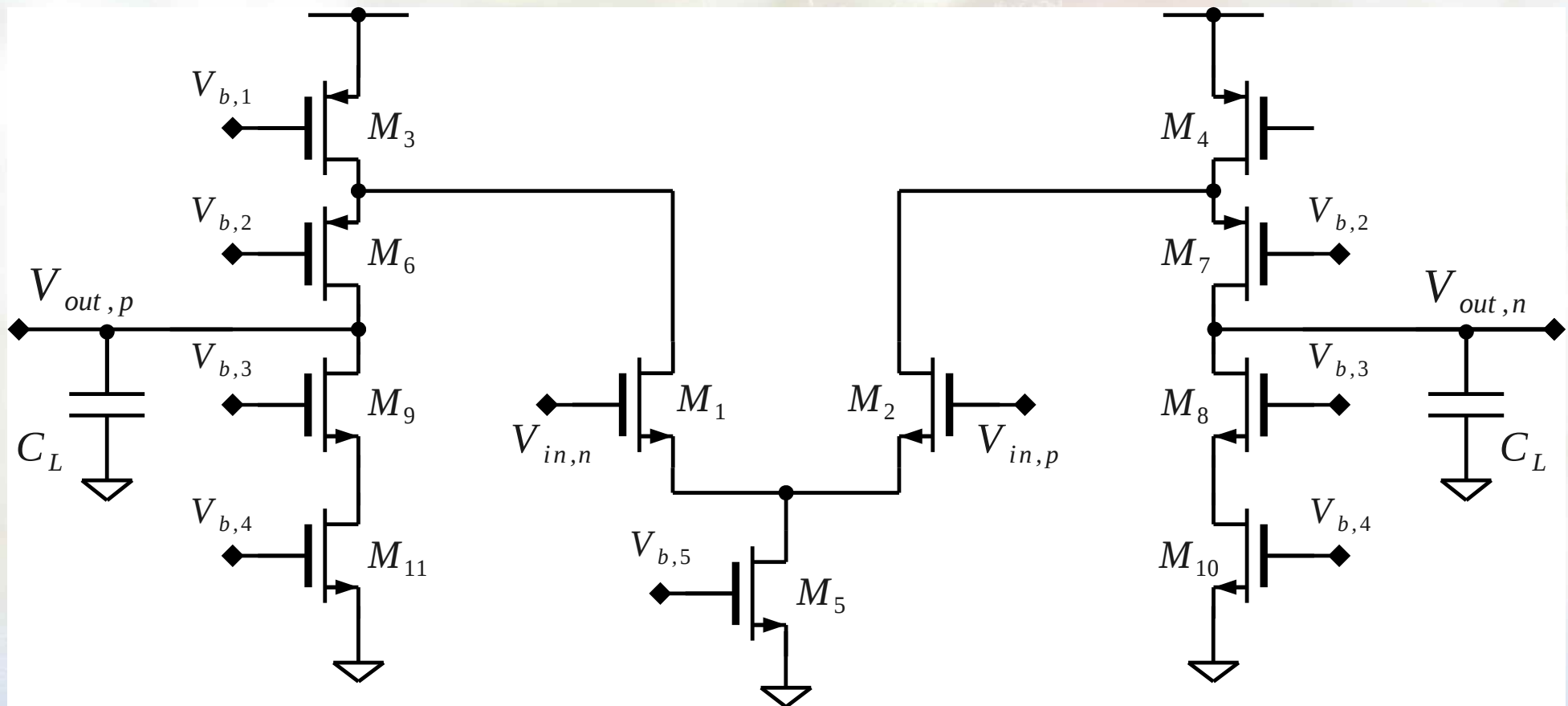

Why folded-cascode?

Consider the CMR in buffer configuration

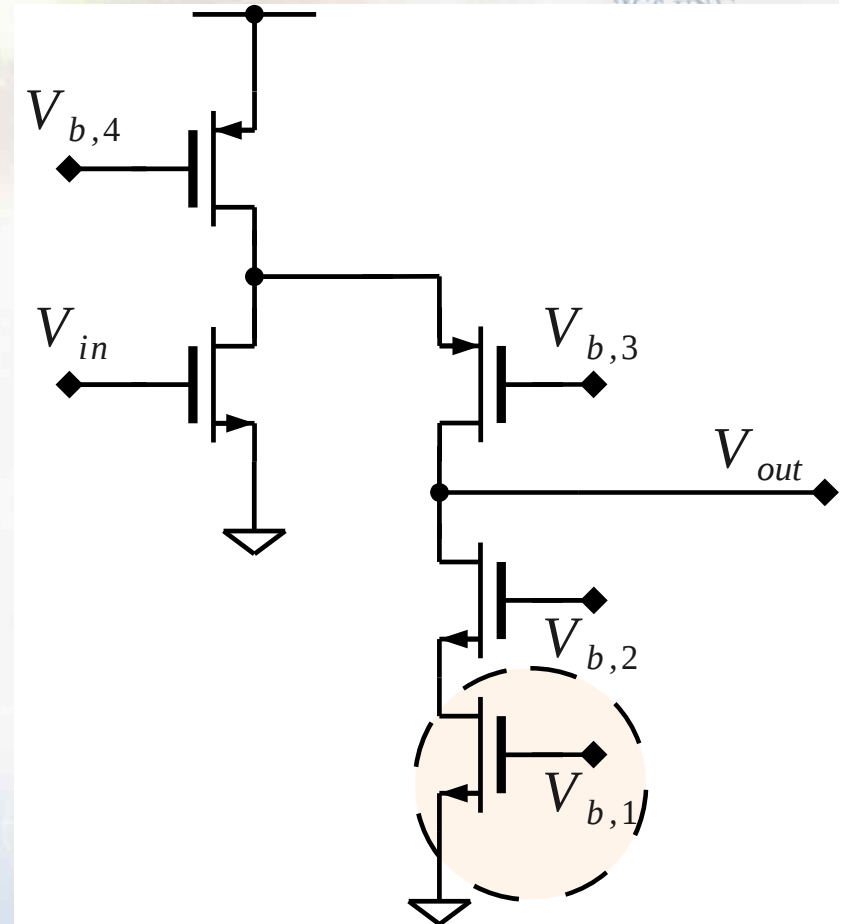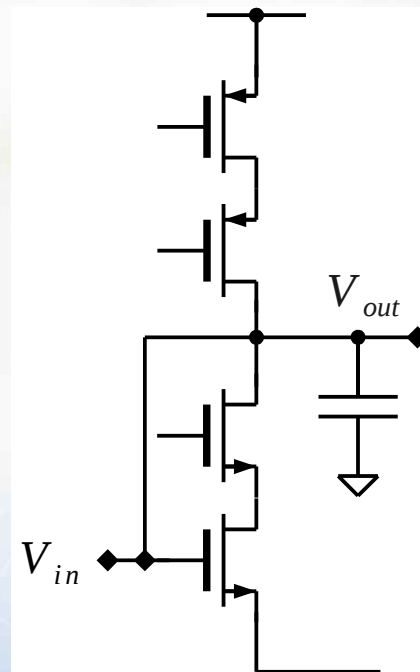In telescopic OTA, the swing will be very small since bias transistor "locks" the voltage level



Folded-cascode, how it works




Gain

Transconductance
Impedances

Swing

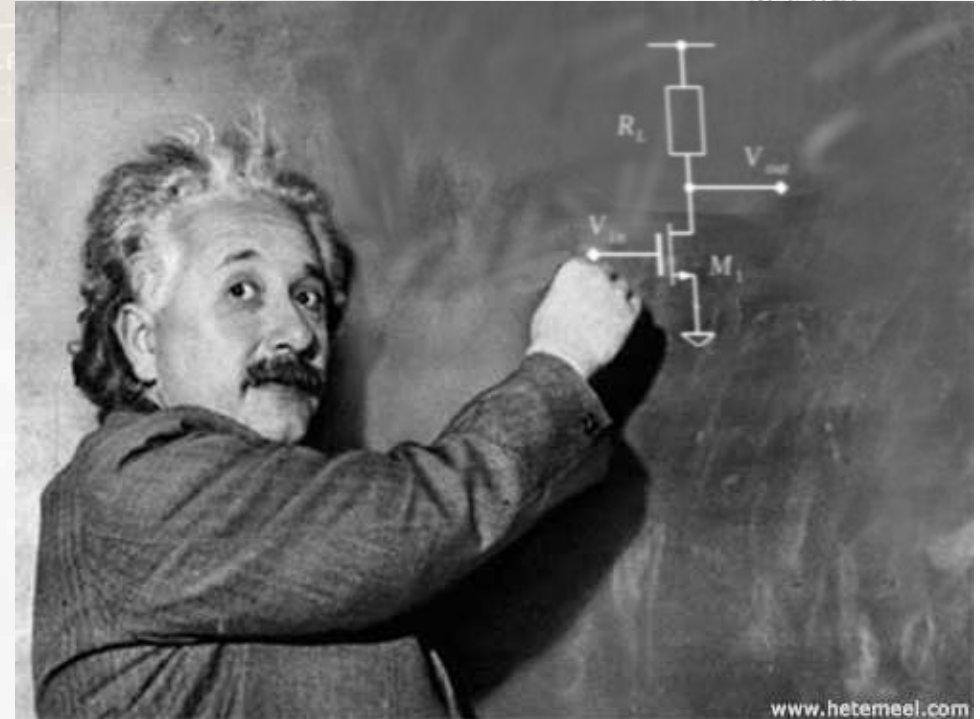Common-mode range
Output range
Input range



Other practical concerns wrt. current




Feedback with resistors

An OP given with a certain current drive capability.

What is the maximum swing?

What is the DC level?

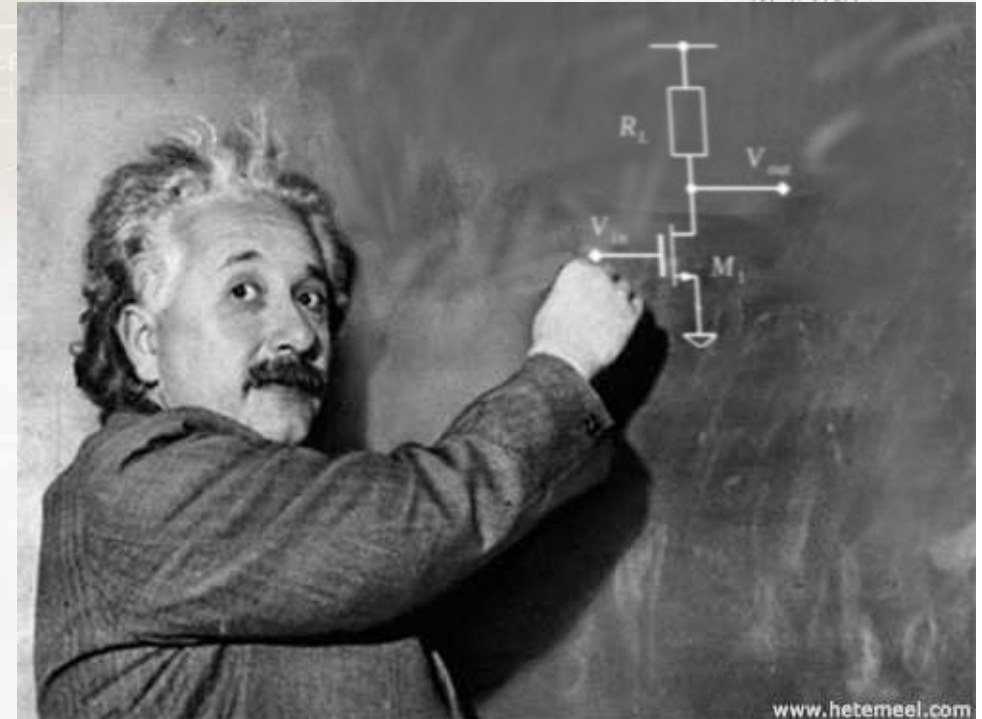

Other practical concerns wrt. bandwidth




Various unwanted effects

Limited gain

Offset error

Bandwidth

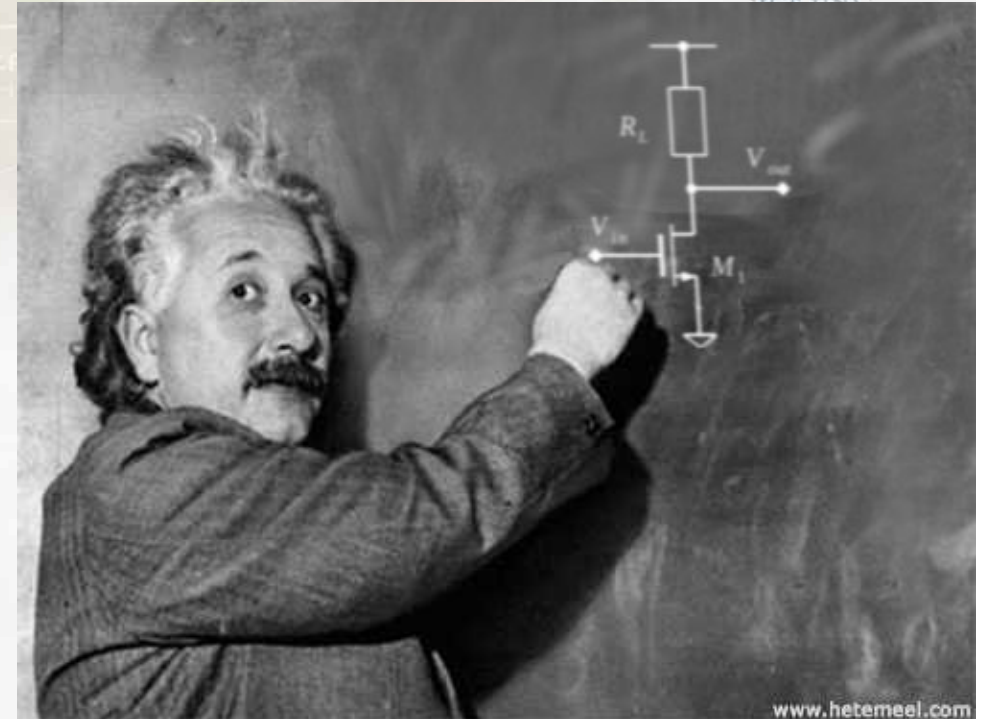

www.hetemeel.com

OP/OTA Compilation



Cookbook recipes

Hand-outs with step-by-step explanation of the design of OP/OTAs

http://www.es.isy.liu.se/courses/ANIK/download/opampRef/ANTIK_0NNN_LN_opampHandsouts_A.pdf

Compensation techniques

http://www.es.isy.liu.se/courses/ANIK/download/opampRef/ANTIK_0NNN_LN_opampCompensationTable_A.pdf

What did we do today?



Operational amplifiers

Circuit-level aspects

Simulation aspects

Some terminology

Some top-level tips-and-tricks

What will we do next time?

Noise

Circuit noise

Thermal noise

Flicker noise

Distortion

What sets the (non)linearity in our CMOS devices?



Lecture 8, ANIK

Noise and distortion