



Lecture 3, Opamps

Operational amplifiers, high-gain, high-speed

What did we do last time?

Multi-stage amplifiers

Increases gain

Increases number of poles

Frequency domain

Stability

Phase margin

What will we do today?

Wrap-up the discussion on compensation and stability

Two-stage amplifiers

Three compensation methods

Operational amplifiers

Characteristics

Operation

The problem: Stability, cont'd

Bode plot

What happens to the transfer characteristics?

Phase margin


Feedback factor

Step response

Settling


Oscillations

Critically damped at 70 degrees

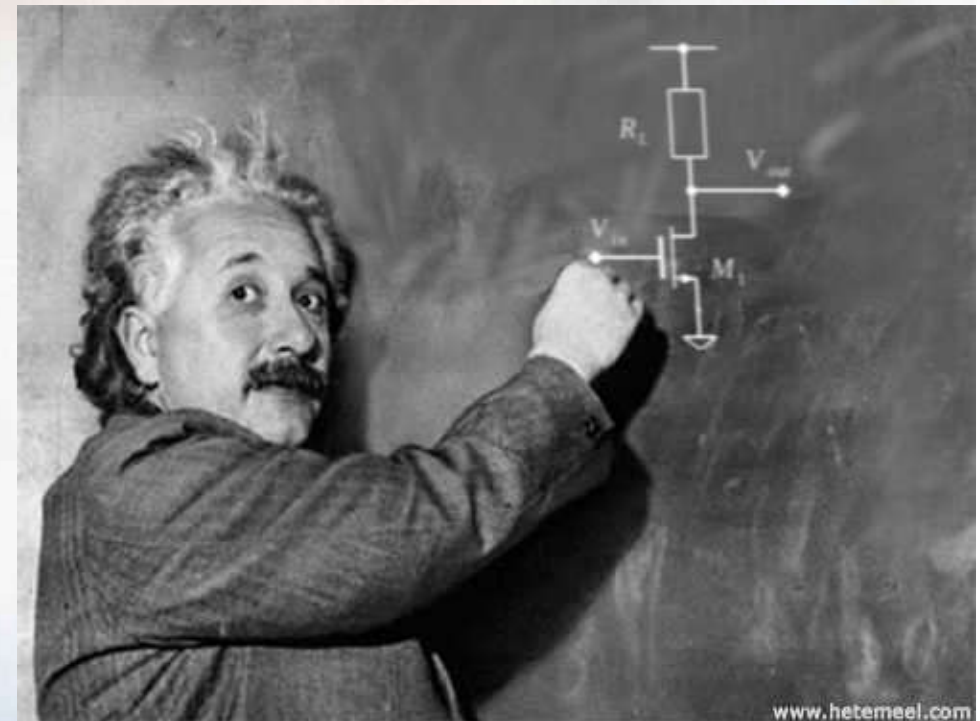

We need to be a bit more systematic

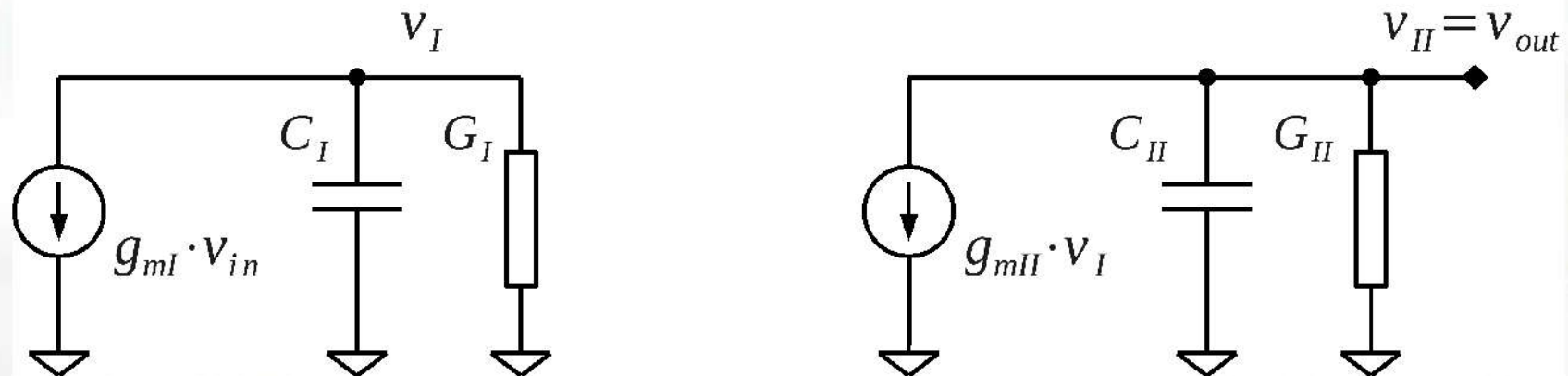One model (high-impedance load) and focus on two-pole



$$p_1 = \frac{G_I}{C_I}, \quad p_2 = \frac{G_{II}}{C_{II}}, \quad A_1 = \frac{g_{mI}}{G_I}, \quad A_2 = \frac{g_{mII}}{G_{II}}$$

Dominant pole assumption (output)

Assuming pole splitting, $p_2 \gg p_1$, gives us

$$A(s) = \frac{A_1 \cdot A_2}{\left(1 + \frac{s}{p_{11}}\right) \cdot \left(1 + \frac{s}{p_{12}}\right)} \approx \frac{A_1 \cdot A_2}{1 + \frac{s}{p_1} + \frac{s^2}{p_1 \cdot p_2}}$$

This implies: $\omega_{ug} \approx A_1 \cdot A_2 \cdot p_1$ and

$$\phi_m = 180 - \arg A(j\omega_{ug}) = 180 - \operatorname{atan} \frac{\omega_{ug}}{p_1} - \operatorname{atan} \frac{\omega_{ug}}{p_2} \approx 90 - \operatorname{atan} \frac{\omega_{ug}}{p_2}$$

$$\phi_m \approx 90 - \operatorname{atan} \left(A_0 \cdot \frac{p_1}{p_2} \right)$$

The formulas (dominant load!)

Unity-gain frequency


$$\omega_{ug} \approx \frac{g_{mI} \cdot g_{mII}}{G_I \cdot G_{II}} \cdot \frac{G_{II}}{C_{II}} = \frac{g_{mI} \cdot g_{mII}}{G_I \cdot C_{II}}$$

Phase margin

$$\phi_m \approx 90 - \operatorname{atan} \frac{\omega_{ug}}{p_2} = 90 - \operatorname{atan} \frac{\frac{g_{mI} \cdot g_{mII}}{G_I \cdot C_{II}}}{\frac{G_I}{C_I}} = 90 - \operatorname{atan} \frac{g_{mI} \cdot g_{mII} \cdot C_I}{G_I^2 \cdot C_{II}}$$

etc., etc., etc. -- We need to be a bit more organized...


Compensation, poles are too close

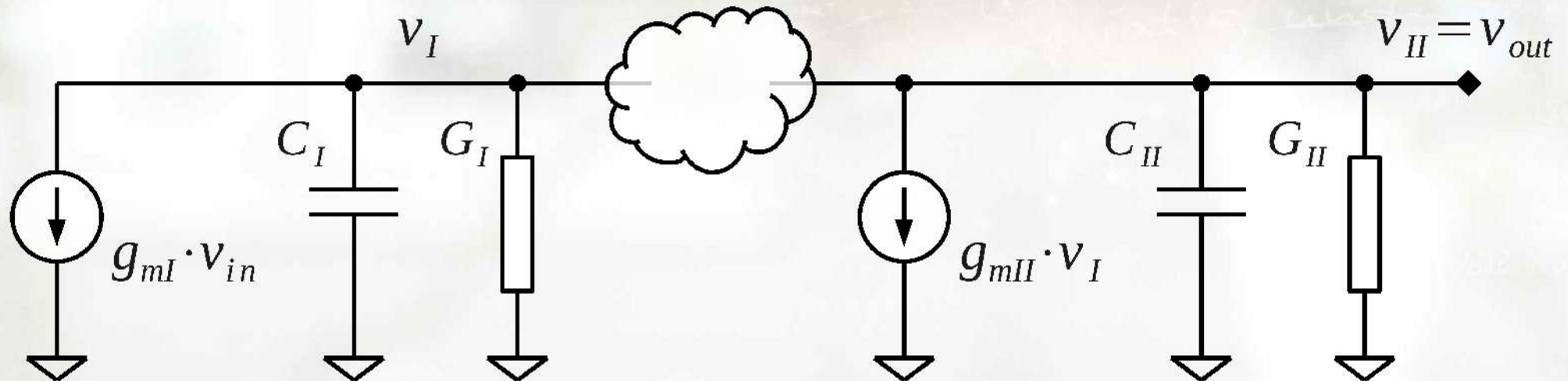

The "cloud" could be a capacitor or series resistor-capacitor.


Poles and zeros 1

Stable?

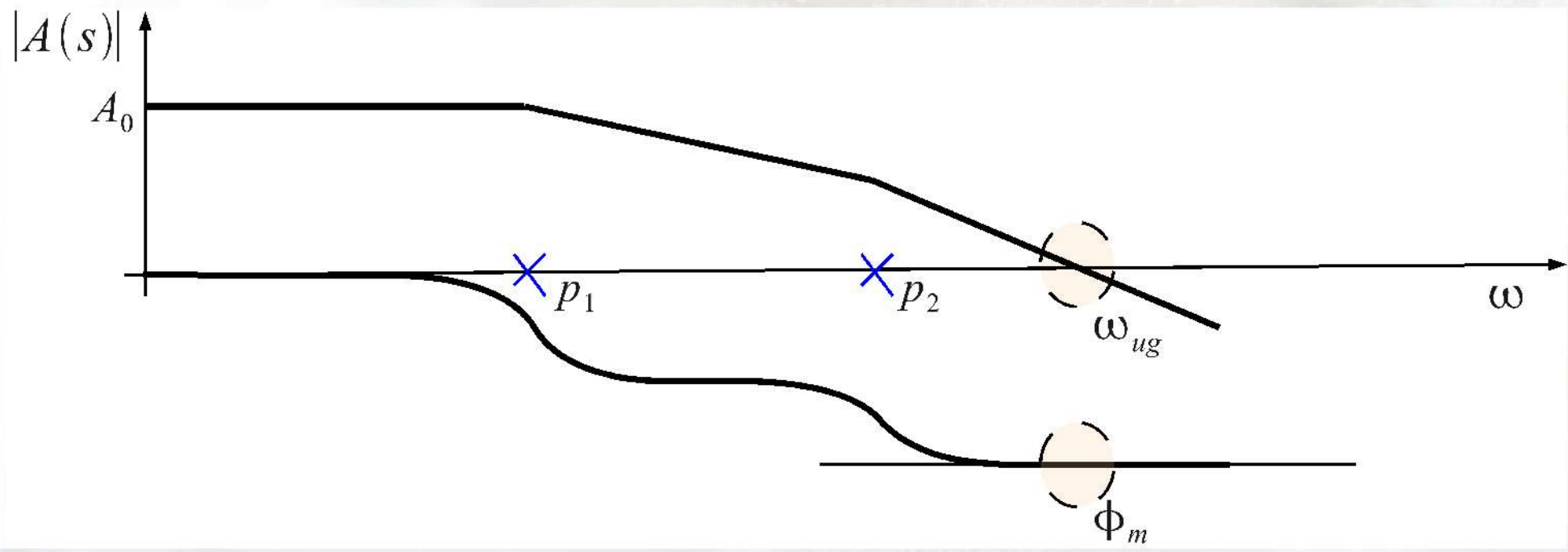


Poles and zeros 2

Stable?

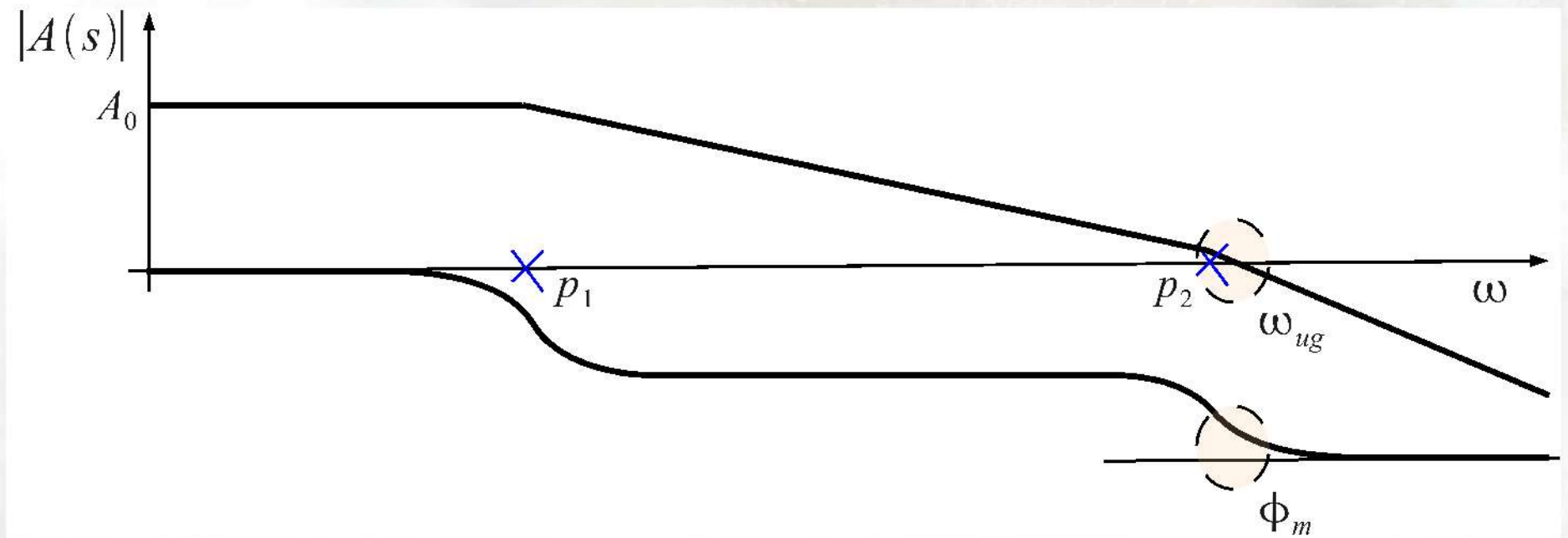

Compensation

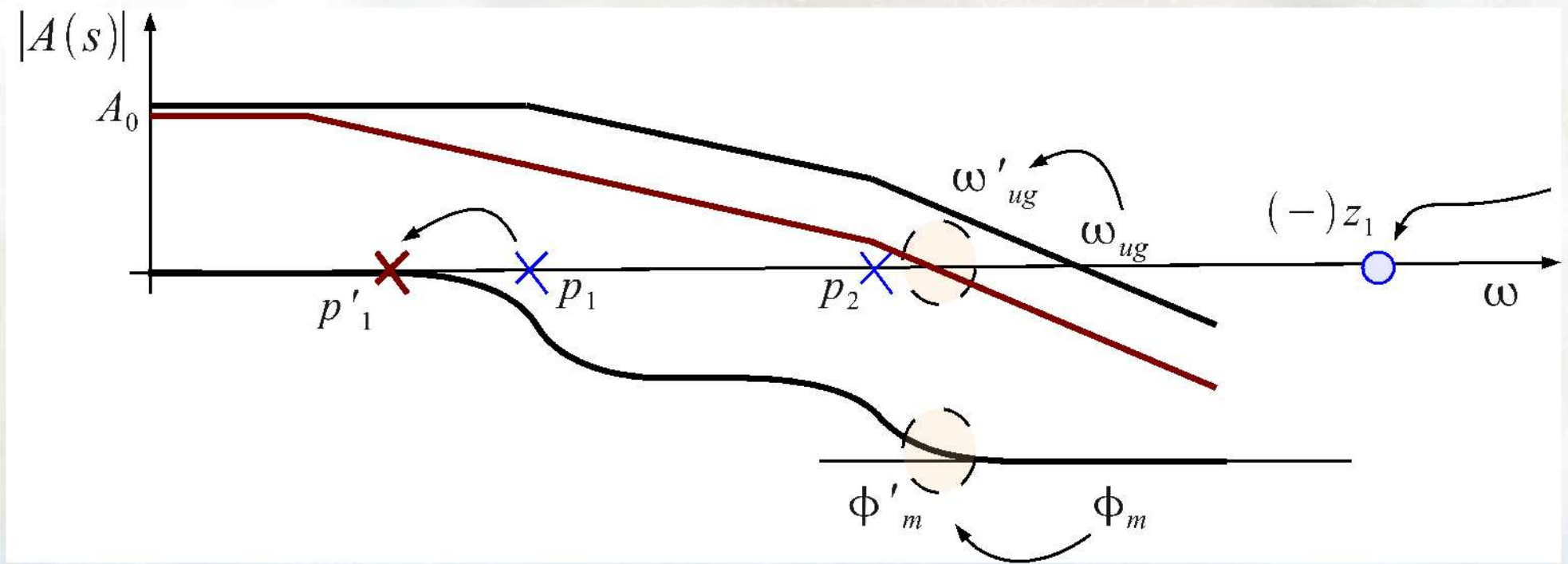What is the cost associated with compensation?



Compensation, two cases:

1) "Internal" node sees a low-impedance node

Typically: output load dominates, drive a capacitive load

Load-compensation, i.e., increase cap externally

2) "Internal" node sees a high-impedance node

Typically: internal load dominates, drive a resistive load

Miller-compensation, i.e., utilize the second-stage gain to multiply C_C

As always, some exceptions to the rule:



Nested compensation, active compensation, ... and more ...

Compensation compiled:



Miller

Load compensation

Cap

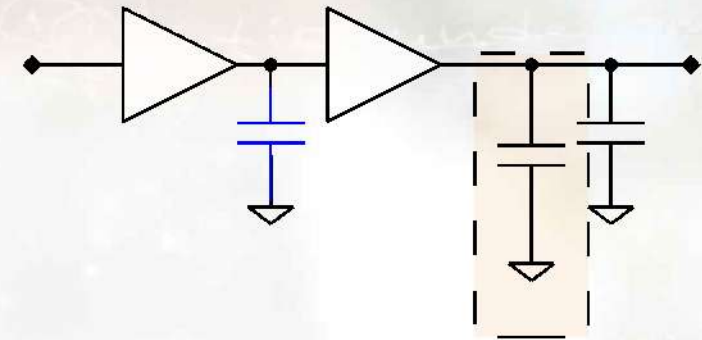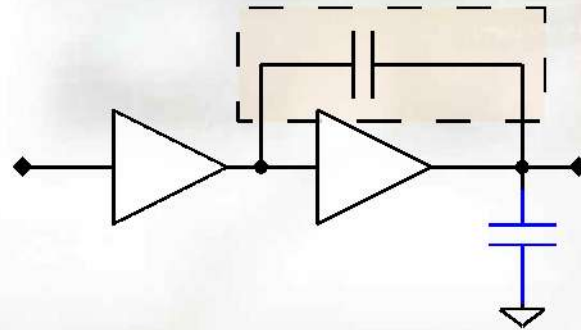

Cap + Res

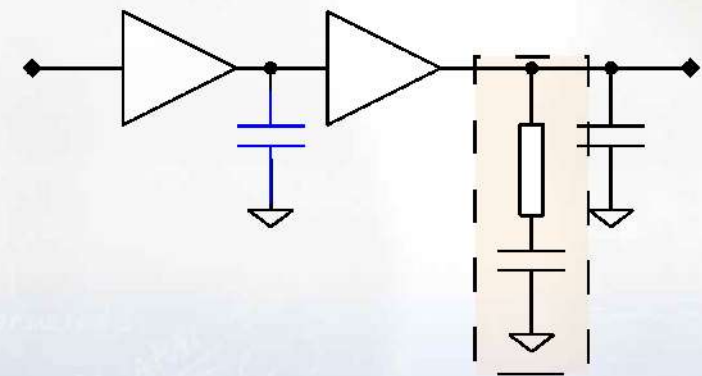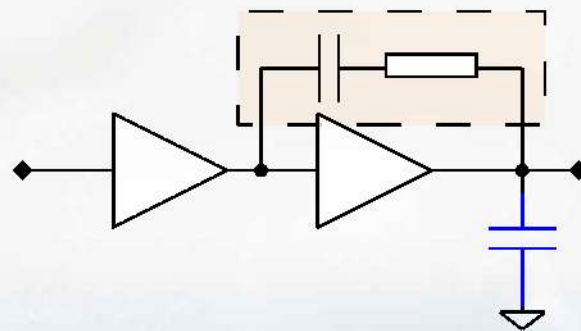

Compensation, Miller capacitance

Introduced zero	Parasitic pole	Dominant pole	Unity-gain
$z_1 = \frac{g_{mII}}{C_C}$	$p_2 = \frac{-g_{mII}}{C_{II}}$	$p_1 = \frac{-G_I \cdot G_{II}}{g_{mII} \cdot C_C}$	$\omega_{ug} = \frac{g_{mI}}{C_C}$

Introduced zero	Parasitic pole	Phase margin
$z_1 \approx 10 \cdot \omega_{ug}$	$p_2 \approx 2.2 \cdot \omega_{ug}$	≈ 60

Dominant pole moves "down", parasitic pole moves "up"

Parasitic zero added (harmful for phase margin)

Compensation, Nulling resistor 1

Introduced zero	Parasitic poles	Dominant pole	Unity-gain
$z_1 = \frac{g_{mII}}{C_C} \cdot \frac{1}{1 - R_Z \cdot g_{mII}}$	$p_2 = \frac{-g_{mII}}{C_{II}}, p_3 = \frac{-1}{R_Z \cdot C_{II}}$	$p_1 = \frac{-G_I \cdot G_{II}}{g_{mII} \cdot C_C}$	$\omega_{ug} = \frac{g_{mI}}{C_C}$

$$R_Z = \frac{1}{g_{mII}} \cdot \left(1 + \frac{C_{II}}{C_C} \right)$$

Introduced zero	Parasitic pole	Phase margin
$z_1 \rightarrow p_2$	$p_3 \approx 1.73 \cdot \omega_{ug}$	≈ 60

Compensation, Nulling resistor 2

Introduced zero	Parasitic poles	Dominant pole	Unity-gain
$z_1 = \frac{g_{mII}}{C_C} \cdot \frac{1}{1 - R_Z \cdot g_{mII}}$	$p_2 = \frac{-g_{mII}}{C_{II}}, \quad p_3 = \frac{-1}{R_Z \cdot C_{II}}$	$p_1 = \frac{-G_I \cdot G_{II}}{g_{mII} \cdot C_C}$	$\omega_{ug} = \frac{g_{mI}}{C_C}$

$$R_Z = \frac{1}{g_{mII}}$$

Introduced zero	Parasitic pole	Phase margin
$z_1 \rightarrow \infty$	$p_2 \approx 1.73 \cdot \omega_{ug}, \quad p_3 > 10 \cdot \omega_{ug}$	≈ 60

Rule-of-thumb for hand-calculation

Use e.g. MATLAB to support calculations for understanding

```
/site/edu/es/ANTIK/antikLab/m/antikPoleZero.m
```

```
/site/edu/es/ANTIK/antikLab/m/antikSettling.m
```

In the end, use the simulator.

It has to be robust over temperature and other variations.

Hand calculations are incorrect per definition

Model corresponds quite well with circuit once you have identified the different stages

See for example exercises


Operational amplifiers

Operational amplifiers (OP)

drive resistive loads

have zero output impedance, zero input impedance, infinite gain

act like a voltage source

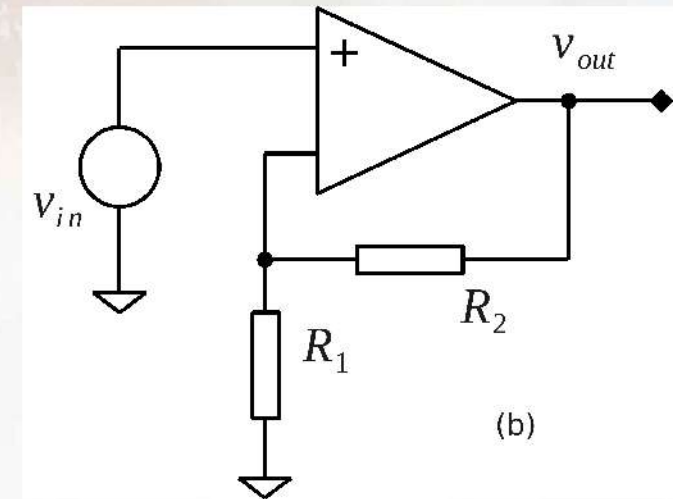

Operational transconductance amplifiers (OTA)

drive capacitive loads

have infinite output impedance, zero input impedance, infinite gain

act like a current source

Why do you want controlled feedback?

Gain is now under control!


No variation with g_m/g_{ds} , instead it is given by passive components

"Unlimited" drive capability

Isolation of input and output

Linearization

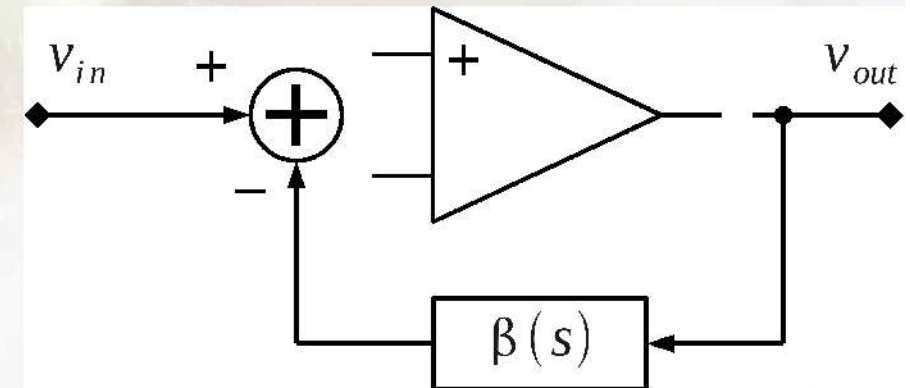Remember, it is a regulation loop. It is designed to track the changes, anything added in the loop will be suppressed.



Practical concerns

Limited gain


Open-loop gain vs. closed-loop gain

Bandwidth

Speed

Offset error

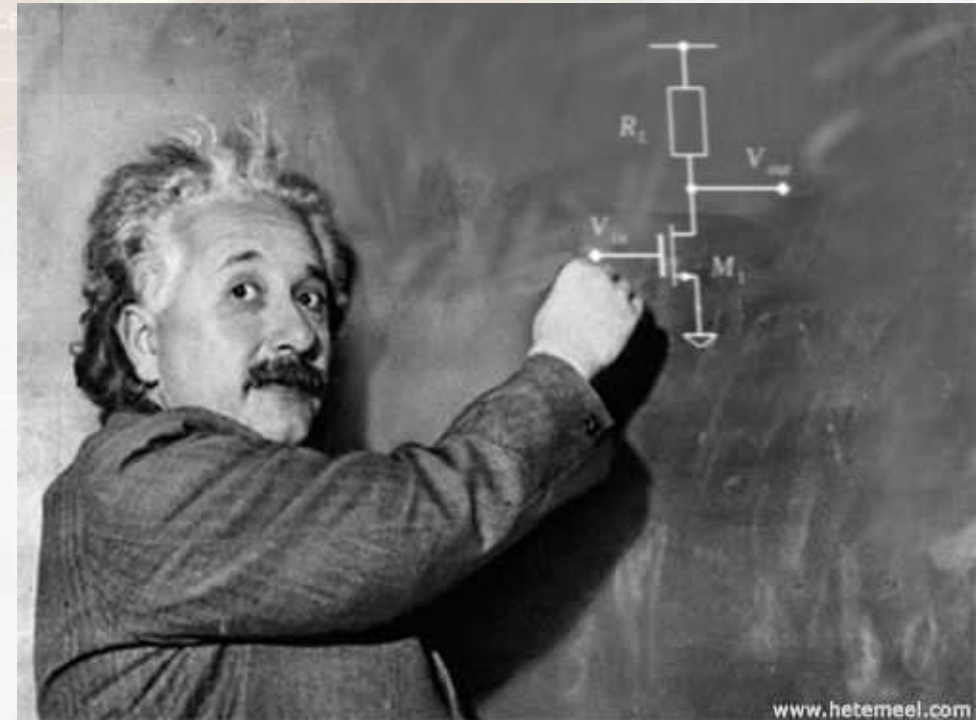
Mismatch will cause an offset -
how do we handle this?



Limited gain

Ideal case:
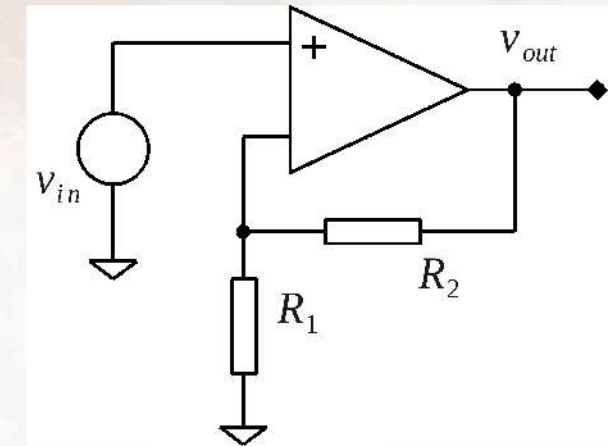
$$\frac{R_1}{R_1 + R_2} \cdot v_{out} = v_{in} \Rightarrow \frac{v_{out}}{v_{in}} = \frac{R_1 + R_2}{R_1} = \Gamma$$



Non-ideal gain case:

$$v_{out} = A_0 \cdot \left[v_{in} - \frac{R_1}{R_1 + R_2} \cdot v_{out} \right] \Rightarrow \frac{v_{out}}{v_{in}} = \frac{1}{\frac{1}{A_0} + \frac{R_1}{R_1 + R_2}} =$$


$$= \frac{R_1 + R_2}{R_1} \cdot \frac{1}{1 + \frac{R_1 + R_2}{A_0 \cdot R_1}} = \frac{\Gamma}{1 + \frac{\Gamma}{A_0}}$$

Bandwidth

Single-pole (ignore effect of impedance):

$$\frac{V_{out}}{V_{in}} = \frac{\Gamma}{1 + \frac{\Gamma}{A_0} \cdot \left(1 + \frac{s}{p_1}\right)}$$
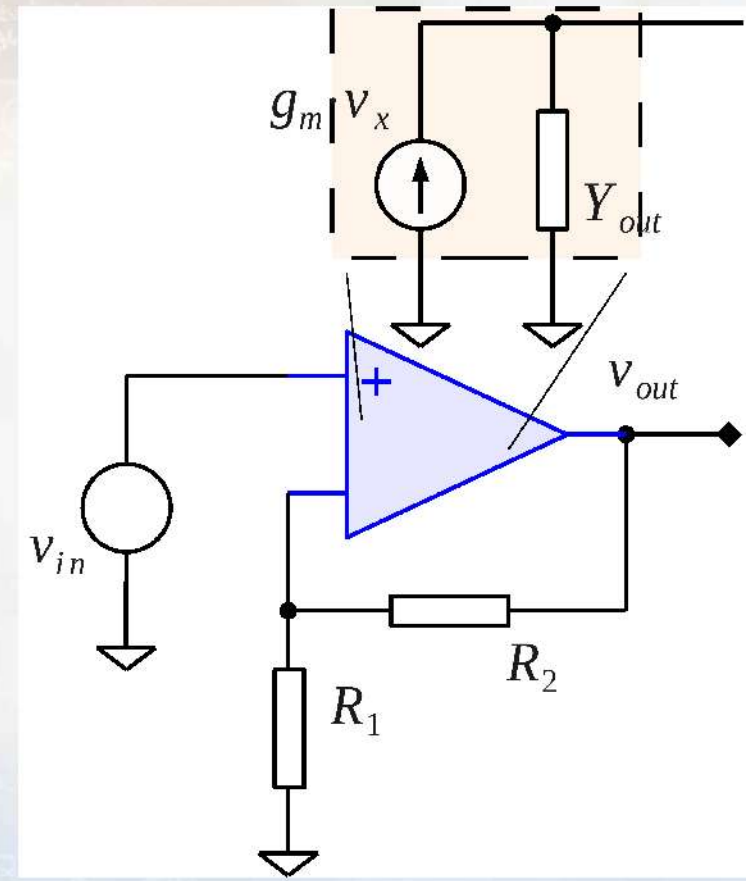
$$\frac{V_{out}}{V_{in}} = \frac{\frac{\Gamma}{1 + \Gamma/A_0}}{1 + \frac{\Gamma/A_0 \cdot s}{1 + \Gamma/A_0} \cdot \frac{1}{p_1}} \approx \frac{\Gamma}{1 + \frac{s}{p_1 \cdot A_0/\Gamma}}$$



The amplifier will band-limit the system!


More detailed model

$$v_x = \frac{R_1}{R_1 + R_2} \cdot v_{out}$$

$$g_m (v_{in} - v_x) + (0 - v_{out}) Y_{out} + \frac{0 - v_{out}}{R_1 + R_2} = 0$$

$$g_m v_{in} = v_{out} \cdot \left[Y_{out} + \frac{1 + R_1 g_m}{R_1 + R_2} \right]$$
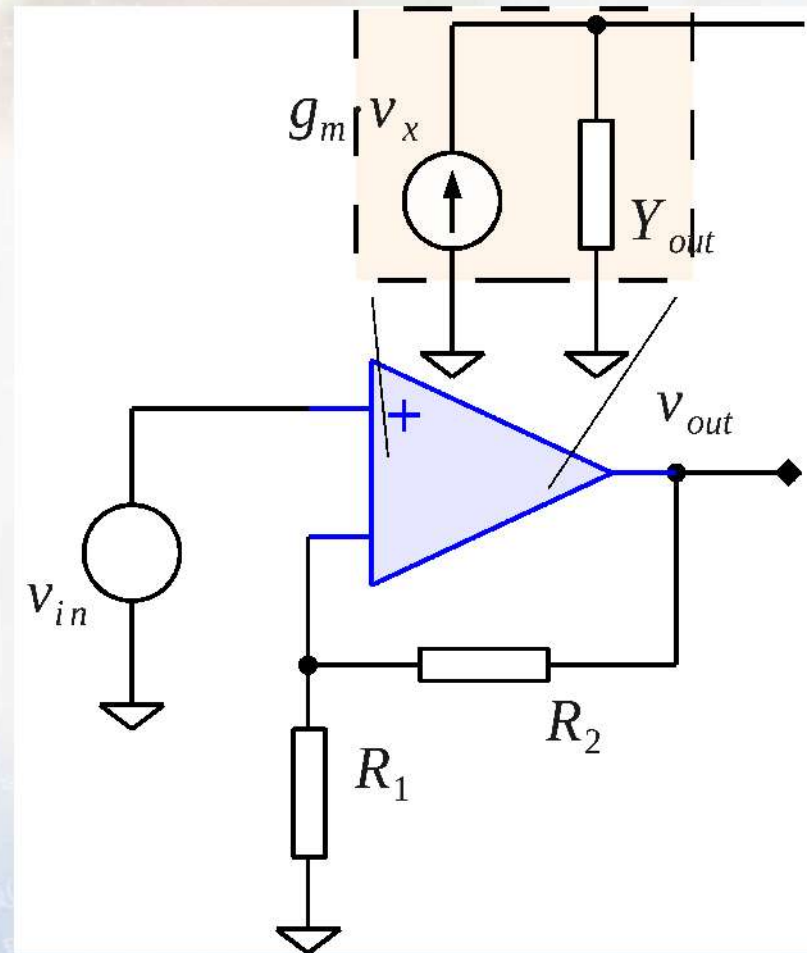
$$\frac{v_{out}}{v_{in}} = \frac{\Gamma}{1 + \frac{1}{g_m R_1} + \frac{\Gamma}{g_m / Y_{out}}}, \text{ etc., etc.}$$




Other practical concerns wrt. current

Feedback with resistors

An OP given with a certain current drive capability will put requirements on the resistor sizes

What is the maximum swing?

What is the DC level?

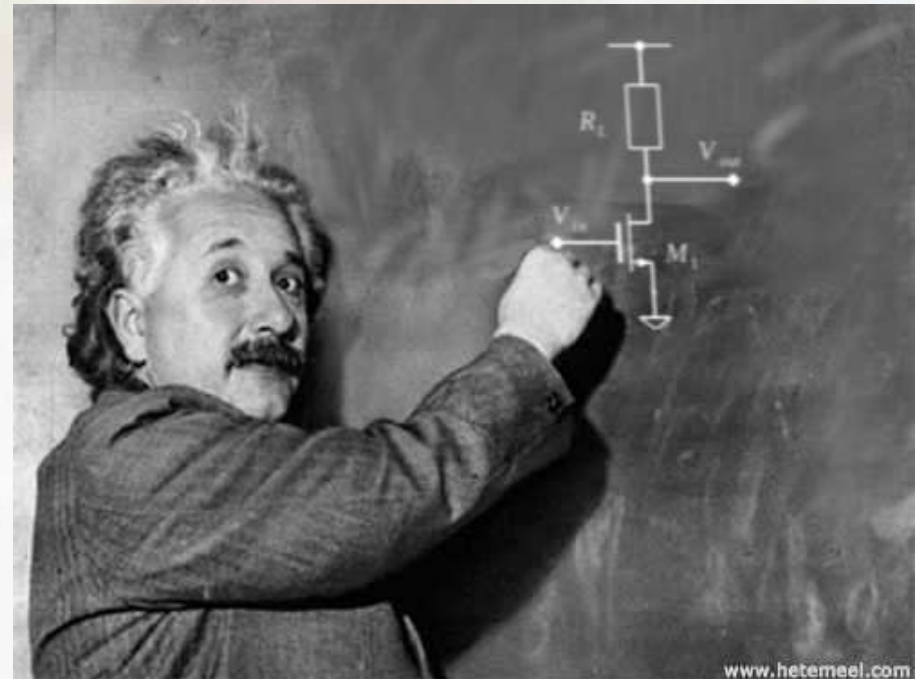

Other practical concerns wrt. gain

Integrator


Effect of limited gain on integration operation. Maximum integration is A_0 .

Low-pass filter

Effect on the filter bandwidth

How fast?

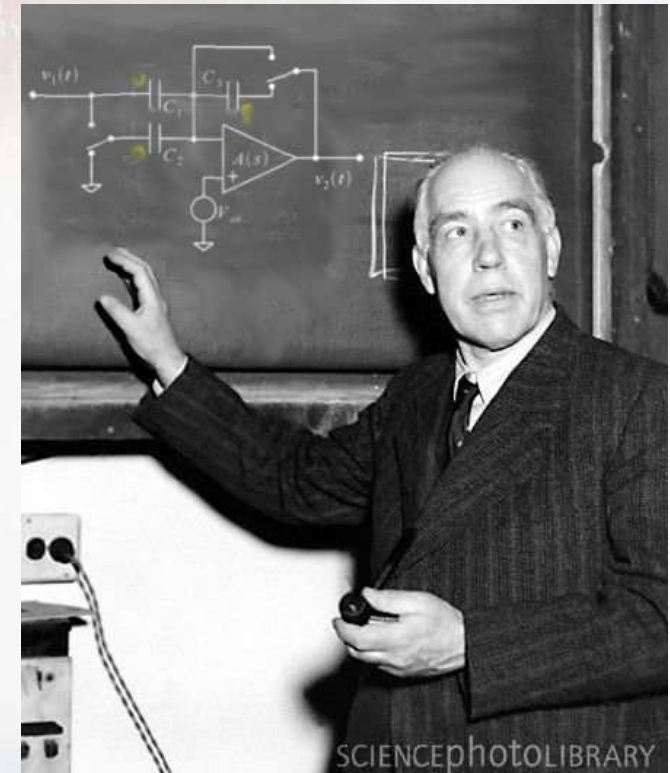A closed-loop gain of 10 and a bandwidth of 25 MHz



The "741 amplifier"


Texas instruments

opa 336 - what is the bandwidth?

opa 358 - what is the DC gain?

Analog Devices

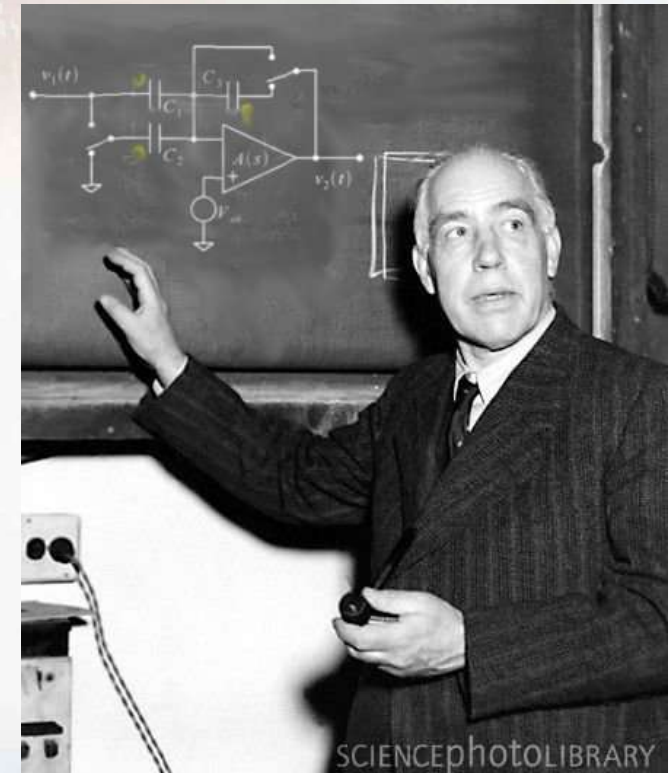AD854x - what is the DC gain, or what is the open-loop bandwidth?



SCIENCEPHOTOLIBRARY

Operational amplifier architectures

Examples

Telescopic

Two-stage

Folded-cascode

Current-mirror

Essentially just cascaded stages of different kinds


Telescopic OTA

Stack many cascodes on top of each-other and use gain-boosting, etc.


Omitted, since it is not applicable for modern processes.

The swing is eaten up.


Two-stage OP/OTA

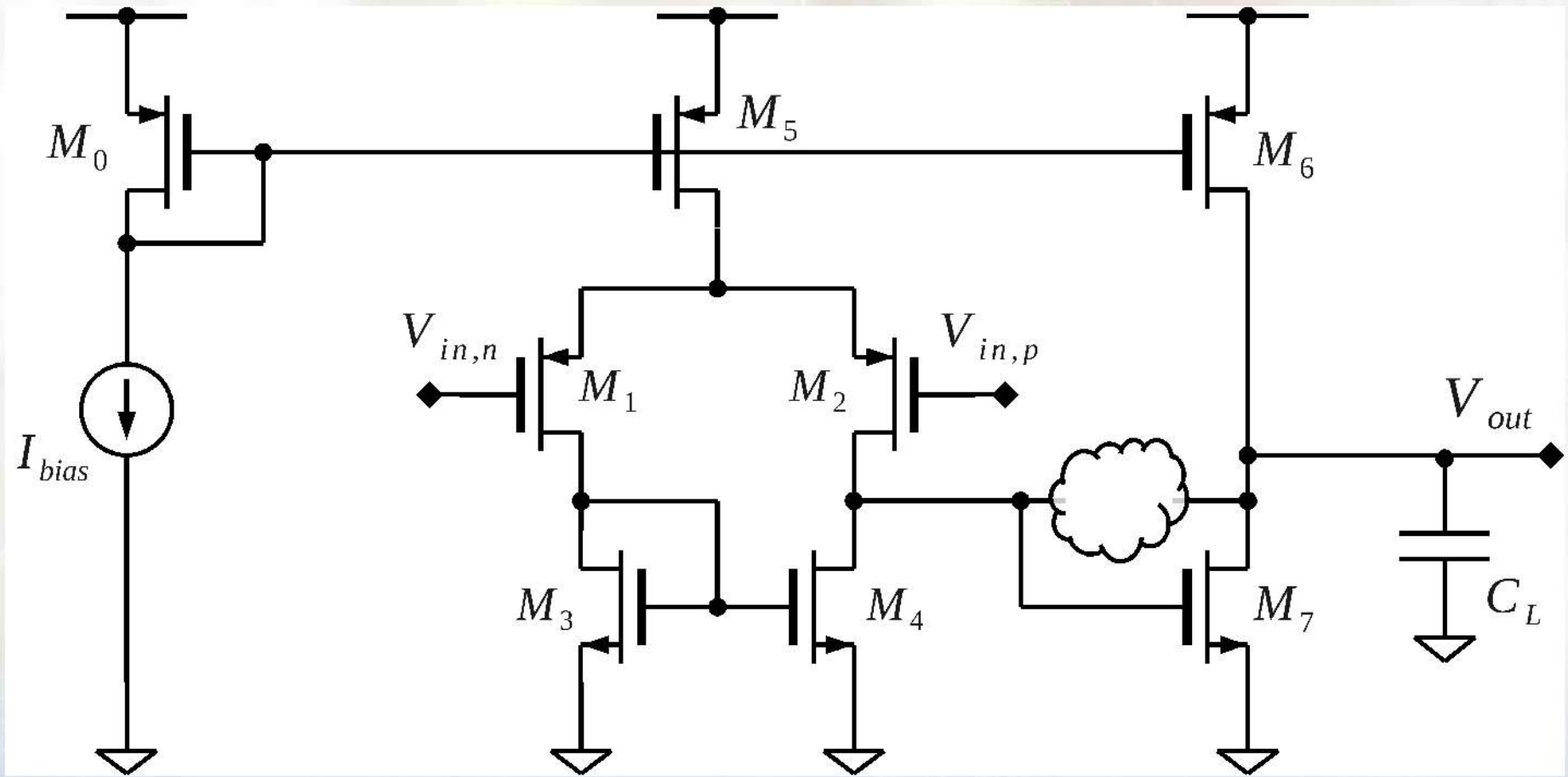

Current-mirror OP/OTA

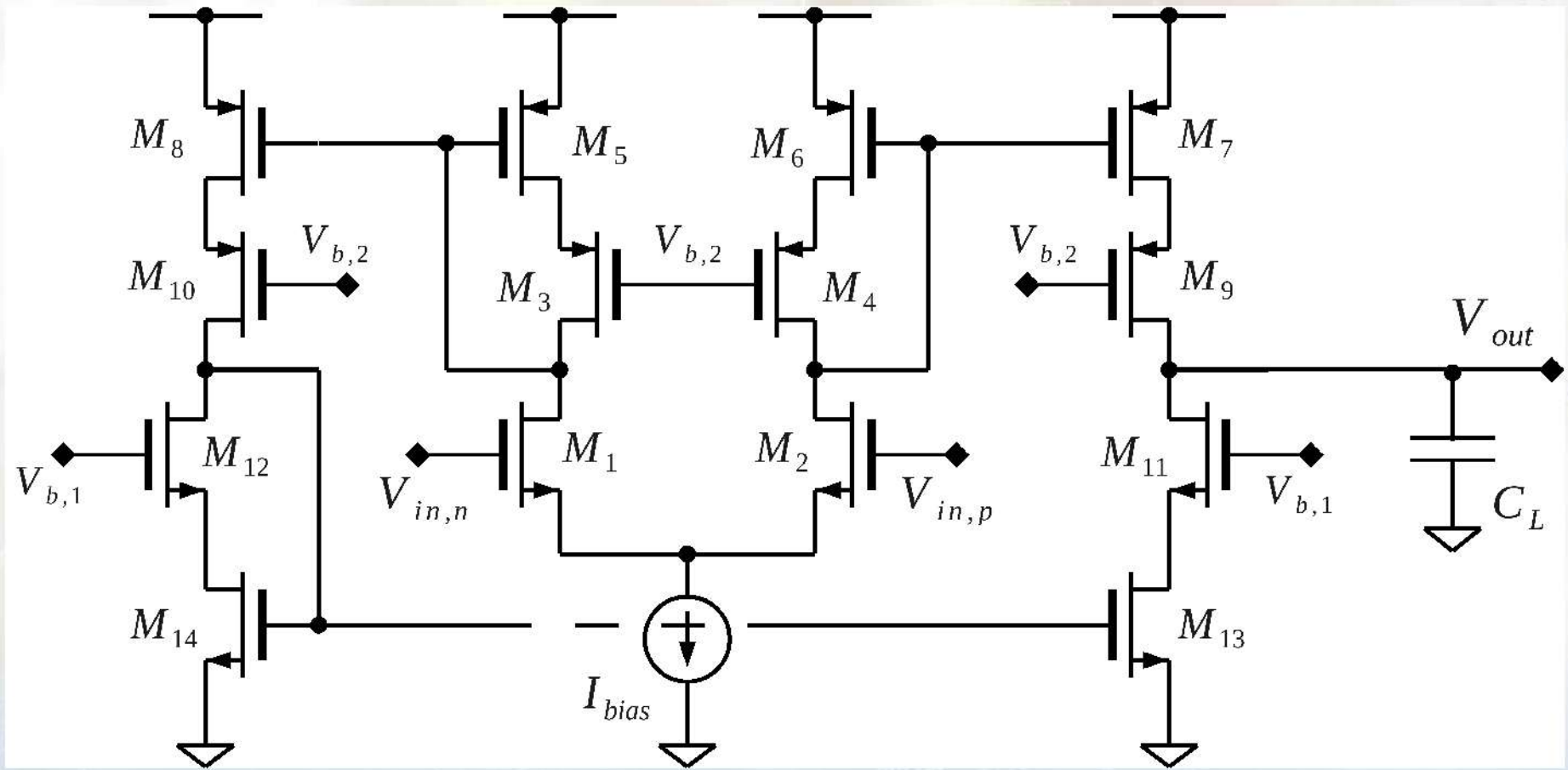

Folded-cascode OP/OTA

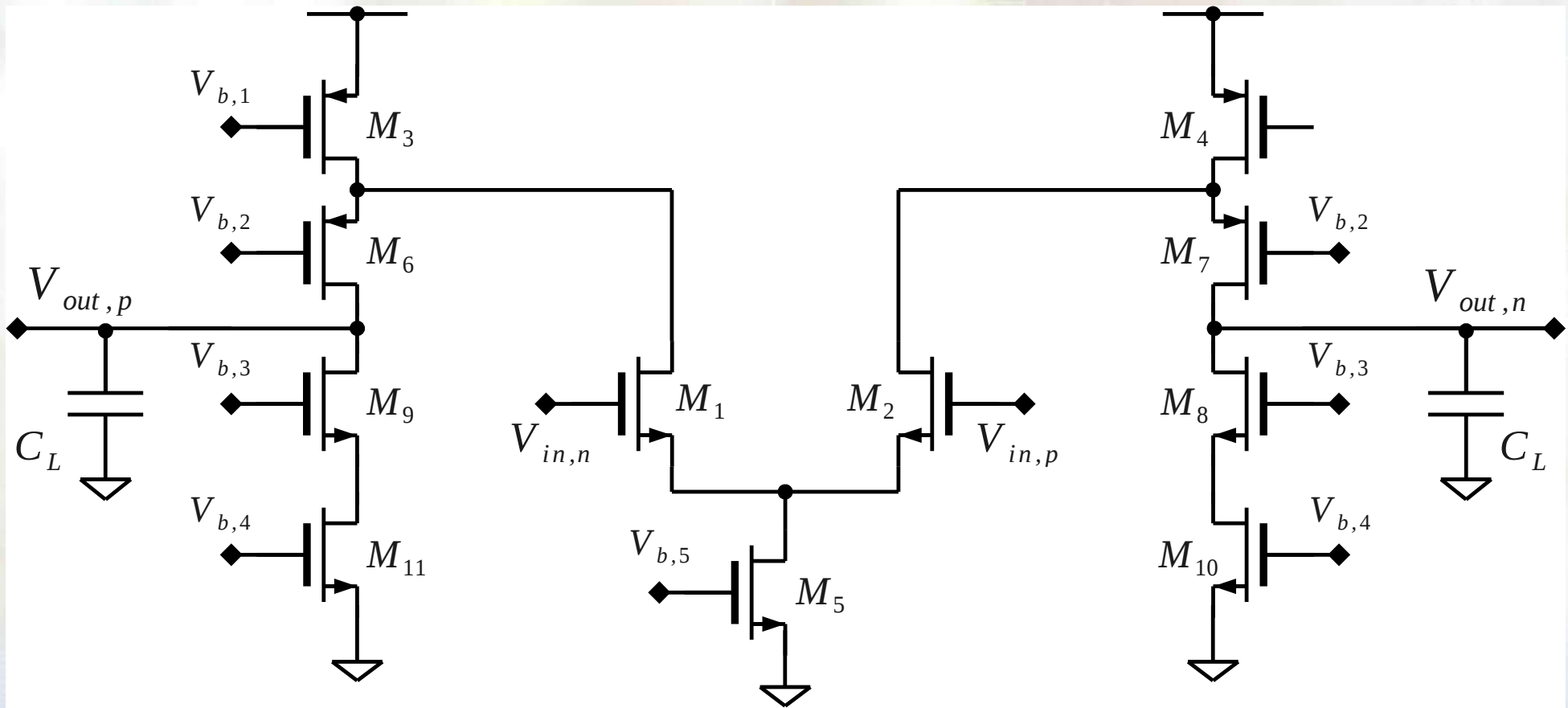

OP/OTA Compilation

Cookbook recipes

Hand-outs with step-by-step explanation of the design of OP/OTAs

http://www.es.isy.liu.se/courses/ANDA/download/opampRef/ANTIK_0N_NN_LN_opampHandsouts_A.pdf

Compensation techniques

http://www.es.isy.liu.se/courses/ANDA/download/opampRef/ANTIK_0N_NN_LN_opampCompensationTable_A.pdf

Amplifier classes

Not really covered in this course.

Different classes, such as

Class A, B, AB, C, D, E, F, G, H, I, K, S, T, Z, etc.

Class A

Essentially the common-source stage

Class AB

Essentially a push-pull configured class A

What did we do today?

Wrapped up the CMOS part of the course

Wrapped a discussion on stability and compensation

Looked on the opamp

macro level

chip level

What will we do next time?

Distortion

How is linearity of analog circuits defined?

What other cost measures are there to define analog quality?

Noise

What are the fundamental limits on performance and range?

What are the mathematical tools to find them?