

TSEI05 Analog Timediscrete Integrated Circuits

- Lecture 11
 - Transmission Lines, Applications

Kent Palmkvist
ISY

kentp@isy.liu.se



When is transmission line effects important?

- Wavelength vs wire length


$$\text{conductor length} \geq \lambda = c / f$$

 - Examples
 - Phone wire: length = 5 km => problem when frequency > 50 kHz (ADSL uses up to at least 2 MHz)
 - CPU clock signal: 2.4 GHz => length > 10 cm (lower if taking dielectric constant into account)



High frequency systems

- TV antenna system
 - 75 ohm antenna
 - How to split signal to two different rooms
 - $75-75/2 = 37.5 \Omega$ series resistor
 - Loose 50% power!
- VGA screen extension cord
 - Possible problem if connector have different impedance compared to wire



Termination

- Assume driver low impedance ($\ll Z_0$)
- Assume receiver end high impedance ($\gg Z_0$), mostly capacitive load
- End resistor only to GND
 - Give high current when '1'
- End resistor to both GND and VCC
 - Reduce DC current
 - Calculate max current as thevenin equivalent (DC point + $R1//R2$ internal resistance)
 - Select $R1$ and $R2$ such that $R1//R2$ equal Z_0
 - Lower current, but both when '0' and '1'



5

Forking wires

- Common wire from driver, forking to reach two receivers
- End resistor in forked wire
 - If Z_0 in whole network, then fork gives reflection
 - If $2Z_0$ in wires after fork point then no reflection
 - Use $2Z_0$ also for termination
 - Requires both wire impedance $2Z_0$ as well as resistive termination of $2Z_0$



6

Daisy-chain configuration

- End resistor using daisy-chain configuration
 - Single wire runs to all elements in sequence
 - Have short main wire to gate input length
 - Drawback: reflection in receiver connections
 - Receiver is high impedance, mostly capacitive load
 - Assume $Z_0 = \sqrt{L/C}$, long wires
 - Termination of wire from driver into $C//Z_0$

$$Z_L(\omega) = \frac{1}{(j\omega C)} \parallel Z_0(\omega) = \frac{Z_0(\omega) \frac{1}{j\omega C}}{Z_0(\omega) + \frac{1}{j\omega C}} = \frac{Z_0(\omega)}{1 + j\omega C Z_0(\omega)}$$



7

Daisy-chain configuration, cont.

- Reflection in first receiver connection

- Calculate the reflection parameter R for this case

$$R(\omega) = \frac{Z_L(\omega) - Z_0(\omega)}{Z_L(\omega) + Z_0(\omega)} = \frac{\frac{Z_0(\omega)}{1 + j\omega C Z_0(\omega)} - Z_0(\omega)}{\frac{Z_0(\omega)}{1 + j\omega C Z_0(\omega)} + Z_0(\omega)} = \frac{Z_0(\omega) - Z_0(\omega) - j\omega C Z_0(\omega) Z_0(\omega)}{Z_0(\omega) + Z_0(\omega) + j\omega C Z_0(\omega) Z_0(\omega)}$$

$$= \frac{\frac{1}{1 + j\omega C Z_0(\omega)} - 1}{\frac{1}{1 + j\omega C Z_0(\omega)} + 1} = \frac{1 - 1 - j\omega C Z_0(\omega)}{1 + 1 + j\omega C Z_0(\omega)} = \frac{-j\omega C Z_0(\omega)}{2 + j\omega C Z_0(\omega)}$$

- High frequency components (large ω) are reflected!
- End resistor placement: Not in front of gate.
 - Use an extension of the wire followed by a termination (daisychain gate and termination resistor).



8

Source terminator

- Add serie resistor between driver output and transmission line
 - Cut waveform in half before going out on transmission line
 - Reflection at end is +1 (high impedance receiver => open end)
 - Total voltage at end is $2 \cdot \text{wave} = 2 \cdot 1/2 \text{ signal} = 1!$ Full swing!
 - Reflected signal is killed at the source when arriving due to the source termination
 - Drive current goes to zero when reflected wave arrives



9


Serie resistor selection

- Cascading driver internal resistance with serie resistance. Sum must equal Z_0
- NOTE: Not possible to daisy chain receivers in source termination case!
- How close must source termination be?
 - A small stub between the driver and source termination will produce reflection (e.g., bonding wires + pcb wires)
 - The stub is inductive => large impedance for high frequency

TSE05 ANTIK
Kent Palmkvist

Department of Electrical Engineering
Linköping University

kentp@isy.liu.se
http://www.es.isy.liu.se



10


Comparison end vs source termination

- Source usually resistive plus small inductance
- End usually capacitive
- Mismatch between Z_0 and capacitive load in end termination probably worse than serie resistor mismatch (usually less reflections in source termination)
- Worst case drive current is $\Delta V/2Z_0$. For end termination with $V_{cc}/2$ bias this is also true (voltage swing is only half, but Z_0 impedance)

TSE05 ANTIK
Kent Palmkvist

Department of Electrical Engineering
Linköping University

kentp@isy.liu.se
http://www.es.isy.liu.se



11


AC Biasing

- Use a capacitance in series with the end termination resistance R , $R=Z_0$
- Must have a DC balanced signal (equal time in 1 and 0 state)
- Waste less current (split terminator always have a current from V_{cc} to Gnd)
- The driving circuit does not see any difference

TSE05 ANTIK
Kent Palmkvist

Department of Electrical Engineering
Linköping University

kentp@isy.liu.se
http://www.es.isy.liu.se



12


Accuracy requirements for termination

- Problem knowing both transmission line impedance and resistor value
- Safe choice: source and end termination
 - Kill reflections in both ends

TSE05 ANTIK
Kent Palmkvist

Department of Electrical Engineering
Linköping University

kentp@isy.liu.se
http://www.es.isy.liu.se



How to fit a 5mm wide cable to a 1 mm chip

- Physical scaling of dimensions
- Tapered connections

