

**Written Test**  
**TSTE80,**  
**Analog and Discrete-time Integrated Circuits**

---

Date:	January 12, 2006
Time:	8-12
Place:	TER2
Max.no of points:	70; 40 from written test, 15 for project, 15 from assignments
Grades:	30 for 3, 42 for 4, and 56 for 5.
Allowed material:	All types of calculators except laptops. All types of official tables and handbooks. Textbooks: Johns & Martin: Analog Integrated Circuit Design. Razavi: Design of Analog CMOS Integrated Circuits. Sedra&Smith: Microelectronic Circuits. Dictionaries.
Examiner:	Sune Söderkvist
Responsible teacher:	Sune Söderkvist Tel.: 281355.
Correct (?) solutions:	Solutions and results will be displayed in House B, entrance 25-27, ground floor.

**Students instructions**

- The CMOS transistor operation regions, small-signal parameters, and noise characteristics are found on the last page of this exam.
- Generally, do not just answer yes or no to a short question. You always have to answer with figures, formulas etc., otherwise no or fewer points will be given.
- You may write down your answers in Swedish or English.


**Good Luck!**

## 1. Large-signal analysis

For the amplifier in **Figure 1**,  $0 \leq V_{in} \leq 1.5$  V and  $V_{DD} = 3$  V. The transistors have following parameter values:

	N-channel	P-channel
$V_{T,0}$	0.5 V	0.6 V
$\mu_0 C_{ox}$	20 nA/V <sup>2</sup>	6 nA/V <sup>2</sup>
$\lambda$	0.03 V <sup>-1</sup>	0.05 V <sup>-1</sup>
$\gamma$	0.5 V <sup>1/2</sup>	0.3 V <sup>1/2</sup>
$\phi_F$	0.4 V	0.4 V

- Let  $V_{bias1} = 2.5$  V and  $V_{bias2} = 2$  V and determine the output swing, i.e.  $V_{out,min}$  and  $V_{out,max}$ , when both transistors are operating in the saturation region. (3p)
- Determine  $W/L$  for both transistors if their drain currents shall be limited to  $I_D \leq 0.1$   $\mu$ A at the limit of saturation.  $V_{bias1} = 2.5$  V and  $V_{bias2} = 2$  V. (3p)
- Determine the limit values of  $V_{bias1}$  and  $V_{bias2}$  allowing both M1 and M2 to operate in the saturation region, independent of the variations of  $V_{in}$ . ( $0 \leq V_{in} \leq 1.5$  V) (2p)

 

**Figure 1:** Amplifier.

## 2. Small-signal analysis


Once again, look at the capacitive-loaded amplifier in **Figure 1**. Assume that the transistors small-signal parameters are  $g_{m1}$ ,  $g_{mbs1}$ ,  $g_{ds1}$  and  $g_{m2}$ ,  $g_{mbs2}$ ,  $g_{ds2}$  respectively.

- Sketch a small-signal equivalent circuit and determine an exact expression for the transfer function  $H(s) = V_{out}(s)/V_{in}(s)$ . The bulk effect can **not** be neglected. However, all capacitors but  $C_L$  can be neglected. Also, determine the DC gain. (4p)
- Determine an exact expression for the small-signal input impedance,  $Z_{in}(s)$ . (3p)
- Determine an exact expression for the small-signal output resistance,  $r_{out}$ . (1p)

### 3. Noise in CMOS circuits

The transistors M1 and M2 in the circuit shown in **Figure 2** generate thermal noise while the biasing voltage  $V_{b1}$  and the biasing currents  $I_{bias1}$  and  $I_{bias2}$  are assumed to be noise less. Both transistors are biased in saturation and are here modeled by the small-signal parameters  $g_m$  and  $g_{ds}$ .

- Derive the total output noise spectral density. (5p)
- Which transistor gives the largest contribution of the generated noise if the input referred noise spectral density is considered? (1p)
- Propose one approach to increase the maximum signal-to-noise ratio, SNR for the circuit shown in **Figure 2** without changing the input signal power. Which design parameters should be changed to obtain this improvement? (2p)

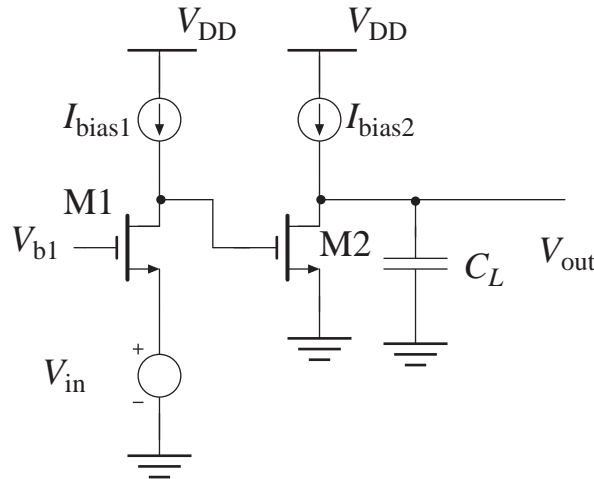


**Figure 2:** A noisy analog circuit.

### 4. Switched Capacitor Circuit

A switched capacitor circuit in clock phase 1, i.e., time  $t$ ,  $t + 2\tau$ ,  $t + 4\tau$ , etc. is shown in **Figure 3**. Assume that the input signal is constant between clock phase 1 and 2, i.e.,  $V_{in}(t) = V_{in}(t + \tau)$ .

- Express the output voltage,  $V_{out}(z)$ , as a function of the input voltage,  $V_{in}(z)$ , for clock phase 1 of the switched capacitor circuit shown in **Figure 3**. Assume that the operational amplifier is ideal. Motivate your answer carefully. (4p)
- Is the circuit insensitive to capacitive parasitics? Motivate your answer carefully. (1p)
- Express the output voltage,  $V_{out}(z)$ , as a function of the input voltage,  $V_{in}(z)$  and offset voltage,  $V_{os}$ , for clock phase 1 of the switched capacitor circuit shown in **Figure 3**. Assume that the OTA suffers from an offset voltage,  $V_{os}$ . (3p)

 

**Figure 3:** An SC circuit in clock phase 1.

## 5. A mixture of questions

- a) In an active RC filter we need to have an operational amplifier with the following performance

Performance measure	Value
$A_0$	80 dB
$f_u$	100 MHz
$C_L$	5 pF
Slew rate	80 V/ $\mu$ s
Output range	[0.5 - 2.8] V
Common-mode range	[0.1 - 2.0] V
$V_{DD}$	3.3 V
Power consumption	$\leq 10$ mW

How would you design the operational amplifier? Draw the block diagram of the operational amplifier and give a specification of each block in your design, like the one above and the name of the type of building block and the type of the input transistors. (3p)

- b) The same task as in a) but here we have an operational transconductance amplifier that will be used in an SC filter. (2p)
- c) In analog filters tuning circuits are commonly used. Explain why tuning is required in analog circuits. Also, explain the basic principle of tuning in analog active-RC filters. (2p)
- d) State benefits and drawbacks with fully differential circuit compared with their single-ended counterpart. (1p)

# Transistor formulas and noise

## 1 CMOS transistors

**Current and threshold voltage formulas and operating regions for an NMOS transistor**

Cut-off:  $V_{GS} < V_T$   $I_D \approx 0$

Linear:  $V_{GS} - V_T > V_{DS} > 0$   $I_D \approx \frac{\mu_0 C_{ox}}{2} \frac{W}{L} (2(V_{GS} - V_T) - V_{DS}) V_{DS}$

Saturation:  $0 < V_{GS} - V_T < V_{DS}$   $I_D \approx \frac{\mu_0 C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$

All regions:  $V_T = V_{T,0} + \gamma(\sqrt{2\phi_F - V_{BS}} - \sqrt{2\phi_F})$

**Small-signal parameters**

Linear:  $g_m \approx \mu_0 C_{ox} \frac{W}{L} V_{DS}$   $g_{ds} \approx \mu_0 C_{ox} \frac{W}{L} (V_{GS} - V_T - V_{DS})$

Saturation:  $g_m \approx \sqrt{2\mu_0 C_{ox} \frac{W}{L} I_D}$   $g_{ds} \approx \lambda I_D$

## 2 Circuit noise

**Thermal noise in CMOS transistors**

The thermal noise spectral density at the gate of a CMOS transistor is

$$\frac{\bar{v}^2}{\Delta f} = \frac{8kT}{3} \frac{1}{g_m}$$

**Thermal noise in resistors**

The thermal noise spectral density of a resistor is modeled as a parallel noise current source

$$\frac{\bar{i}^2}{\Delta f} = \frac{4kT}{R}$$

**Flicker noise in CMOS transistors**

The flicker noise spectral density at the gate of a CMOS transistor is

$$\frac{\bar{v}^2}{\Delta f} = \frac{K}{WLC_{ox}f}$$