

Written Test TSTE80, Analog and Discrete-time Integrated Circuits

Date:	August 10, 2006
Time:	14-18
Place:	TER2
Max.no. of points:	25
Grades:	10p for 3, 15p for 4, and 20p for 5.
Allowed material:	All types of calculators except laptops. All types of official tables and handbooks. Textbooks: Johns & Martin: Analog Integrated Circuit Design. Razavi: Design of Analog CMOS Integrated Circuits. Sedra&Smith: Microelectronic Circuits. Dictionaries.
Examiner:	Sune Söderkvist
Responsible teacher:	Sune Söderkvist. Tel.: 281355.
Correct (?) solutions:	Solutions and results will be displayed in House B, entrance 25-27, ground floor.

Graded exams are returned on examiner's office times, tuesdays and fridays at 11.00-13.00 from week no. 34

Students instructions

- The CMOS transistor operation regions, small-signal parameters, and noise characteristics are found on the last page of this exam.
- Generally, do not just answer yes or no to a short question. You always have to answer with figures, formulas etc., otherwise no or fewer points will be given.
- You may write down your answers in Swedish or English.

For students who has studied earlier variants of the course :

The conditions for the test is the same as before, i.e. every problem gives max. 8 points and you get credits for project and assignments as before. Mark 3 require 30 p totalt, mark 4 require 42 p and mark 5 require 56 p. Please, tell me on the wrapper if this is of interest.

Good Luck!

Exercise 1.

The circuit in **Figure 1** is used to establish an appropriate bias voltage V_{bias} to an operational amplifier. The transistors have following parameter values:

	N-kanal	P-kanal
V_{t0} [V]	0.47	0.62
$\mu_0 C_{ox}$ [mA/V^2]	180	58.5
λ [V^{-1}]	0.03	0.05
γ [$V^{1/2}$]	0.62	0.41
ϕ_F [V]	0.43	0.41

a) Show that all transistors are saturated in this circuit. (1.5p)

b) Determine $\frac{W}{L}|_i$, $i = 1, 2, 3$, for transistors M_i , $i = 1, 2, 3$, if $V_{DD} = 3.3$ V, $V_{bias} = 0.6$ V and $I_D = 5 \mu$ A.

If the potential V_x is just above 2.05 V it shows that $\frac{W}{L}|_2 = \frac{W}{L}|_1$. Choose $V_x = 2.05$ V here.

Do not neglect the bulk effect neither the channel-length modulation. (3.5p)

 


Figure 1: A bias circuit.

Exercise 2.

Sketch a small-signal equivalent circuit and determine the input resistans r_{in} and the output resistans r_{out} for the wide-swing current mirror in **Figure 2**. All transistors are biased to operate in the saturation region. Assume that the transistors small-signal parameters are g_{m1} , g_{ds1} , g_{m2} , g_{ds2} and g_{m3} , g_{ds3} respectively. (5p)

 


Figure 2: A wide swing current mirror.

Exercise 3.

A switched capacitor circuit in clock phase 1 is shown in **Figure 3**. The value of V_{in} changes only at time t , $t + 2\tau$, $t + 4\tau$, and so on, i.e., $V_{in}(t) = V_{in}(t + \tau)$.

- Express the output voltage, $V_{out}(z)$, as a function of the input voltage, $V_{in}(z)$, for clock phase 1. Assume that the operational amplifier is ideal and that $C_3 = 2C_1$. (4p)
- Is the circuit insensitive to capacitive parasitics? Motivate your answer carefully. (1p)

 


Figure 3: A switched-capacitor circuit in clock phase 1.

Exercise 4.

Figure 4 shows a simplified small-signal model of an OTA, including a compensation capacitor C .

 


Figure 4: A small-signal model of a two-stage OTA.

- Derive an expression for the transfer function $H(s) = V_{out}/V_{in}$. (3p)
- Determine an approximation of $H(s)$ assuming that $g_{mII} \gg g_I$, $g_{mII} \gg g_{II}$, $g_{mII} \gg g_I$, and also that $C_c \gg C_I$ and $C_{II} \gg C_I$. Also assume that C_{II} and C_c is of the same order.

Determine DC gain A_0 , poles and zeros and also an approximation of unity-gain frequency ω_u , from this approximation assuming that the poles are well separated ($|p_2| \gg |p_1|$). (2p)

Exercise 5.

Consider the two cascaded common-source stages in **Figure 5**, where only the thermal noise generated in the transistors is of interest. The current sources are ideal and hence noiseless. Let the output load capacitance be given by C_L and parasitic capacitances are only given by gate-source capacitances, C_{gs} . Further $I_{bias1} = I_{bias2} = I_{bias}$. The transistors are identical with the small signal parameters $g_{m1} = g_{m2} = g_m$ and $g_{ds1} = g_{ds2} = g_{ds}$. Both transistors operate in the saturation region.

 


Figure 5: A noisy multi-stage amplifier.

- Determine an expression for the spectral density R_{out} of the output thermal noise assuming that the noise from the transistors are uncorrelated. (2p)
- Assume that $C_L \gg C_{gs}$ and derive an approximation for the total output noise power $P_{out,noise}$ using the noise-bandwidth concept. (Express $P_{out,noise}$ in small signal parameters, in C_L and in constants.) (2p)
- Express $P_{out,noise}$ in I_{bias} and answer following questions. (Motivate!)
 How to change I_{bias} if you want to decrease $P_{out,noise}$?
 How will that affect the DC-gain of the circuit? (1p)

Transistor formulas and noise

1 CMOS transistors

Current and threshold voltage formulas and operating regions for an NMOS transistor

Cut-off: $V_{GS} < V_{tn}$ $I_D \approx 0$

Linear: $0 < V_{DS} < V_{eff}$ $I_D \approx \alpha(2V_{eff} - V_{DS})V_{DS}$

Saturation: $V_{DS} > V_{eff}$ $I_D \approx \alpha V_{eff}^2 (1 + \lambda(V_{DS} - V_{eff}))$

All regions: $V_{tn} = V_{t0n} + \gamma(\sqrt{2\phi_F - V_{BS}} - \sqrt{2\phi_F})$

$$V_{eff} = V_{GS} - V_{tn}$$

Small-signal parameters

Linear: $g_m \approx 2\alpha V_{DS}$ $g_{ds} \approx 2\alpha(V_{GS} - V_{tn} - V_{DS})$

Saturation: $g_m \approx 2\sqrt{\alpha I_D}$ $g_{ds} \approx \lambda I_D$

Constants: $\alpha = \frac{1}{2}\mu_{0n}C_{ox}\frac{W}{L}$ $\lambda = \sqrt{\frac{2K_s\epsilon_0}{qN_A\phi_0}} \cdot \frac{1}{L}$ $\gamma = \frac{\sqrt{2qN_AK_s\epsilon_0}}{C_{ox}}$

2 Circuit noise

Thermal noise in CMOS transistors

The thermal noise spectral density at the gate of a CMOS transistor is

$$\frac{\bar{v}^2}{\Delta f} = \frac{8kT}{3} \cdot \frac{1}{g_m}$$

Thermal noise in resistors

The thermal noise spectral density of a resistor is modeled as a parallel noise current source

$$\frac{\bar{i}^2}{\Delta f} = \frac{4kT}{R}$$

Flicker noise in CMOS transistors

The flicker noise spectral density at the gate of a CMOS transistor is

$$\frac{\bar{v}^2}{\Delta f} = \frac{K}{WLC_{ox}f}$$