

## SOLUTIONS. Exam Aug 10, 2006

### TSTE80 Analog and Discrete-time Integrated Circuits.

#### Excercise 1.

a) A PMOS transistor is saturated when  $V_{SD} > V_{eff} = V_{SG} - V_{tp}$ .

Transistor **M1**:  $V_{SD1} = V_{DD} - V_x = V_{SG1}$  i.e.  $V_{SD1} > V_{SG1} - V_{tp1}$ , so **M1** works in saturation.

Transistor **M2**:  $V_{SD2} = V_x - V_{bias} = V_{SG2}$  i.e.  $V_{SD2} > V_{SG2} - V_{tp2}$ , so **M2** works in saturation.

A NMOS transistor is saturated when  $V_{DS} > V_{eff} = V_{GS} - V_{tn}$ .

Transistor **M3**:  $V_{DS3} = V_{bias} - 0 = V_{GS3}$  i.e.  $V_{DS3} > V_{GS3} - V_{tn3}$ , so **M3** works in saturation.

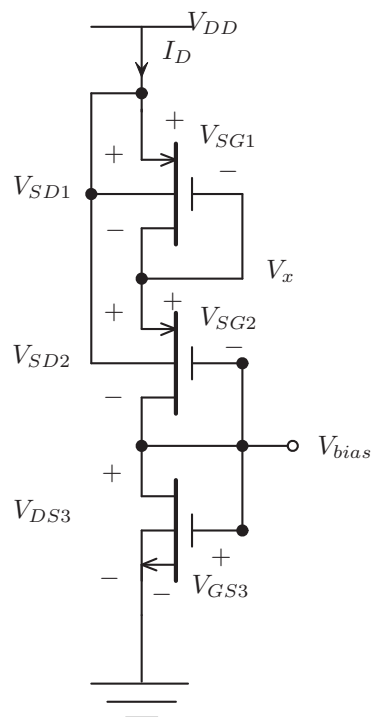


Figure 1: A bias circuit.

b) First note that  $I_{D1} = I_{D2} = I_{D3} = I_D$

Transistor **M1**:  $V_{SB1} = 0$  i.e.  $V_{tp1} = V_{t0p}$ .

Enclosed page of formulas gives:

$$\left(\frac{W}{L}\right)_1 = \frac{I_D}{\frac{1}{2}\mu_{0p}C_{oxp}V_{eff1}^2(1 + \lambda_p(V_{SD1} - V_{eff1}))} \quad (1)$$

$$I_D = 5 \mu \text{ A}, \mu_{0p}C_{oxp} = 58.5 \mu \text{ A/V}^2,$$

$$V_{eff1} = V_{SG1} - V_{t0p} = V_{DD} - V_x - V_{t0p} = 3.3 - 0.6 - 0.62 = 2.08 \text{ V},$$

$$\lambda_p = 0.05.$$

Further  $V_{SD1} = V_{SG1}$  gives  $V_{SD1} - V_{eff1} = V_{t0p} = 0.62 \text{ V}$ .

Now equation (1) gives:

$$\left(\frac{W}{L}\right)_1 \approx 0.42 \quad (2)$$

Transistor **M2**:  $V_{SB2} = V_{S2} - V_{B2} = V_x - V_{DD} = -1.25 \text{ V}$ .

Enclosed page of formulas gives:

$$V_{tp2} = V_{t0p} + \gamma(\sqrt{2\phi_F - V_{SB2}} - \sqrt{2\phi_F}) = 0.62 + 0.41(\sqrt{2.07} - \sqrt{0.82}) = 0.8386 \text{ V} \quad (3)$$

$$\left(\frac{W}{L}\right)_2 = \frac{I_D}{\frac{1}{2}\mu_{0p}C_{oxp}V_{eff2}^2(1 + \lambda_p(V_{SD2} - V_{eff2}))} \quad (4)$$

$$I_D = 5 \mu \text{ A}, \mu_{0p}C_{oxp} = 58.5 \mu \text{ A/V}^2,$$

$$V_{eff2} = V_{SG2} - V_{tp2} = V_x - V_{bias} - V_{tp2} = 2.05 - 0.6 - 0.8386 = 0.6114 \text{ V},$$

$$\lambda_p = 0.05.$$

Further  $V_{SD2} = V_{SG2}$  gives  $V_{SD2} - V_{eff2} = V_{tp2} = 0.8386 \text{ V}$ .

Now equation (4) gives:

$$\left(\frac{W}{L}\right)_2 \approx 0.44 \quad (5)$$

Transistor **M3**:  $V_{BS3} = 0$  i.e  $V_{tn3} = V_{t0n} = 0.47$ .

$$\left(\frac{W}{L}\right)_3 = \frac{I_D}{\frac{1}{2}\mu_{0n}C_{oxn}V_{eff3}^2(1 + \lambda_n(V_{DS3} - V_{eff3}))} \quad (6)$$

$$I_D = 5 \mu \text{ A}, \mu_{0n}C_{oxn} = 180 \mu \text{ A/V}^2,$$

$$V_{eff3} = V_{GS3} - V_{t0n} = V_{bias} - 0 - V_{tp2} = 0.6 - 0.47 = 0.13 \text{ V},$$

$$\lambda_n = 0.03.$$

Further  $V_{DS3} = V_{GS3}$  gives  $V_{DS3} - V_{eff3} = V_{t0n} = 0.47 \text{ V}$ .

Now equation (6) gives:


$$\left(\frac{W}{L}\right)_3 \approx 3.24 \quad (7)$$

Answer:  $\left(\frac{W}{L}\right)_1 \approx 0.42$ ,  $\left(\frac{W}{L}\right)_2 \approx 0.44$  and  $\left(\frac{W}{L}\right)_3 \approx 3.24$

## Exercise 2.

**Figure 2** gives the complete small signal equivalent circuit (SSEC):  
Notice that:

- $V_{gs1} = V_{g1} - V_{s1} = V_{in}$
- $V_{gs2} = V_{g2} - V_{s2} = V_{in}$
- $V_{gs3} = 0 - V_{s3} = -V_x$
- $V_{gs4} = 0 - V_{s4} = -V_y$

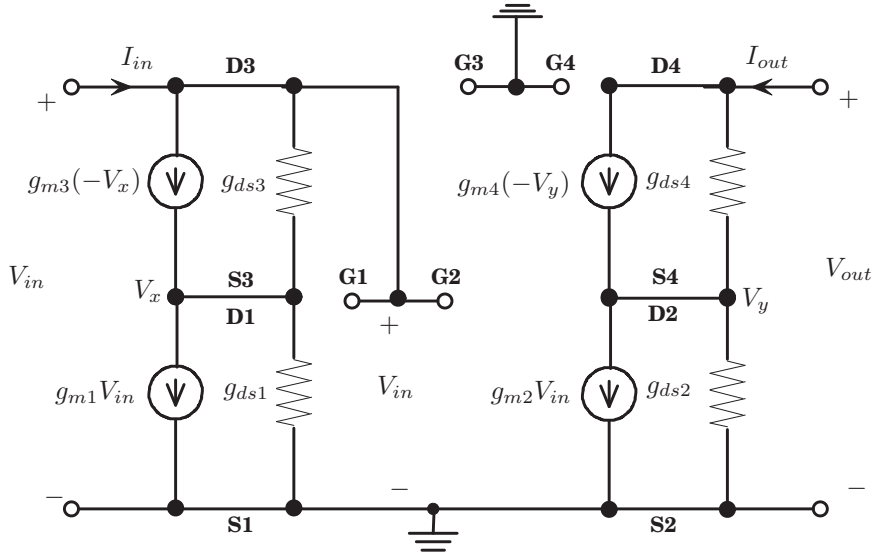

**Figure 2:** Small signal equivalent circuit.

Determine  $r_{in}$

KCL gives:

$$I_{in} = g_{m3}(-V_x) + (V_{in} - V_x)g_{ds3} \quad (8)$$

$$I_{in} = V_{in}g_{m1} + V_xg_{ds1} \quad (9)$$

Equations (8) and (9) give the input resistance:

$$r_{in} = \frac{V_{in}}{I_{in}} = \frac{g_{ds1} + g_{ds3} + g_{m1}}{g_{m1}(g_{ds3} + g_{m3}) + g_{ds1}g_{ds3}} \quad (10)$$

Determine  $r_{out}$  (OBS! Put  $V_{in}$  to zero when calculating  $r_{out}$ )

KCL gives:

$$I_{out} = g_{m4}(-V_y) + (V_{out} - V_y)g_{ds4} \quad (11)$$


$$I_{out} = V_{in}g_{m2} + V_yg_{ds2} \quad (12)$$

Putting  $V_{in} = 0$  gives the output resistans:

$$r_{out} = \frac{V_{out}}{I_{out}} = \frac{g_{ds2} + g_{ds4} + g_{m4}}{g_{ds2}g_{ds4}} \quad (13)$$

### Exercise 3.

- a) This exercise is solved using the charge redistribution analysis. First, the reference direction of the charge is chosen. Next, the charge of the capacitors are computed for time  $t$ ,  $t + \tau$ , and  $t + 2\tau$ .

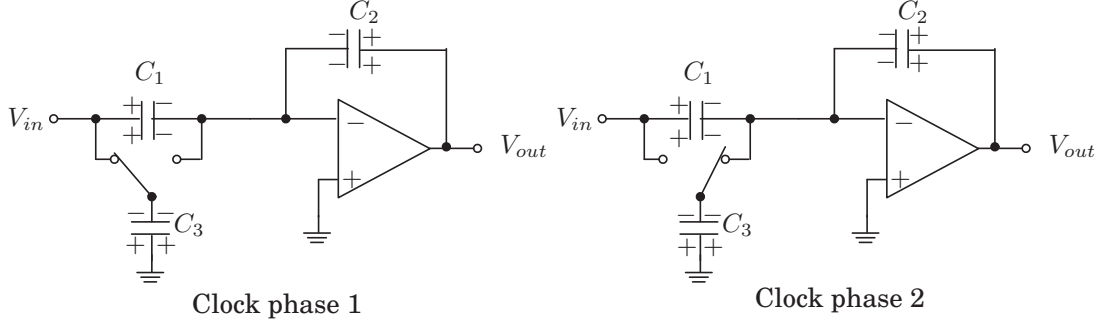

**Figure 3:** A switched-capacitor circuit in clock phase 1 and clock phase 2.

For time  $t$ :

$$\begin{aligned} q_1(t) &= (V_{in}(t) - 0)C_1 \\ q_2(t) &= (V_{out}(t) - 0)C_2 \\ q_3(t) &= (0 - V_{in}(t))C_3 \end{aligned} \quad (14)$$

For time  $t + \tau$ :

$$\begin{aligned} q_1(t + \tau) &= (V_{in}(t + \tau) - 0)C_1 \\ q_2(t + \tau) &= (V_{out}(t + \tau) - 0)C_2 \\ q_3(t + \tau) &= (0 - 0)C_3 \end{aligned} \quad (15)$$

For time  $t + 2\tau$ :

$$\begin{aligned} q_1(t + 2\tau) &= (V_{in}(t + 2\tau) - 0)C_1 \\ q_2(t + 2\tau) &= (V_{out}(t + 2\tau) - 0)C_2 \\ q_3(t + 2\tau) &= (0 - V_{in}(t + 2\tau))C_3 \end{aligned} \quad (16)$$

Equations for the charge conservation:

1) The capacitors can not discharge through the opamp, so the total charge on the capacitors at the end of clock cycle 1 is equal to the total charge on the capacitors during the whole clock cycle 2:

$$-q_1(t) - q_2(t) - q_3(t) = -q_1(t + \tau) - q_2(t + \tau) - q_3(t + \tau) \quad (17)$$

2) Since no charge can be given by opamp the total charge on  $C_1$  and  $C_2$  must be the same at  $t + 2\tau$  as at  $t + \tau$ :

$$-q_2(t + \tau) - q_3(t + \tau) = -q_2(t + 2\tau) - q_3(t + 2\tau) \quad (18)$$

Equations (14) and (15) together with equation(17) give:

$$V_{in}(t)C_1 + V_{out}(t)C_2 - V_{in}(t)C_3 = V_{in}(t + \tau)C_1 + V_{out}(t + \tau)C_2 \quad (19)$$

Equations (15) and (16) together with equation(18) give:

$$V_{in}(t + \tau)C_1 + V_{out}(t + \tau)C_2 = V_{in}(t + 2\tau)C_1 + V_{out}(t + 2\tau)C_2 \quad (20)$$

Equations (19) and (20) yields:

$$V_{in}(t)C_1 + V_{out}(t)C_2 - V_{in}(t)C_3 = V_{in}(t + 2\tau)C_1 + V_{out}(t + 2\tau)C_2 \quad (21)$$

Setting  $2\tau = T$  gives the differens equation:

$$C_1V_{in}(t) + C_2V_{out}(t) - C_3V_{in}(t) = C_1V_{in}(t + T) + C_2V_{out}(t + T) \quad (22)$$

Z-transforming (22) gives:

$$C_1V_{in}(z) + C_2V_{out}(z) - C_3V_{in}(z) = C_1zV_{in}(z) + C_2zV_{out}(z) \quad (23)$$


Rewriting (23):

$$V_{out}(z) = \frac{C_1 - C_3 - zC_1}{-C_2 + zC_2} \cdot V_{in}$$

Using that  $C_3 = 2C_1$  finally gives:

$$\underline{\underline{V_{out}(z) = -\frac{C_1(z+1)}{C_2(z-1)} \cdot V_{in}}} \quad (24)$$

b) Switches, capacitors, and the operational amplifier introduce parasitic capacitors into the circuit as is shown in Figure 4.

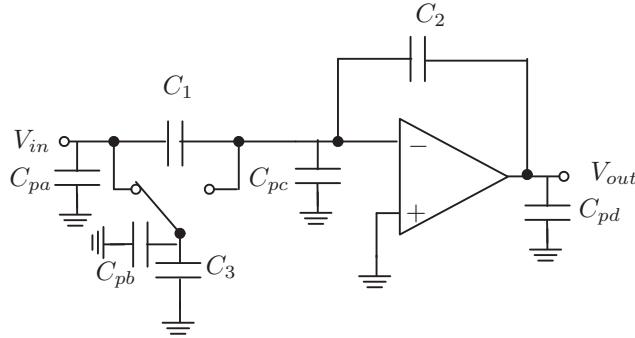

**Figure 4:** SC-circuit with parasitics in clock phase 1.

- $C_{pa}$  is connected between the ideal input voltage source and ground where the input source can source/sink as much charge as is required. Hence, this parasitics do not change the transfer function.
- $C_{pb}$  is in parallel with  $C_3$  and thereby it **will change** the transfer function.
- $C_{pc}$  is connected between ground and virtual ground thereby not change the transfer function.
- $C_{pd}$  is always connected to the ideal output of the operational amplifier and ground and thereby will not be a part of the transfer function.


Hence, the circuit **is sensitive** to capacitive parasitics when the transfer function is of concern.

#### Exercise 4.

a) Using KCL in node **A** and node **B** respectively in **Figure 5** gives:

$$\mathbf{A:} \quad g_{mI}V_{in} + (g_I + sC_I)V_x + sC_c(V_x - V_{out}) = 0 \quad (25)$$

$$\mathbf{B:} \quad g_{mII}V_x + (g_{II} + sC_{II})V_{out} + sC_c(V_{out} - V_x) = 0 \quad (26)$$

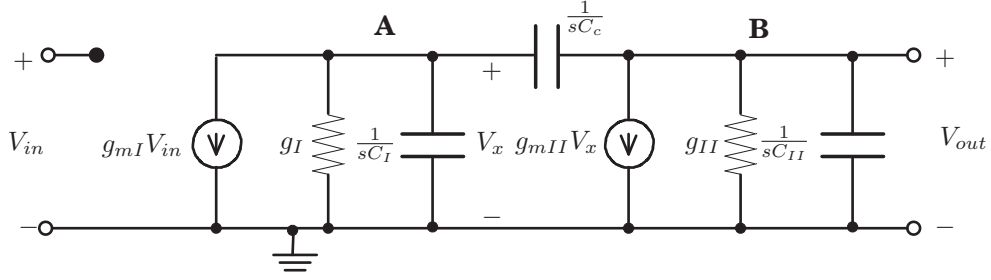

**Figure 5:** A small-signal model of a two-stage OTA.

Equation (26) gives:

$$V_x = -\frac{g_{II} + sC_{II} + sC_c}{g_{mII} - sC_c} V_{out} \quad (27)$$

Equation (27) inserted in (25) gives the transfer function:

$$H(s) = \frac{V_{out}}{V_{in}} = \frac{g_{mI}(g_{mII} - sC_c)}{g_I g_{II} + s((C_{II} + C_c)g_I + (C_I + C_c)g_{II} + C_c g_{mII}) + s^2(C_I C_{II} + C_c(C_I + C_{II}))} \quad (28)$$

b) Assuming that  $g_{mII} \gg g_I$ ,  $g_{mII} \gg g_{II}$ ,  $g_{mII} \gg g_I$ ,  $C_c \gg C_I$ ,  $C_{II} \gg C_I$  and that  $C_{II}$  and  $C_c$  is of the same order, equation (28) gives:

$$H(s) = \frac{V_{out}}{V_{in}} = \frac{g_{mI}(g_{mII} - sC_c)}{g_I g_{II} + sC_c g_{mII} + s^2 C_c C_{II}} \quad (29)$$

$s = 0$  in equation (29) gives the DC gain:

$$A_0 = \frac{g_{mI} g_{mII}}{g_I g_{II}} \quad (30)$$

The nominator in equation (29) gives one zero  $z_1$  at

$$z_1 = \frac{g_{mII}}{C_c} \quad (31)$$

To determine the poles look at the denominator  $N(s)$  of equation (29):

$$N(s) = g_I g_{II} + sC_c g_{mII} + s^2 C_c C_{II} = C_c C_{II} \left( \frac{g_I g_{II}}{C_c C_{II}} + s \frac{g_{mII}}{C_{II}} + s^2 \right) \quad (32)$$

With the poles  $p_1$  and  $p_2$  the denominator can be written as:

$$C_c C_{II} (s - p_1)(s - p_2) = C_c C_{II} (p_1 p_2 - (p_1 + p_2)s + s^2) \quad (33)$$

As  $|p_2| \gg |p_1|$  equation (33) can be approximated as:

$$C_c C_{II}(p_1 p_2 - (p_1 + p_2)s + s^2) \approx C_c C_{II}(p_1 p_2 - p_2 s + s^2) \quad (34)$$

Identification between equations (32) and (34):

$$p_2 = -\frac{g_{mII}}{C_{II}} \quad (35)$$

$$p_1 p_2 = \frac{g_I g_{II}}{C_c C_{II}} \Rightarrow p_1 = -\frac{g_I g_{II}}{g_{mII} C_c} \quad (36)$$

As  $|p_2| \gg |p_1|$  the unity-gain frequency  $\omega_u$  is approximately given by  $\omega_u \approx A_0 |p_1|$  i.e.


$$\omega_u \approx A_0 |p_1| = \frac{g_{mI} g_{mII}}{g_I g_{II}} \cdot \frac{g_I g_{II}}{g_{mII} C_c} = \frac{g_{mI}}{C_c} \quad (37)$$

Answer:


$$\underline{\underline{A_0 = \frac{g_{mI} g_{mII}}{g_I g_{II}}, z_1 = \frac{g_{mII}}{C_c}, p_1 = -\frac{g_I g_{II}}{g_{mII} C_c}, p_2 = -\frac{g_{mII}}{C_{II}}, \omega_u \approx \frac{g_{mI}}{C_c}}} \quad (38)$$

### Exercise 5.

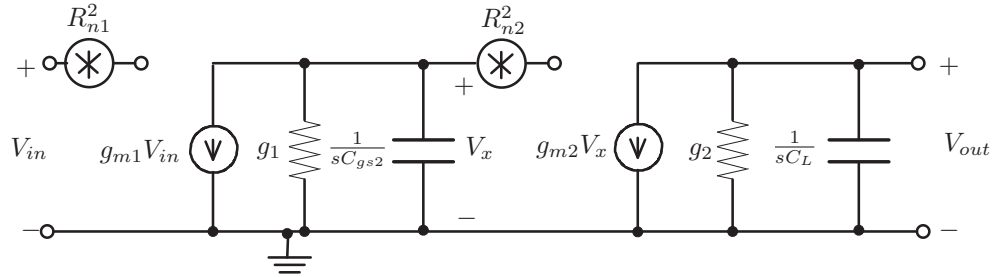a) **Figure 6a** gives a small-signal equivalent circuit, including noise-sources.



a)

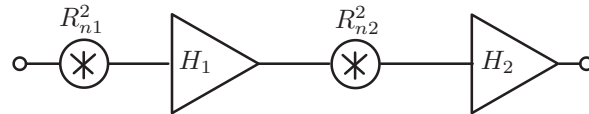

b)

**Figure 6:** a) A small-signal equivalent. b) Equivalent circuit for determining output noise spectral density

As the noise sources are uncorrelated the output noise spectral density can be computed as **Figure 5b)** describes, i.e. by the following formula

$$R_{out}(\omega) = |H_1(\omega)|^2 |H_2(\omega)|^2 R_{n1}(\omega) + |H_2(\omega)|^2 R_{n2}(\omega) \quad (39)$$

where  $H_1(\omega)$  is the transfer function for the first stage and  $H_2(\omega)$  the transfer function for the second stage.

From **Figure 5a**)  $H_1(s) = V_x(s)/V_{in}(s)$  and  $V_x(s) = -g_{m1}V_{in}(s) \cdot \frac{1}{g_{ds1} + sC_{gs2}}$  which yields

$$H_1(s) = -\frac{g_{m1}}{g_{ds1} + sC_{gs2}} \Rightarrow H_1(\omega) = -\frac{g_{m1}}{g_{ds1} + j\omega C_{gs2}} \quad (40)$$

In the same way  $H_2(s)$  is calculated to:

$$H_2(s) = -\frac{g_{m2}}{g_{ds2} + sC_L} \Rightarrow H_2(\omega) = -\frac{g_{m2}}{g_{ds2} + j\omega C_L} \quad (41)$$

Equations (39)-(41) gives following spectral density of the output noise (here we also utilize that  $g_{m1} = g_{m2} = g_m$  and  $g_{ds1} = g_{ds2} = g_{ds}$ ):

$$R_{out}(\omega) = R_{n1}(\omega) \frac{g_m^2}{g_{ds}^2 + \omega^2 C_{gs2}^2} \cdot \frac{g_m^2}{g_{ds}^2 + \omega^2 C_L^2} + R_{n2}(\omega) \frac{g_m^2}{g_{ds}^2 + \omega^2 C_L^2} \quad (42)$$

Using that  $R_{n1}(\omega) = R_{n2}(\omega) = \frac{8kT}{3} \frac{1}{g_m}$  (from enclosed page of formulas) equation (42) gives:

$$R_{out}(\omega) = \frac{8kT}{3} \cdot \frac{1}{g_m} \cdot \frac{g_m^2}{g_{ds}^2 + \omega^2 C_L^2} \left( \frac{g_m^2}{g_{ds}^2 + \omega^2 C_{gs2}^2} + 1 \right) \quad (43)$$

Which gives the answer:

$$\underline{\underline{R_{out}(\omega) = \frac{8kT}{3} \cdot \frac{g_m}{g_{ds}^2 + \omega^2 C_L^2} \left( \frac{g_m^2}{g_{ds}^2 + \omega^2 C_{gs2}^2} + 1 \right)}} \quad (44)$$

b) Equation (43) gives the amplitude spectrum of the circuit:

$$|H(\omega)| = \left( \frac{g_m^2}{g_{ds}^2 + \omega^2 C_L^2} \left( \frac{g_m^2}{g_{ds}^2 + \omega^2 C_{gs2}^2} + 1 \right) \right)^{\frac{1}{2}} \quad (45)$$

Eqn.(45) shows that we have a lowpass-filter with maximum at  $\omega = 0$  and that

$$|H(0)| = \left( \frac{g_m^2}{g_{ds}^2} \left( \frac{g_m^2}{g_{ds}^2} + 1 \right) \right)^{\frac{1}{2}} \quad (46)$$

The 3 dB cut-off frequency  $\omega_0$  determines of the relation  $|H(\omega_0)| = \frac{1}{\sqrt{2}} \cdot |H(\omega)|_{max}$  i.e.  $|H(\omega_0)| = \frac{1}{\sqrt{2}} \cdot |H(0)|$  in our example. For convenience in this example we can rewrite this condition as:

$$|H(\omega_0)|^2 = \frac{1}{2} \cdot |H(0)|^2 \quad (47)$$

Eqns. (45)-(47) give:

$$\frac{g_m^2}{g_{ds}^2 + \omega_0^2 C_L^2} \left( \frac{g_m^2}{g_{ds}^2 + \omega_0^2 C_{gs2}^2} + 1 \right) = \frac{1}{2} \cdot \frac{g_m^2}{g_{ds}^2} \left( \frac{g_m^2}{g_{ds}^2} + 1 \right) \quad (48)$$

Rewriting eqn. (48) gives:

$$\frac{1}{1 + \left( \frac{\omega_0 C_L}{g_{ds}} \right)^2} \left( \frac{g_m^2}{g_{ds}^2 \left( 1 + \left( \frac{\omega_0 C_{gs2}}{g_{ds}} \right)^2 \right)} + 1 \right) = \frac{1}{2} \cdot \left( \frac{g_m^2}{g_{ds}^2} + 1 \right) \quad (49)$$



As  $C_L \gg C_{gs2}$  we put  $C_{gs2}$  to zero which gives the approximation:

$$\frac{1}{1 + \left(\frac{\omega_0 C_L}{g_{ds}}\right)^2} \approx \frac{1}{2} \quad (50)$$

Eqn. (5) gives the 3 dB cut-off frequency:

$$\omega_0 \approx \frac{g_{ds}}{C_L} \Rightarrow f_{3dB} \approx \frac{g_{ds}}{2\pi C_L} \quad (51)$$

The noise-bandwidth concept gives that:

$$P_{out,noise} \approx R_{out} \cdot |H(\omega_0)|^2 \cdot \frac{\pi}{2} \cdot f_{3dB} = \frac{8kT}{3} \cdot \frac{1}{g_m} \cdot \frac{g_m^2}{g_{ds}^2} \left(\frac{g_m^2}{g_{ds}^2} + 1\right) \cdot \frac{\pi}{2} \cdot \frac{g_{ds}}{2\pi C_L} \quad (52)$$

Which gives the answer:

$$\underline{\underline{P_{out,noise} \approx \frac{2kT}{3} \cdot \frac{g_m}{g_{ds}} \left(\frac{g_m^2}{g_{ds}^2} + 1\right) \cdot \frac{1}{C_L}}} \quad (53)$$

c) As  $g_m \sim \sqrt{I_D}$  and  $g_{ds} \sim I_D$  and  $I_D = I_{bias}$  in this example we have:

$$P_{out,noise} \sim \frac{1}{\sqrt{I_{bias}}} \left(\frac{1}{I_{bias}} + 1\right) \quad (54)$$

Obviously  $P_{out,noise}$  will decrease if  $I_{bias}$  is increased.

The DC gain is

$$|H(0)| = \left(\frac{g_m^2}{g_{ds}^2} \left(\frac{g_m^2}{g_{ds}^2} + 1\right)\right)^{\frac{1}{2}}$$

I.e.

$$|H(0)|^2 \sim \frac{1}{I_{bias}} \left(\frac{1}{I_{bias}} + 1\right) \quad (55)$$

Which shows that also the DC gain will decrease if  $I_{bias}$  is increased.