

Addition and subtraction

TSTE18 Digital Arithmetic Seminar 2

Oscar Gustafsson

- ▶ **Ripple-carry addition**
- ▶ **Solutions to slow ripple-carry addition**
 - ▶ **Redundant number systems**
 - ▶ Carry-acceleration
- ▶ Multi-operand addition

Binary addition

- ▶ Add the two binary numbers

$$X = \sum_{i=-L}^{M-1} x_i 2^i \text{ and } Y = \sum_{i=-L}^{M-1} y_i 2^i \quad (1)$$

- ▶ The result can be written as

$$S = c_M + \sum_{i=-L}^{M-1} s_i 2^i \quad (2)$$

where

$$s_i = x_i \oplus y_i \oplus c_i$$


and

$$c_{i+1} = \text{majority}(x_i, y_i, c_i) = x_i y_i + y_i c_i + x_i c_i = x_i y_i + (x_i \oplus y_i) c_i$$

with $c_{-L} = c_n = 0$

Binary addition

 - ▶ These equations are often realized with a full adder cell employing three inputs, x_i , y_i , and c_i , and two outputs, s_i and c_{i+1}




- ▶ Note that the signals of a full adder cell computes the expression

$$2c_{i+1} + s_i = x_i + y_i + c_i \quad (3)$$

Binary addition

- ▶ Gate level realization

 - ▶ Several full adders are connected to form a ripple carry adder



Redundant adders

- ▶ Redundant example:

Value	7	6	5	4	3	2	1	0	Signal
75	0	1	0	0	1	0	1	1	x_i
94	+	0	1	0	1	1	1	0	y_i
169		0	2	0	1	2	1	2	s_i

- ▶ Constant gate delay!

Addition

- ▶ Ripple carry adders are the base line adders
- ▶ Gate delay linear in the word length

- ▶ Example

Value	7	6	5	4	3	2	1	0	Signal
75	0	1	0	0	1	0	1	1	x_i
94	+	0	1	0	1	1	1	0	y_i
	0	0	0	1	1	1	0		c_i
169		1	0	1	0	1	0	0	s_i

- ▶ Becomes problematic for high-speed implementations
- ▶ Can be improved in two different ways
 - ▶ Compute the carries in parallel (carry-acceleration)
 - ▶ Do not compute the carries (redundant number systems)

Carry-save representation

- ▶ A practical redundant number system is the carry-save representation
- ▶ Consider a ripple carry adder where the carries are not connected to the next stage
- ▶ Three words can be added and the result is represented using two outputs (carry and sum)

- ▶ Example

Value	7	6	5	4	3	2	1	0	Signal
75	0	1	0	0	1	0	1	1	x_i
-98	1	0	0	1	1	1	0		y_i
7	+	0	0	0	0	0	1	1	z_i
30	\oplus	0	0	0	1	1	1	1	c_i
-46	+	1	1	0	1	0	0	1	s_i
-16		1	1	0	1	1	2	0	

Carry-save representation

- ▶ Carry-save representation can be seen as a representation using a digit-set $\{0, 1, 2\}$
- ▶ Two's complement representation can be straightforwardly used (the MSD has negative sign)

Carry-save representation

- ▶ Consider a three digit CS representation:

Value	Representation
6	022
5	021
4	020
3	012
	011
2	010
	002
	122
1	001
	121
0	000
	120
	112
-1	111
-2	110
	102
	222
-3	101
	221
-4	100
	220
-5	
-6	212
-7	211
-8	210
	202
	201
	200

Carry-save representation

- ▶ Assume that the result should be converted to a number in the corresponding three-bit two's complement range $[-4, 3]$

Value	Representation
3	011
2	010
1	002
	122
	001
	121
0	000
	120
	112
-1	111
-2	110
-3	102
-4	101
	222
	101
	221
	100
	220
	212

Carry-save representation

- ▶ The result of a carry-save addition will never give two in the least significant digit (despite being a valid CS representation)

Value	Representation
3	011
2	010
1	001
	121
0	000
	120
-1	111
-2	110
-3	101
-4	100
	221
	100
	220

- ▶ If both MSBs are either one or zero, the sign of the result is well defined
- ▶ If exactly one of the MSBs is one, it is not possible to determine the sign directly
- ▶ Note that -1 has a unique representation (although there are many bit-patterns corresponding to -1)
- ▶ Hence, a quick way to detect zero is to add -1 and check for all ones among the digits

Carry-save representation

- ▶ However, the carry-save representation is possibly shift unsafe
- ▶ Consider the following example

Value	Bits
2	0 1 0
-2	1 1 0
0	+ 0 0 0
-4	ϕ 1 0
-4	1 0 0
-8	ϕ 0 0 0

- ▶ Why does it work?
 - ▶ All three-bit two's complement arithmetic is performed modulo 8 (the effect of ignoring the carry output)
 - ▶ Hence, $-8 \pmod 8 = 0$

Carry-save representation

- ▶ Focus on the two most significant positions
- $$\begin{array}{cccc}
 c_{M+1} & c_M & c_{M+1} & c_M \\
 s_{M+1} & s_M & s_M & s_M
 \end{array}$$
- ▶ In the example we neglected the carry output twice
 - ▶ Consider extending the wordlength

Value	Bits
2	0 1 0
-2	1 1 0
0	+ 0 0 0
4	0 1 0
-4	+ 1 1 0
0	ϕ 0 0 0

Carry-save representation

- ▶ Consider shifting the carry-save result one position to the right

Value	Bits
-2	1 1 0
-2	+ 1 1 0
-4	ϕ 1 0 0

- ▶ Note that the other representations of 0 works OK
 - ▶ $000 \Rightarrow 000.0$
 - ▶ $120 \Rightarrow 112.0 = -4 + 2 + 2 \times 1$
 - ▶ $112 \Rightarrow 111.2 = -4 + 2 + 1 + 2 \times \frac{1}{2}$
- ▶ How can this be solved?

Carry-save representation

- ▶ Shifting this representation is OK!
- | Value | Bits |
|-------|-----------|
| 2 | 0 0 1 0 |
| -2 | + 1 1 1 0 |
| 0 | ϕ 0 0 0 |
- ▶ So extending the word length helps – But not really the solution!
 - ▶ The sum sign-bit is always the same after sign extension / right shift
 - ▶ Problem occurs when the neglected carry bit is different from the carry sign bit, as the neglected carry bit is the correct bit to shift in

Carry-save representation

- ▶ Consider the troublesome cases (remember that the result should be in the range $[-4, 3]$)

c_{M+1}	s_M	c_M	Value	Correct	Comment
0	0	1	1	1	Overflow
0	1	1	2	0	
1	0	0	0	2	
1	1	0	1	1	Overflow

- ▶ Remaining cases

c_{M+1}	s_M	c_M	Value	Correct
0	0	0	0	0
0	1	0	1	1
1	0	1	1	1
1	1	1	2	2

Carry-save representation

- ▶ Truth table

c_{M+1}	s_M	c_M	Value
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	2
1	0	1	1
1	1	0	1
1	1	1	2

- ▶ Can replace the sign-bits as

$$c'_M = c_{M+1} \oplus s_M \oplus c_M$$

$$s'_M = c_{M+1}$$

Carry-save representation

- ▶ Redo the example

Value	Bits
2	0 1 0
-2	1 1 0
0	+ 0 0 0
0	⊕ 0 0 0
0	+ 0 0 0
0	⊕ 0 0 0

Redundant adders

- ▶ What about adding two redundant numbers?
- ▶ Let us consider a higher radix and come back to radix-2 later
- ▶ Adding two (non-redundant) radix-4 numbers

i	7	6	5	4	3	2	1	0	Signal
	0	3	0	1	2	3	1	2	x_i
+	1	1	3	2	0	1	3	3	y_i
	1	4	3	3	2	4	4	5	s_i

- ▶ In general it will be enough to use digits up to $2(r - 1)$ to represent the sum of two non-redundant numbers

Redundant adders

- ▶ Add two redundant numbers

i	7	6	5	4	3	2	1	0	Signal
	0	3	4	1	2	4	1	5	x_i
+	1	2	3	2	0	0	5	3	y_i
	1	5	7	3	2	4	6	8	s_i

- ▶ The required range increases for each term
- ▶ Would like to move the results to within a suitable range ($2(r - 1)$, in this case 6)
- ▶ Worst case result is 12, which is $2 \cdot 4 + 4$, leading to that we propagate a “carry”, called transfer digit, of two to the next stage and keep an interim digit 4

Redundant adders

- ▶ The largest incoming transfer digit is, thus, 2
- ▶ Hence, if we can make sure that the interim digit is at most 4, there will never be any further carries generated
- ▶ Example

i	7	6	5	4	3	2	1	0	Signal
	0	3	4	1	2	4	1	5	x_i
+	1	2	3	2	0	0	5	3	y_i
	1	5	7	3	2	4	6	8	Partial result
	0	1	1	0	0	1	1	-	transfer digit
	1	1	3	3	2	4	2	4	interim digit
	0	2	2	3	3	2	5	3	4
									result

Signed-digit representations

- ▶ Last time we saw that a radix- r representation should have digits in the range $0 \leq x_i \leq r - 1$ to be non-redundant
- ▶ This can be generalized to $-\alpha \leq x_i \leq \beta$ leading to a signed-digit representation, i.e., the digit may have a sign
- ▶ A signed-digit representation can be either redundant or non-redundant
 - ▶ $\alpha + \beta = r - 1$: non-redundant
 - ▶ $\alpha + \beta \geq r$: redundant (compare with $x_i \geq r$)
- ▶ Define the *redundancy index* as $\rho = \alpha + \beta - r + 1$
- ▶ If $\rho \geq 1$, the representation is redundant
- ▶ For radix-2, the most common SD representation is the binary signed digit with $x_i \in \{-1, 0, 1\}$
- ▶ Here, $\alpha = 1$, $\beta = 1$, and $\rho = 1$

Generalized carry-free addition

- ▶ The earlier described constant time addition can be described as follows
 1. Compute digit-wise sums for each position, $p_i = x_i + y_i$
 2. Divide the sum into a transfer digit, t_{i+1} , and an interim digit, $w_i = p_i - t_{i+1}r$
 3. Add the interim digit and the incoming transfer digit to obtain the sum $s_i = w_i + t_i$

Generalized carry-free addition

- ▶ Assume the transfer digit is in the range $t_{\min} \leq t_i \leq t_{\max}$ and the interim digit is in the range $w_{\min} \leq w_i \leq w_{\max}$
- ▶ Clearly, we should have $t_{\max} + w_{\max} = \beta$ and $t_{\min} + w_{\min} = -\alpha$ (if not α and β can be changed)
- ▶ The interim sum is bounded as $-2\alpha \leq p_i \leq 2\beta \Rightarrow -2\alpha \leq w_i + rt_{i+1} \leq 2\beta$
- ▶ For the largest digit-wise sum it must hold that

$$w_{\min} + rt_{\min} \leq -2\alpha$$

$$w_{\max} + rt_{\max} \geq 2\beta$$

- ▶ Combining these equations with those above leads to

$$t_{\min} \leq -\frac{\alpha}{r-1}$$

$$t_{\max} \geq \frac{\beta}{r-1}$$

- ▶ In addition, $w_{\max} - w_{\min} \geq r - 1$ to result in all intermediate values possible for the encoding

Binary signed-digit addition

- ▶ The main obstacle to avoid is that the incoming transfer digit and the interim digit are both 1 or both -1 as the result will not be within the correct range
- ▶ One way to solve this is to do the computation in a third step as

1. Compute digit-wise sums for each position, $p_i = x_i + y_i$
2. Divide the sum into a transfer digit, t_{i+1} , and an interim digit, w_i , based on the preliminary incoming transfer digit, e_{i-1} , where $e_j = 0$ if $x_j \geq 0$ and $y_j \geq 0$

p_i	e_{i-1}	t_{i+1}	w_i
2	-	1	0
1	0	1	-1
1	1	0	1
0	0	0	0
-1	0	0	-1
-1	1	-1	1
-2	0	-1	0

3. Add the interim digit and the incoming transfer digit to obtain the sum $s_i = w_i + t_i$

Generalized carry-free addition

- ▶ For the previous scheme to operate properly one of the following two cases are required:
 - ▶ $r \geq 3, \rho \geq 3$
 - ▶ $r \geq 3, \rho = 2, \alpha \neq 1, \beta \neq 1$
- ▶ This means that binary signed-digit can not utilize the generalized carry-free addition
- ▶ However, a limited carry-propagation addition algorithm is available

Binary signed-digit addition

- ▶ Example

i	4	3	2	1	0	Signal
	1	0	-1	0	-1	x_i
+	0	-1	0	1	-1	y_i
	1	-1	-1	1	-2	p_i
	0	1	1	0	1	e_i
0	-1	0	0	-1	-	transfer digit
	1	1	-1	1	0	interim digit
0	0	1	-1	0	0	result