

Addition and subtraction

TSTE18 Digital Arithmetic Seminar 3

Oscar Gustafsson

- ▶ Ripple-carry addition
- ▶ Solutions to slow ripple-carry addition
 - ▶ Redundant number systems
 - ▶ Carry-acceleration
- ▶ Multi-operand addition

Carry look-ahead addition

- ▶ The carry can either take on a value independent on the carry input or the exact value of the carry input
- ▶ These cases are

a_i	b_i	c_{i+1}	Case
0	0	0	No carry-propagation (kill)
0	1	c_i	Carry-propagation (propagate)
1	0	c_i	Carry-propagation (propagate)
1	1	1	Carry-generation (generate)

- ▶ We can define propagate, p_i , and generate, g_i at bit-level as

$$p_i = a_i \oplus b_i \text{ and } g_i = a_i b_i \tag{1}$$

Carry look-ahead addition

- ▶ The carry output can then be expressed as

$$c_{i+1} = g_i + p_i c_i \tag{2}$$

- ▶ For the next stage the expression becomes

$$\begin{aligned} c_{i+2} &= g_{i+1} + p_{i+1} c_{i+1} = g_{i+1} + p_{i+1} (g_i + p_i c_i) \\ &= g_{i+1} + p_{i+1} g_i + p_{i+1} p_i c_i \end{aligned} \tag{3}$$

- ▶ For $N + 1$ -th stage we have

$$\begin{aligned} c_{i+(N+1)} &= g_{i+N} + p_{i+N} g_{i+(N-1)} + p_{i+N} p_{i+N-1} g_{i+(N-2)} + \\ &\quad + \dots + p_{i+(N-1)} \dots p_{i+1} p_i c_i \end{aligned} \tag{4}$$

Carry look-ahead addition

- ▶ Hence, it is possible to compute all carries in parallel

$$\begin{aligned}
 c_{i+1} &= g_i + p_i c_i \\
 c_{i+2} &= g_{i+1} + p_{i+1} g_i + p_{i+1} p_i c_i \\
 c_{i+3} &= g_{i+2} + p_{i+2} g_{i+1} + p_{i+2} p_{i+1} g_i + p_{i+2} p_{i+1} p_i c_i \\
 c_{i+4} &= g_{i+3} + p_{i+3} g_{i+2} + p_{i+3} p_{i+2} g_{i+1} + p_{i+3} p_{i+2} p_{i+1} g_i + \\
 &\quad p_{i+3} p_{i+1} p_i c_i \\
 &\dots
 \end{aligned}$$

- ▶ This will lead to high fan-out for the signals p_j and g_j and high fan-in gates for higher order terms


Carry look-ahead addition

- ▶ These terms can be grouped as

$$\begin{aligned}
 c_{i+(N+1)} &= \underbrace{g_{i+N} + p_{i+N} g_{i+(N-1)} + p_{i+N} p_{i+N-1} g_{i+(N-2)} + \dots +}_{G_{i+N;i}} \\
 &\quad + \underbrace{p_{i+N} p_{i+N-1} \dots p_{i+1} p_i}_{P_{i+N;i}} c_i \\
 &= G_{i+N;i} + P_{i+N;i} c_i
 \end{aligned}$$

where $G_{i+N;i}$ is called group generate and $P_{i+N;i}$ group propagate as they correspond to the generate and propagate signals for the group of bits $i + N$ to i

 - ▶ The group generate and propagate signals can be computed before the incoming carry is known to speed up the output carry generation



Prefix problem

- ▶ The prefix problem is that of computing the results

$$b_k = a_1 \circ a_2 \circ \dots \circ a_k, \quad 1 \leq k \leq n \quad (5)$$

for all k where \circ is an associative operator

- ▶ As can be seen, each result b_k depends on all previous inputs a_i , $i \leq k$ as for the carry problem
- ▶ This also has applications in e.g. sorting

Parallel prefix addition

- ▶ The carry signal in position k can be written as

$$c_{k+1} = G_{k:l} + P_{k:l} c_l \quad (6)$$

- ▶ Similarly, the sum signal in position k for an adder using N bits is then expressed as

$$s_k = a_k \oplus b_k \oplus c_k = p_k \oplus (G_{(k-1):0} + P_{(k-1):0} c_n) = p_k \oplus c_k \quad (7)$$

- ▶ Of interest to compute all group generate and group propagate originating from the LSB position, i.e., $G_{k:0}$ and $P_{k:0}$ for $1 \leq k \leq W \Rightarrow$ parallel prefix.

Parallel prefix addition

- ▶ For parallel prefix adders, we introduce the dot operator • as

$$\begin{bmatrix} g_k \\ p_k \end{bmatrix} = \begin{bmatrix} g_i \\ p_i \end{bmatrix} \bullet \begin{bmatrix} g_j \\ p_j \end{bmatrix} \triangleq \begin{bmatrix} g_i + p_i g_j \\ p_i p_j \end{bmatrix} \quad (8)$$

- ▶ Adders based on dot operators are commonly referred to as parallel prefix adders
- ▶ The group generate and propagate for bits k to l can be written as


$$\begin{bmatrix} G_{k:l} \\ P_{k:l} \end{bmatrix} \triangleq \begin{bmatrix} g_k \\ p_k \end{bmatrix} \bullet \begin{bmatrix} g_{k+1} \\ p_{k+1} \end{bmatrix} \bullet \dots \bullet \begin{bmatrix} g_l \\ p_l \end{bmatrix} \quad (9)$$

Parallel prefix addition

- ▶ The idempotency leads to the very useful property that overlapping groups does not cause any problems

$$\begin{bmatrix} G_{k:n} \\ P_{k:n} \end{bmatrix} = \begin{bmatrix} G_{k:l} \\ P_{k:l} \end{bmatrix} \bullet \begin{bmatrix} G_{m:n} \\ P_{m:n} \end{bmatrix}, \quad k \geq l, m \geq n, m \geq l - 1, \quad (10)$$

which can be illustrated as below

 

Parallel prefix addition

- ▶ The dot-operator is associative

$$\begin{bmatrix} g_k \\ p_k \end{bmatrix} = \left(\begin{bmatrix} g_i \\ p_i \end{bmatrix} \bullet \begin{bmatrix} g_j \\ p_j \end{bmatrix} \right) \bullet \begin{bmatrix} g_l \\ p_l \end{bmatrix} = \begin{bmatrix} g_i \\ p_i \end{bmatrix} \bullet \left(\begin{bmatrix} g_j \\ p_j \end{bmatrix} \bullet \begin{bmatrix} g_l \\ p_l \end{bmatrix} \right)$$

- ▶ Idempotent


$$\begin{bmatrix} g_k \\ p_k \end{bmatrix} = \begin{bmatrix} g_k \\ p_k \end{bmatrix} \bullet \begin{bmatrix} g_k \\ p_k \end{bmatrix}$$

- ▶ But not commutative

$$\begin{bmatrix} g_k \\ p_k \end{bmatrix} = \begin{bmatrix} g_i \\ p_i \end{bmatrix} \bullet \begin{bmatrix} g_j \\ p_j \end{bmatrix} \neq \begin{bmatrix} g_j \\ p_j \end{bmatrix} \bullet \begin{bmatrix} g_i \\ p_i \end{bmatrix}$$


Parallel prefix addition

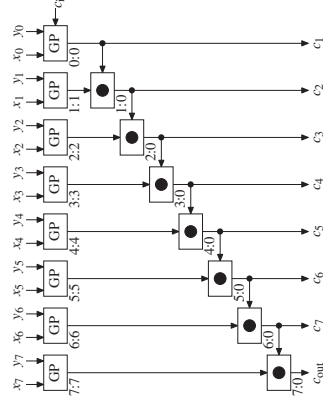- ▶ Of interest to compute all group generate and group propagate originating from the LSB position, i.e., $G_{k:0}$ and $P_{k:0}$ for $1 \leq k \leq W$
- ▶ Can be computed sequentially



Parallel prefix addition

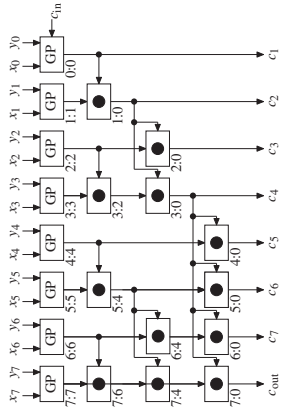
- ▶ Can also use the properties of the dot product and compute it in parallel



- ▶ Many different structures for computing the dot product trees have been proposed trading dot operators, fan-out, wire length, etc.

Parallel prefix addition

 
- ▶ Often a simplified view is used to represent the dot-products




- ▶ This is the so called Ladner-Fischer parallel prefix structure

Parallel prefix addition

 - ▶ The Ladner-Fischer approach is optimal in the number of stages and is composed as




- ▶ For size 16 this gives

 

- ▶ However, the worst fan-out is $N/2$ leading to problems in VLSI implementations

Parallel prefix addition

 - ▶ An alternative depth-optimal structure was proposed by Kogge and Stone as




for size 16

- ▶ Here, the fan-out is decreased to 4 (2 with buffers) at the cost of more dot operators (49 compared to 32 for Ladner-Fischer)

Parallel prefix addition

 
- ▶ Another useful structure is the Brent-Kung approach as



- ▶ For this, the depth is increased but the fan-out and operator count is low

Parallel prefix addition

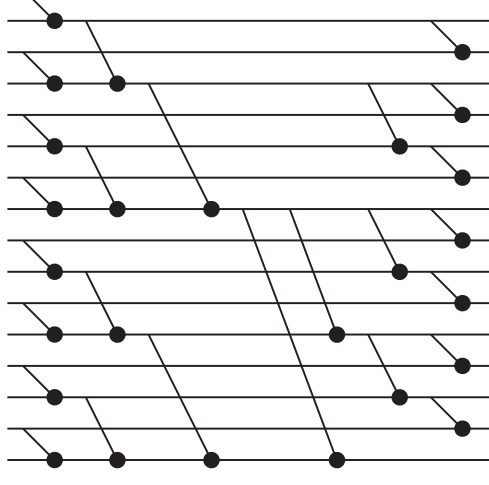- ▶ A 16-input Brent-Kung parallel prefix network




Parallel prefix addition

- ▶ Clearly, there are other trade-off available in terms of operators, depth, and maximum fan-out
- ▶ For those considered here with 16 inputs

Structure	Depth	Operators	Fan-out
Serial	15	15	1
Ladner-Fischer	4	32	8
Kogge-Stone	4	49	4 (2 with buffers)
Brent-Kung	6	26	3 (1 with buffers)
- ▶ Many more available with different trade-offs between these factors

Carry-select and conditional sum addition

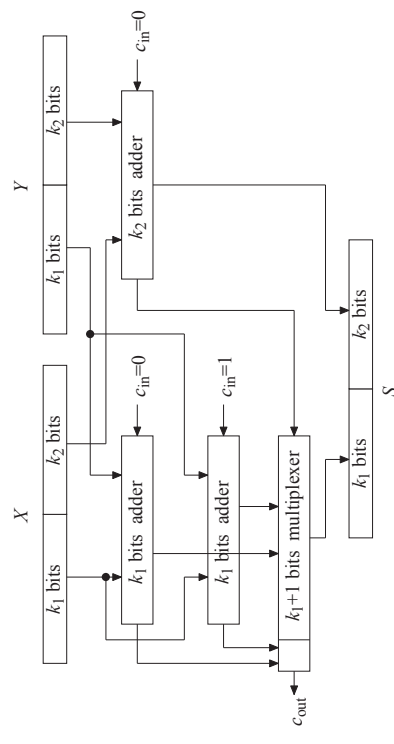- ▶ At any stage of the adder, the carry signal is either zero or one(!)
- ▶ Precompute both results and select the correct result once the correct carry arrives
- ▶ Carry-select adder



Carry-select and conditional sum addition


- ▶ The carry-select adder can of course be separate into several stages
- ▶ Breaking a word of length N into N/w stages of size w where $w \approx \sqrt{N}$ gives a good initial estimate of a suitable partitioning with delay $\propto \sqrt{N}$
- ▶ Best selection depends on the gate delays of the adders and the multiplexers
- ▶ Typically an increasing length provides slightly better results since the later adders have more time to finish because of the additional multiplexer delays for the incoming carry
- ▶ High fan-out for the carry signal controlling the multiplexers

Carry-select and conditional sum addition

- ▶ Each precomputation adder can in turn be split into a carry-select adder
- ▶ If this is done until the wordlength of each adder is one a conditional sum adder is obtained
- ▶ For each bit segment there are only two alternatives, $c_{in} = 0$ or $c_{in} = 1$
- ▶ Hence, the number of adders does not increase
- ▶ Can be seen as restructuring the multiplexer tree
- ▶ Example: derive an eight-bit conditional sum adder iteratively

Carry-skip addition

 
- ▶ Utilize the carry propagation information to skip parts of the carry-chain



- ▶ Breaking a word of length N into N/w parts of size w where $w \approx \sqrt{N}$ gives a good initial estimate of a suitable partitioning with delay $\propto \sqrt{N}$
- ▶ Note that $p_i = x_i \oplus y_i$ is often computed in the full adder anyway
- ▶ High-fan in for and-gate computing $P_{(b+c):c}$ (or $c_{c+1}P_{(b+c):c}$)

Manchester carry-chains

 
- ▶ Utilizing the ideas of the generate, propagate, and kill signals earlier defined as simple network of switches can be used for carry propagation as



- ▶ This is referred to as a Manchester carry-chain
- ▶ Each switch can be replaced with a transistor (plus buffers or inverters at appropriate places) to obtain simple and fast carry-propagation
- ▶ This is an efficient way to realize short ripple-carry adders in e.g. carry-select and carry-skip adders

Multi-operand addition

 - ▶ When adding more than two values, one can of course simply connect carry-propagation adders



- ▶ However, for high-speed realization it is not efficient to have multiple accelerated carry-propagation adders

Multi-operand addition

- ▶ Instead, carry-save adders are normally used and an accelerated carry-propagation adder is used to accumulate the sum and carry vectors at the end

