

Solution to lecture 12 exercises

12-100 a)

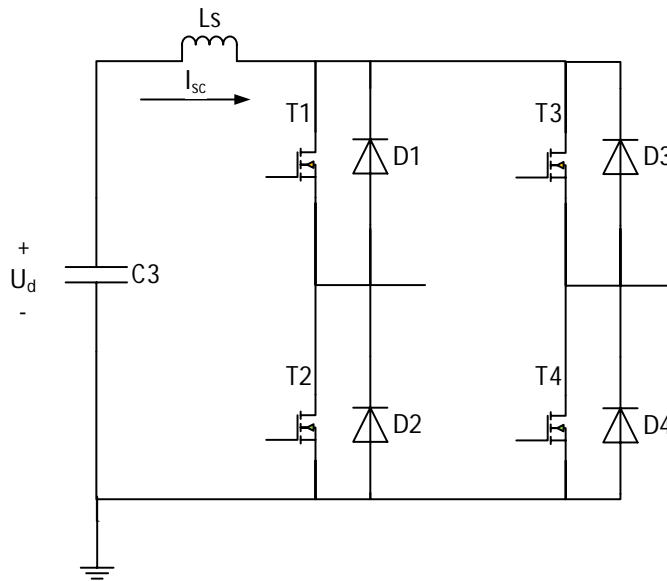


Figure 1

- $U_d = 15 \text{ V}$
- $L_s = 50 \text{ nH}$
- $C_3 = 560 \text{ }\mu\text{F}$

The full bridge of the Lab3 circuit is fed through the V_{in} supply which is having a capacitor C_3 connected according to the equivalent circuit in Figure 1 above.

The short circuit current can be calculated using the formula below based on the

surge impedance $\sqrt{\frac{L_s}{C_3}}$.

$$\hat{I}_{sc} = \frac{U_d}{\sqrt{\frac{L_s}{C_3}}}$$

$$\sqrt{\frac{L_s}{C_3}} = 9.4 \text{ mohm}$$

$$\hat{I}_{sc} = 1.6 \text{ kA}$$

Tomas Jonsson

The actual Lab 3 circuit (Figure 2) includes additional resistors R1, R3 = 0.56 ohm, in order to provide significant limitation of short circuit current.

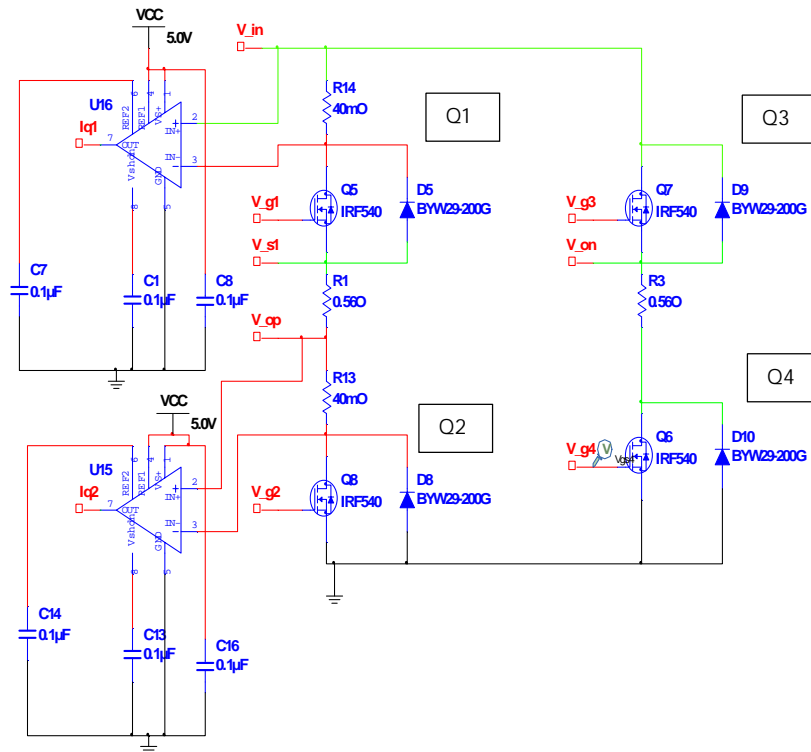


Figure 2

The total circuit involved at short circuit through Q1 and Q2, includes R14, R1 and R13 giving a total resistance of 0.64 ohm. The resulting short circuit current will be:

$$\frac{U_d}{R_{14}+R_1+R_{13}} = \frac{15}{0.64} = 23.4 \text{ A}$$

12-100 b)

The MOSFET, IRF540, which is used in the Lab 3 full-bridge inverter has the following absolute maximum current rating data:

- Continuous drain current, $I_D = 28\text{A}$
- Pulsed drain current, $I_{DM} = 110\text{A}$

Consequently, the calculated short circuit current is below both the pulsed and the continuous current which means no critical stresses are obtained.