

# TSTE19 Power Electronics

Lecture 11


Tomas Jonsson

ISY/EKS


# Outline

- Converter control
- Snubber circuits
- Lab 3 introduction
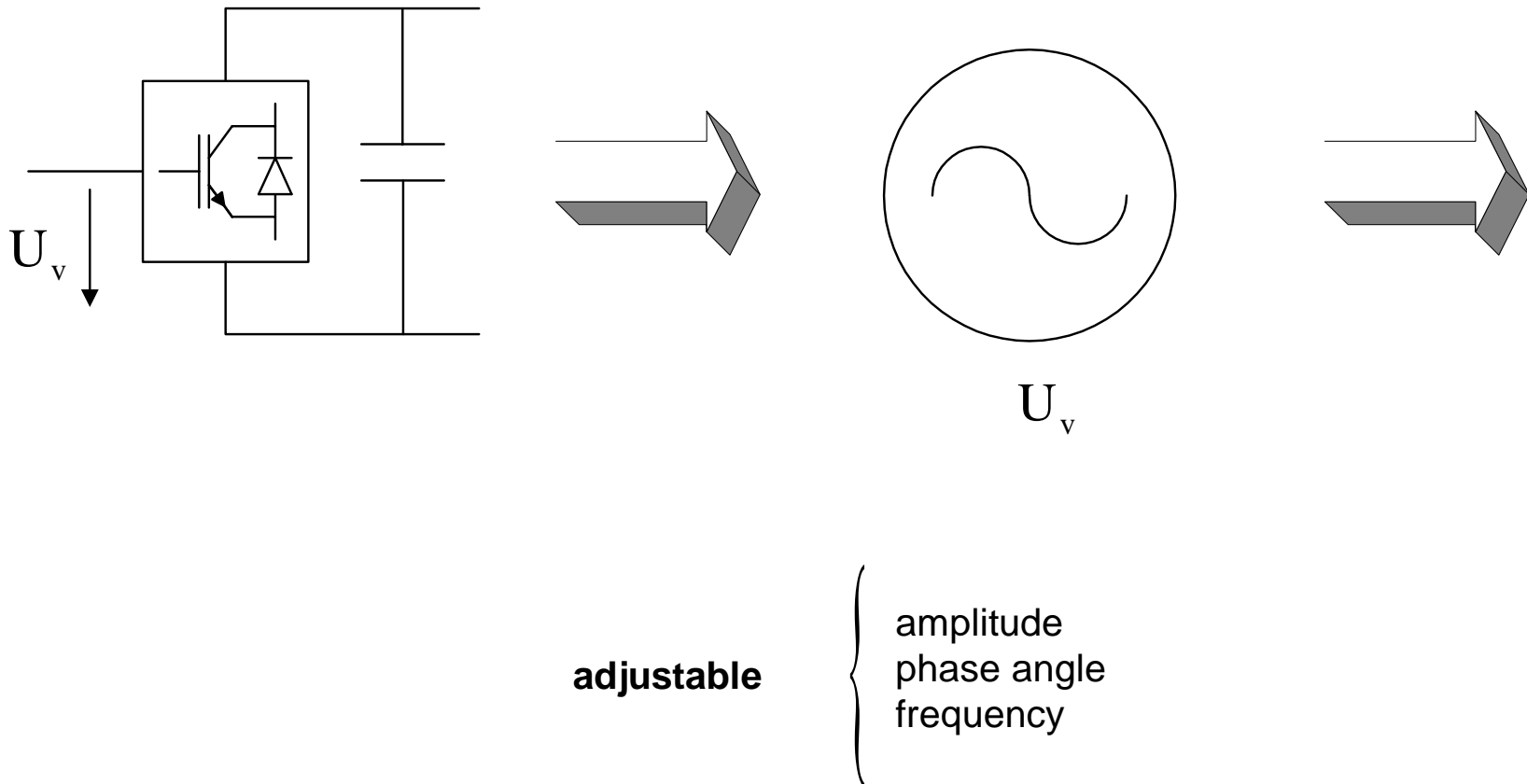
# Basic control principle. Voltage Source Converter (VSC)



# Control of Active and Reactive Power

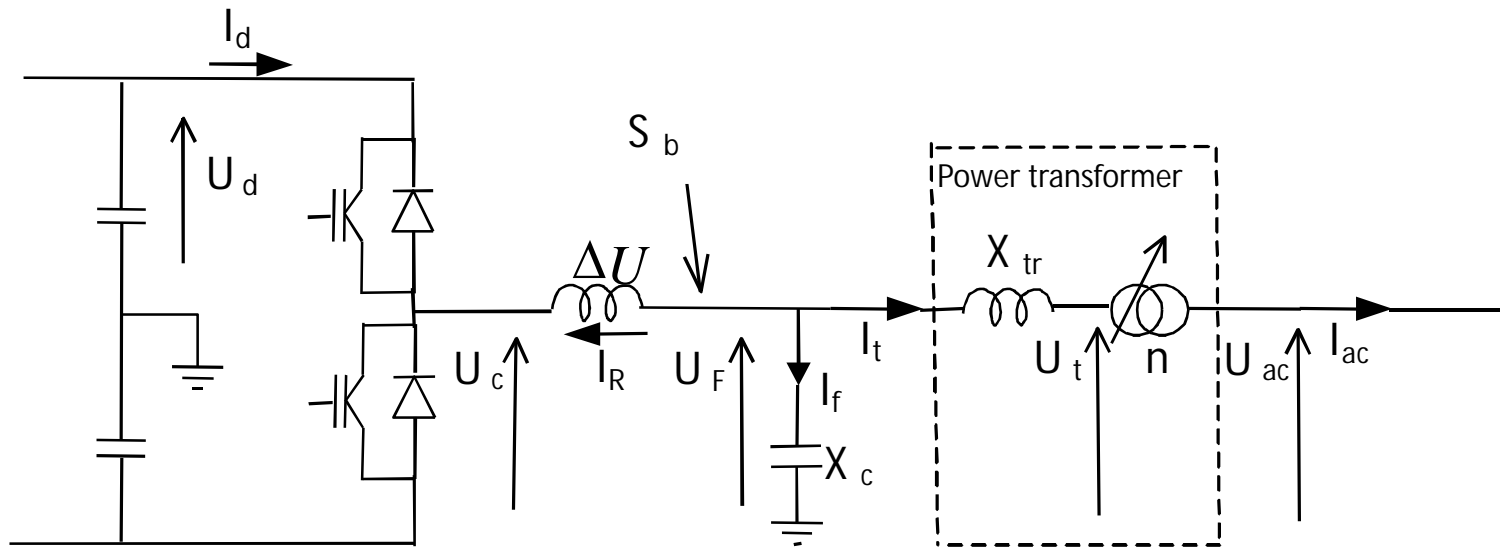


$$\vec{S}_b = P + jQ = \sqrt{3} \times \vec{U}_F \times \vec{I}_R^*$$

$$P = \frac{U_F \times U_C \times \sin \delta}{\omega L}$$


$$Q = -\frac{U_F \times (U_F - U_C \times \cos \delta)}{\omega L}$$

# Control of Active Power

## Rectifier

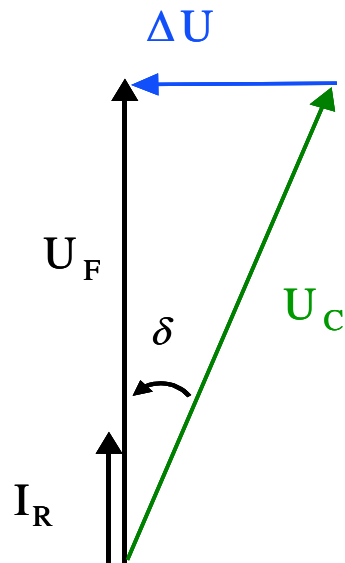


## Inverter

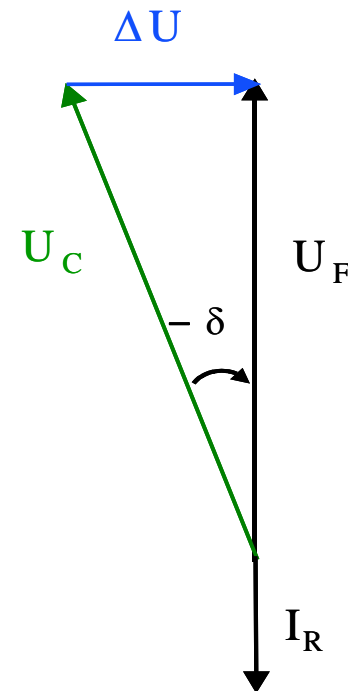


If the  $U_C$  is in phase-lag, the active power flows from AC to DC side (rectifier)  
 If the  $U_C$  is in phase-lead, the active power flows from DC to AC side (inverter)

# Control of Reactive Power

Reactive power  
consumption

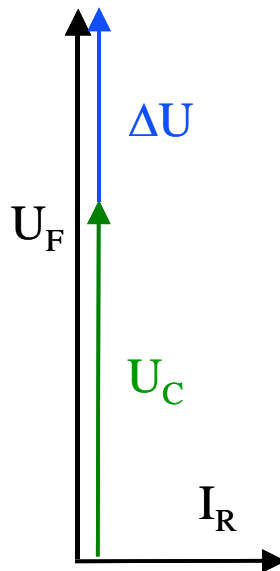


Reactive power  
generation

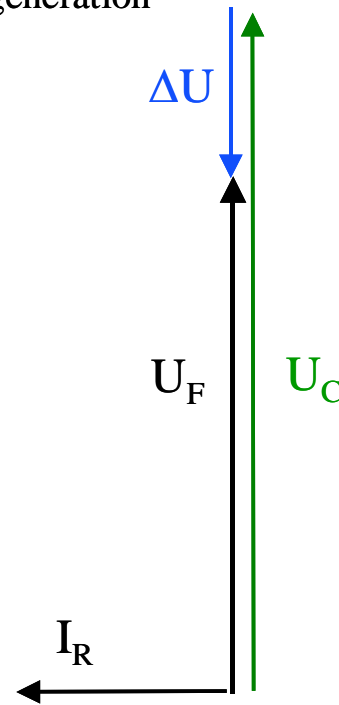


If  $U_F > U_C$ , there is reactive power consumption.

If  $U_C > U_F$ , there is reactive power generation.

# Control of P and Q in 4 quadrants

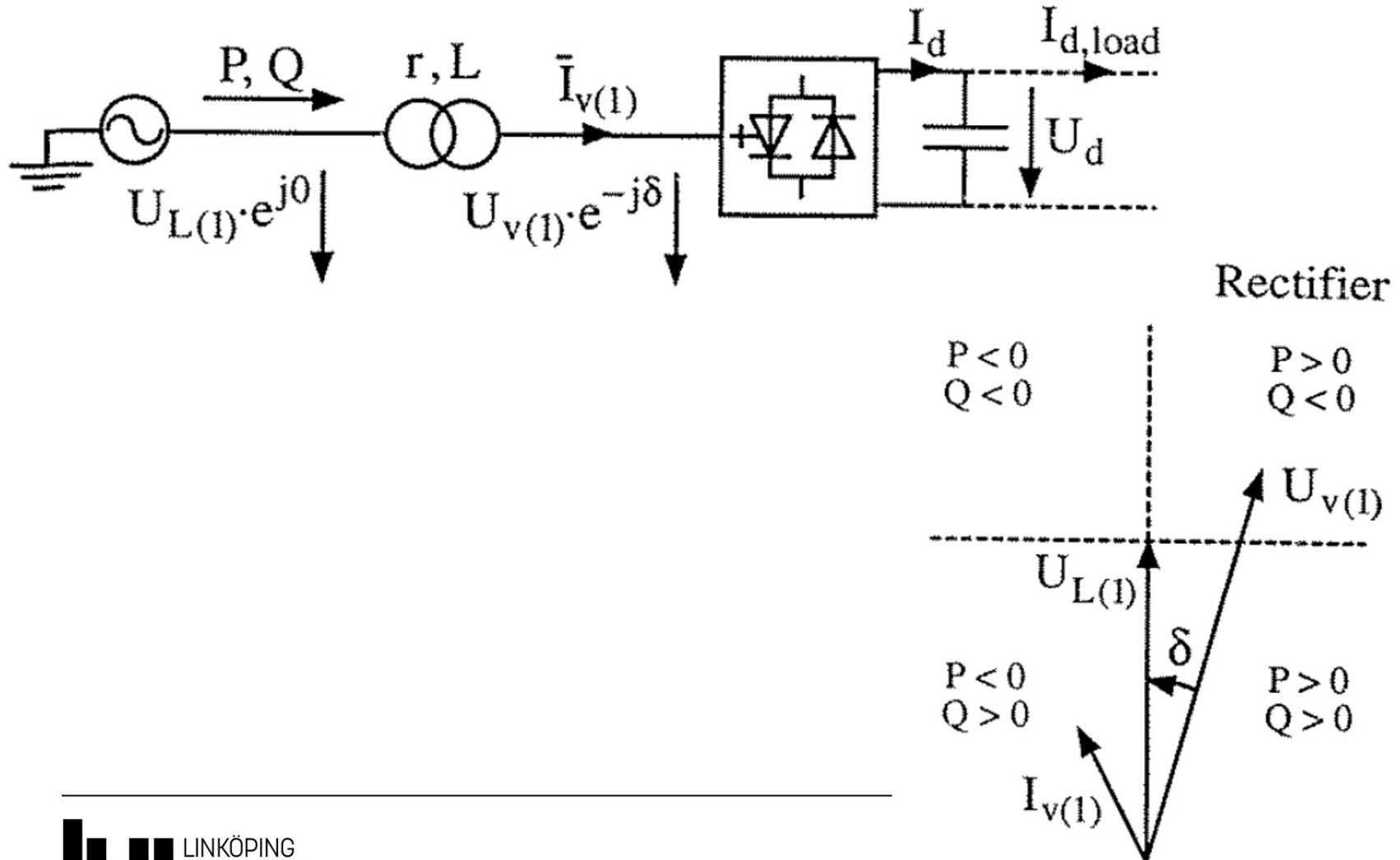


# Calculation of Control Signal

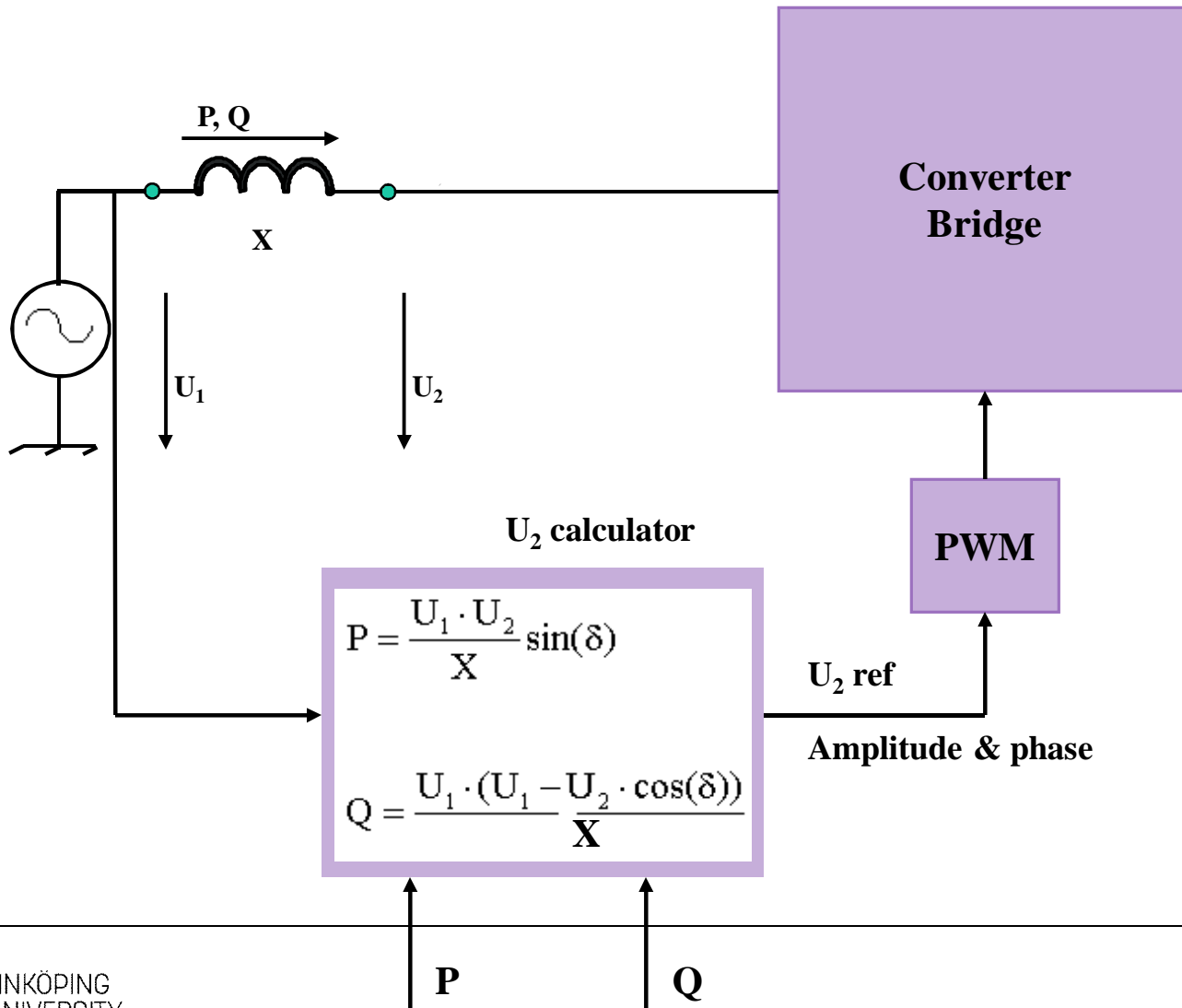



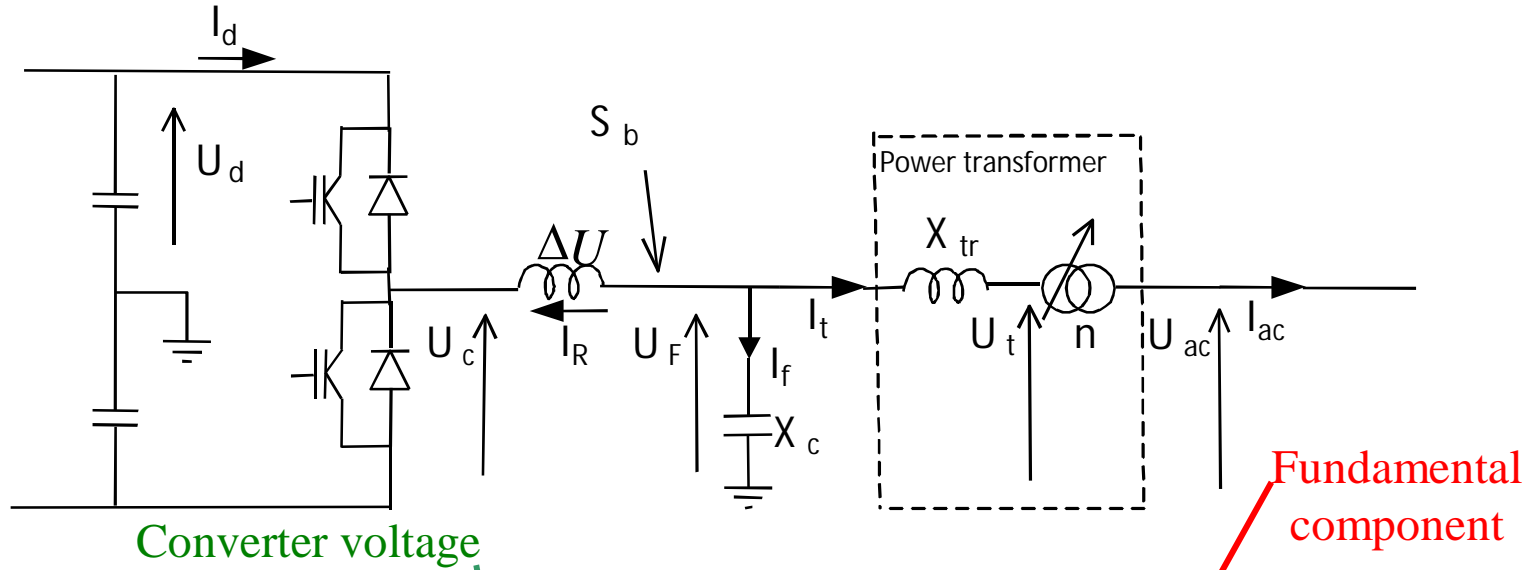
# Voltage Source Converter with Pulse Width Modulation




Converter voltage

Fundamental component

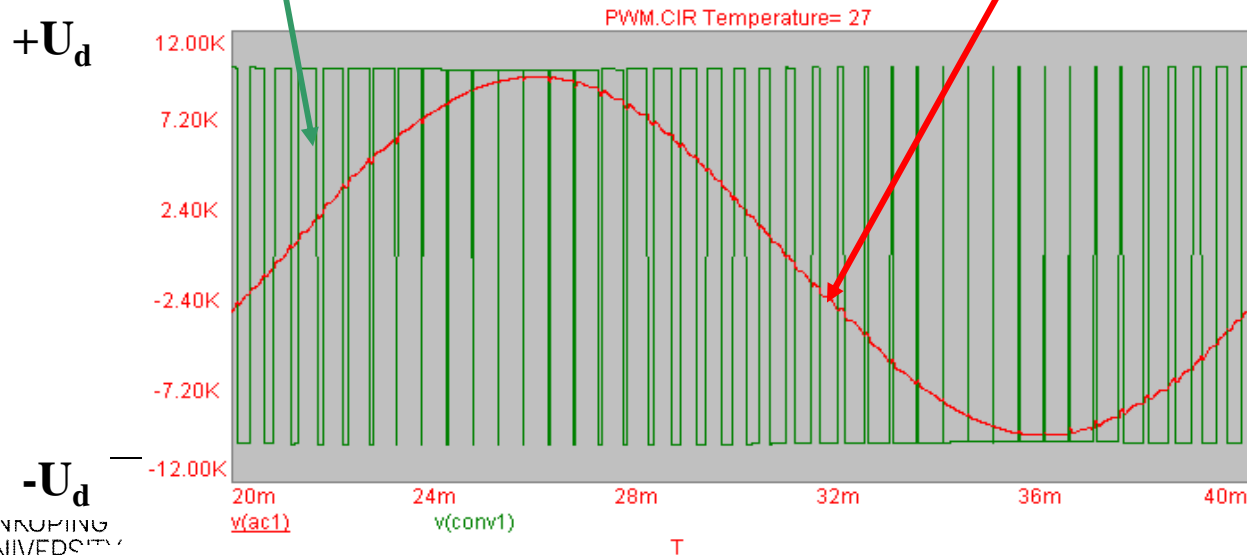


# PWM- generation of pulses

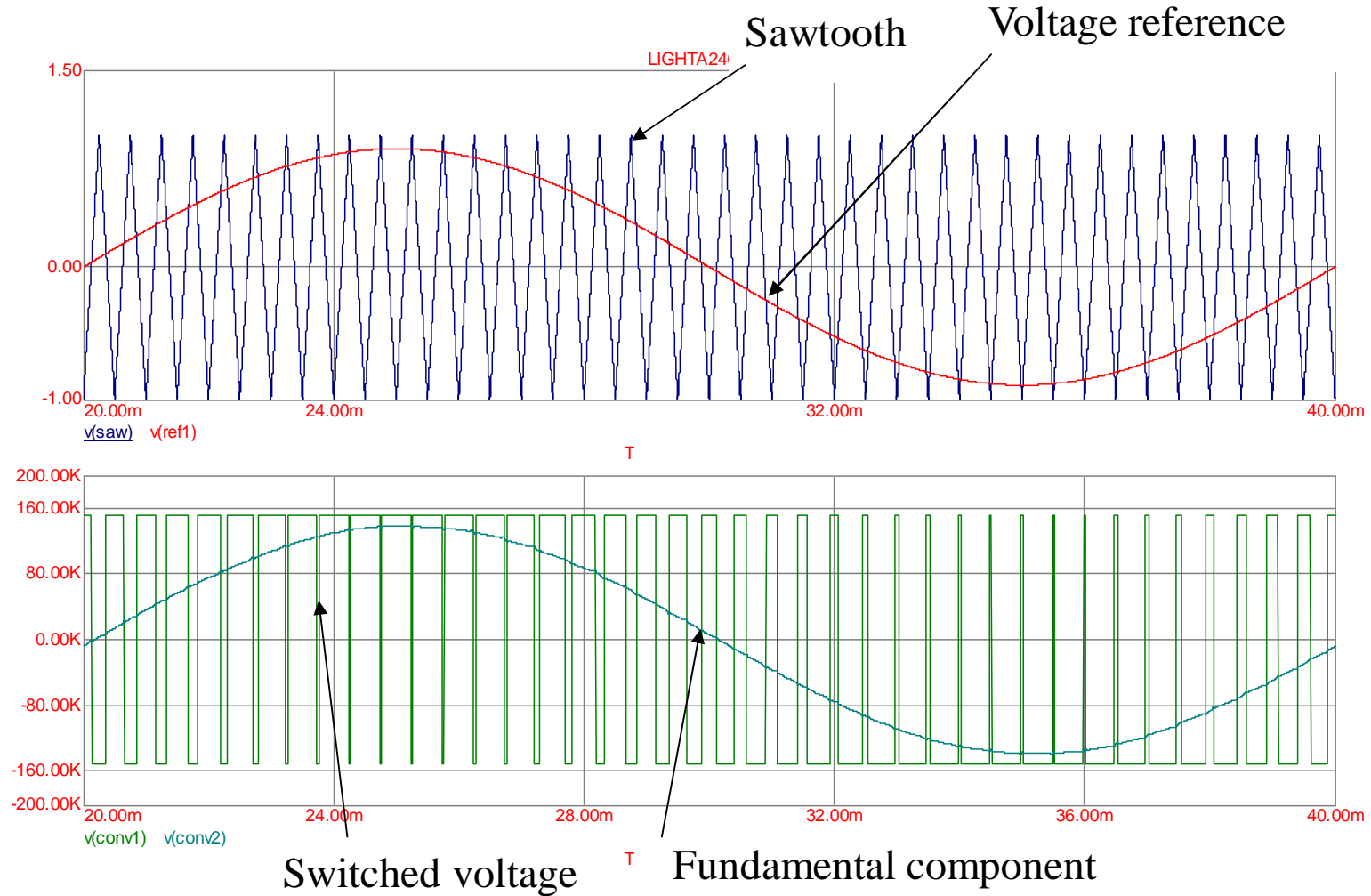

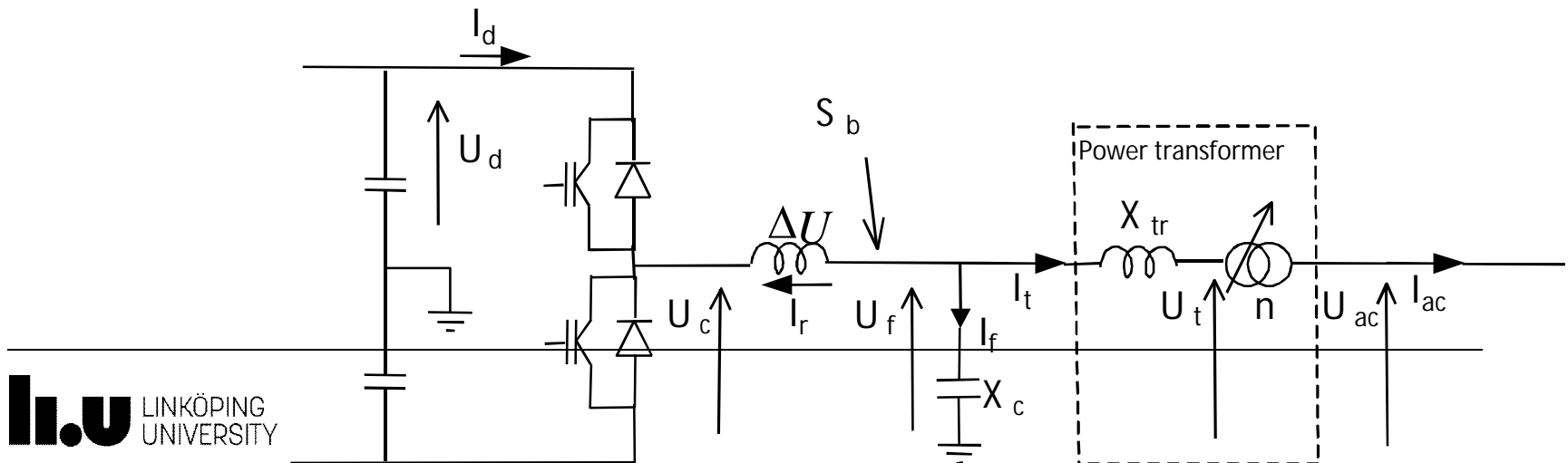
# Feed-forward control

- $U_c = U_f + L \frac{di_r}{dt}$
- $U_{cRef} = (Feedforward) + (Feedback)$
- $U_{cRef} = U_f + L \frac{di_r}{dt} + k(i_r - i_{rRef})$ 
  - $i_{rRef} = \hat{I}_{rRef} \cos(\omega t + \varphi)$



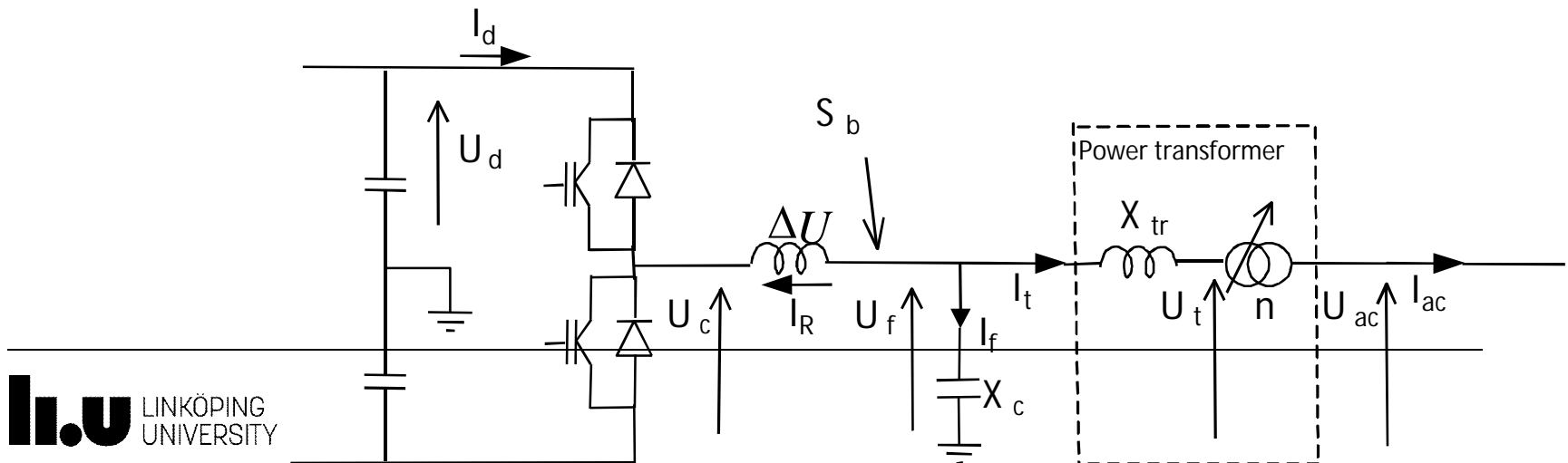
# Vector control


- $\bar{U}_c = \bar{U}_f + j\omega L \bar{I}_R$
- $\bar{I}_{rDQ} = i_r e^{-j\omega t} = \begin{cases} I_{rD} = i_r \cos \omega t \\ I_{rQ} = i_r \sin \omega t \end{cases}$
- $\bar{U}_{cDQref} = \bar{U}_{fDQ} + j\omega L \bar{I}_{rDQ} + k(\bar{I}_{rDQ} - \bar{I}_{rDQref})$
- PLL required to define  $\omega t$




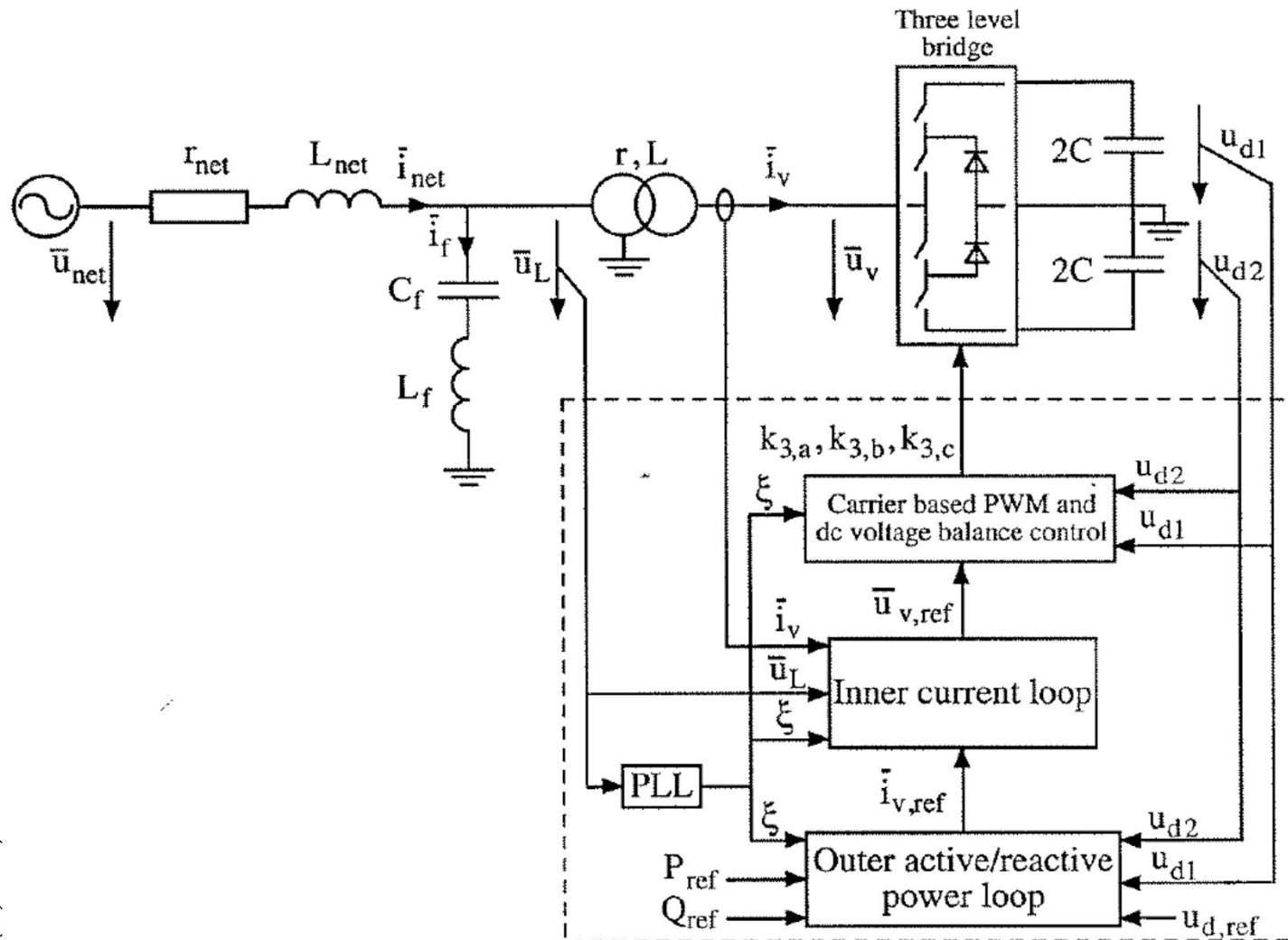
# System with feed-forward and vector control





# Control of AC - DC – AC converter

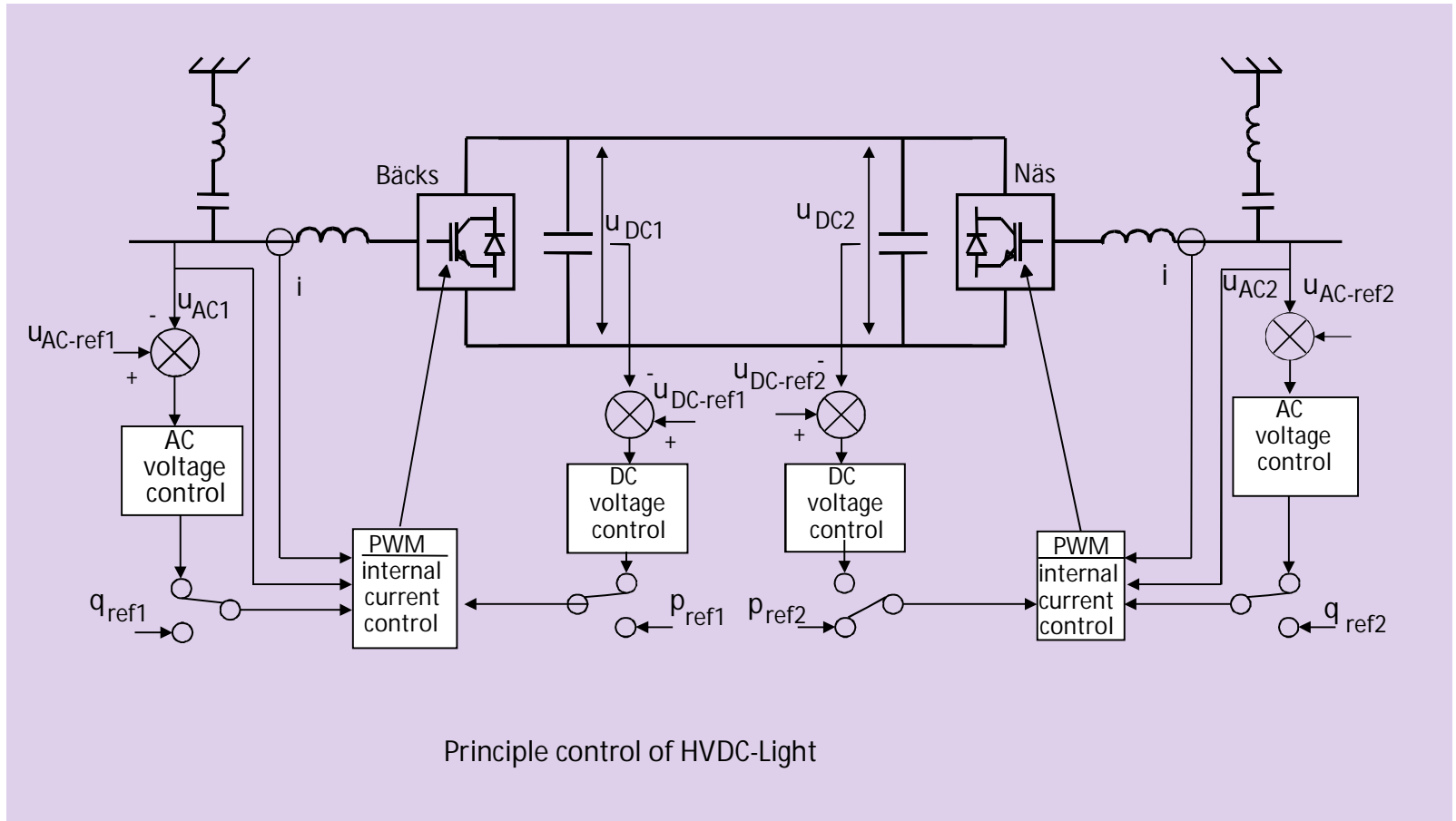

# DC Power versus DC voltage

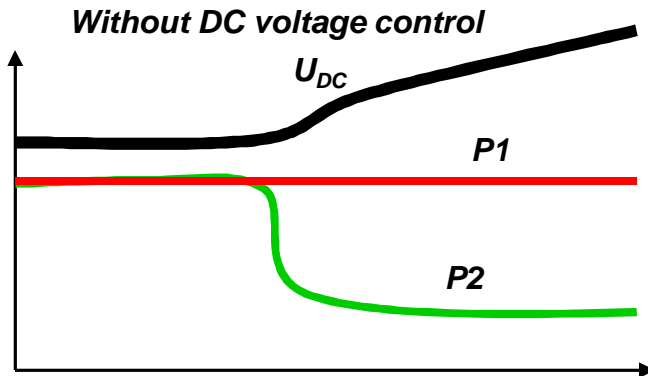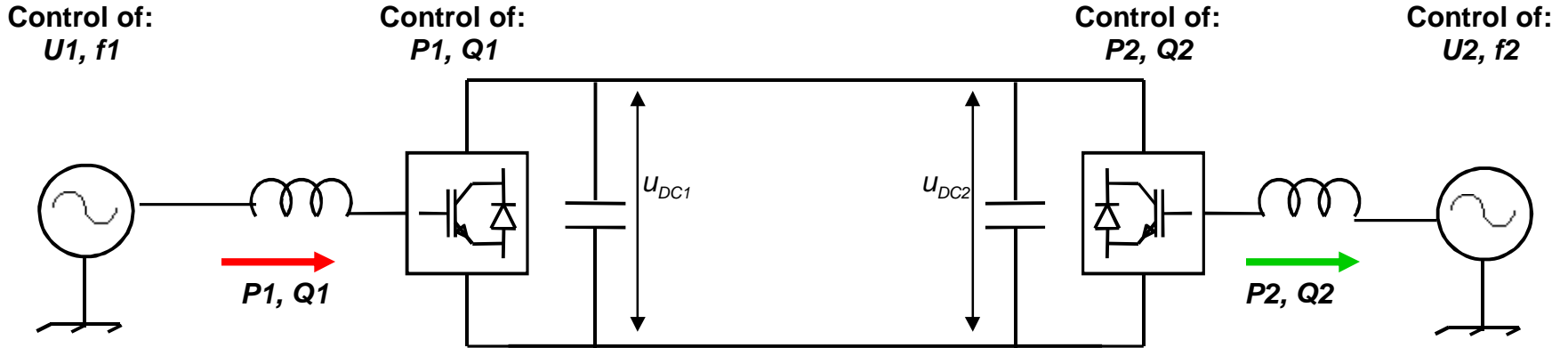

# DC voltage control

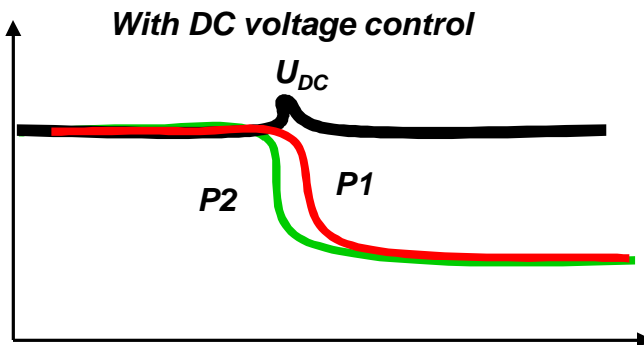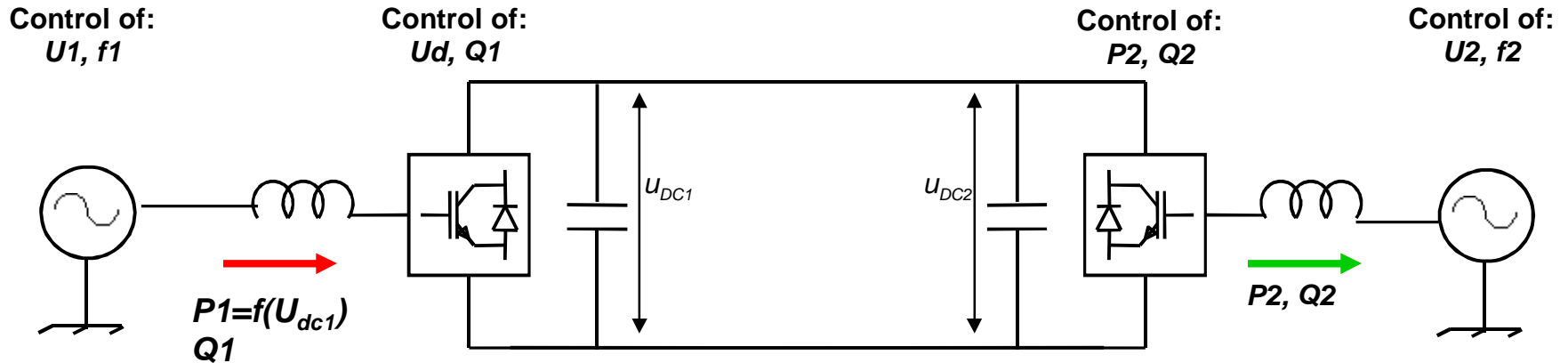



# Lecture 11


## Snubber circuits

# Problem with switching converters

- Switches turns on/off while conducting large currents
  - Recovery time create large power dissipation
- $di/dt$  generates EMI (Electromagnetic interference)
- Small size requires higher switching frequencies


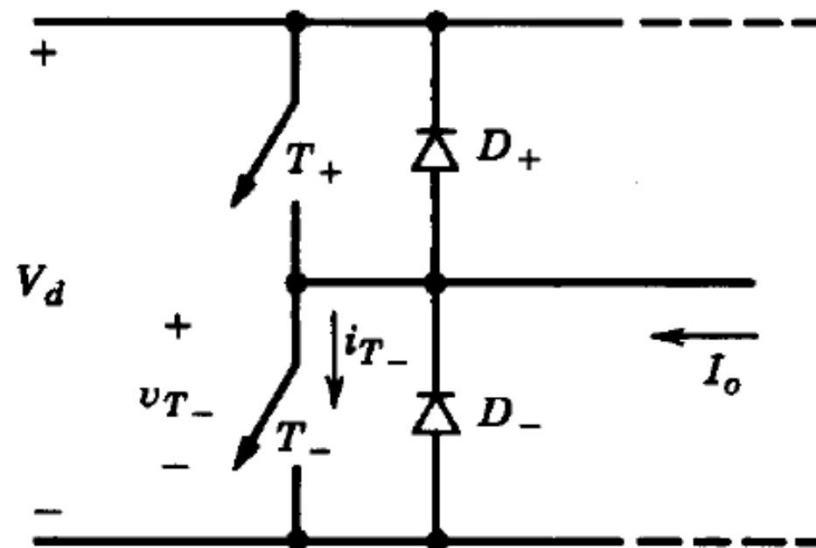
## Example, full bridge leg

- Finite  $di/dt$  and  $dv/dt$
- Parasitics:  $L, C, R$
- $I_o$  can be both positive and negative



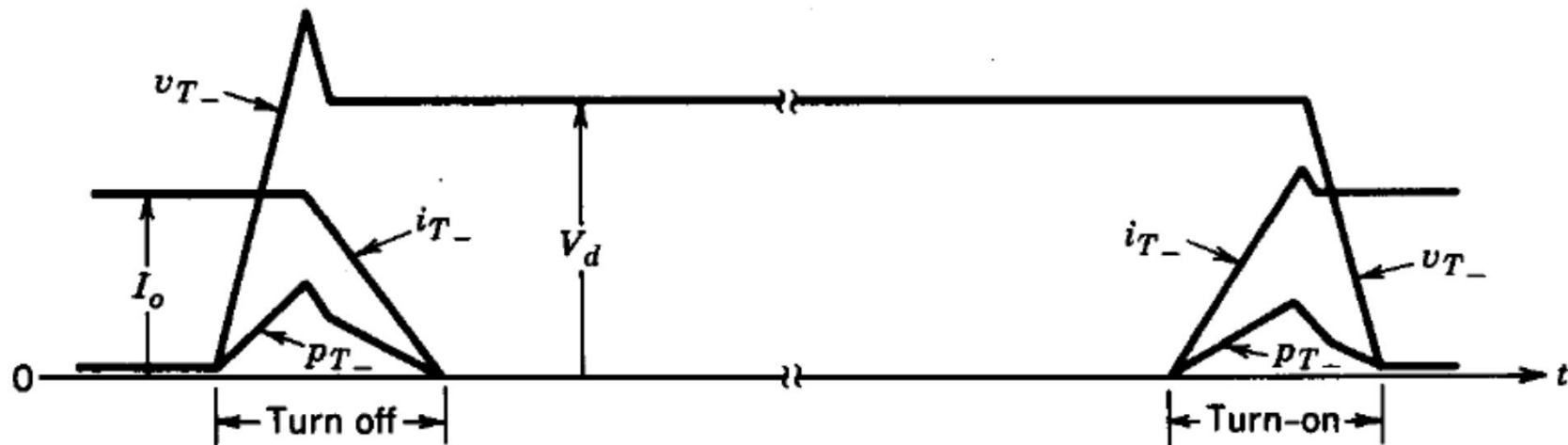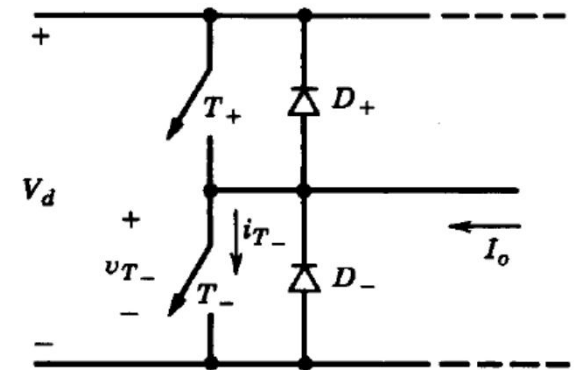
# Hard switching waveform

- Stray inductance gives voltage overshoot
- Stray capacitance gives current overshoot
- Parasitics limits  $di/dt$  and  $dv/dt$
- $P_{T-} = v_{T-} \cdot i_{T-}$


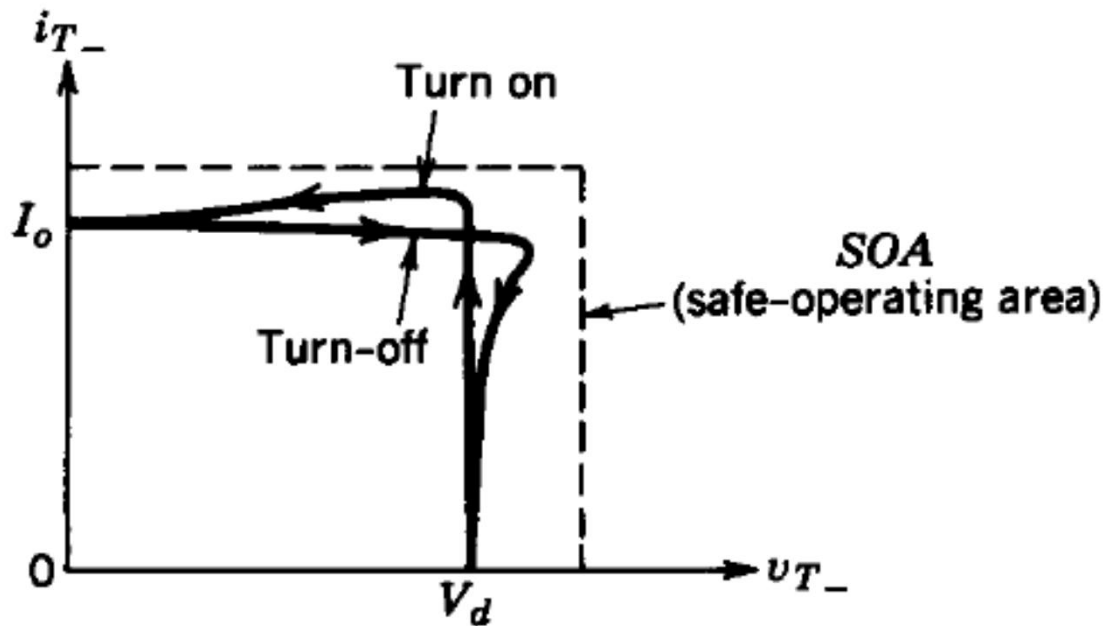
# Switch voltage and current

- Short moments of high power dissipation
- Device must cope with the power dissipation
- Overshoot increases required SOA





# Component characteristic goal

- High  $di/dt$  and  $dv/dt$  to reduce power loss
- Short recovery time diodes
- Components must cope with short time full power dissipation
- Large stress on components due to power dissipation changes (material stress etc)
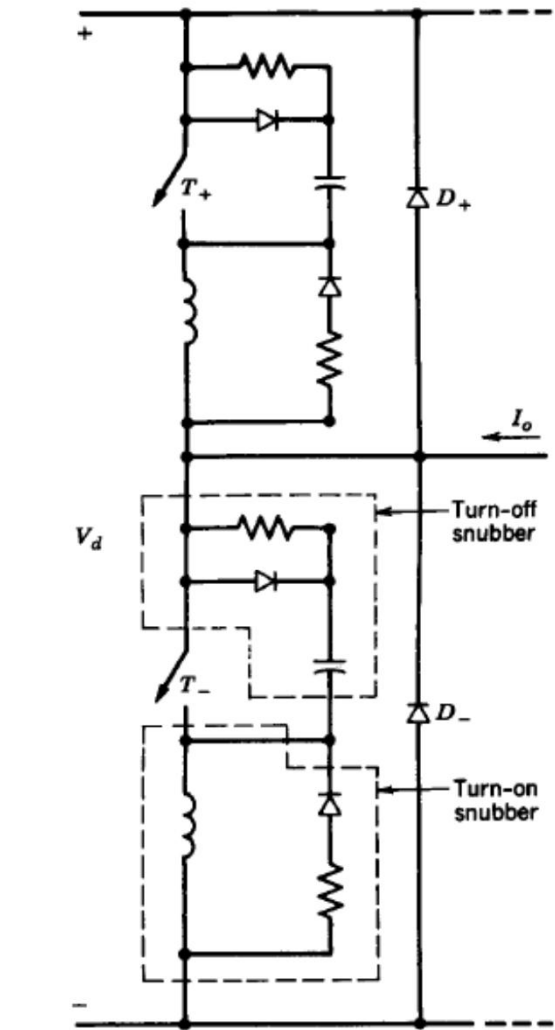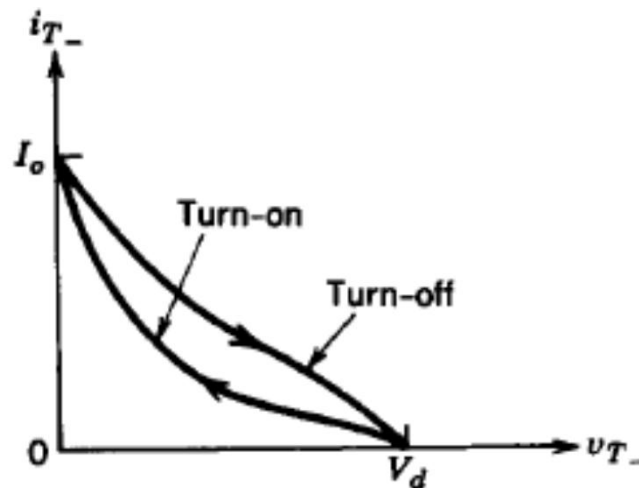
# Snubber circuits

- Connected in parallel/serial with the switches
- Turn-on snubber
  - Inductor limits  $di/dt$
  - Capacitance limits  $dv/dt$
- Power now lost in snubber instead of switch



# Snubber circuits

- Protect semiconductors
  - Limit voltages applied during turn-off transients
  - Limit device currents during turn-on transients
  - Limit the rate of rise ( $di/dt$ ) of currents
  - Limit the rate of rise ( $dv/dt$ ) of voltages
  - Shape the switching trajectory at turn on and turn off
- Three major classes
  - Unpolarized series RC snubbers
  - Polarized RC snubbers
  - Polarized LR snubbers





# Diode snubbers

- $L_\sigma$  stray inductance
- R C snubber circuit
- Problem when switch turns on
  - Current starts to flow in wrong direction
  - When diode turns off then  $L_\sigma$  tries to force continued current

- Diode breakdown if

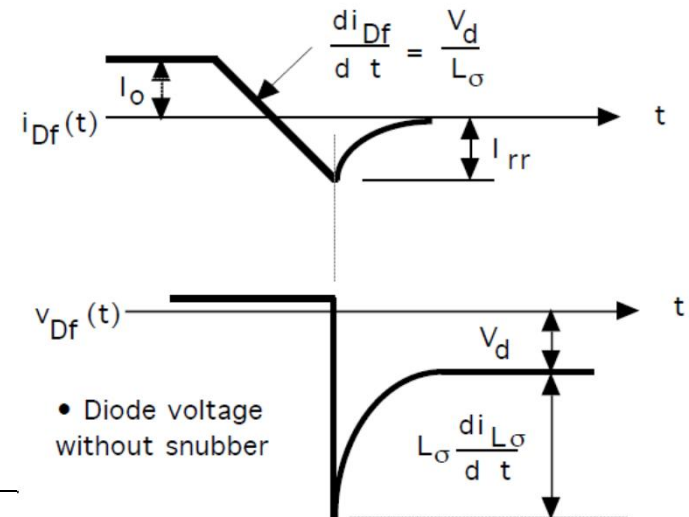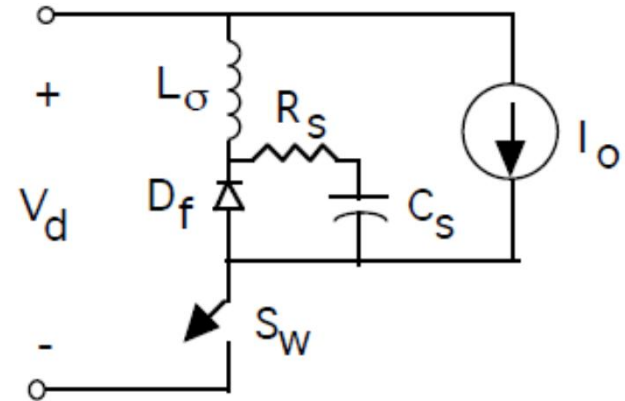
$$V_d + L_\sigma \frac{di_{L\sigma}}{dt} > BV_{VB}$$





# Snubber circuits for controlled switches

- Step-down example
  - $L_\sigma = L_1 + L_2 + L_3$  stray inductances
- Voltage and current overshoot due to inductances
- Three snubber types
  - Turn-off, turn-on, over-voltage

Step-down converter

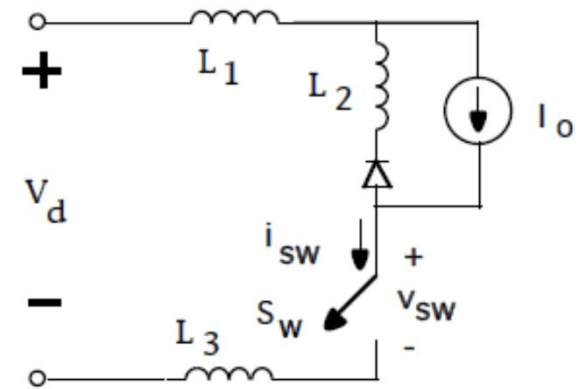

Switch current and voltage waveforms

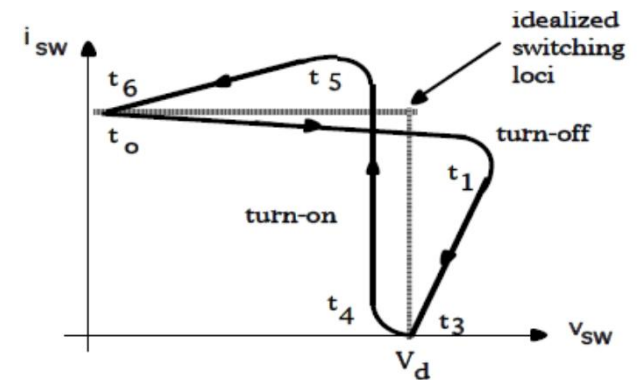
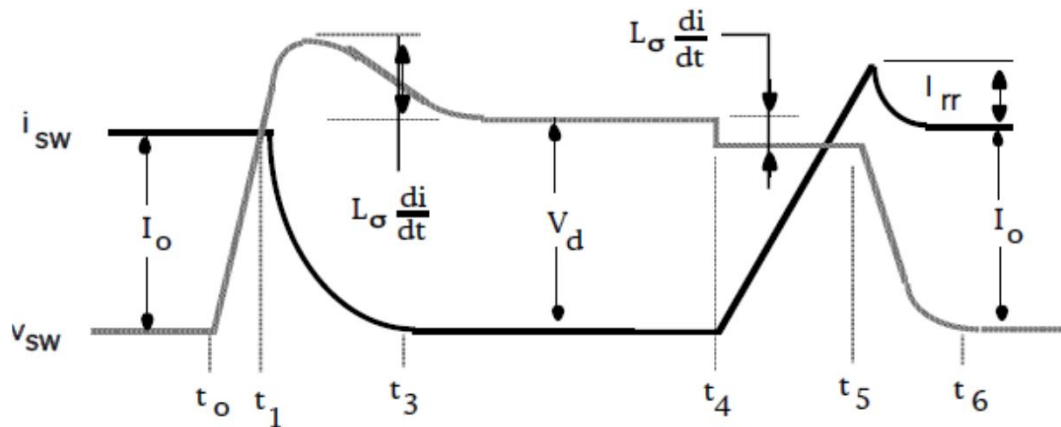


# Turn-off snubber circuit for controlled switches

- Diode to only include  $R_s$  at switch turn-on
- Simplified circuit for switch turn-off


$$i_{sw}(t) = I_0 \left( 1 - \frac{t}{t_{fi}} \right)$$

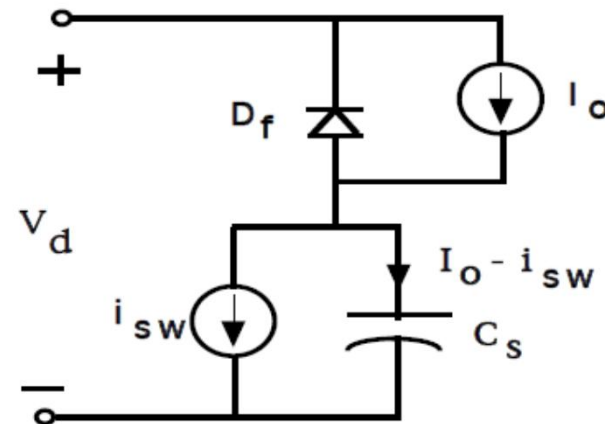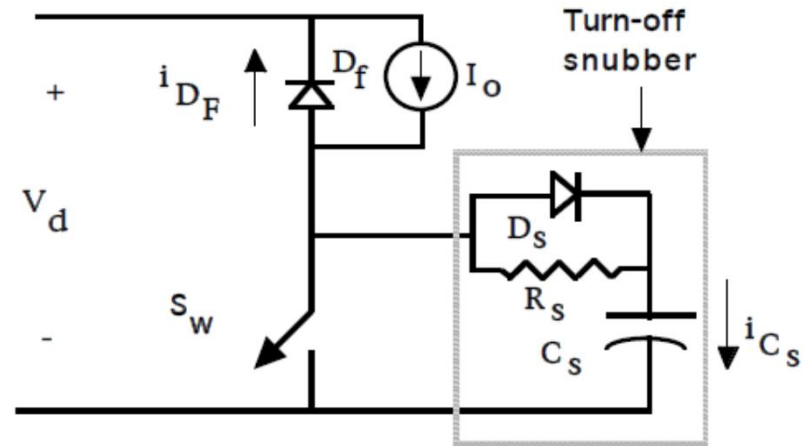- Switch current at switch turn-off not affected by snubber circuit




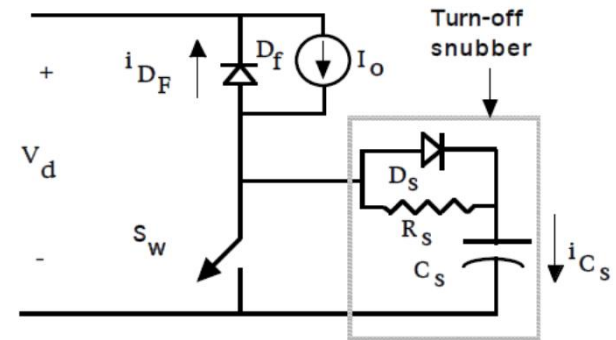
# Overtoltage snubber function

- At transistor switch-off completed  $t = 0$ 
  - $V_{COV} = V_D$
  - $I_0$  goes through  $D_f$
  - Fast switch give  $i_{L\sigma}(t=0) = I_0$





inductor current decays to zero

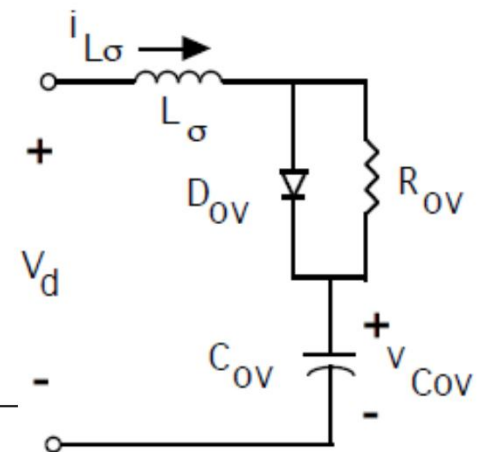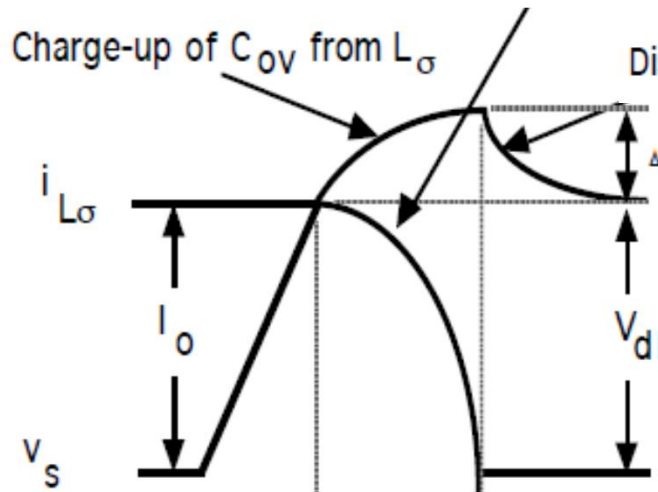
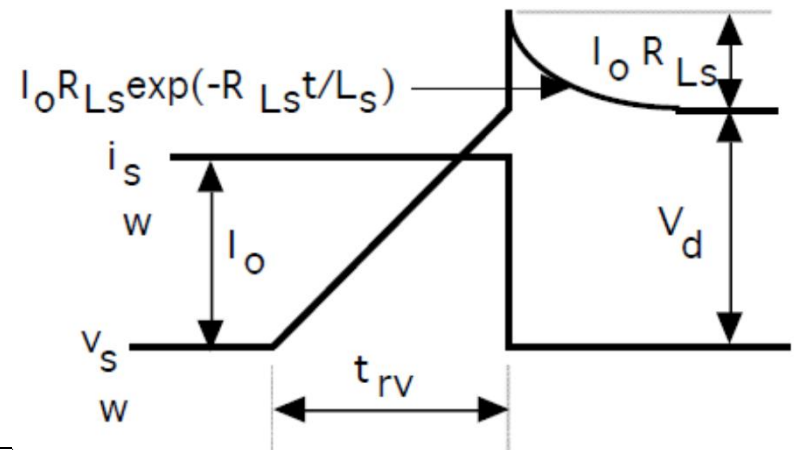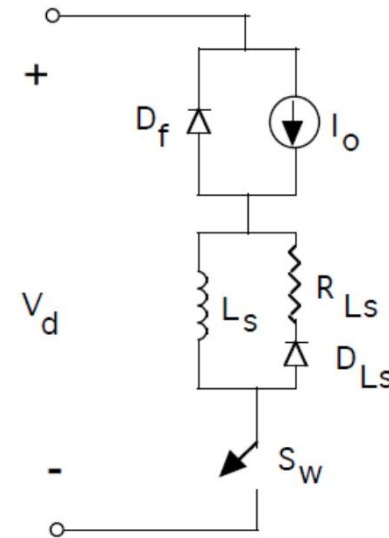
# Turn-on snubber

- To limit  $di/dt$  through switch at turn-on
- Turn-off Thyristors (GTO, IGCT) has limited  $di/dt$  capability
- At switch turn-off, stored energy in  $L_s$  must be dissipated.
- $D_{LS}$  and  $R_{LS}$  forms discharge circuit for the inductor  $L_s$



[www.liu.se](http://www.liu.se)