

TSTE19 Power Electronics

Lecture 6

Tomas Jonsson


ISY/EKS

Outline

- DC power supplies
- DC-DC Converter
 - Step-down (buck)
 - Step-up (boost)
- Other converter topologies (overview)

Basic use of DC-DC converter

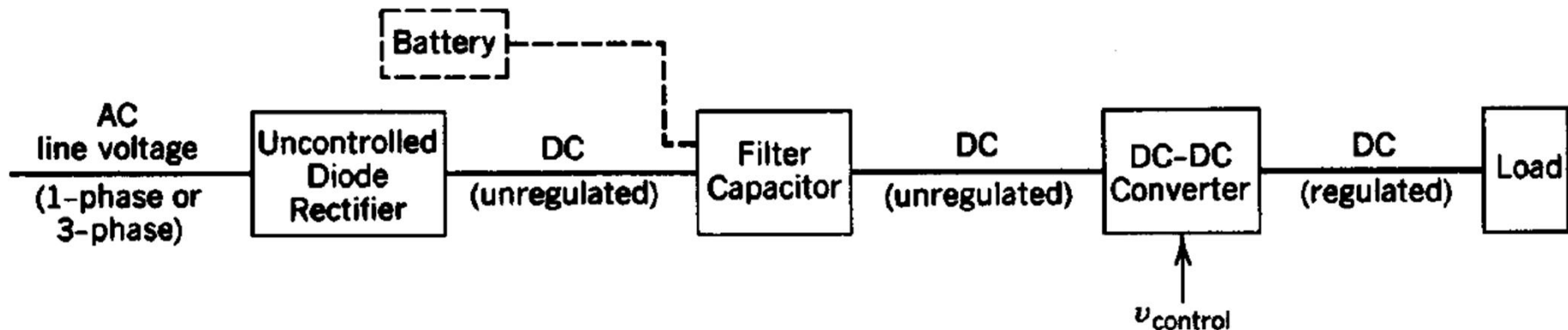- Unregulated DC input, controlled DC output
 - Regulated DC may be larger or smaller than the unregulated DC voltage
 - Input to DC-DC converter may vary a lot





DC Power supplies

- Regulated output
 - Defined tolerance of output voltages
- Isolation
 - No direct electric connection to supply voltage
- Multiple outputs
 - Both positive and negative possible
 - Various current and voltage ratings


Linear power supply

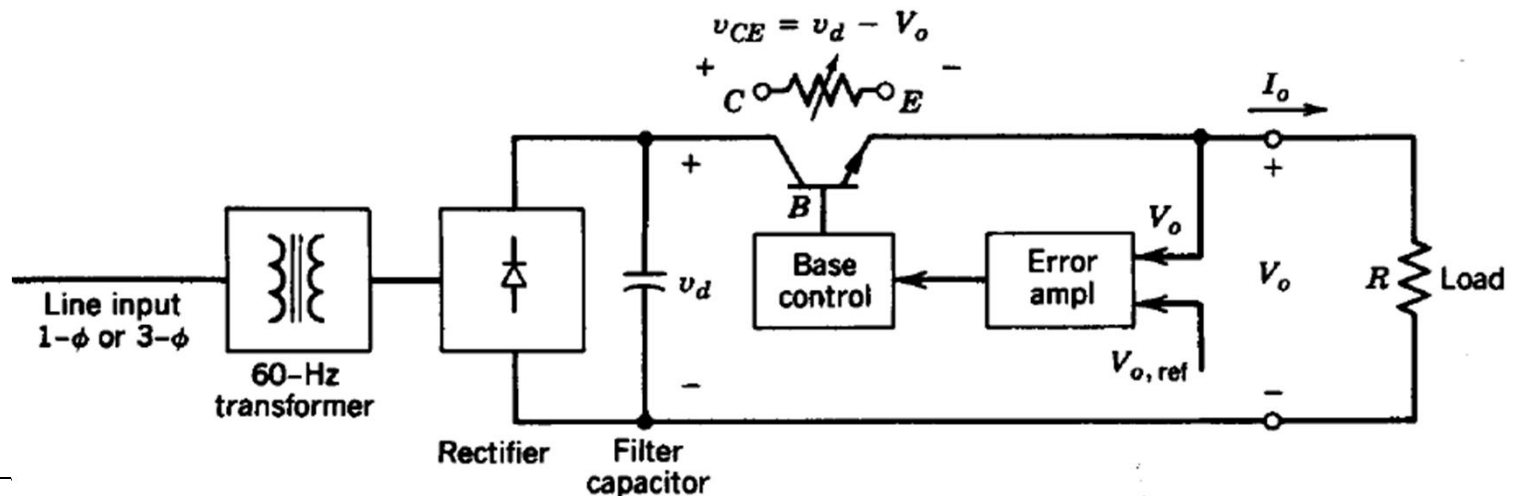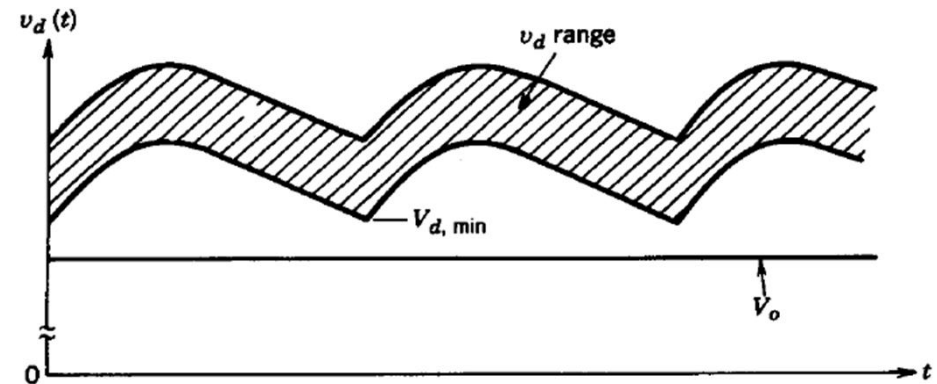- Bulky transformer
 - Low frequency
- Poor efficiency
 - 30 – 60 %
- Low EMI




Switch-mode dc power supply schematic

- Small size
- High efficiency

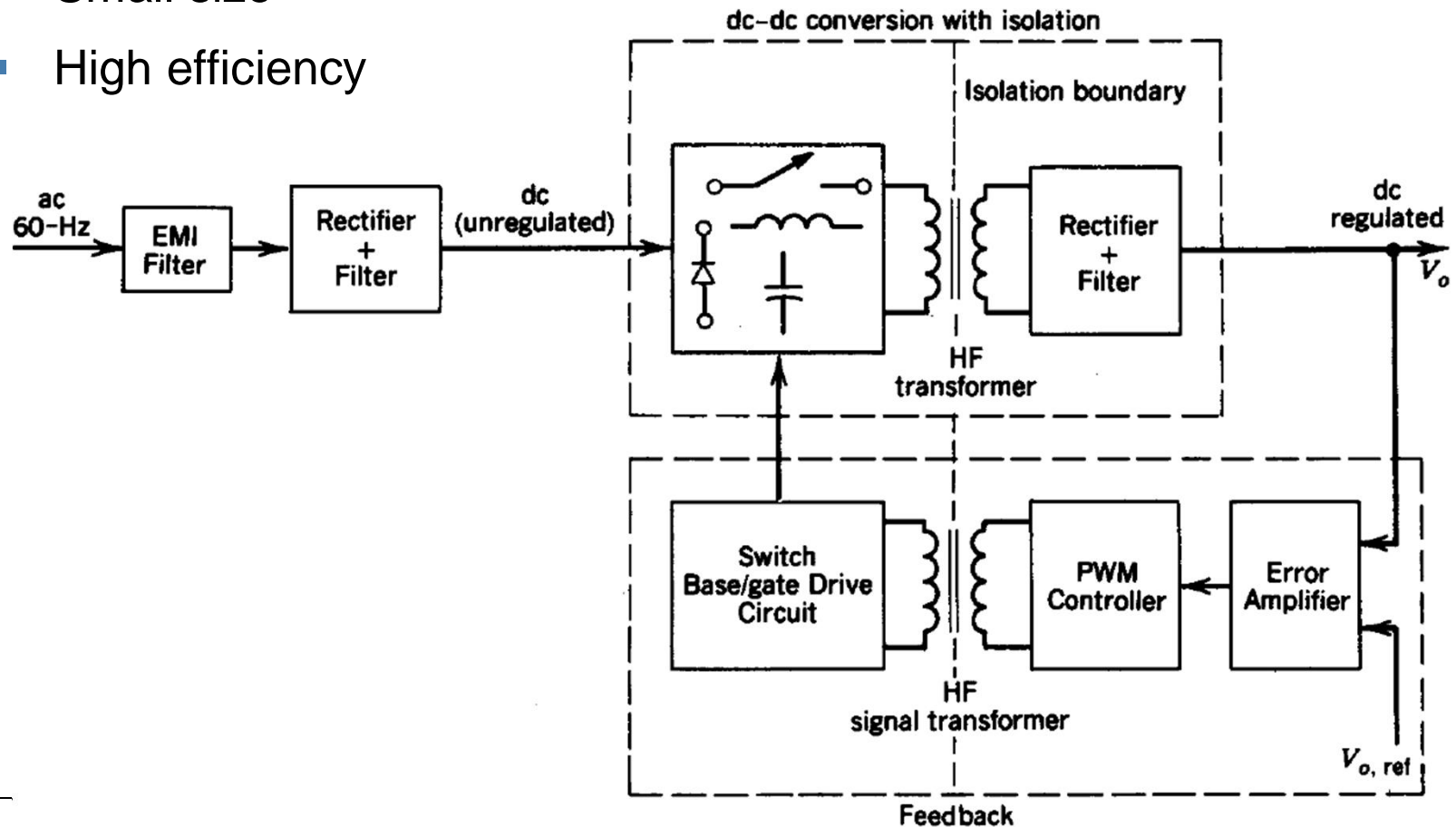



Multiple voltages

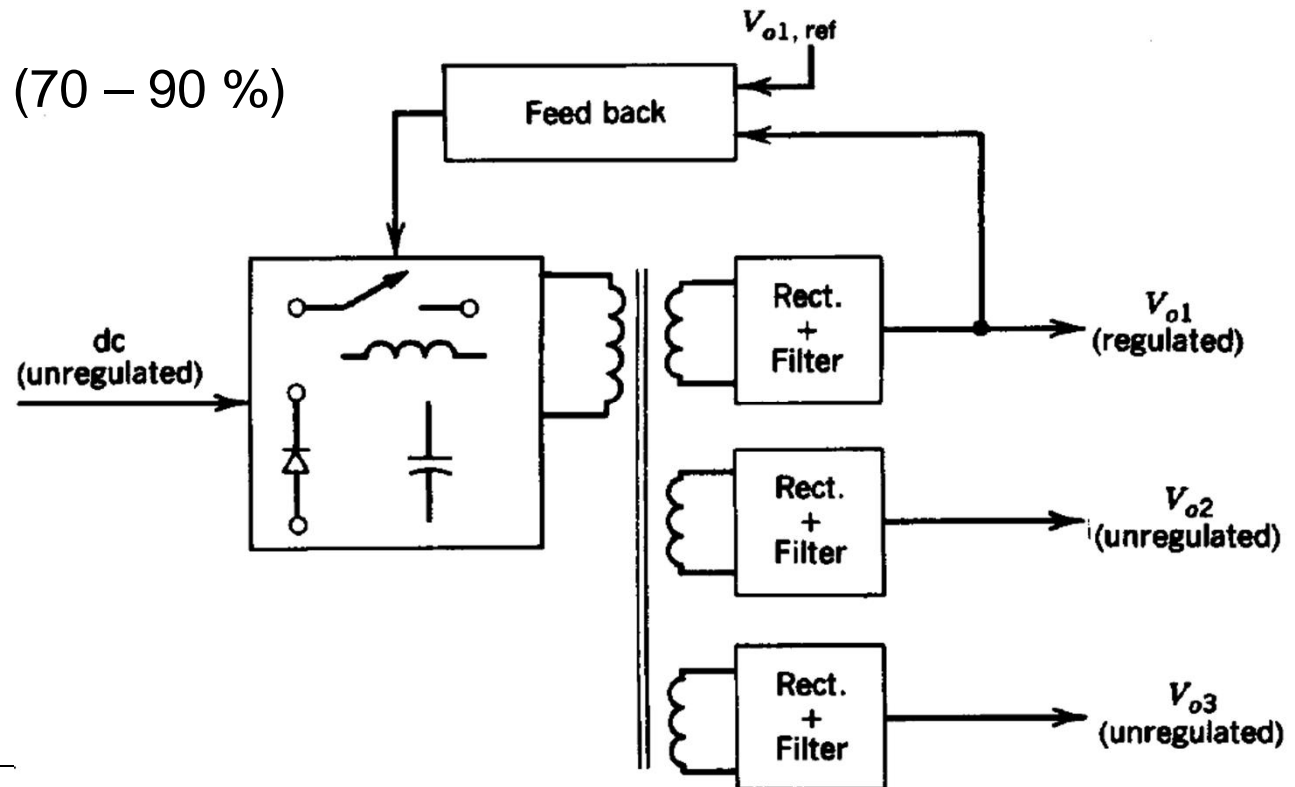- Linear control may be applied if multiple controlled voltages are required
- High efficiency (70 – 90 %)



Step down converter principle

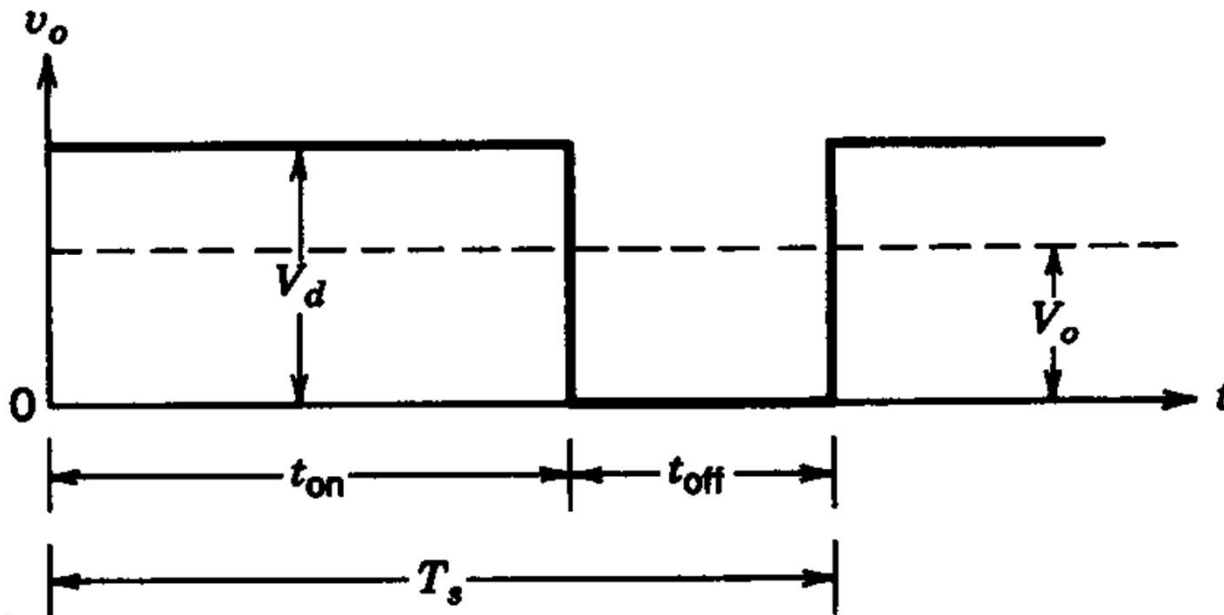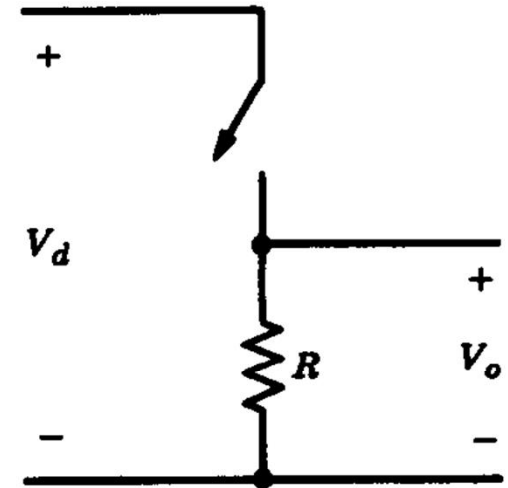- $V_d > V_o$
- T_s constant, t_{on} t_{off} changing
- Large ripple on V_d



DC/DC-converter control

- Pulse width modulation, PWM, to control switching
- Switching frequency f_s

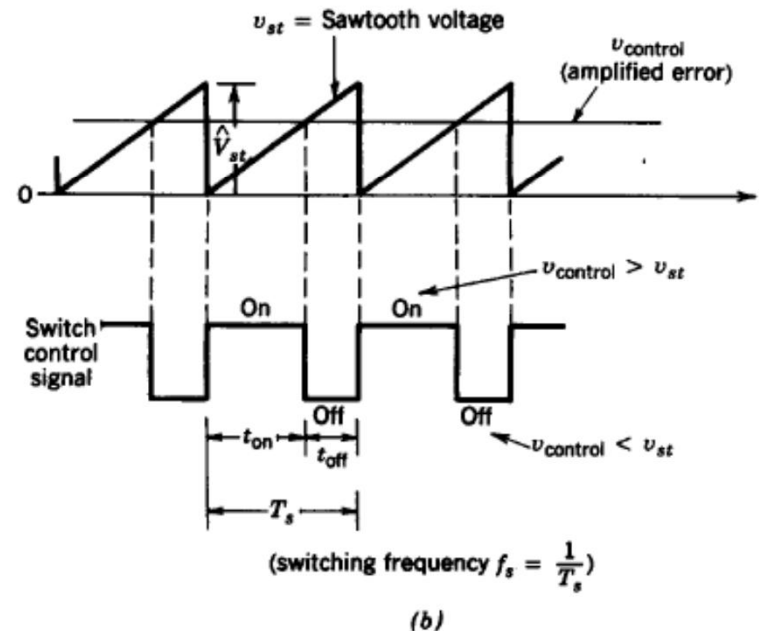
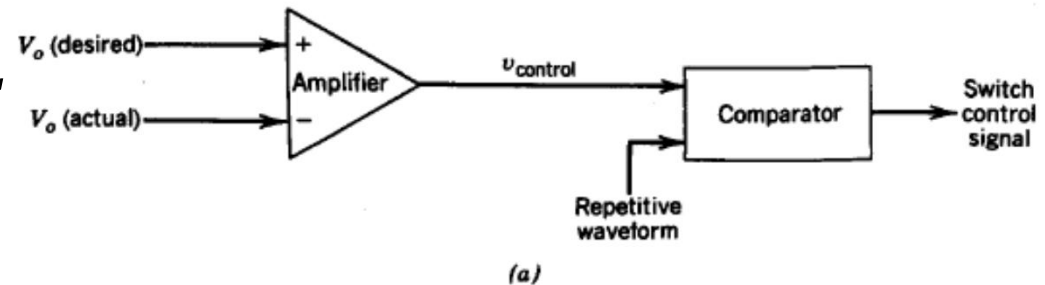



Figure 7-3 Pulse-width modulator: (a) block diagram; (b) comparator signals.

PWM waveform, duty cycle

- Switch duty cycle (duty ratio)


$$D = \frac{t_{on}}{T_s} = \frac{v_{control}}{V_{st}}$$

$$0 < D < 1$$

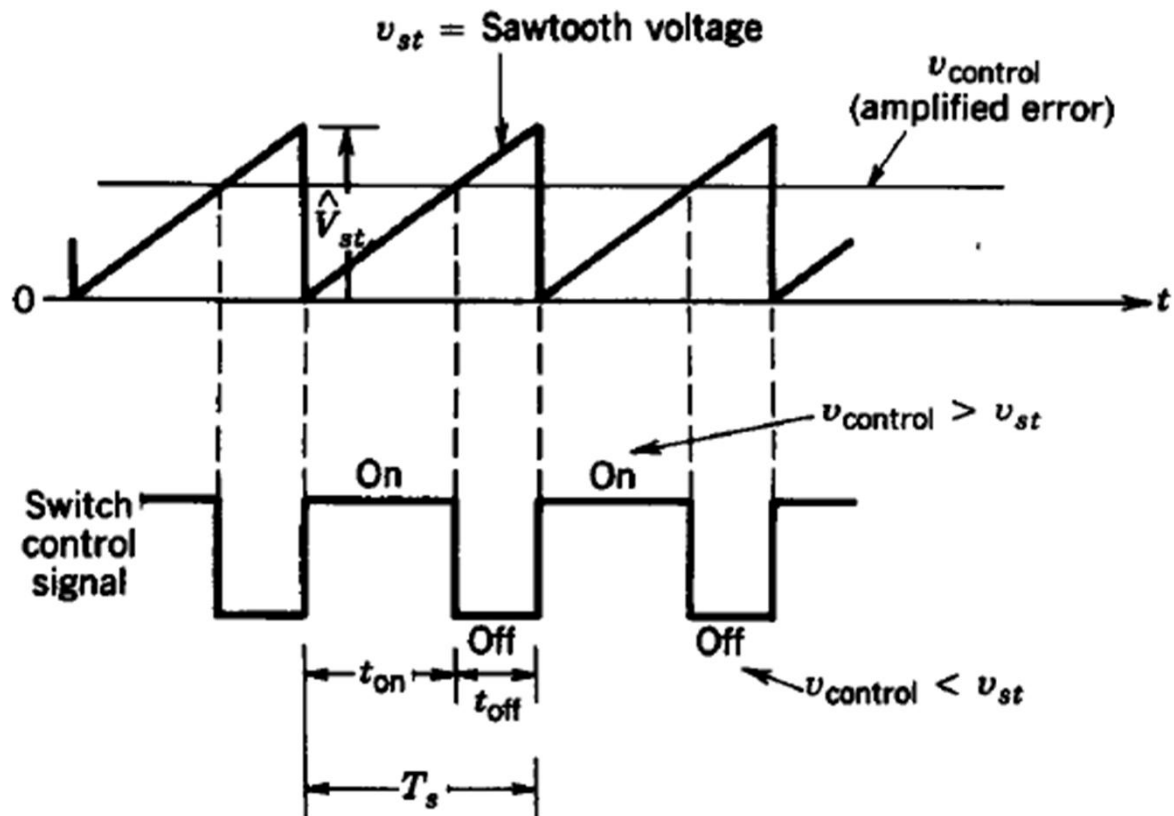

Step-down (buck) converter

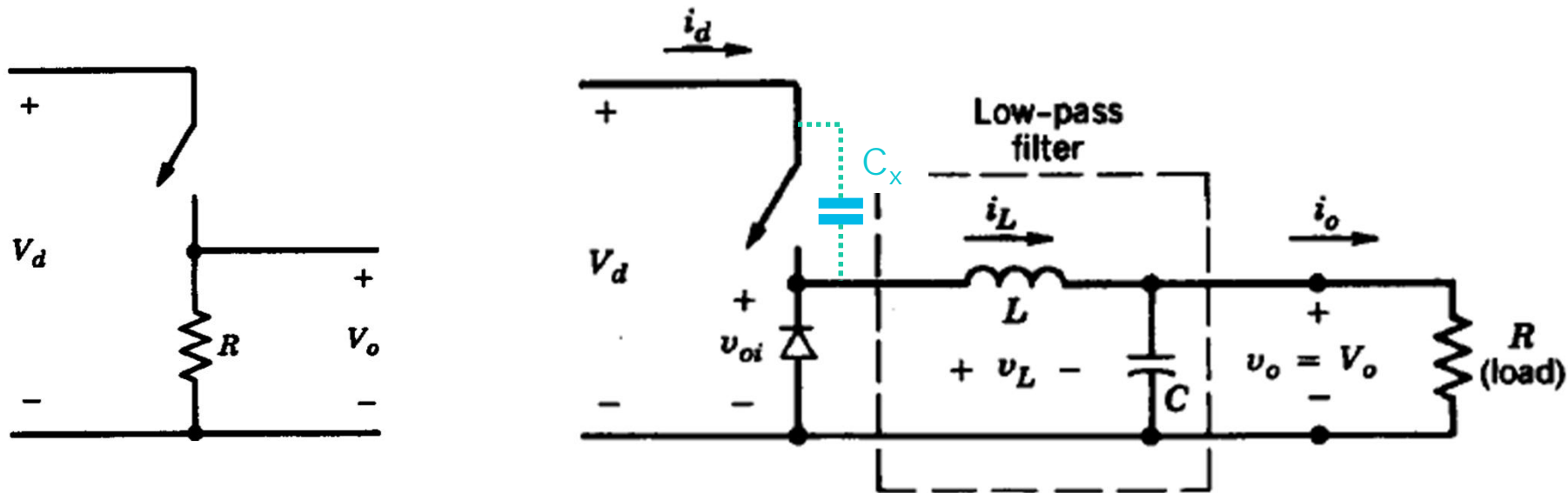
- Add filter to reduce ripple voltage compared to principle
- Diode added to protect switch
 - $V_L \rightarrow$ infinity if no diode and instantaneous switching!
 - Parasitic capacitances C_x would be charged by the inductor current



Step-down converter waveforms




- $T_s = t_{on} + t_{off}$
- Average output voltage

$$V_o = \frac{t_{on}}{T_s} V_d = DV_d$$

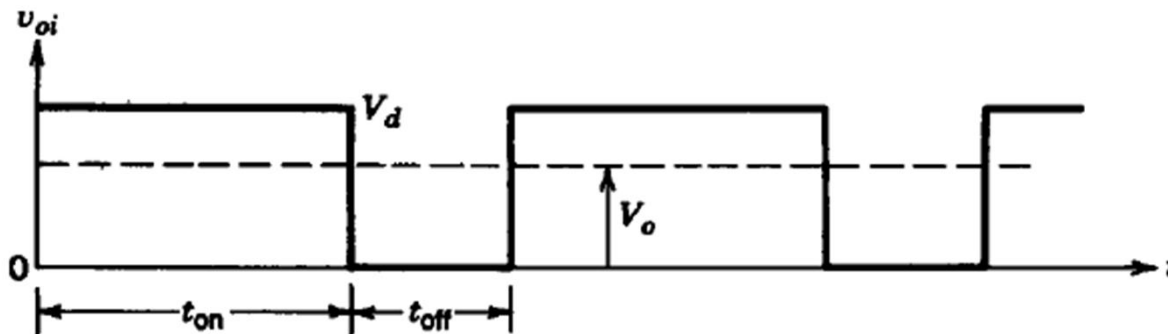


Input voltage before low-pass filter

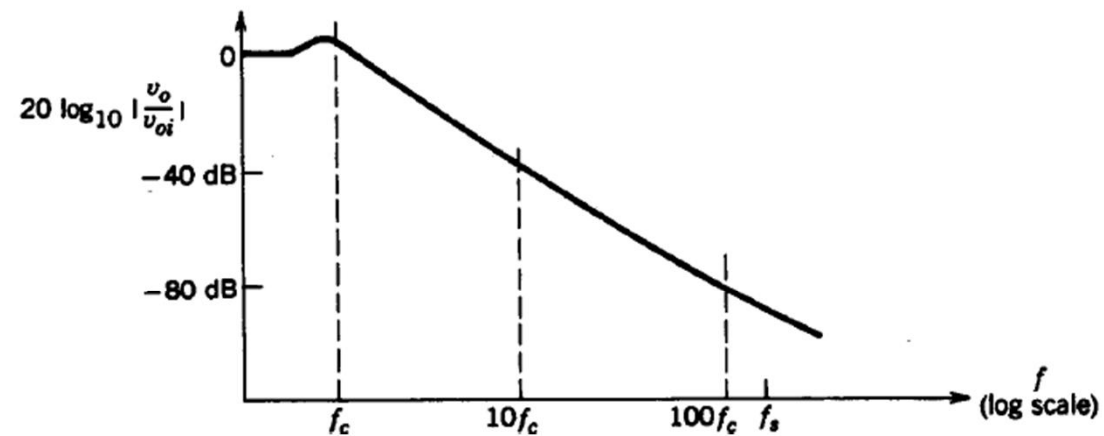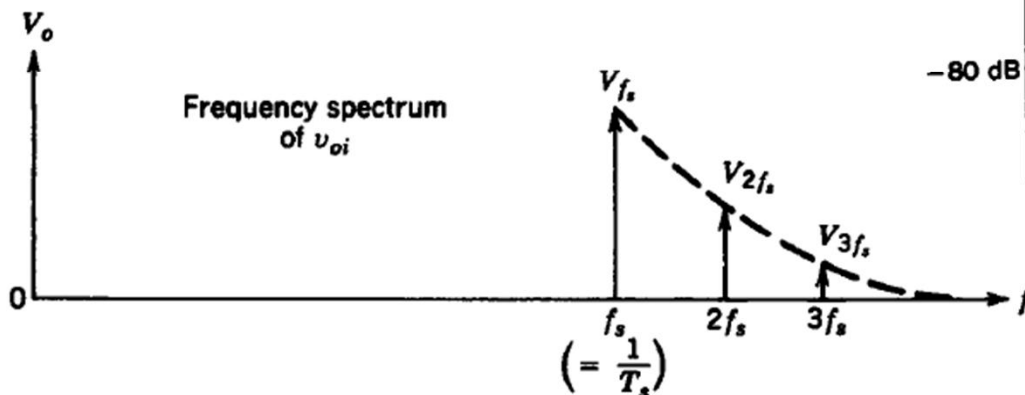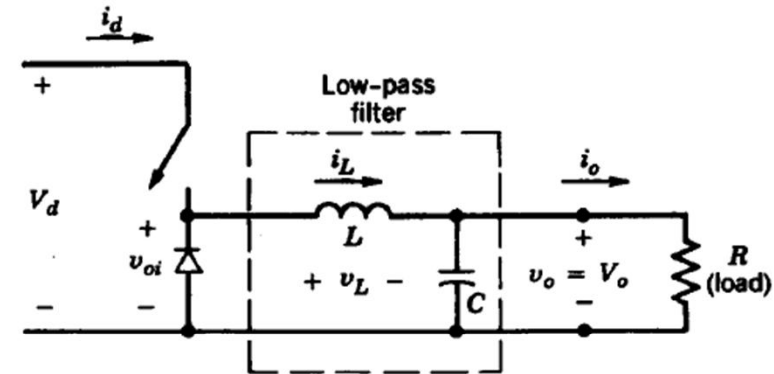- $V_{oi} = V_d$ when switch on
- When switch off
 - $V_{oi} = 0$ if $i_L > 0$
 - $V_{oi} = V_o$ if $i_L = 0$
- LP filter $BW(f_c) \ll f_s$




Current Conduction modes

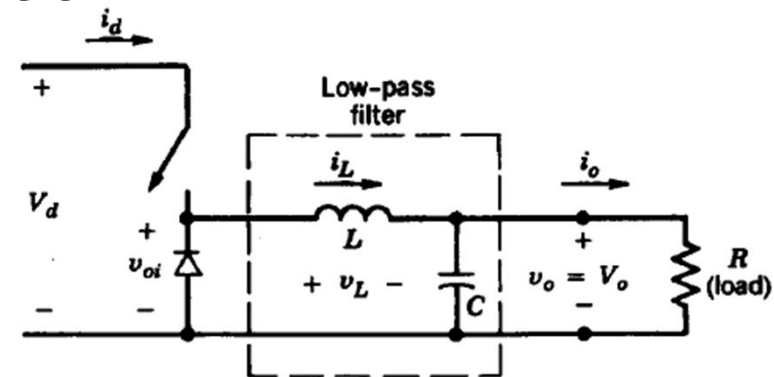- Average i_L equals i_o
- Two current conduction modes (i_L)
 - Continuous current conduction
 - Non-continuous current conduction
- Converter characteristics different depending on mode
- Both modes can be supported by a converter
 - Mode selected depending on load





Continuous Conduction mode

- Switch on (diode off)

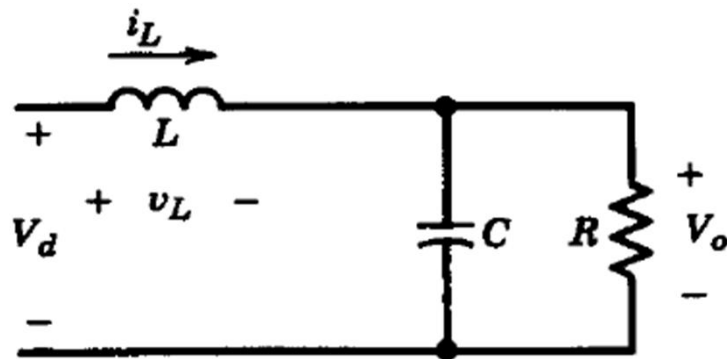

- Switch off (diode on)

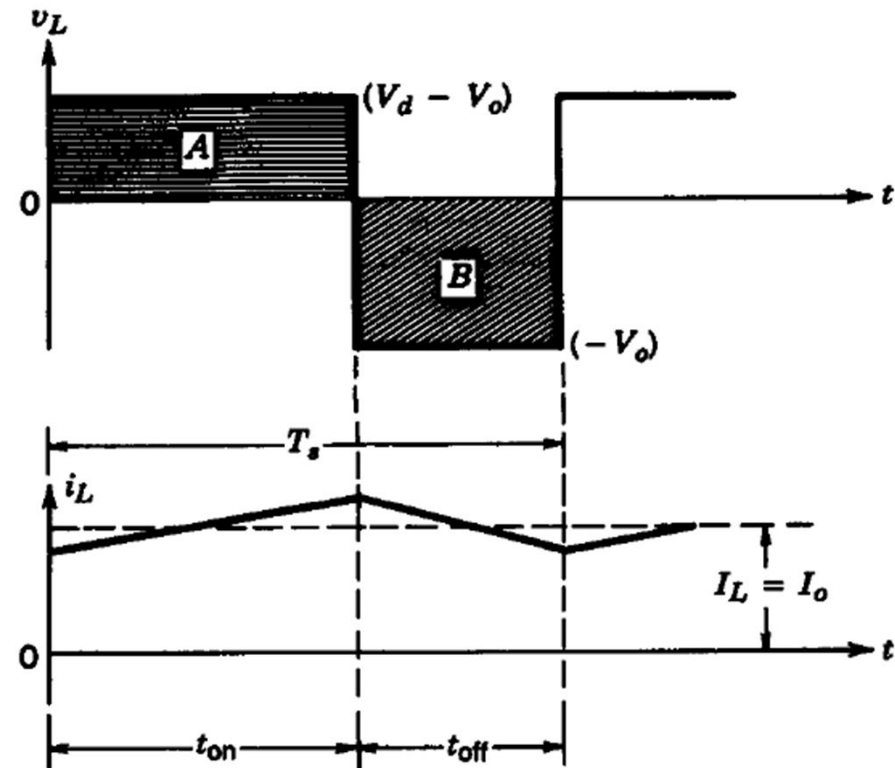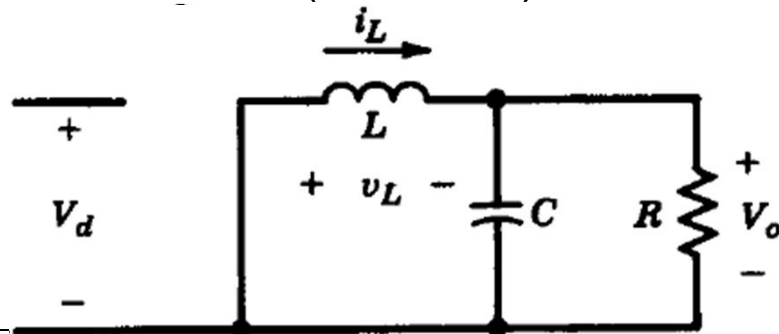

Continuous conduction mode, cont.


- i_L never zero
- Steady state $\Rightarrow A = B$ $t_{on}(V_d - V_o) = V_o(T_s - t_{on}) \Rightarrow \frac{V_o}{V_d} = \frac{t_{on}}{T_s} = D$
- Average v_{oi} output voltage, average v_i zero in steady state

$$\frac{V_d t_{on} + 0 t_{off}}{T_s} = V_o$$

- No power loss in converter

$$P_d = P_o \Rightarrow V_d I_d = V_o I_o$$

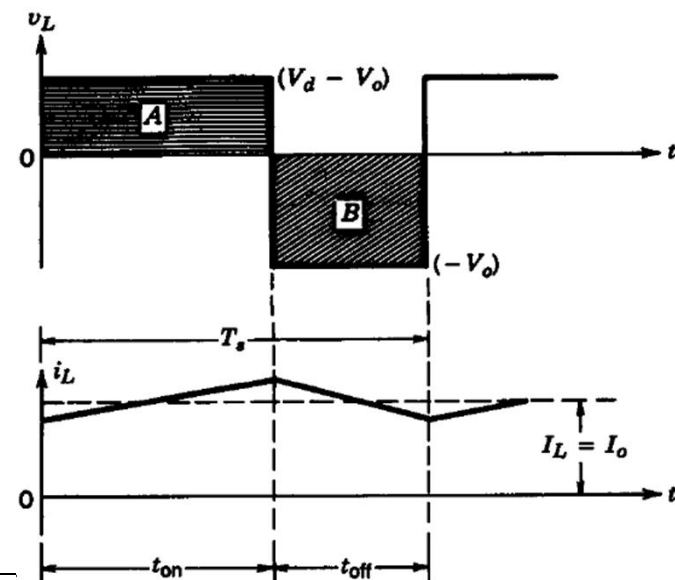- $\frac{I_o}{I_d} = \frac{V_d}{V_o} = \frac{1}{D}$
- DC transformer with turns ratio equal to D
- i_d still slanted square wave



Discontinuous/Continuous Conduction mode boundary

- i_L reach zero at end of period

- Average I_o



$$I_{LB} = \frac{1}{2} i_{L,peak} = \frac{t_{on}}{2L} (V_d - V_o)$$

$$I_{LB} = \frac{DT_s}{2L} (V_d - V_o)$$

$$I_{LB} = \frac{DT_s}{2L} V_d (1 - D)$$

- For fixed input voltage V_d

- $I_{LB,max}$ at 50% duty cycle

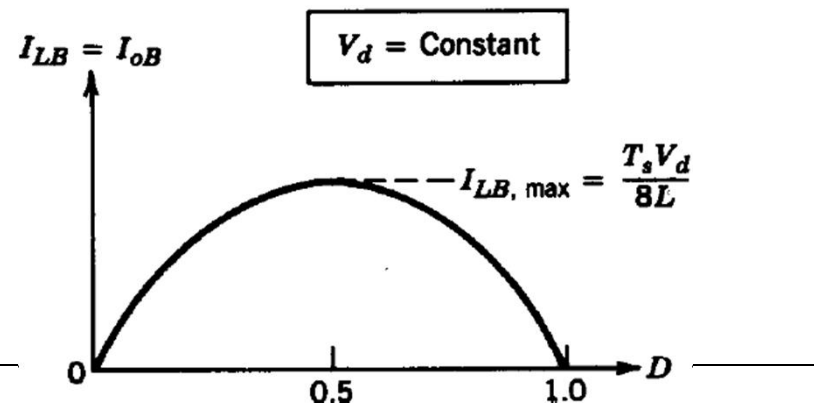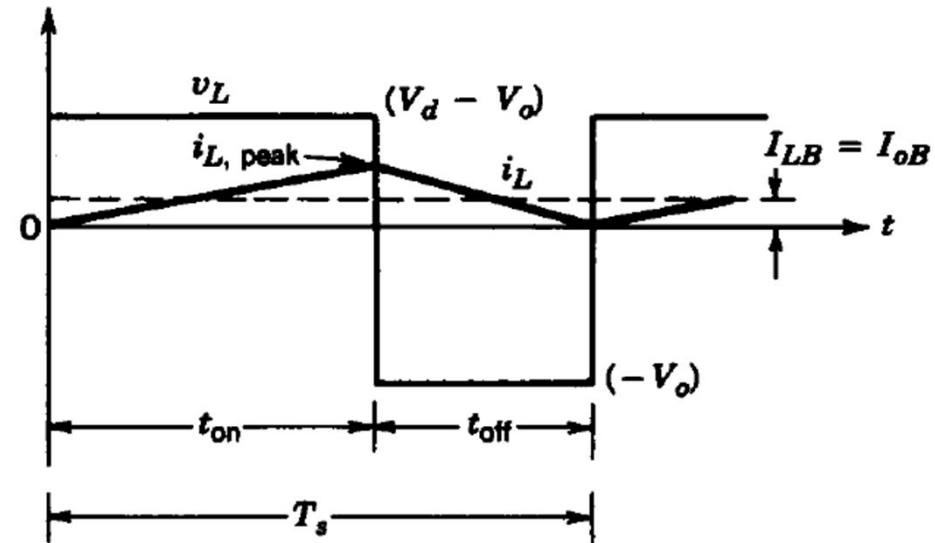

Discontinuous conduction mode

$$(V_d - V_o)DT_s + (-V_o)\Delta_1 T_s = 0$$

$$\frac{V_o}{V_d} = \frac{D}{(D + \Delta_1)}$$


$$i_{L,peak} = \frac{V_o}{L} \Delta_1 T_s$$

$$I_o = i_{L,peak} \frac{D + \Delta_1}{2}$$

$$I_o = \frac{V_o T_s}{2L} (D + \Delta_1) \Delta_1 = \frac{V_d T_s}{2L} D \Delta_1$$


$$\Delta_1 = \frac{I_o}{4I_{LB,max} D}$$
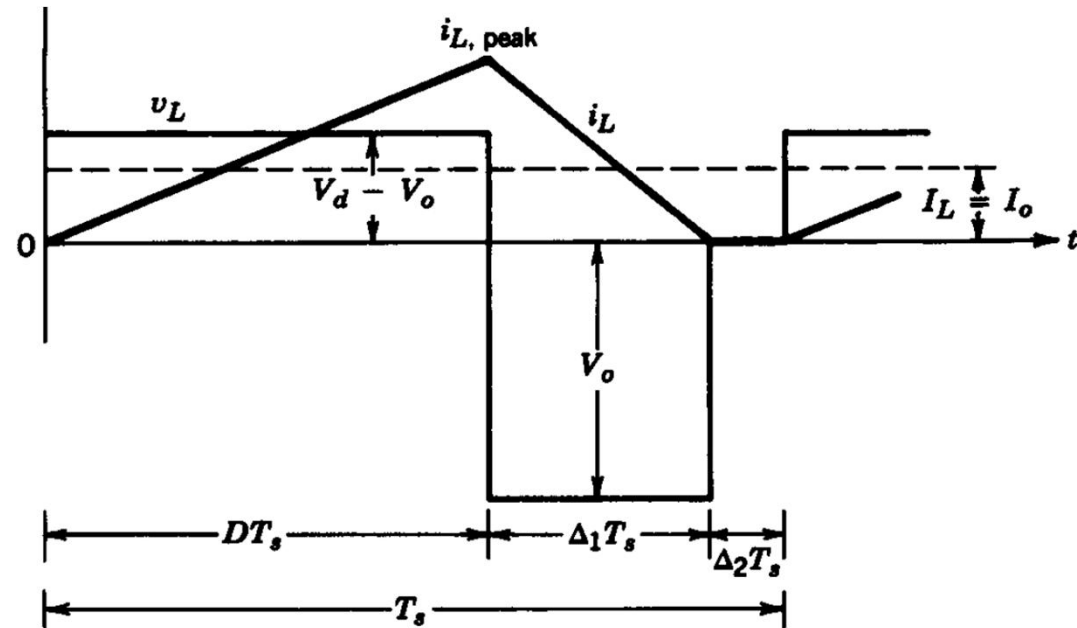
$$\frac{V_o}{V_d} = \frac{D^2}{D^2 + \frac{1}{4} (I_o / I_{LB,max})}$$




Constant V_d step-down characteristic

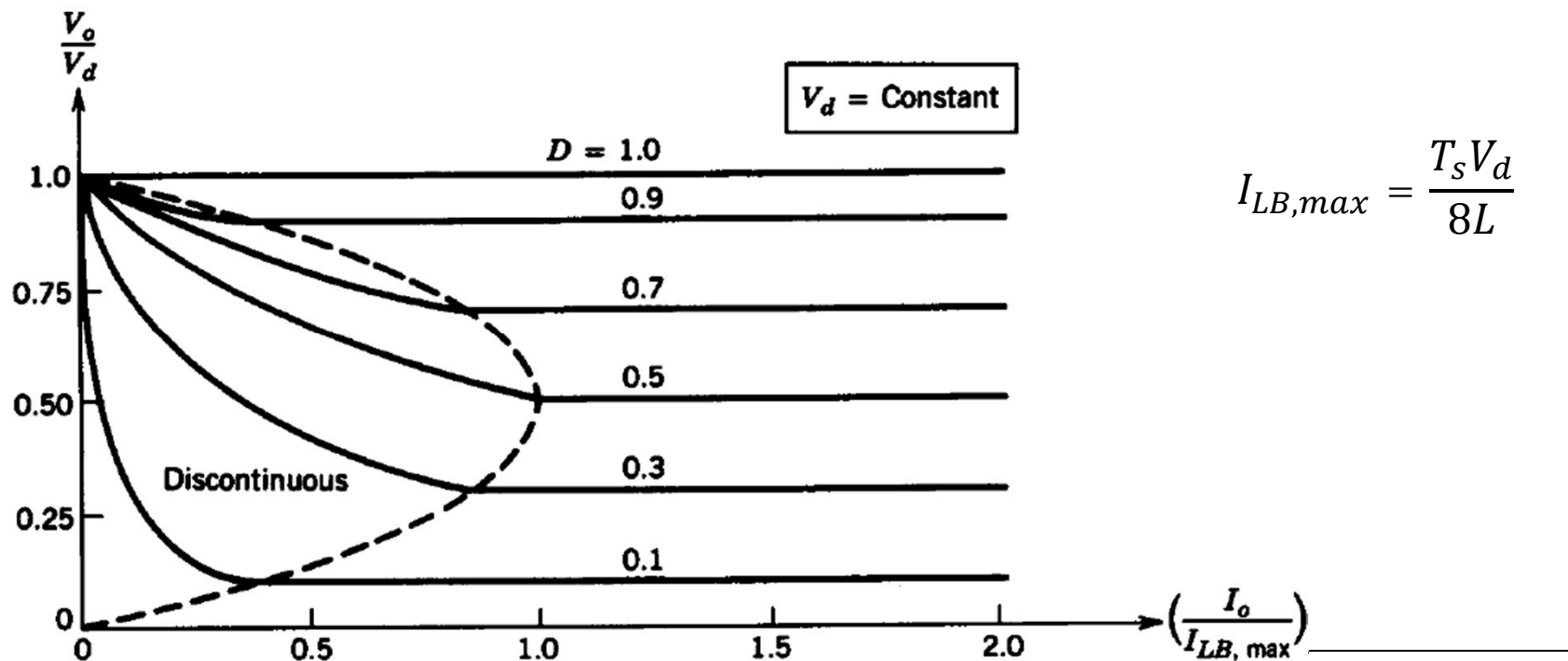- Very low load result in increased output voltage!



Discontinuous conduction mode with constant V_o

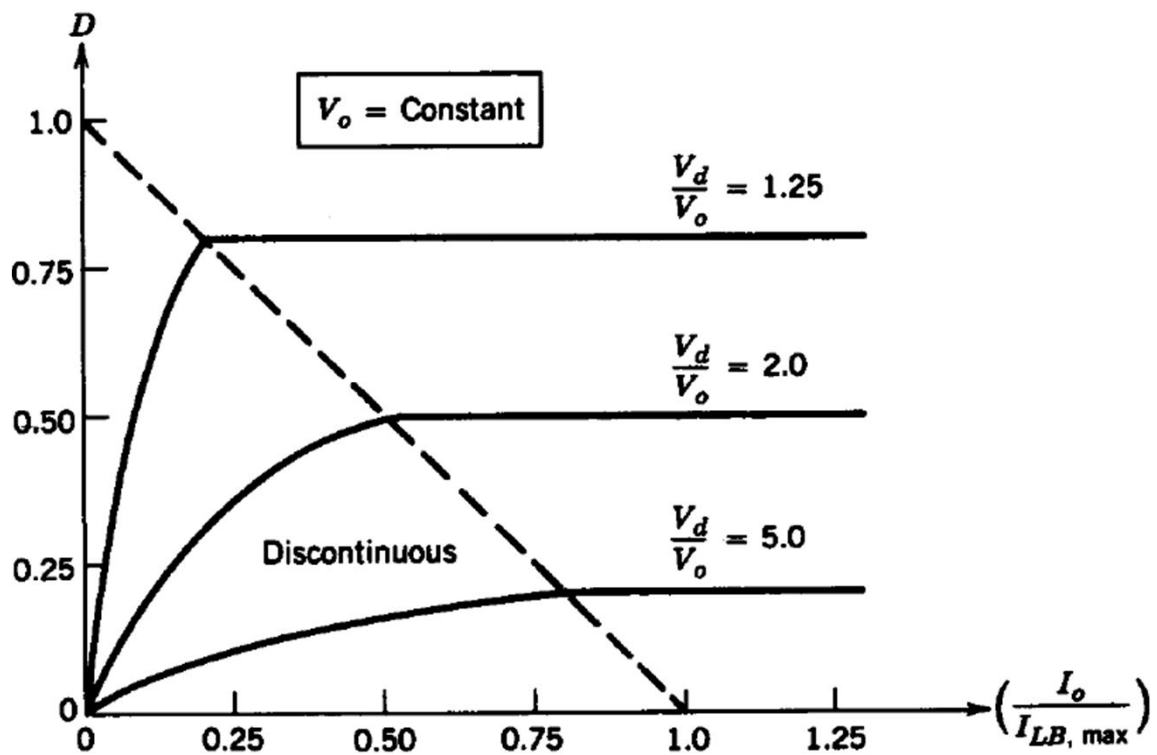- $I_{LB,max} = \frac{T_s V_o}{2L}$
- Control ratio for constant V_o



Output voltage ripple





- Assuming:
 - ripple current in C
 - Average current in R

$$\Delta V_o = \frac{\Delta Q}{C} = \frac{1}{C} \frac{1}{2} \frac{\Delta I_L T_s}{2} = \frac{\Delta I_L T_s}{4C}$$

$$\Delta I_L = \frac{V_o}{L} (1 - D) T_s$$

$$\frac{\Delta V_o}{V_o} = \frac{1}{8} \frac{T_s^2 (1 - D)}{LC} =$$
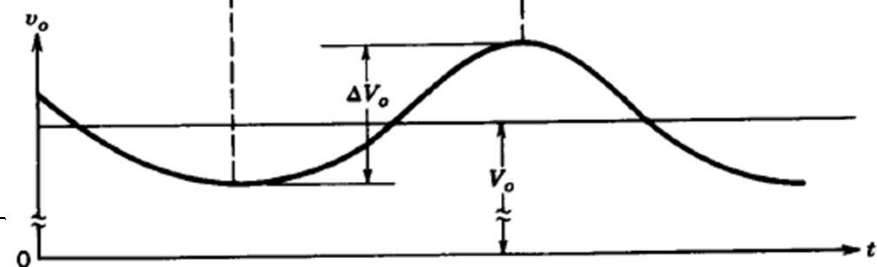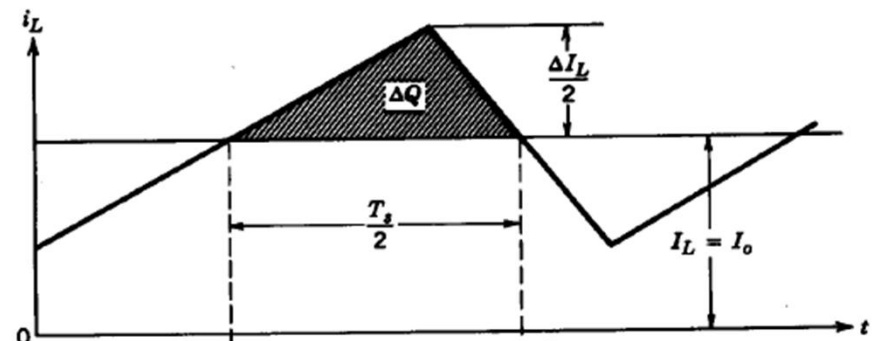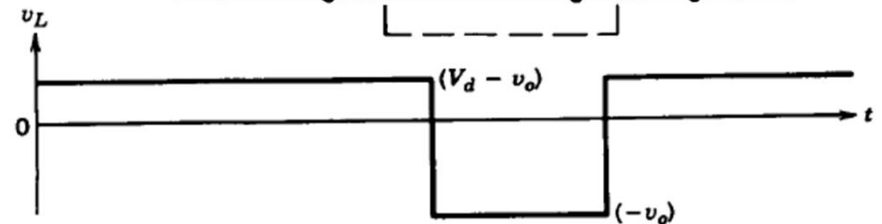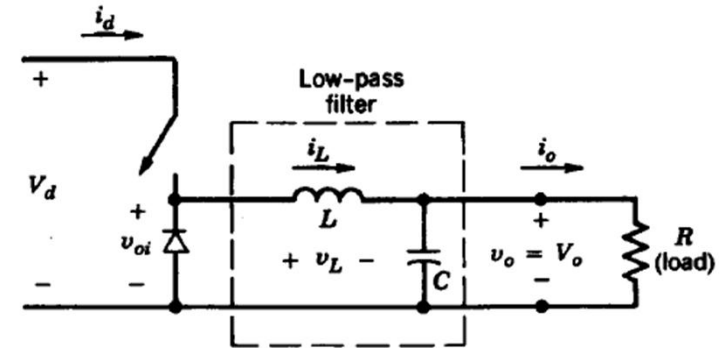
$$= \frac{\pi^2}{2} (1 - D) \left(\frac{f_c}{f_s} \right)^2$$



Step-down (buck) converter summary

- Output vs input



$$\frac{V_o}{V_d} = D$$

$$\frac{I_o}{I_d} = \frac{1}{D}$$

- High ripple current

$$I_{Lpeak} = 2I_o$$

- Practical for D not lower than 0.2

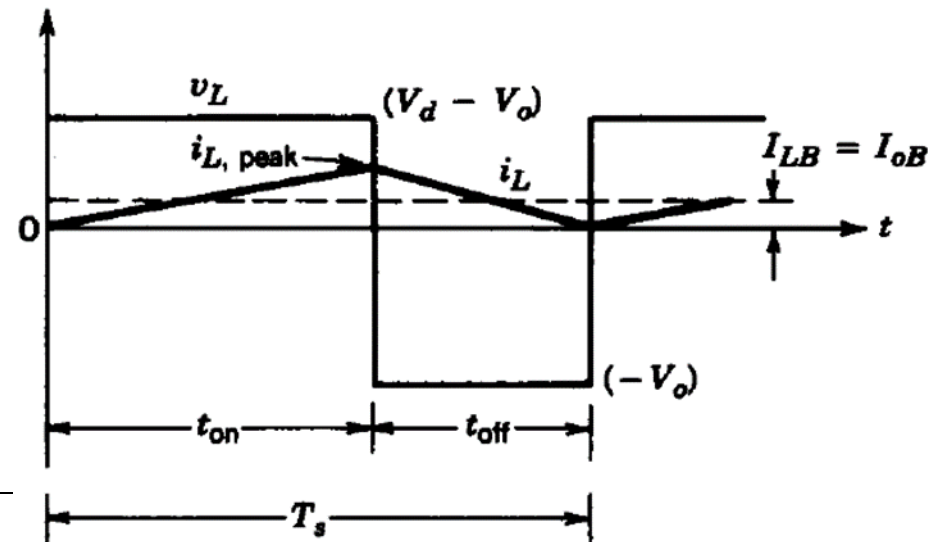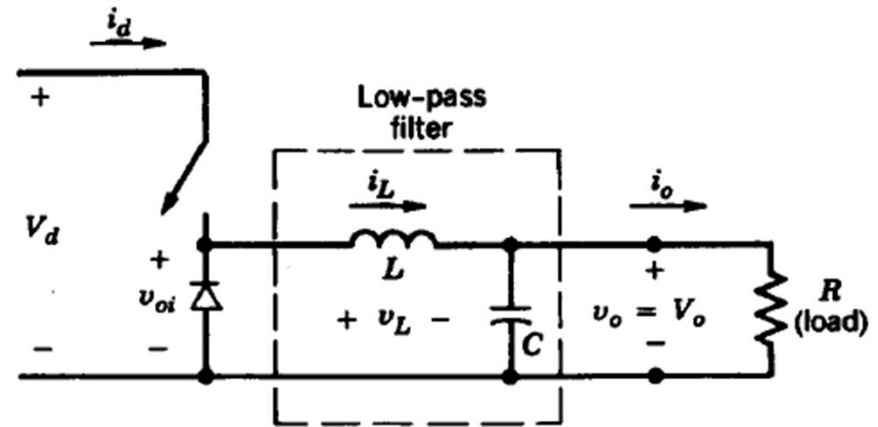


Lecture 6

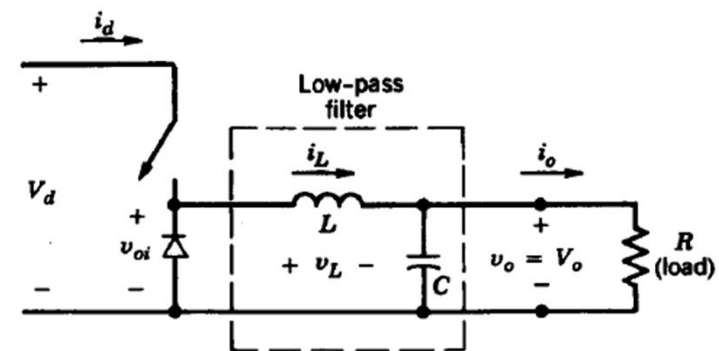Exercises, buck-converter


7-1

- In a step-down converter, consider all components to be ideal. Let $v_o \approx V_o$ be held constant at 5 V by controlling the switch duty ratio D .
- Calculate the minimum inductance L required to keep the converter operation in a continuous-conduction mode under all conditions if:
 V_d is 10-40 V , $P_o \geq 5$ W, and $f_s = 50$ kHz.




7-2

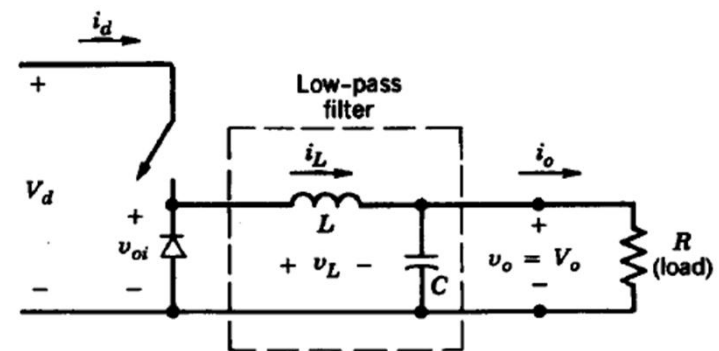- Consider all components to be ideal. Assume $V_o = 5\text{ V}$, $f_s = 20\text{ kHz}$, $L = 1\text{ mH}$, and $C = 470\text{ }\mu\text{F}$.
- Calculate ΔV_o (peak-peak) if $V_d = 12.6\text{ V}$, and $I_o = 200\text{ mA}$.




Step-up (boost) converter

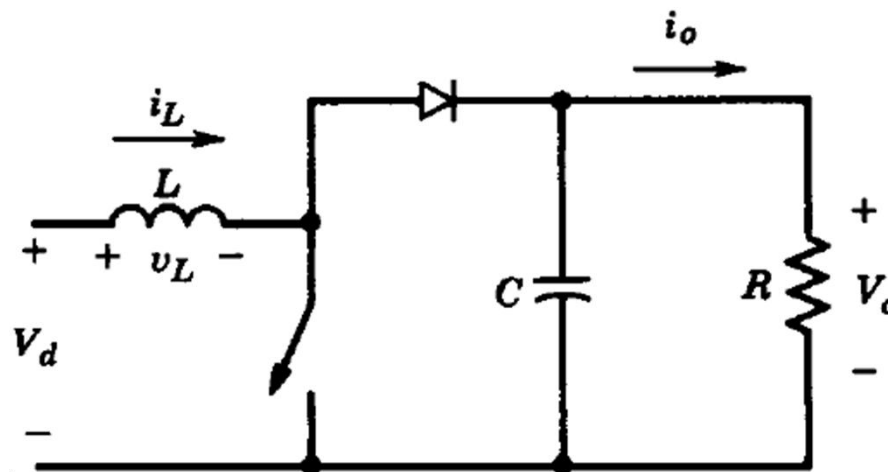- Output must be larger than input voltage
 - Otherwise is V_d driving V_o directly $\Rightarrow V_o = V_d$
- Load energy into inductor, then output energy into load while still consuming energy from source
- C large enough to give $v_o(t) \gg V_o$





Step-up converter waveform, continuous conduction mode

- Switch on, diode off

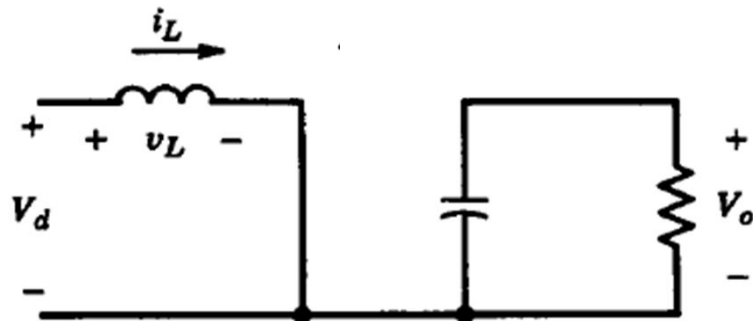

- Switch off, diode on

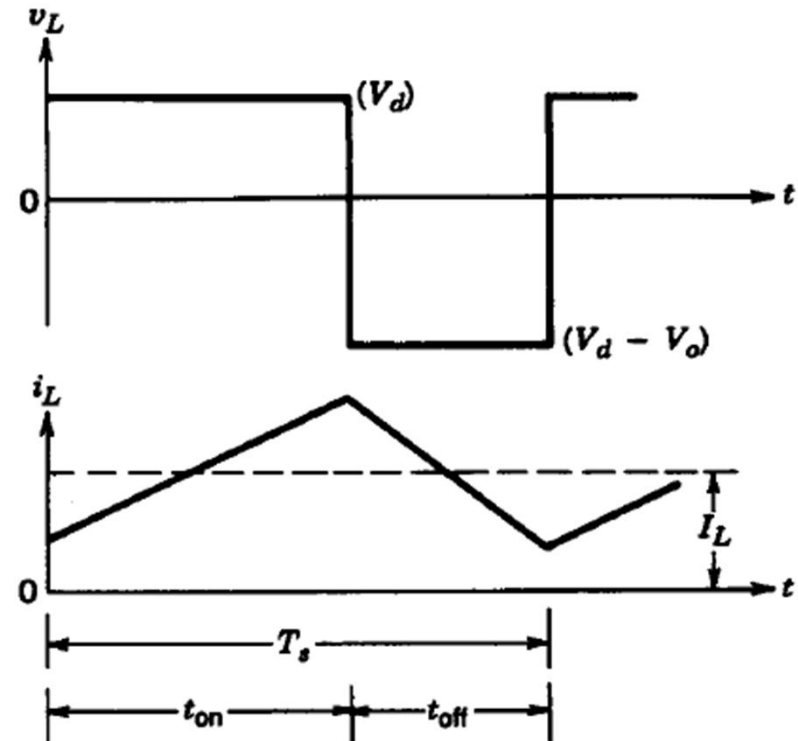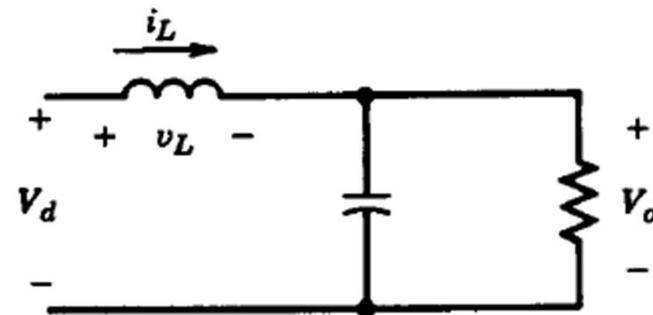



Step-up converter, continuous mode

$$V_d t_{on} + (V_d - V_o) t_{off} = 0$$

$$V_o/V_d = \frac{T_s}{t_{off}} = \frac{1}{1-D}$$

Lossless circuit: $V_d I_d = V_o I_o$

$$\Rightarrow \frac{I_o}{I_d} = (1-D)$$

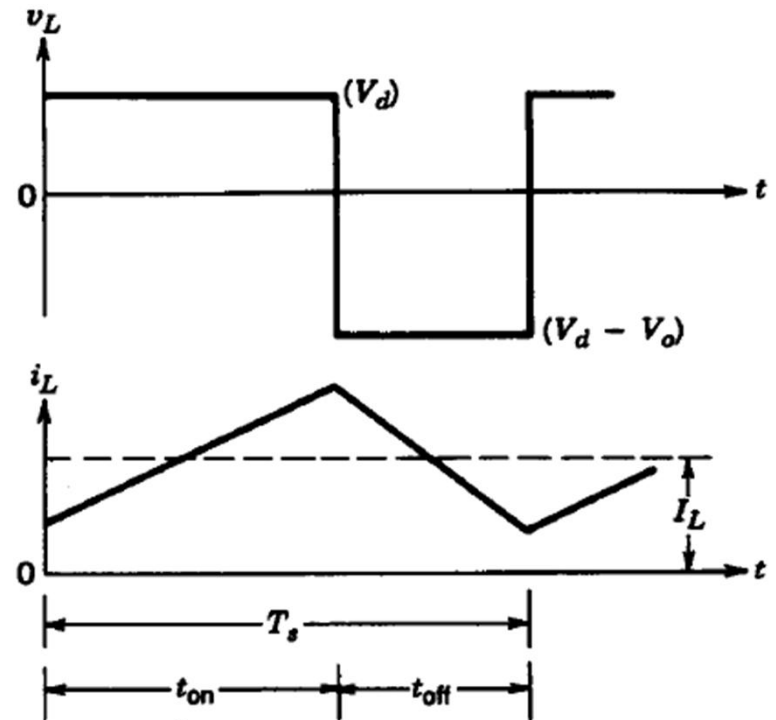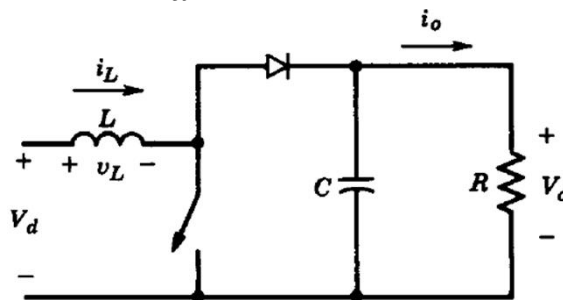



Boundary between continuous and discontinuous mode

$$I_{LB} = \frac{1}{2} i_{L,peak} = \frac{1}{2} \frac{V_d}{L} t_{on}$$

$$I_{LB} = \frac{T_s V_o}{2L} D(1 - D)$$



$$I_{oB} = \frac{T_s V_o}{2L} D(1 - D)^2$$
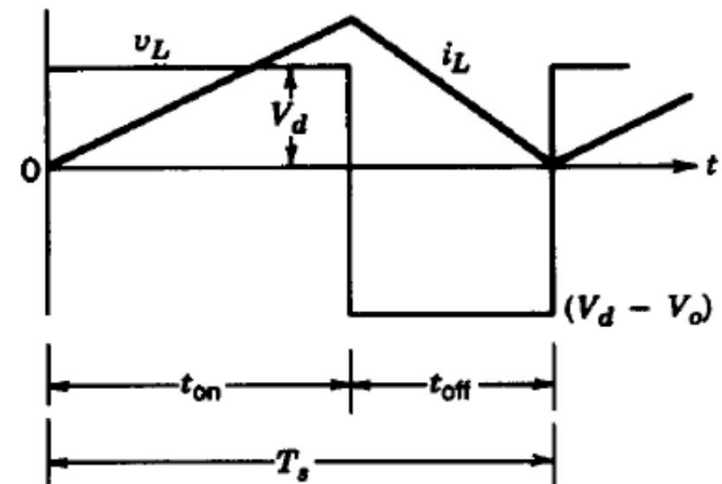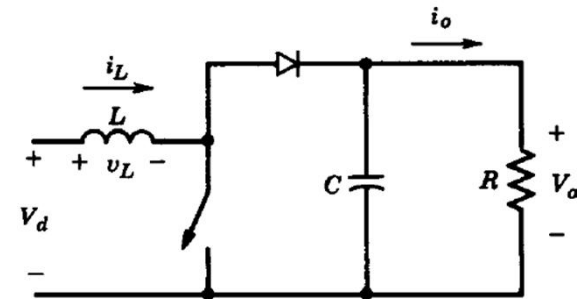
$$L = \frac{T_s V_o}{2I_{oB}} D(1 - D)^2$$



Boundary between continuous and discontinuous mode
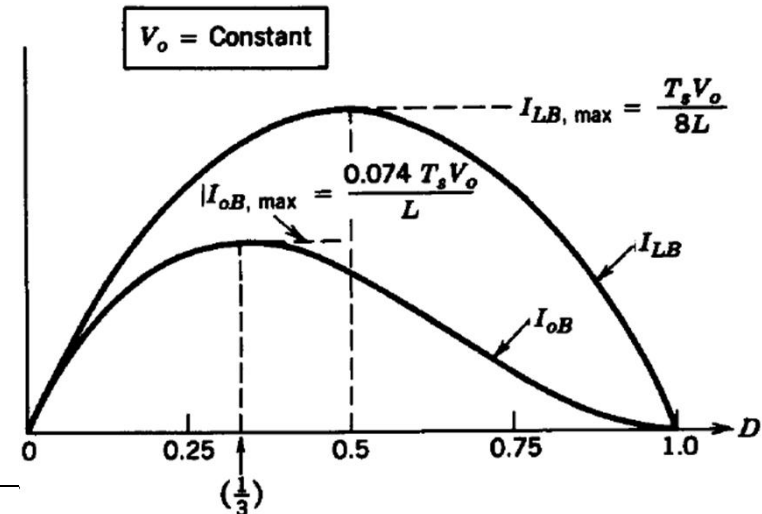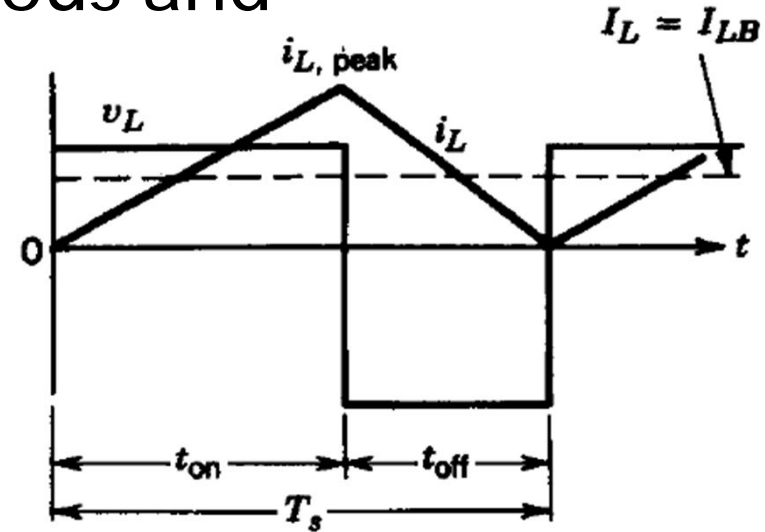
$$\begin{aligned}
 &V_o \text{ constant} \\
 &I_{LB} \text{ max when } D = 0.5 \\
 &I_{LB, \max} = \frac{T_s V_o}{8L} \\
 &I_{oB} \text{ max when } D = 1/3 \\
 &I_{oB, \max} = \frac{2}{27} \frac{T_s V_o}{L} = 0.074 \frac{T_s V_o}{L} \\
 &I_{LB} = 4D(1 - D)I_{LB, \max} \\
 &I_{oB} = \frac{27}{4} D(1 - D)^2 I_{oB, \max}
 \end{aligned}$$



Step-up, discontinuous mode

$$V_d DT_s + (V_d - V_o) \Delta_1 T_s = 0$$

$$\frac{V_o}{V_d} = \frac{\Delta_1 + D}{\Delta_1}$$

$$\frac{I_o}{I_d} = \frac{\Delta_1}{\Delta_1 + D}$$


$$\frac{I_o}{I_d} = \frac{\Delta_1}{\Delta_1 + D}$$

$$I_d = \frac{V_d}{2L} DT_s (D + \Delta_1)$$

$$I_o = \frac{T_s V_d}{2L} D \Delta_1$$


Controller
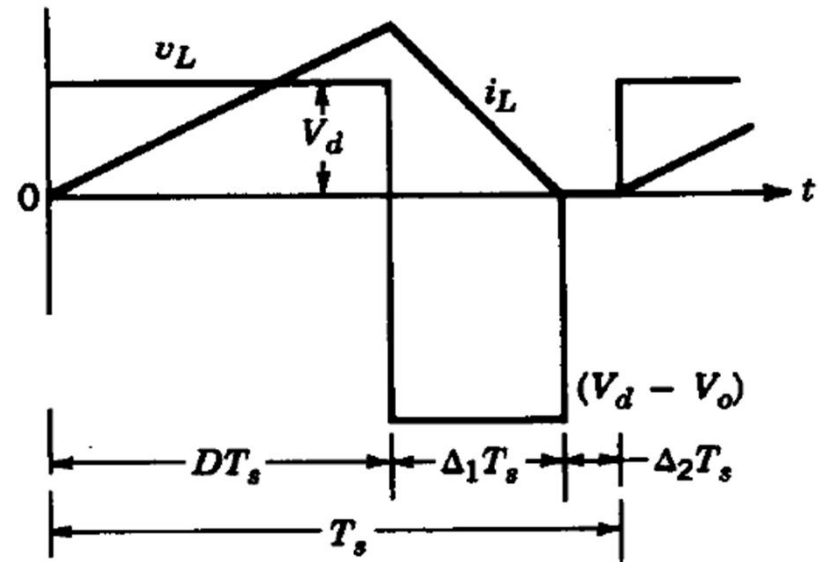
$$D = \left[\frac{4}{27} \frac{V_o}{V_d} \left(\frac{V_o}{V_d} - 1 \right) \frac{I_o}{I_{oB,max}} \right]^{1/2}$$




Step up converter characteristics, V_o constant

$$I_{oB,max} = 0.074 \frac{T_s V_o}{L}$$

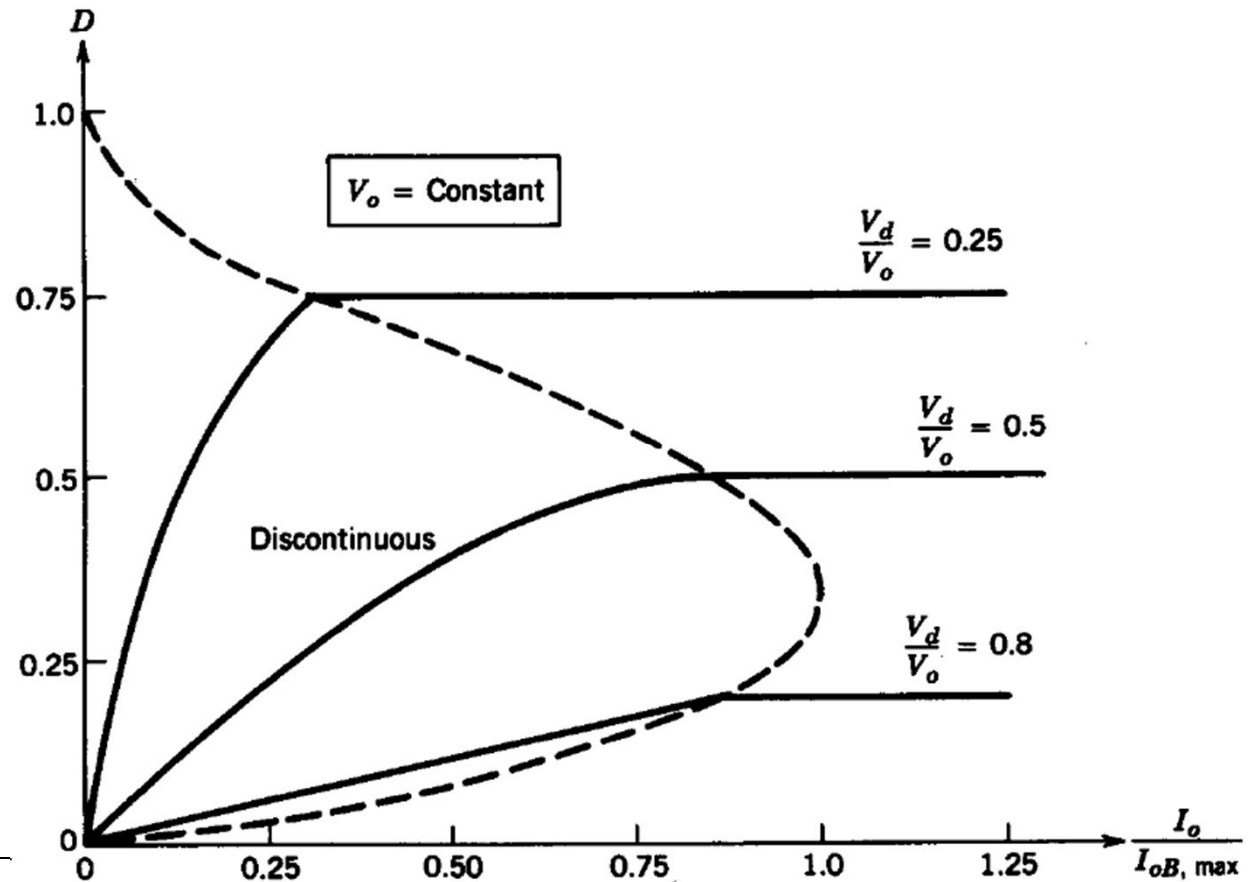

Effects of parasitics

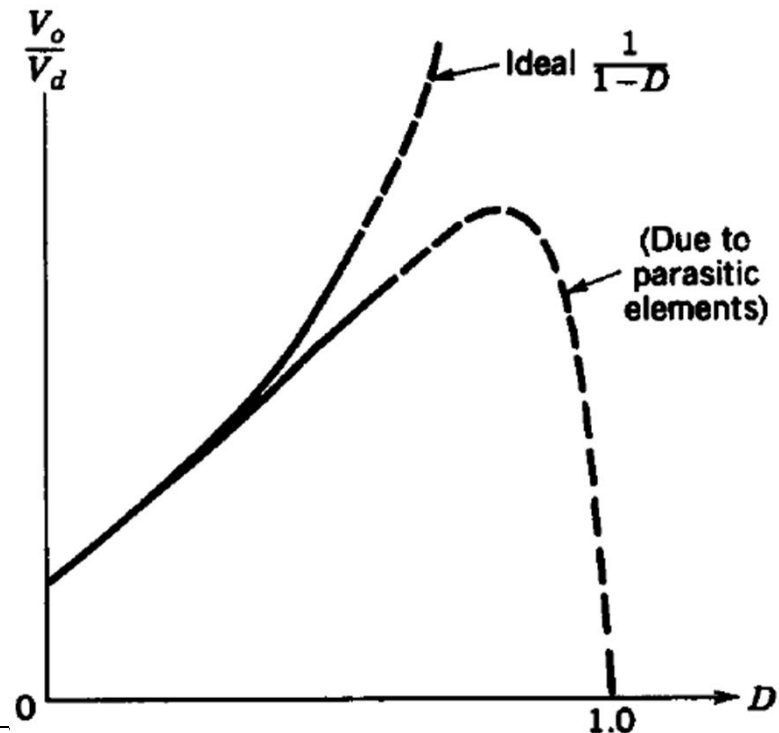- Losses in L, diode, switch, C
- Limited also by acceptable D ratio




Output voltage ripple

$$\Delta V_o = \frac{\Delta Q}{C} = \frac{I_o D T_s}{C}$$

$$\frac{\Delta V_o}{V_o} = \frac{D T_s}{RC} = D \frac{T_s}{\tau}$$

where

$\tau = RC$ time constant

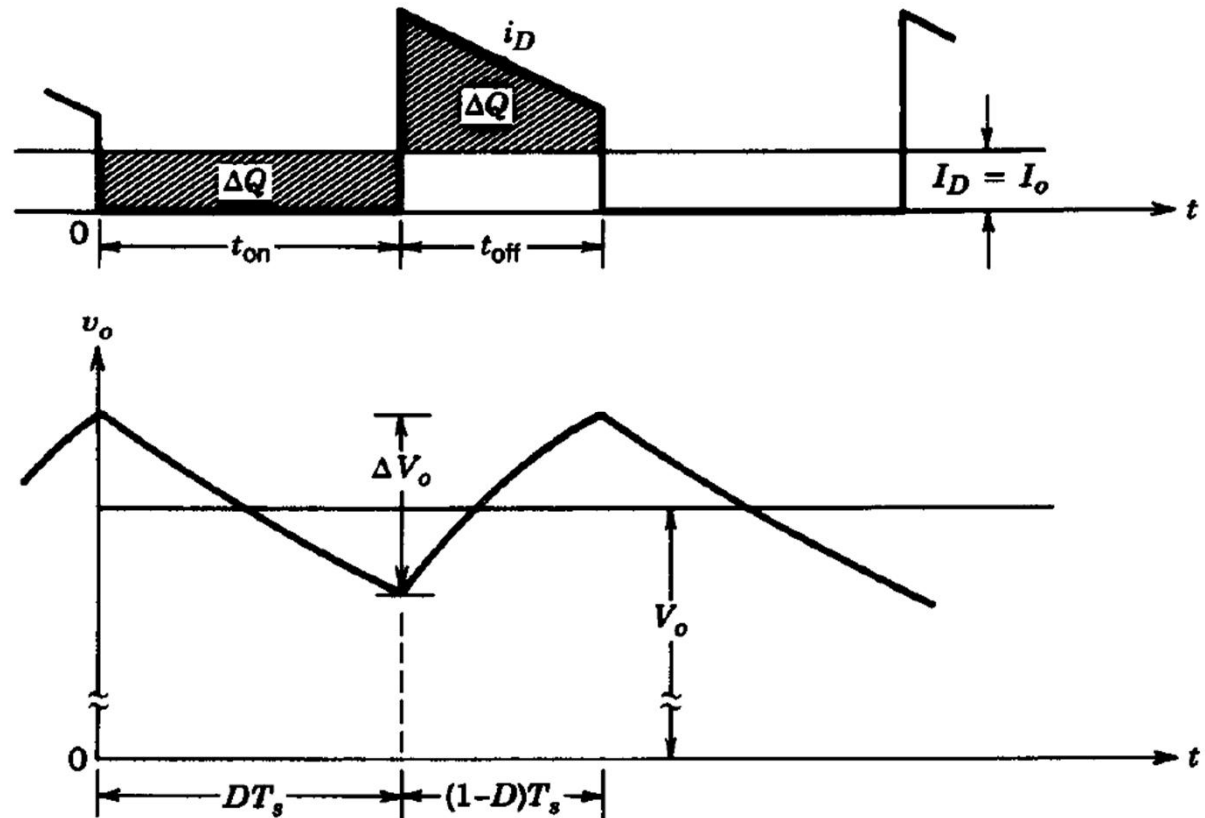


Lecture 6

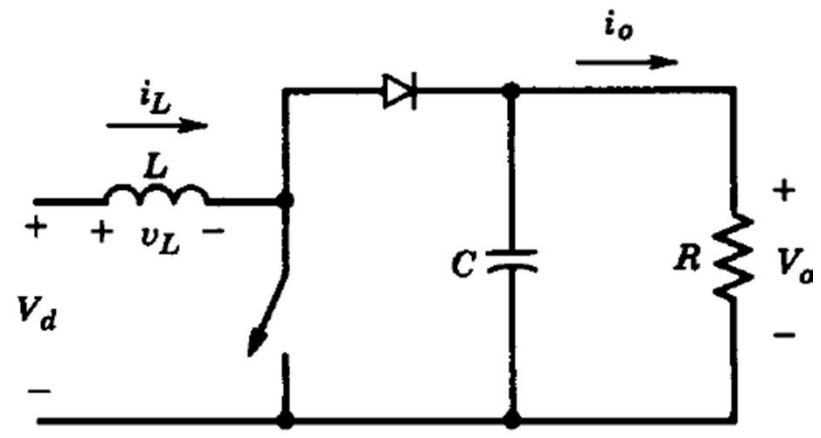Exercises on boost converter


7-7

- In a step-up converter, consider all components to be ideal. Let V_d be 8-16 V, $V_o = 24$ V (regulated), $f_s = 20$ kHz, and $C = 470 \mu\text{F}$.
- Calculate L_{min} that will keep the converter operating in a continuous-conduction mode if $P_o \geq 5$ W.



7-8

- In a step-up converter, $V_d = 12\text{ V}$, $V_o = 24\text{ V}$, $I_o = 0.5\text{ A}$, $L = 150\text{ }\mu\text{H}$, $C = 470\text{ }\mu\text{F}$, and $f_s = 20\text{ kHz}$.
- Calculate ΔV_o (peak-peak).


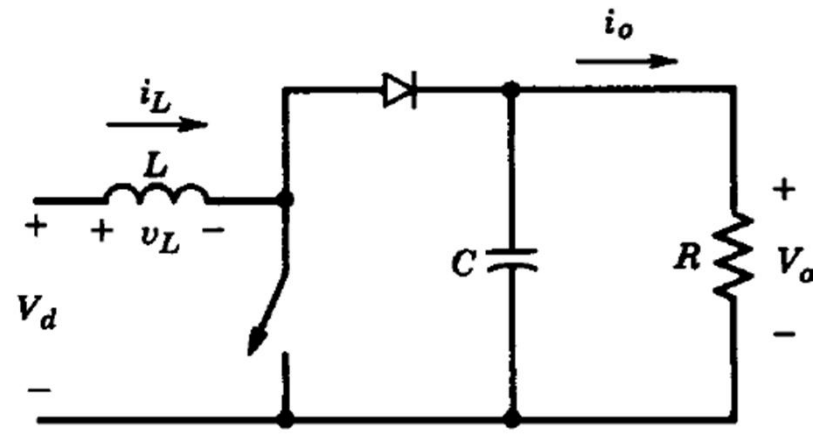


Lecture 6

Other converter topologies


Flyback converter

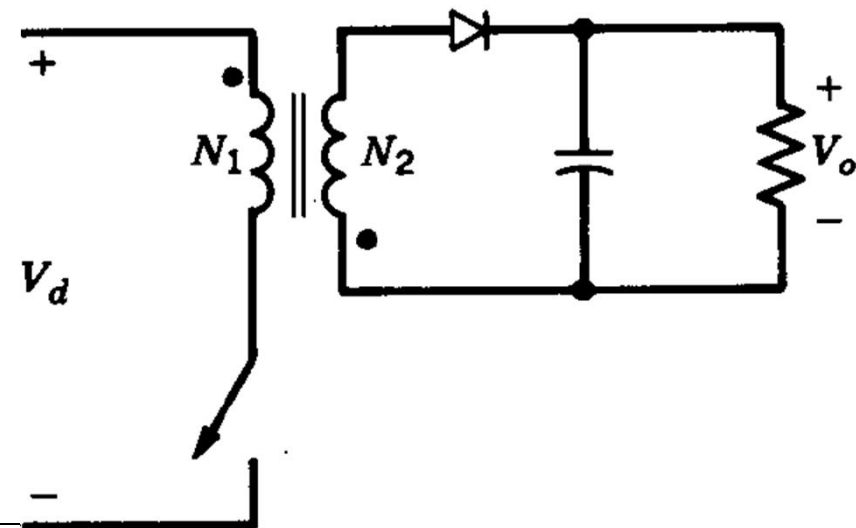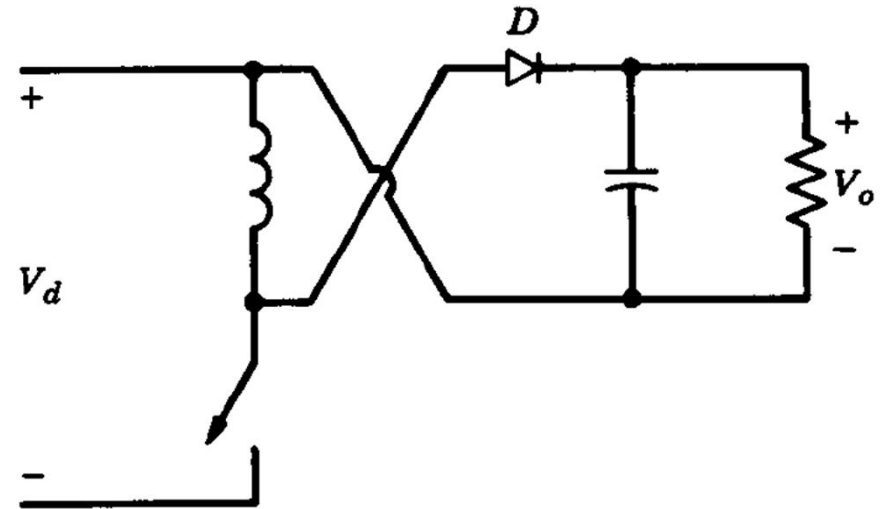- Derived from buck-boost structure
- Second winding gives electric isolation
- Only flux flow in one direction
 - Never negative currents in the transformer



Flyback converter circuit states

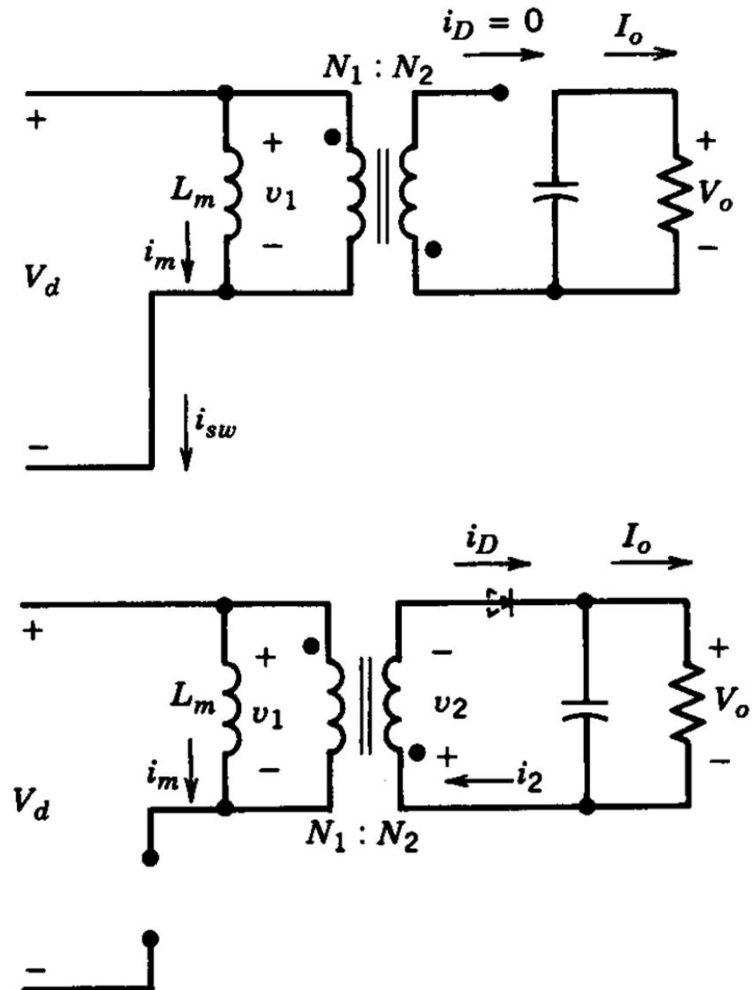- Switch on and switch off
- Continuous conduction mode
 - Incomplete demagnetization
- L_m size important
 - Ideal transformer have infinite L_m




Flyback converter waveforms

- Same control equation as for buck-boost converter


$$D = \frac{t_{on}}{T_s}$$
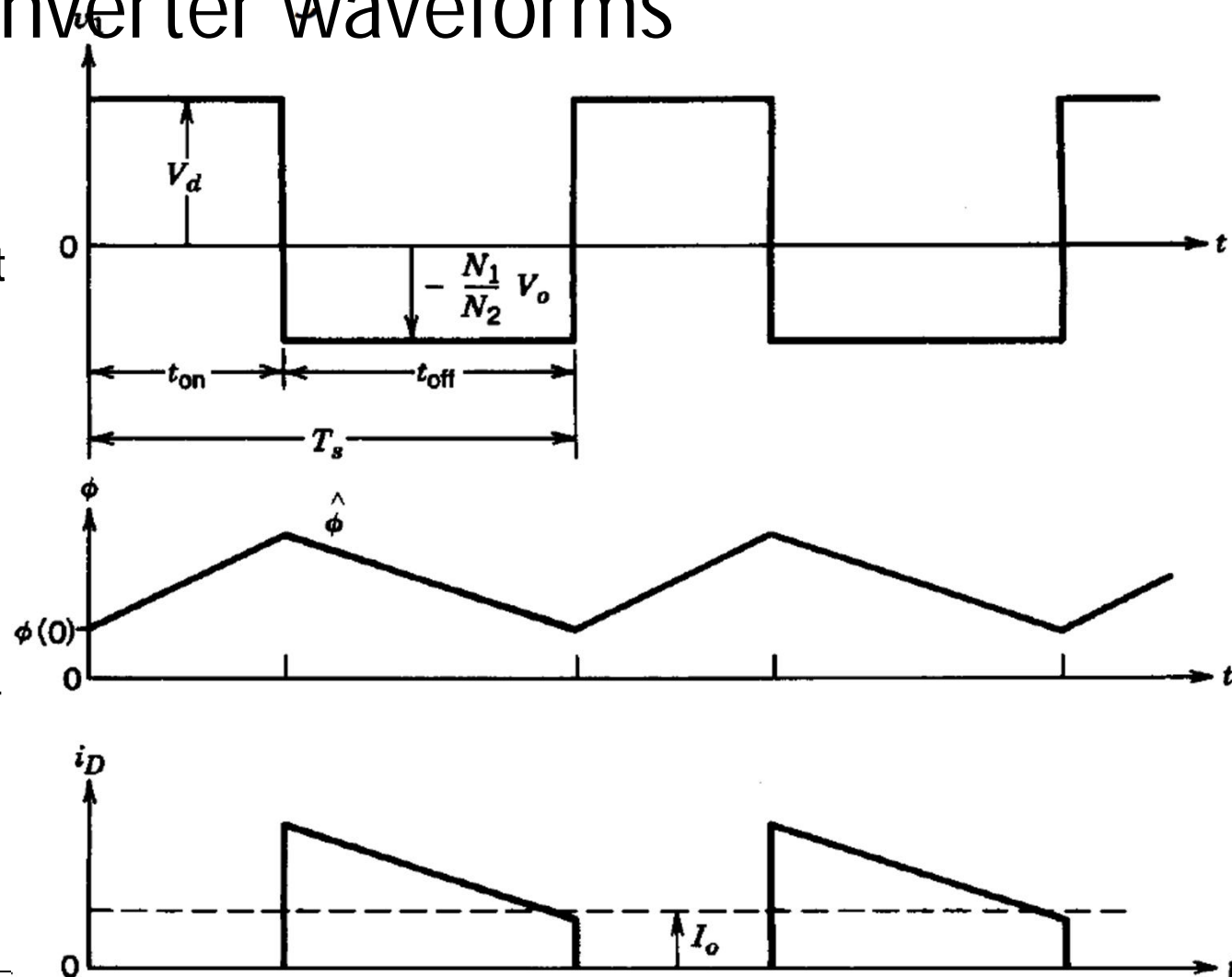
$$\frac{V_o}{V_d} = \frac{N_2}{N_1} \frac{D}{1 - D}$$




Alternative flyback converter topologies

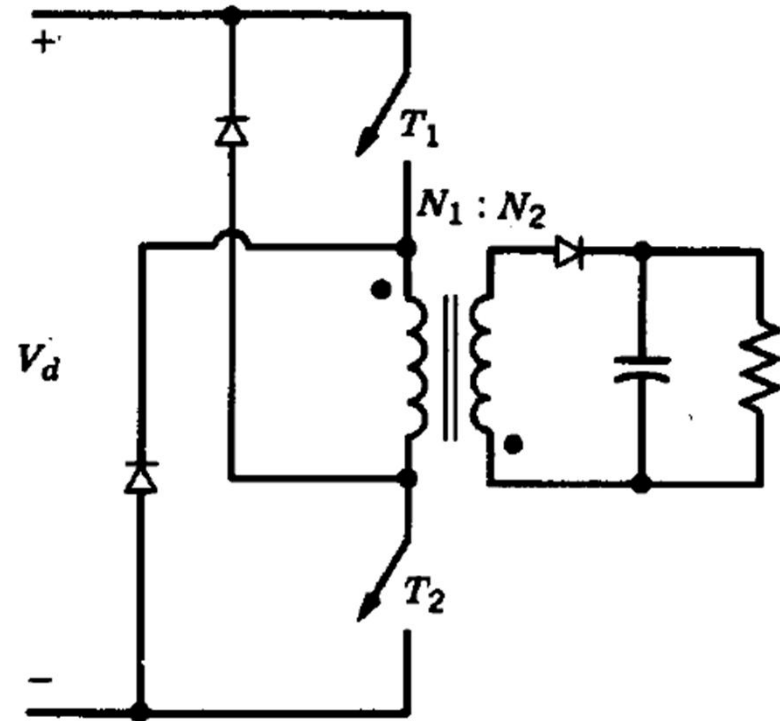- Two transistor flyback
 - Both turn on and off simultaneously
 - Voltage rating half compared to single transistor
 - No snubber necessary because of diodes




Alternative flyback converter topologies

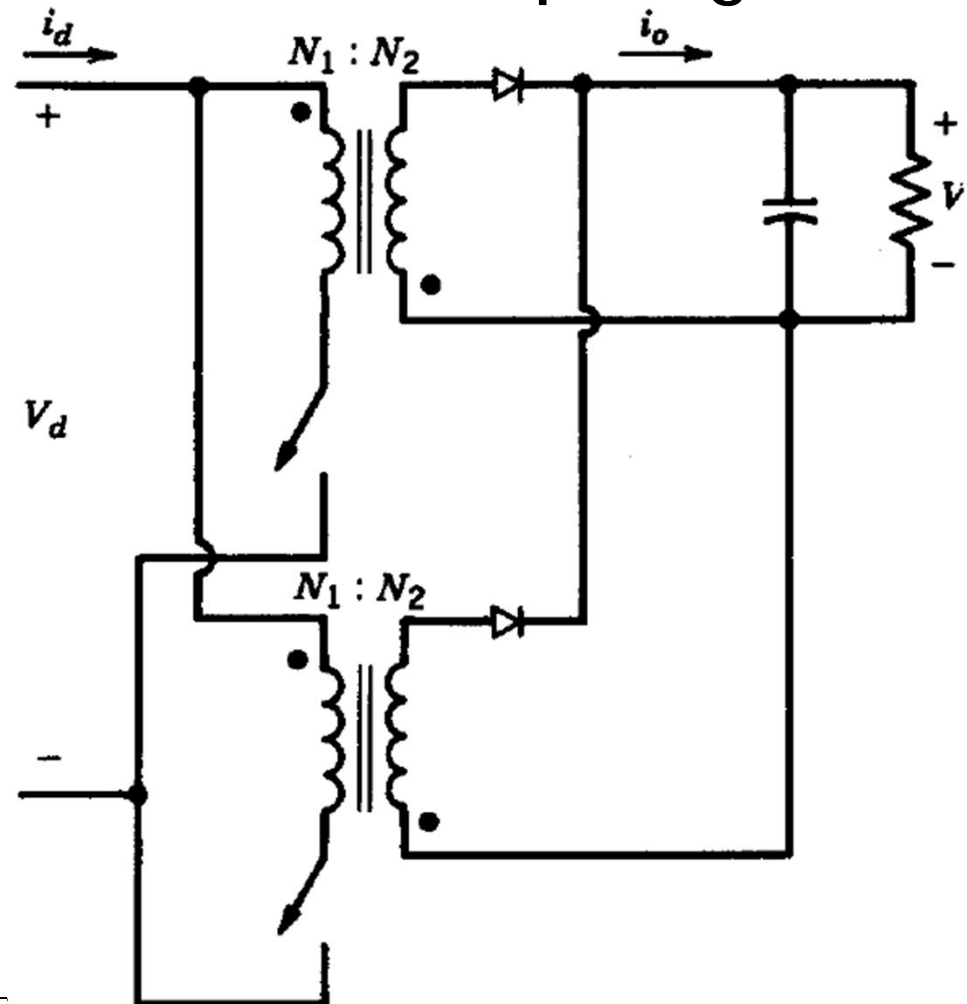- Paralleling flyback converter
 - Same frequency of switching
 - Phase-shifting switches π
- Allow higher power
- Redundancy
- Increased effective switching frequency



Forward converter


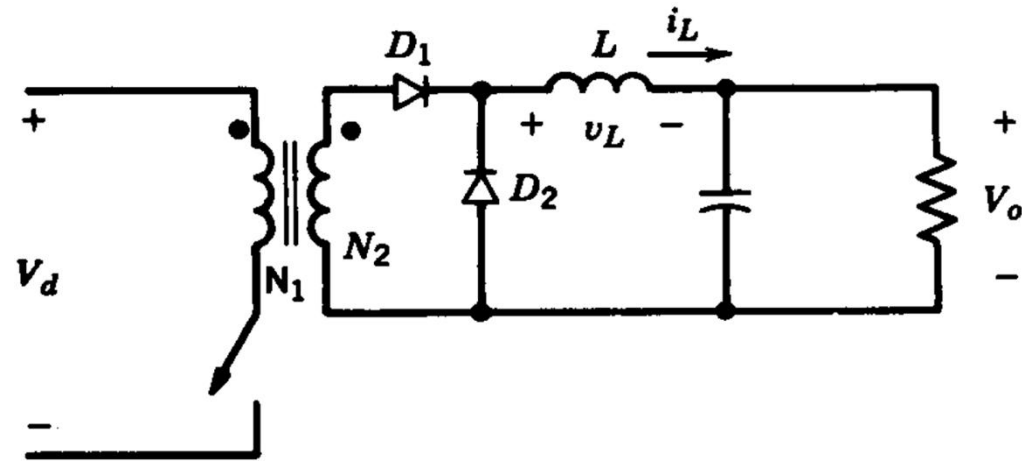
- Derived from step-down converter
- Ideal transformer assumed
 - Transformer magnetizing current not included
 - Converter failure if not taken care of



$$\frac{V_o}{V_d} = \frac{N_2}{N_1} D$$

Practical forward converter

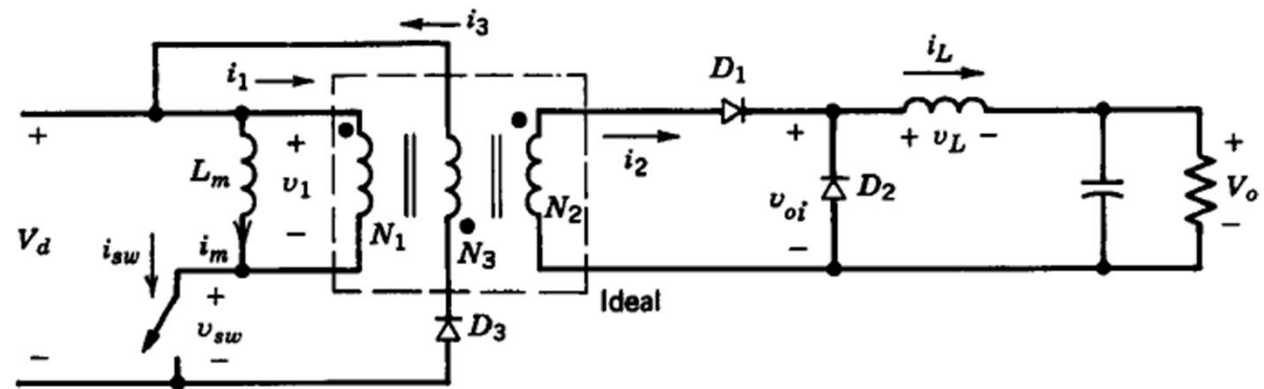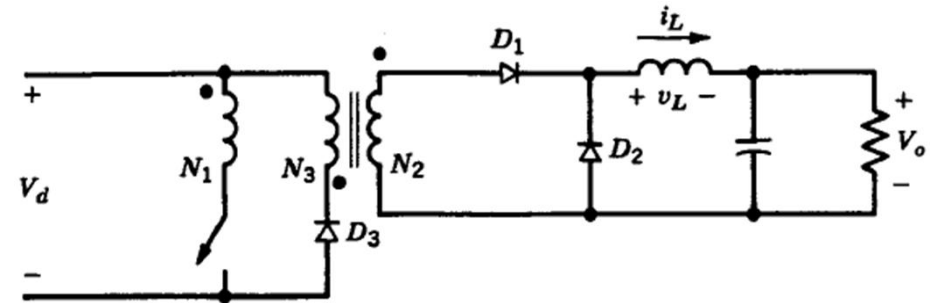- Feed magnetic current back to source
- Requires a third winding





Practical forward converter waveforms

- To guarantee demagnetized transformer

$$\max \frac{t_m}{T_s} = 1 - D$$


$$(1 - D_{max}) = \frac{N_3}{N_1} D_{max}$$

$$D_{max} = \frac{1}{1 + N_3/N_1}$$

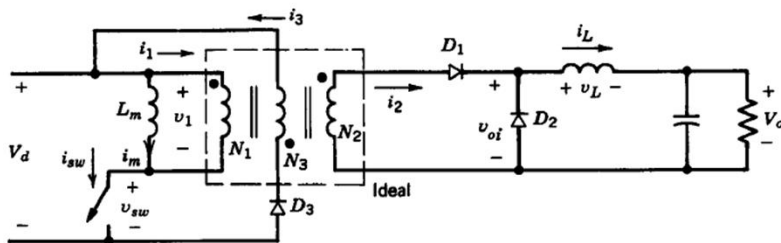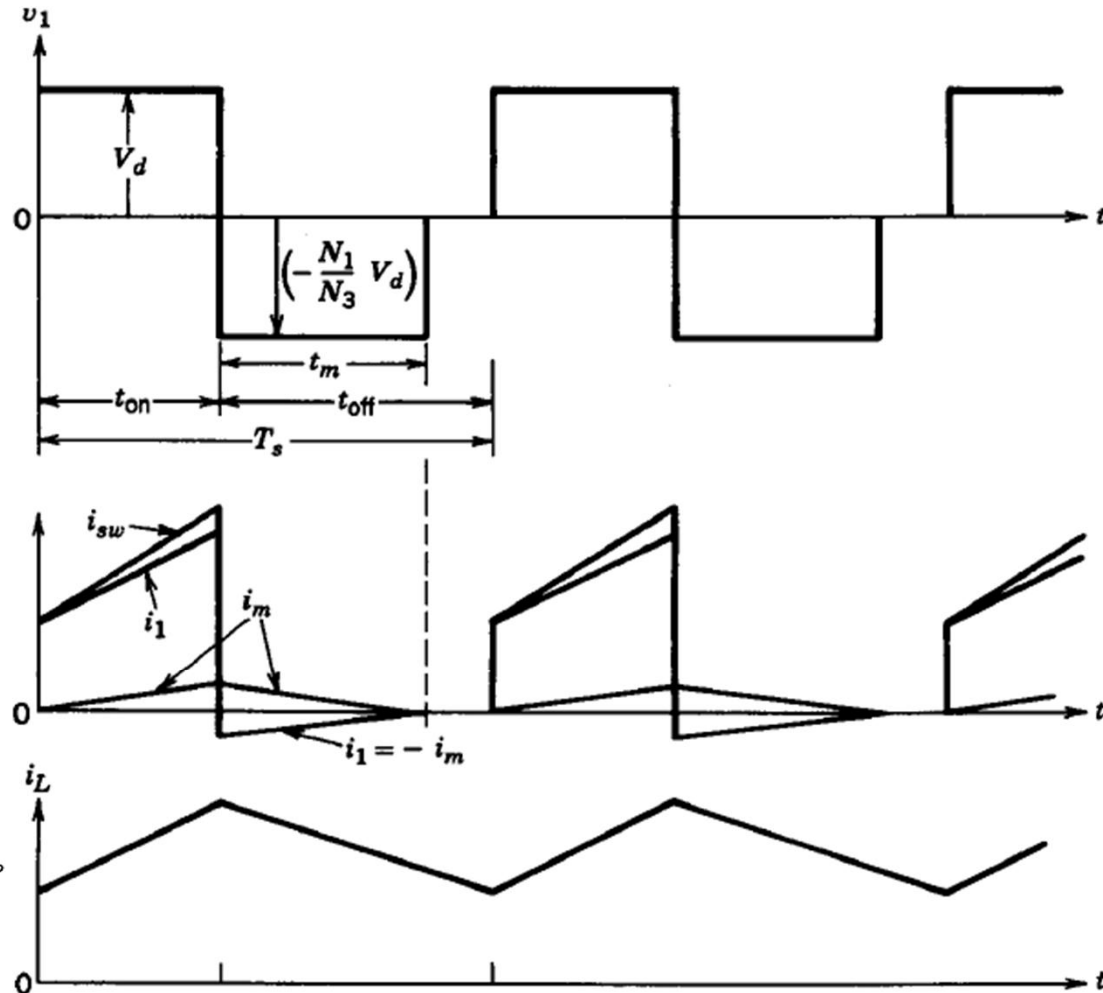


Other forward converter topologies

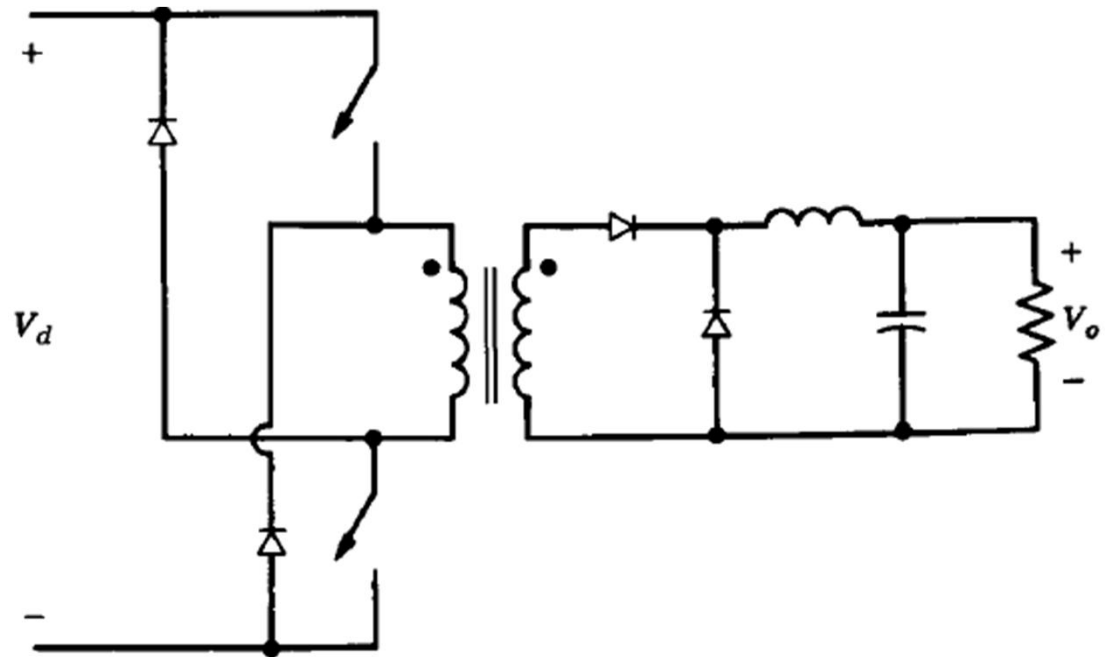- Two-switch forward converter
- Commonly used
- Voltage rating half of single transistor case
- No snubbers necessary



Other forward converter topologies

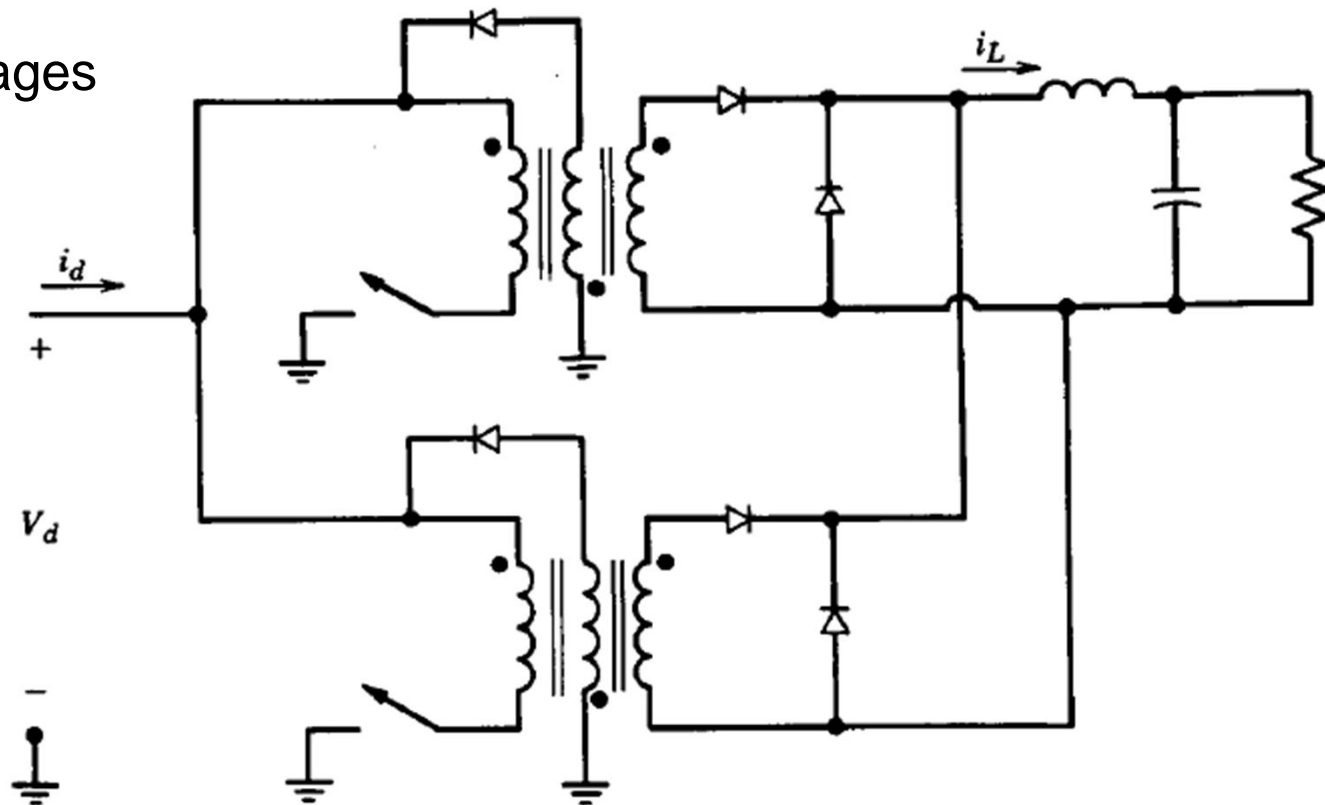- Paralleled forward converter
- Same advantages as paralleled flyback converter





Push-pull converter

- Derived from step-down converter
- Diodes due to leakage inductances
- PWM control


$$\frac{V_o}{V_d} = 2 \frac{N_2}{N_1} D$$

$$0 < D < 0.5$$

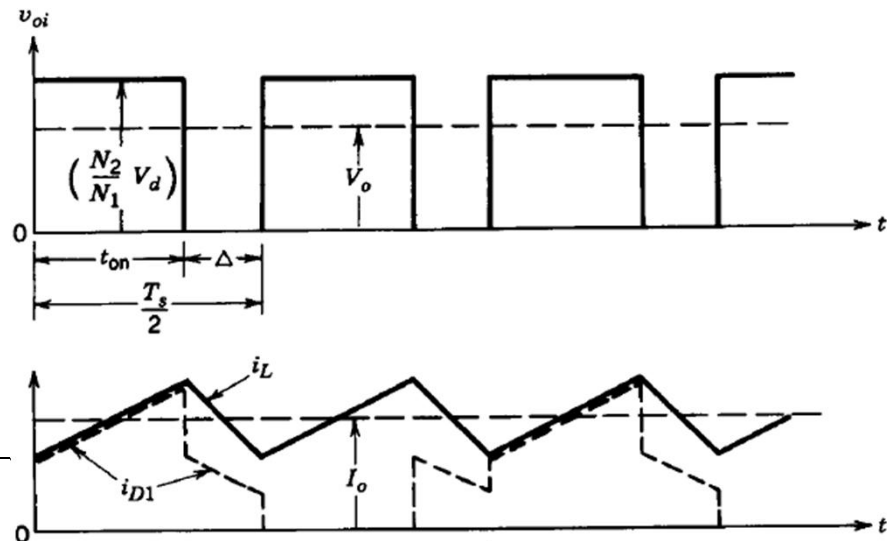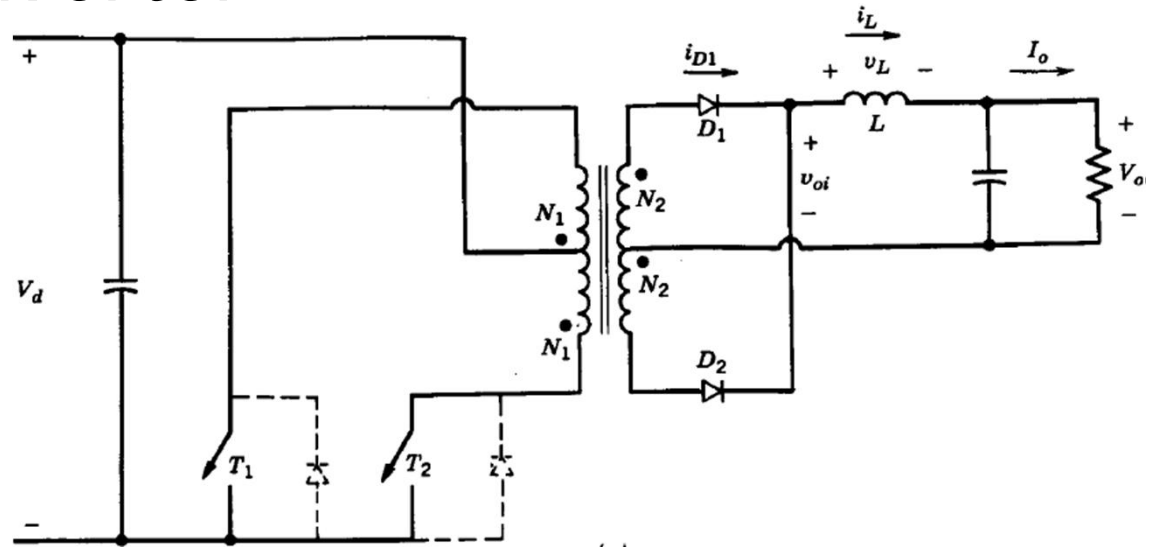


Half-bridge converter

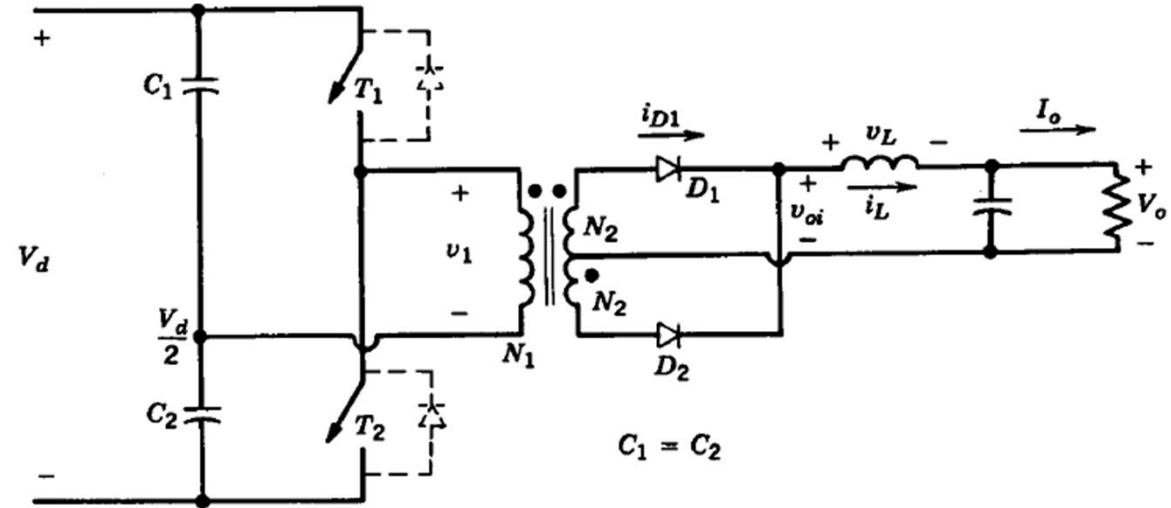- Derived from step-down converter
- Additional diodes for switch protection






$$\frac{V_o}{V_d} = \frac{N_2}{N_1} D$$

$$0 < D < 0.5$$

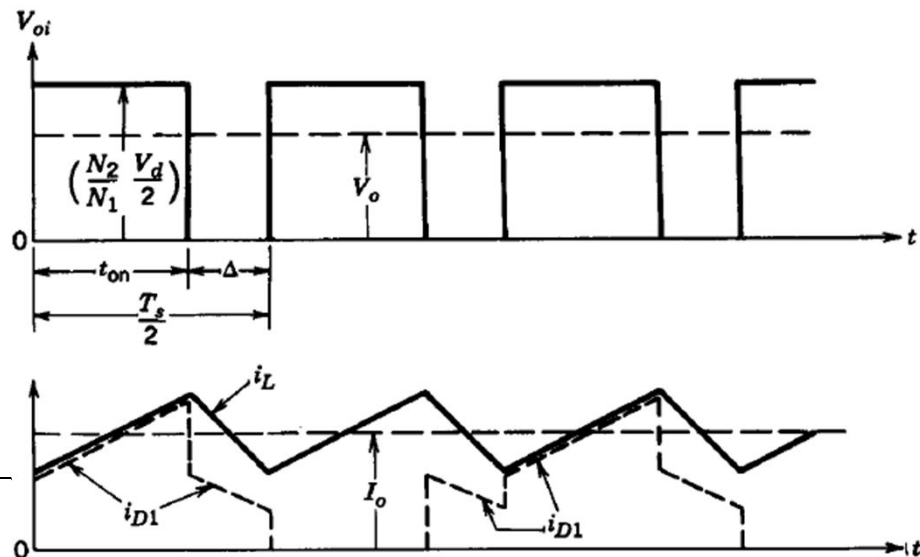

Full-bridge converter

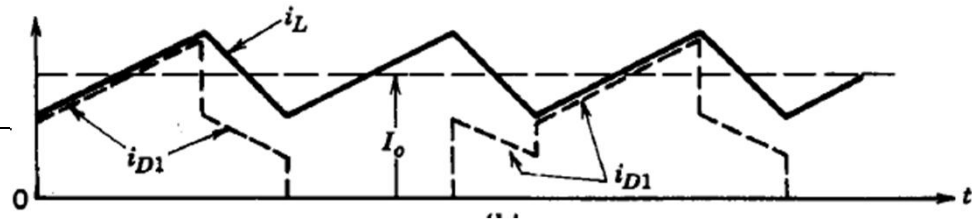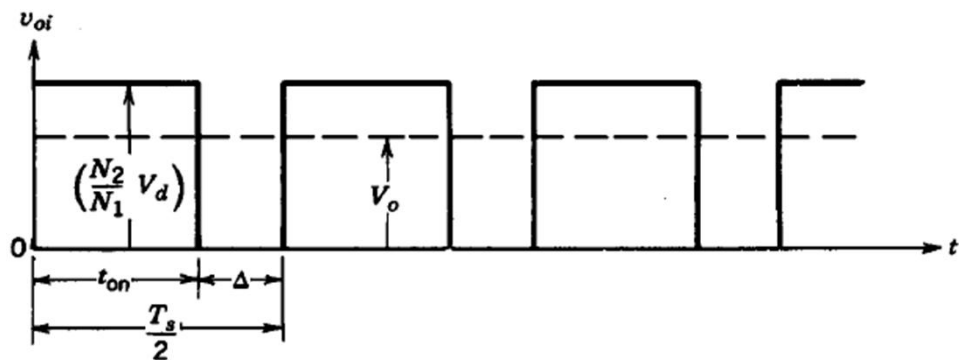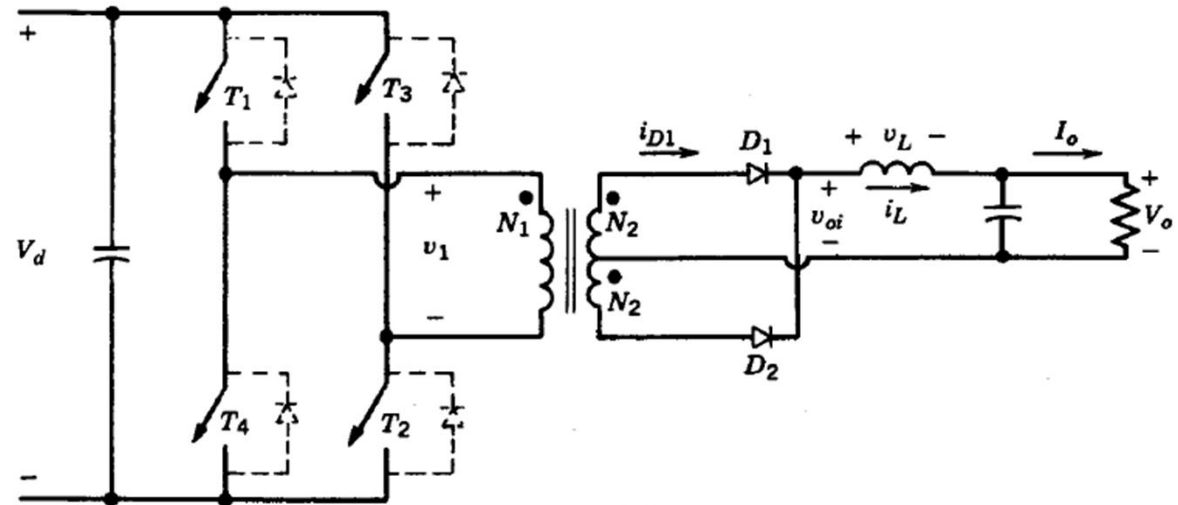- Derived from step-down converter
- Switches carry half the current compared to the half bridge converter



$$\frac{V_o}{V_d} = 2 \frac{N_2}{N_1} D$$


$$0 < D < 0.5$$

Current-source dc-dc converter

- L_d and $D > 0.5$ gives current source input
 - One or both switches always on
- Operates like a step-up converter

$$\frac{V_o}{V_d} = \frac{N_2}{N_1} \frac{1}{2(1-D)}$$

$$D > 0.5$$

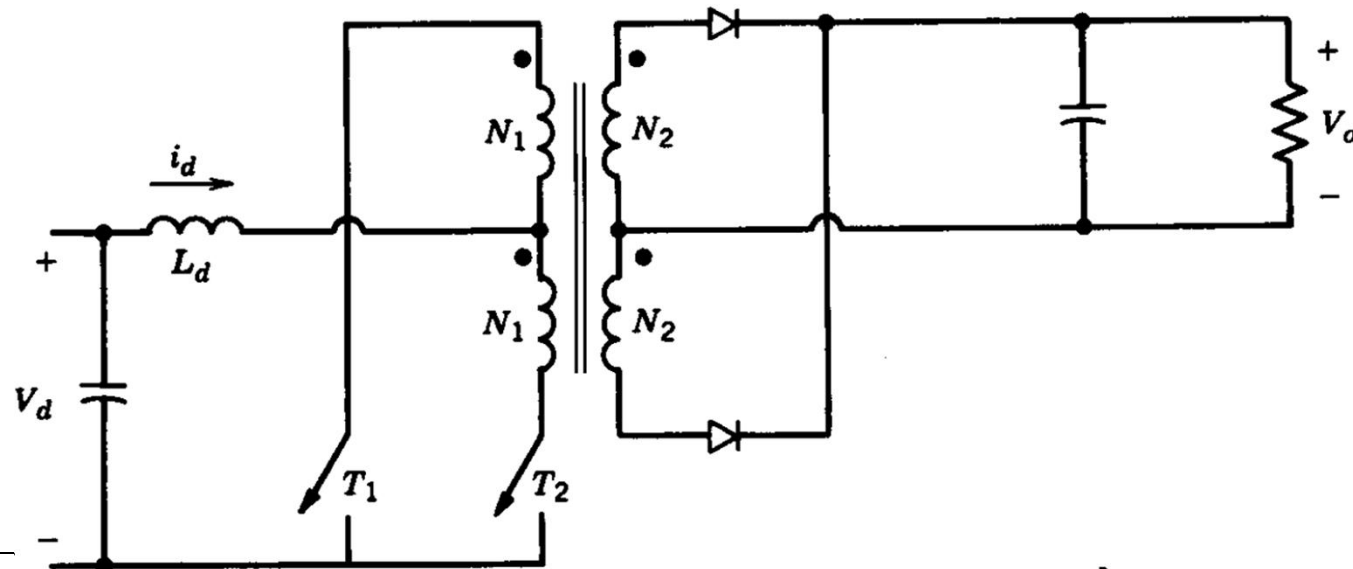

www.liu.se