


TSTE19

Power Electronics


Examination (TEN1)

Time:	Friday 21 December 2012 at 8.00 - 12.00
Place:	KÅRA
Responsible teacher:	Kent Palmkvist, ISY, 28 13 47, 0705 23 31 59 (kentp@isy.liu.se) Will visit exam location at 9 and 11.
Number of tasks:	6
Number of pages:	4
Allowed aids:	Calculator
Notes:	A pass on the exam requires approximately 30 points. Remember to indicate the steps taken when solving problems.
Exam presentation:	Friday 18 January 2013 12.30-13.30 (Kent Palmkvist's office)

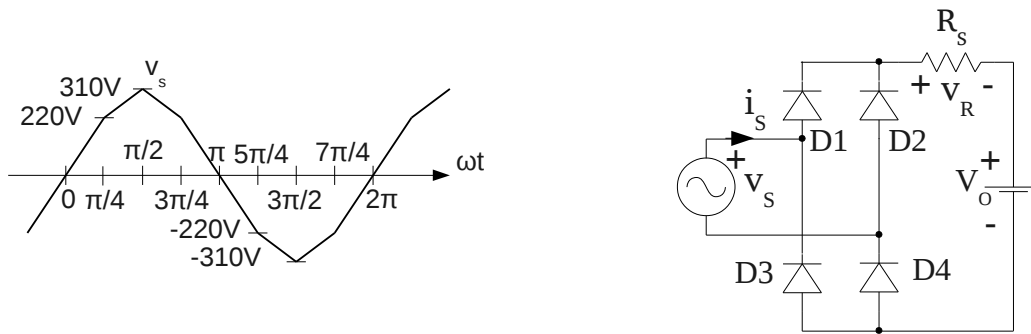1. a) Describe two ways a battery charger may determine if a battery cell is fully charged. (2)
- b) What type of motor have a permanent magnet as a rotor? (2)
- c) Why must the dv/dt be limited when applying a positive voltage across the thyristor, that is, what will happen if dv/dt is too large? (2)
- d) What is a GTO? (2)
- e) What type of load (resistive, inductive, or capacitive) can sometimes be modeled as a current source? (2)




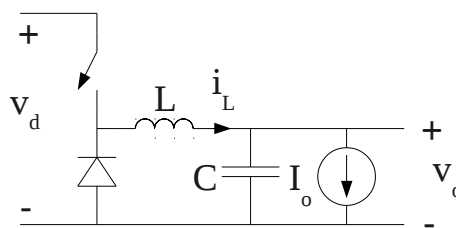2. The rectifier above to the right have a source voltage v_s as shown above to the left. The output voltage V_o is 265V. The series resistance R_s is 15 Ω .
 - a) Draw the input voltage v_s , resistor voltage v_r , and input current i_s shapes, indicate where each diode is on (conducting) or off (not conducting), and at what angles current and voltage changes happen. (4)
 - b) Calculate the peak i_s source current. (4)
 - c) Calculate the i_s source current rms value. (6)



3. The DC-DC converter above is working in continuous conduction mode, $V_d = 12V$, $L = 37.5 \mu H$, $D = 0.25$, $I_o = 1.5A$. Assume C is large.
 - a) Calculate the output voltage V_o . (4)
 - b) Calculate the minimum switching frequency to keep continuous conduction mode. (6)

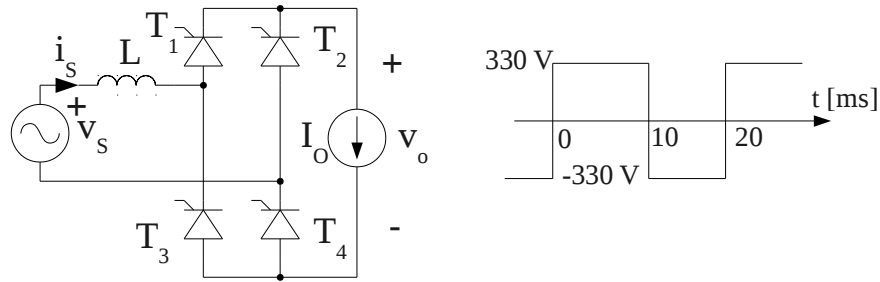4. A computer processor power supply have a 12V input, and the processor dissipates 45W when running at 1.5V (this is the output of DC-DC converter). The efficiency of the DC-DC converter is 90%. The ambient temperature is at most 25 degrees, and the maximum case (processor casing) temperature is 55 degrees.
- How large is the average input current to the DC-DC converter? (4)
 - How much power is dissipated by the DC-DC converter? (4)
 - What is the largest thermal resistance Θ_{ca} allowed for the heat sink. (4)




5. The thyristor based inverter above have the input voltage v_s shown above to the right. The thyristors have a 30 degree firing angle. The current source load I_o is 3A, and the inductor $L = 110$ mH.
- Draw the output voltage v_o and the source current i_s , indicating which thyristor is on (conducting) and off (not conducting). (6)
 - Calculate the average output voltage. (6)
 - Calculate the displacement power factor (DPF) for the input power. (4)
6. A full-bridge single-phase inverter is controlled using voltage cancellation. The output fundamental frequency should be 50 Hz. The input voltage is 310V. The waveform overlap angle α is 60 degrees.
- What are the switching frequency and duty ratio (t_{on}/T_{sw} ratio) of the switches? (2)
 - Calculate the amplitude of output voltage fundamental, v_{o1} . (6)

Formula collection TSTE19 Power Electronics

Fourier series coefficients using symmetry, Table 3.1

Even	$f(-t) = f(t)$	$b_h = 0$	$a_h = \frac{2}{\pi} \int_0^{\pi} f(t) \cos(h\omega t) d(\omega t)$
Odd	$f(-t) = -f(t)$	$a_h = 0$	$b_h = \frac{2}{\pi} \int_0^{\pi} f(t) \sin(h\omega t) d(\omega t)$
Half-wave	$f(t) = -f(t + \frac{1}{2}T)$	$a_h = b_h = 0$ for even h	
		$a_h = \frac{2}{\pi} \int_0^{\pi} f(t) \cos(h\omega t) d(\omega t)$ for odd h	
		$b_h = \frac{2}{\pi} \int_0^{\pi} f(t) \sin(h\omega t) d(\omega t)$ for odd h	
Even quarter-wave	Even and half-wave	$b_h = 0$ for all h	
		$a_h = \frac{4}{\pi} \int_0^{\frac{\pi}{2}} f(t) \cos(h\omega t) d(\omega t)$ for odd h	
		$a_h = 0$ for even h	
Odd quarter-wave	Odd and half-wave	$a_h = 0$ for all h	
		$b_h = \frac{4}{\pi} \int_0^{\frac{\pi}{2}} f(t) \sin(h\omega t) d(\omega t)$ for odd h	
		$b_h = 0$ for even h	

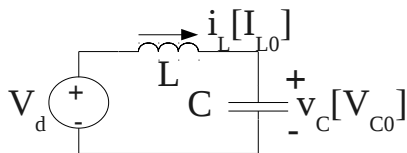
Undamped series resonant circuit, equations 9-3, 9-4



$$i_L(t) = I_{L0} \cos \omega_0(t - t_0) + \frac{V_d - V_{C0}}{Z_0} \sin \omega_0(t - t_0) \quad (9-3)$$

$$v_C(t) = V_d - (V_d - V_{C0}) \cos \omega(t - t_0) + Z_0 I_{L0} \sin \omega_0(t - t_0) \quad (9-4)$$

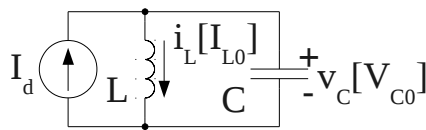Undamped parallel resonant circuit, equations 9-20, 9-21



$$i_L(t) = I_d + (I_{L0} - I_d) \cos \omega_0(t - t_0) + \frac{V_{C0}}{Z_0} \sin \omega_0(t - t_0) \quad (9-20)$$

$$v_C(t) = Z_0 (I_d - I_{L0}) \sin \omega(t - t_0) + V_{C0} \cos \omega_0(t - t_0) \quad (9-21)$$

Integration rules

$$\int_a^b f(x) dx = \int_A^B f(g(t)) g'(t) dt \quad \text{if } a = g(A), \quad b = g(B), \quad \text{and } g \text{ is monotone in } [A, B]$$

$$\int_a^b \sin(x) dx = [-\cos(x)]_a^b$$

$$\int_a^b \cos(x) dx = [\sin(x)]_a^b$$