

Instructions

Describe your calculations clearly and detailed, explaining your methods, assumptions and equations used.

Total no of points = 70. A pass on the exam requires approx. 30 points.

Question 1

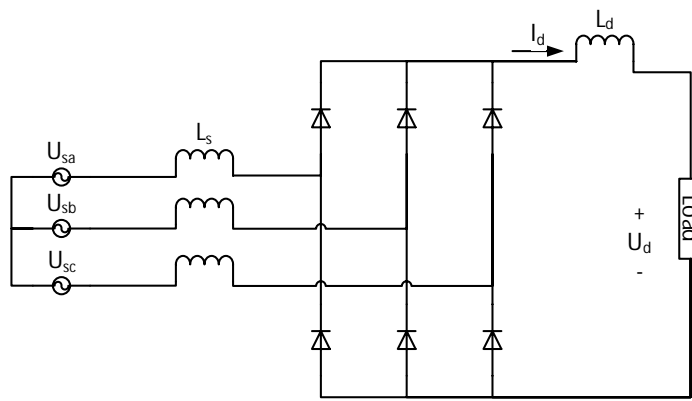


Figure 1

- a) A three phase diode rectifier according to Figure 1 has inductance, L_s , on the ac-side and L_d on the dc-side. Which inductance shall be large in order to obtain continuous current through the dc-load. (2)
- L_d shall be large to create continuous dc-side current with filtering of the ripple present in the voltage from the converter. (3)
- b) List the three most important parameters that defines the commutation of current between two diodes in a rectifier as of Figure 1. Give a short motivation why.
- U_s , L_s and I_d are the decisive parameters for the commutation angle. U_s is the voltage magnitude driving the commutation, giving shorter commutation for higher magnitude. L_s is the inductance to commutate and I_d defines the magnitude of the current to commutate. Both L_s and I_d gives longer commutation duration with increasing values.
- c) In a DC/DC converter, inductance is commonly used for energy transfer between low and high-voltage sides. If the average voltage across the inductance is greater than zero during a time interval, what can you say (2)

about the shape of the inductor current during this interval?

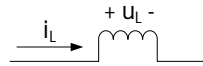


Figure 2

The inductor current will be increasing if the average voltage across the inductor is >0 .

- d) What device parameters are required to determine the conduction losses of a MOSFET if the drain current is known? (2)
The on-state resistance of the MOSFET.
- e) List three types of semiconductors with turn-off capability. (3)
MOSFET, IGBT, GTO, BJT, IGCT has the capability of forced turn-off. Thyristors and diodes has the capability to go to off-state if the current is reduced to zero.

Question 2


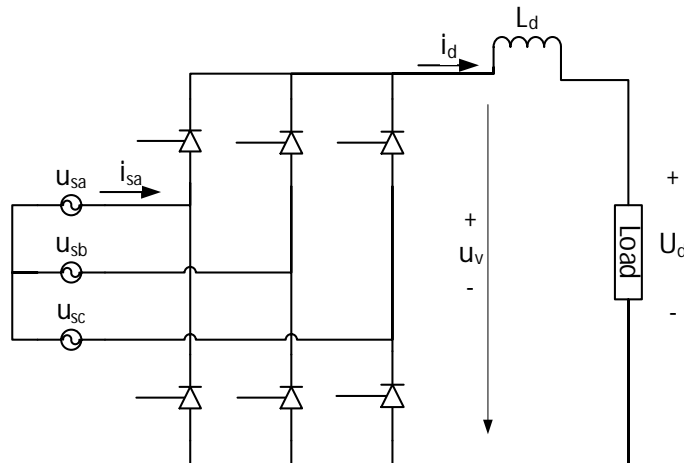



Figure 3

A three phase thyristor rectifier as shown by Figure 3 is connected to a three phase voltage source with the phase-phase voltage $U_s=410$ Vrms. The commutation inductance can be neglected.

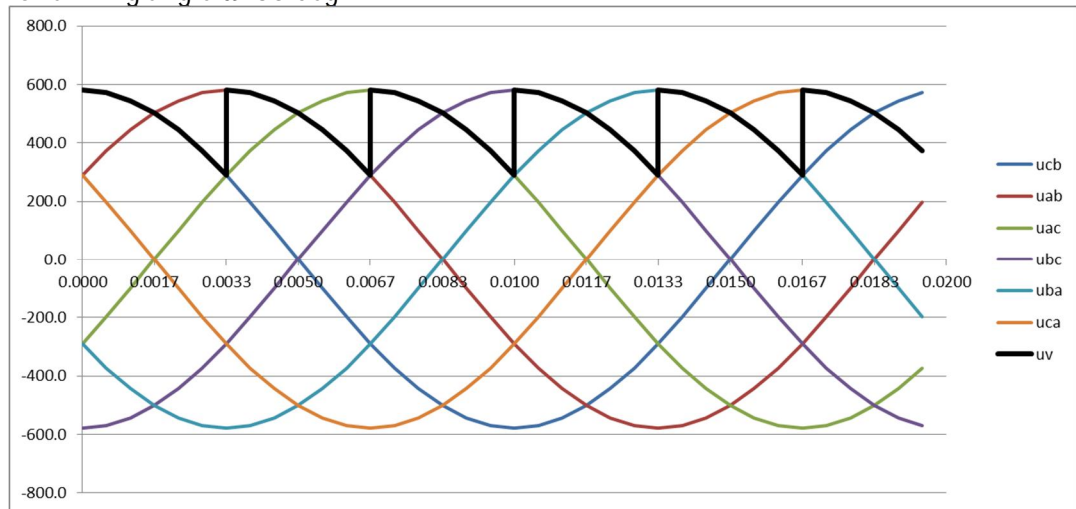- a) Draw the waveform of the converter dc-side voltage U_v (before the inductor L_d) for a firing angle $\alpha=30$ deg. (2)



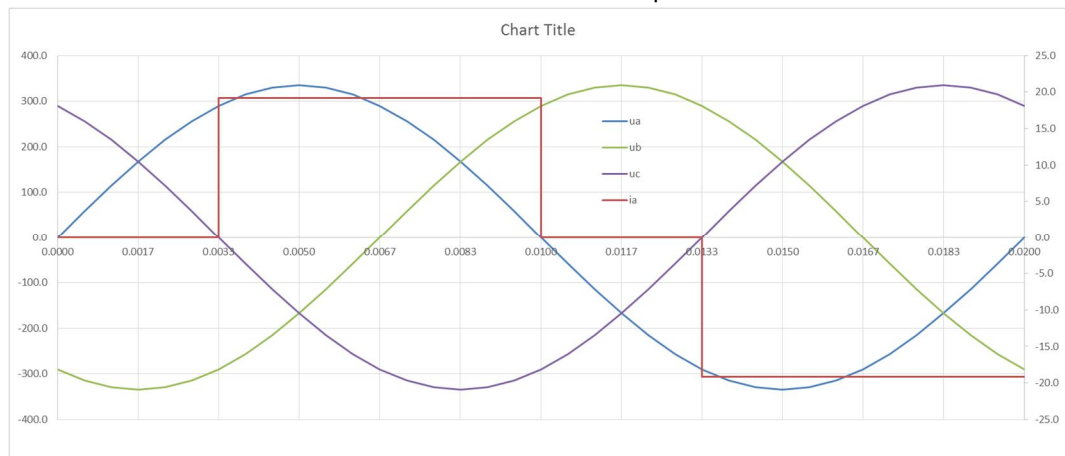- b) Draw the waveform of the source current, i_{sa} , in one phase. (2)



- c) Determine the displacement power factor.
 $DPF = \cos(\text{angle between ac-voltage and current}) = \cos(\alpha) = \cos(30)$
 $= 0.87$
- d) Calculate the dc-load voltage, U_d , and dc-power considering a resistive load of 25 ohm. (5)
- $U_d = 1.35 \cdot 410 \cdot \cos(30) = 479 \text{ V}$
 $I_d = 479 / 25 = 19.2 \text{ A}$
 $P_d = 479^2 / 25 = 9.2 \text{ kW}$ (3)
- e) Calculate the fundamental frequency source rms current (i_{s1}). Assume zero losses of the thyristor converter.
 $\sqrt{3} \cdot U_s \cdot I_{s1} \cdot DPF = P_d, \Rightarrow I_{s1} = 9200 / 410 / 0.87 / \sqrt{3} = 15 \text{ A},$
 $I_{s1} = 0.78 I_d$

Question 3

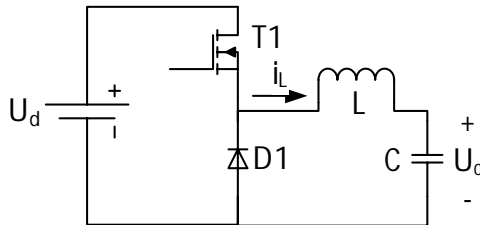


Figure 4

In the buck converter in Figure 4, the current i_L is continuous with an average of 5 A, and with a negligible ripple magnitude. The MOSFET T1 is operated with a switching frequency $f_{sw} = 120$ kHz and a duty cycle in order to keep the capacitor voltage $U_c = 10$ V for an input voltage $U_d = 24$ V.

- Determine the duty cycle of the MOSFET T1. (2)
 $D = 10/24 = 0.42$
- Calculate the conduction losses in the MOSFET T1 if the on-state resistance $R_{ds(on)} = 0.05$ ohm. (3)
 $P_C = D * R_{ds(on)} * i_L^2 = 0.417 * 0.05 * 25 = 0.52$ W
- Calculate the turn-on losses in the MOSFET T1 if the rise time of the drain current is 40 ns. Current rises linearly and voltage is constant. (3)
 $P_{on} = f_{sw} * E_{on} = f_{sw} * U_d * 0.5 t_r * i_L = 0.29$ W
- Calculate the turn-off losses in the MOSFET T1 if the fall time of the drain current is 60 ns. Current rises linearly and voltage is constant. (3)
 $P_{off} = f_{sw} * E_{off} = f_{sw} * U_d * 0.5 t_f * i_L = 0.43$ W
- Determine the maximum allowed thermal resistance of the heatsink (R_{thHA}) for the MOSFET T1 in order to keep the heatsink temperature, $T_H \leq 60$ °C and the junction temperature, $T_J \leq 100$ °C. The MOSFET has a thermal resistance $R_{thJH} = 45.0$ °C/W. The ambient temperature, $T_A = 25$ °C. Note: T_H or T_J will equal the given limits, the other shall be lower. (5)
 $P_{tot} = 1.24$ W. $R_{thHAm_{ax}} = (60 - 25) / 1.24 = 28$ °C/W. $R_{thJA_{max}} = (100 - 25) / 1.24 = 60$ °C/W. $R_{thHAm_{ax}} = 60 - 45 = 15$ °C/W.
 Consequently, the heatsink must have $R_{thHA} < 15$ °C/W. With $R_{thHA} = 15$ °C/W, $T_H = 25 + 1.24 * 15 = 44$ °C, $T_J = 44 + 1.24 * 45 = 99.4$ °C.

Question 4

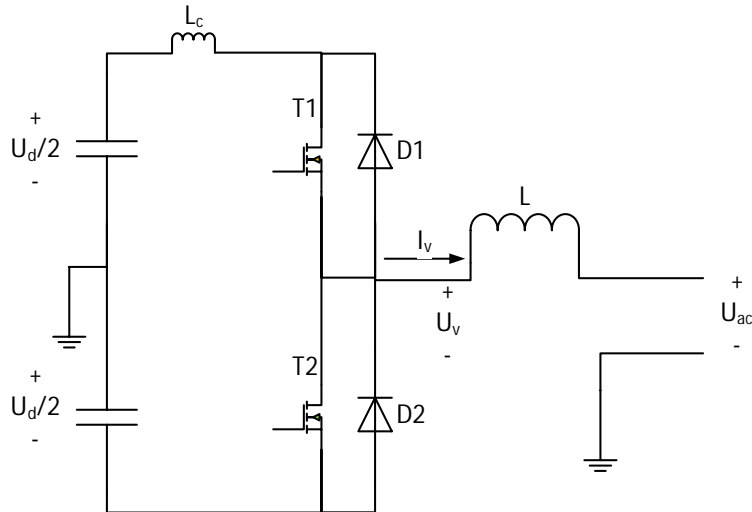


Figure 5

A half-bridge voltage source converter is connected between a dc-source and an ac-load as shown by Figure 5. The control of the switched output voltage is done through pulse width modulation (PWM) with a switching frequency $f_{sw}=950$ Hz, in order to obtain a 50 Hz voltage component with a defined magnitude.

- What is the minimum required dc-side voltage, U_d , required if the magnitude of the 50 Hz voltage component shall be 24V rms when the amplitude modulation ratio, $m_a=0.9$. (5)
- $$U_{vpk}=m_a \cdot U_d/2, \Rightarrow U_d=2 \cdot U_{vpk}/m_a=2 \cdot \sqrt{2} \cdot 24/0.9=75.4 \text{ V} \quad (5)$$
- Calculate the current ripple in the output current, I_v , during the time interval shown in Figure 6. The time is defined based on the switching frequency cycle, $T_{sw}=1/f_{sw}$. During this time interval $U_{ac} = 0.4 \cdot U_d$, for the value of U_d calculated in a). The inductance $L=3$ mH. The initial current $I_v(t=0)=0$.


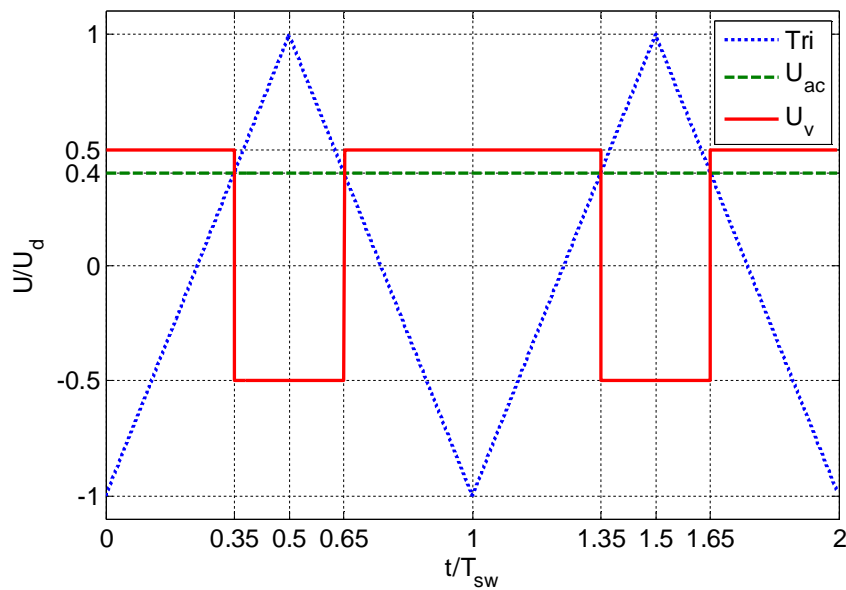


Figure 6

The voltage drop across the inductance L defines the current ripple. $\Delta i_v = \frac{u_L}{L} \Delta t$. The current ripple can be calculated from one time instant to the next, building the waveform. Starting from t_0 we calculate the current at t_1 as: $i_v(t_1) = i_v(t_0) + \Delta i_v(t_1 - t_0) = i_v(t_0) + \frac{(u_v - u_{ac})(t_1 - t_0)}{L}$. The time instants are defined by Figure 6, where time is given relative the switching cycle T_{sw} . The time in seconds is calculated by the relative value divided by f_{sw} . Discrete time and current values are given below the figure.

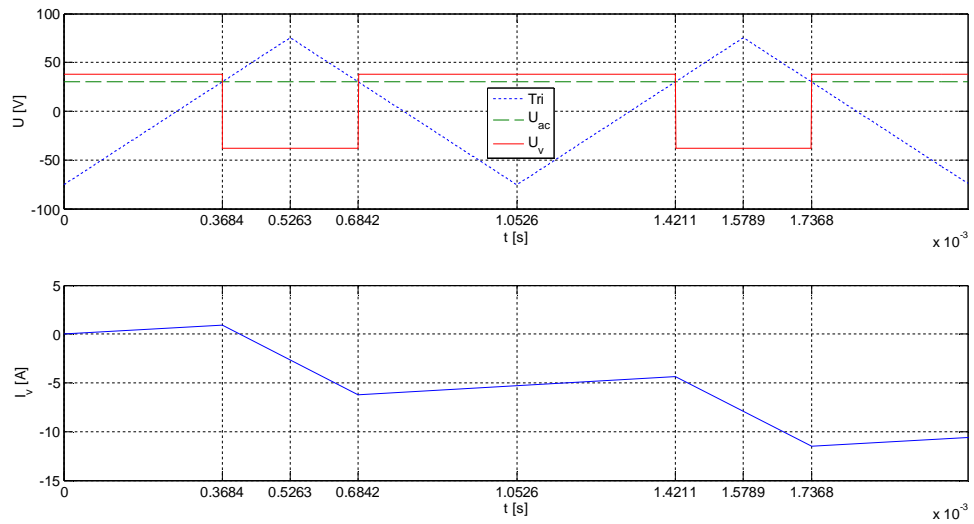

	t0	t1	t2	t3	t4	t5
t [s]	0.0	0.37e-3	0.68e-3	1.42e-3	1.74e-3	2.10e-3
Iv [A]	0.0	0.926	-6.2	-4.4	-11.5	-10.6

Question 5

The half-bridge converter in Figure 5 has a parasitic inductance, L_c , between the dc-source and the half-bridge. Figure 7 the switching waveform of the current through the MOSFET switch T1. The current $I_v=12$ A flows through L out of the converter.

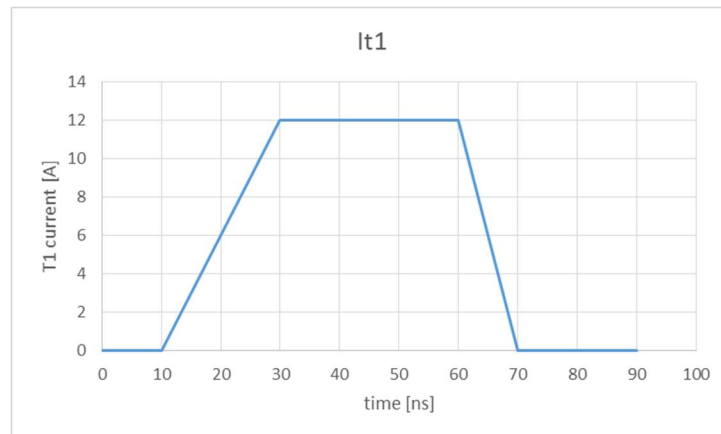


Figure 7

- a) Draw the waveform of the voltage across MOSFET T1, related to the current given in Figure 7 and considering the inductance $L_c=40$ nH. The dc-voltage $U_d=110$ V. (4)


The voltage drop of the inductor at turn-on: $U_{L_{on}} = L_c \cdot dt1/dt = 40e-9 \cdot 12 / (20e-9) = 24$ V.

The MOSFET voltage at turn-on: $U_{t1} = 110 - U_{L_{on}} = 86$ V.

The voltage drop of the inductor at turn-off: $U_{L_{off}} = L_c \cdot dt1/dt = -40e-9 \cdot 12 / (10e-9) = -48$ V.

The MOSFET voltage at turn-off: $U_{t1} = 110 - U_{L_{off}} = 110 + 48 = 158$ V.

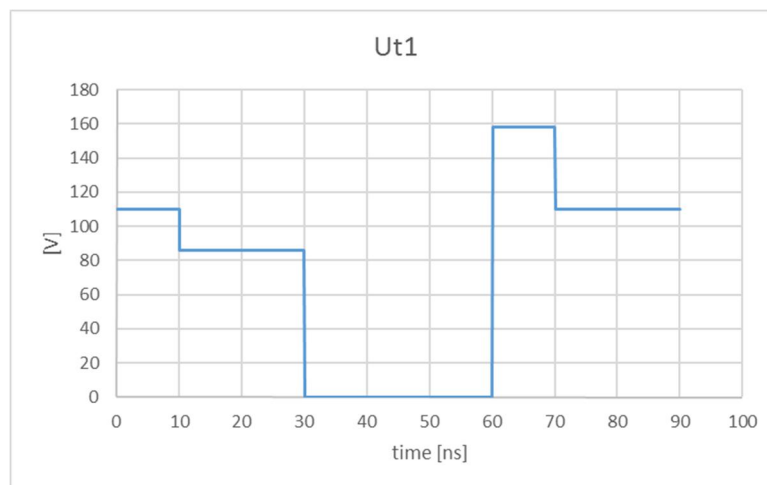The MOSFET voltage at turn-off: $U_{t1} = 110 - U_{L_{off}} = 110 + 48 = 158$ V.



- b) What is the peak voltage across the MOSFET? (4)

$$U_{t1pk} = U_d - L_c \cdot dt1/dt = 110 - 40e-9 \cdot (0-12) / (10e-9) = 158 \text{ V}$$

Question 6

A parallel capacitive snubber shall be designed for limitation of the peak voltage across the MOSFET switches of a half-bridge converter. The snubber, as shown by Figure 8, consists of a diode D_s , which will charge the snubber capacitor C_s during over-voltage but prevent discharge when the MOSFET turns on. The dc-side voltage $U_d=110$ V. The design shall be based on the switching conditions related to a load current $I_v = 12$ A.


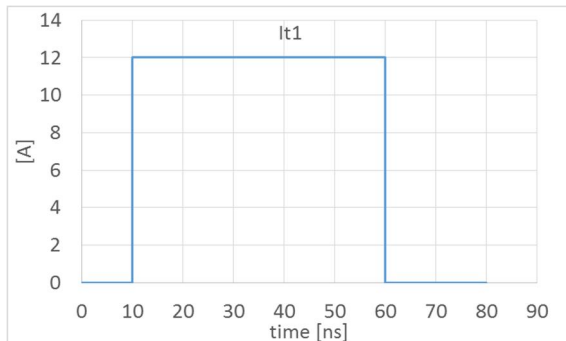
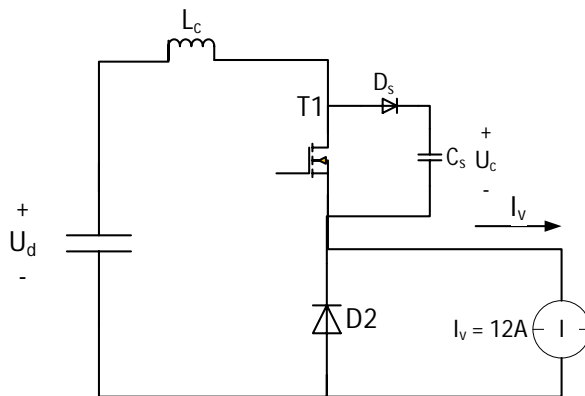


Figure 8

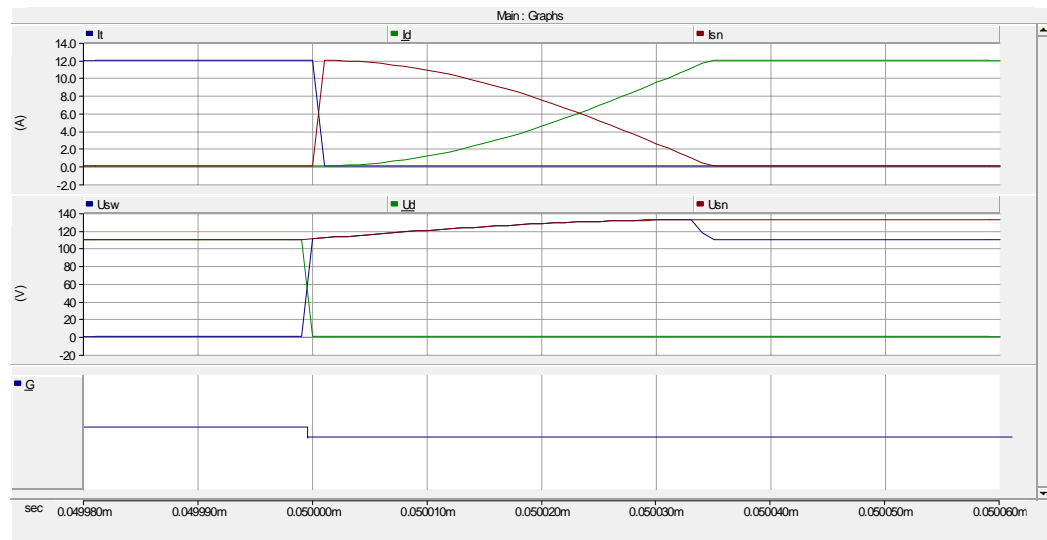- a) Draw the waveforms of the current and voltage related to T1, D2 and C_s . Assume the T1 current turn-off to be instantaneous as shown above. The snubber capacitor is initially charged to $U_c = U_d$ at the instant of T1 turn-off. (4)



- b) Calculate the required snubber capacitance in order to limit the over voltage to 20% when T1 is turned off. (6)


Stored energy in the inductance L_c : $W_L = 0.5 \cdot L_c \cdot I_v^2$. All stored inductor energy will be transferred to the snubber capacitor, giving a voltage increase defined by the capacitor energy relation:

$$W_C = 0.5 \cdot C_s \cdot \Delta U_c^2. W_C = W_{CL} \Rightarrow \Delta U_c = I_v \cdot \sqrt{L_c / C_s}$$

Selecting C_s^* to limit $U_c = 1.2 U_d$ yields: $C_s = L_c \cdot$

$$I_v / \Delta U_c)^2 = 40 \cdot (12 / (0.2 \cdot 110))^2 = 11.9 \text{ nF.}$$

Another way of addressing it is to consider the LC circuit below, where at the instant of T1 turn-off, the inductor carries the current 12 A. The capacitor C_s is initially charged to U_d . The current through the LC circuit will be a quarter-wave of a sinusoidal oscillation with a frequency defined by the series resonance $\omega = \frac{1}{\sqrt{LC}}$. The current starts at its peak value and drops towards zero, following a cosine function. At $i_L = 0$, the diode blocks the current after a quarter of a cycle.

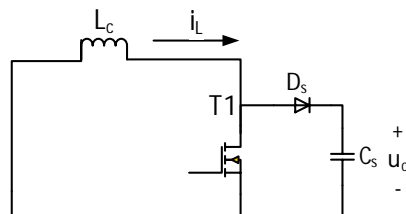

The current and voltage will be defined by the following equations:

$$i_c = i_{L0} \cos \omega t$$

$$u_c = U_d + \frac{1}{C} \int_0^{T/4} i_c dt = U_d + \frac{i_{L0}}{\omega C} \int_0^{\pi/2} \cos \omega t d\omega t = U_d + i_{L0} \sqrt{\frac{L}{C}}$$

Consequently, limiting $u_c = 1.2U_d$ gives the following expression for the snubber capacitance: $C = L \frac{i_{L0}^2}{(0.2U_d)^2}$

Formula collection TSTE19 Power Electronics

Fourier series coefficients using symmetry,

Even	$f(-t) = f(t)$	$b_h = 0$	$a_h = \frac{2}{\pi} \int_0^\pi f(t) \cos(h\omega t) d(\omega t)$
Odd	$f(-t) = -f(t)$	$a_h = 0$	$b_h = \frac{2}{\pi} \int_0^\pi f(t) \sin(h\omega t) d(\omega t)$
Half-wave	$f(t) = -f(t + \frac{1}{2}T)$	$a_h = b_h = 0$ for even h	$a_h = \frac{2}{\pi} \int_0^\pi f(t) \cos(h\omega t) d(\omega t)$ for odd h $b_h = \frac{2}{\pi} \int_0^\pi f(t) \sin(h\omega t) d(\omega t)$ for odd h
Even quart-wave	Even and half-wave	$b_h = 0$ for all h	$a_h = \frac{4}{\pi} \int_0^{\frac{\pi}{2}} f(t) \cos(h\omega t) d(\omega t)$ for odd h , $a_h = 0$ for even h
Odd quarter-wave	Odd and half-wave	$a_h = 0$ for all h	$b_h = \frac{4}{\pi} \int_0^{\frac{\pi}{2}} f(t) \sin(h\omega t) d(\omega t)$ for odd h , $b_h = 0$ for even h

Undamped resonant circuits

Even	$f(-t) = f(t)$	$b_h = 0$	$a_h = \frac{2}{\pi} \int_0^\pi f(t) \cos(h\omega t) d(\omega t)$
Odd	$f(-t) = -f(t)$	$a_h = 0$	$b_h = \frac{2}{\pi} \int_0^\pi f(t) \sin(h\omega t) d(\omega t)$
Half-wave	$f(t) = -f(t + \frac{1}{2}T)$	$a_h = b_h = 0$ for even h	$a_h = \frac{2}{\pi} \int_0^\pi f(t) \cos(h\omega t) d(\omega t)$ for odd h $b_h = \frac{2}{\pi} \int_0^\pi f(t) \sin(h\omega t) d(\omega t)$ for odd h
Even quart-wave	Even and half-wave	$b_h = 0$ for all h	$a_h = \frac{4}{\pi} \int_0^{\frac{\pi}{2}} f(t) \cos(h\omega t) d(\omega t)$ for odd h , $a_h = 0$ for even h
Odd quarter-wave	Odd and half-wave	$a_h = 0$ for all h	$b_h = \frac{4}{\pi} \int_0^{\frac{\pi}{2}} f(t) \sin(h\omega t) d(\omega t)$ for odd h , $b_h = 0$ for even h

Integration rules

$$\int_a^b f(x) dx = \int_A^B f(g(t)) g'(t) dt \text{ if } a = g(A), b = g(B) \text{ and } g \text{ is monotone in } [A, B]$$

$$\int_a^b \sin(x) dx = [-\cos(x)]_a^b$$

$$\int_a^b \cos(x) dx = [\sin(x)]_a^b$$