 



Digital ICs — Lectures

1) Introduction [Ch. 1]	TSEI03/TSTE86
2) Devices [Ch. 3, 4]	TSEI03/TSTE86
3) Interconnect [Ch. 4, 9]	TSTE86
4) Circuits [Ch. 5]	TSEI03/TSTE86
5) Combinational logic [Ch. 6]	TSEI03/TSTE86
6) Sequential circuits [Ch. 7]	TSEI03/TSTE86
7) Synchronization [Ch. 10]	TSTE86
8) Adders [Ch. 11]	TSEI03/TSTE86
9) Multipliers [Ch. 11]	TSTE86
10) Memory [Ch. 12]	TSEI03/TSTE86
11) Manufacturing [Ch. 2]	TSTE86
12) System design [Ch. 8]	TSTE86


On-Chip Noise



Inductive coupling


 


Capacitive coupling

 

Power and ground noise



Noise Margins

  


Noise margin high:
 $NM_H = V_{OH} - V_{IH}$

Noise margin low:
 $NM_L = V_{IL} - V_{OL}$

CMOS Inverter

  


Wire Resistance

 


$$R = \frac{\rho L}{HW}$$

Sheet Resistance
 R_0

 


Resistance of the MOSFET Channel

 


Example : assuming velocity saturation in range $V_{DD} \geq V_{DS} \geq \frac{V_{DD}}{2} \Rightarrow R_{on} = \frac{1}{2} \left(\frac{V_{DD}}{I_{DSAT}} + \frac{V_{DD}/2}{I_{DSAT}} \right) = \frac{3}{4} \cdot \frac{V_{DD}}{I_{DSAT}}$

Parallel Plate Capacitance

 

$$C_{pp} = \epsilon_{di} \frac{WL}{t_{di}} = C_{area} WL$$


Fringing Capacitance

 


Total wire capacitance:

$$C_{wire} = C_{pp} + C_f = C_{area}WL + 2C_{edge}L$$


Interconnect

 


Capacitive Load

 


Simplified Model

 


Parasitic MOSFET Capacitances

 


Gate Capacitance

 

Cut-off

 


Resistive

 

Saturation

Operation Region	C_{gb}	C_{gs}	C_{gd}
Cutoff	$C_{ox}WL_{eff}$	0	0
Triode	0	$C_{ox}WL_{eff}/2$	$C_{ox}WL_{eff}/2$
Saturation	0	$(2/3)C_{ox}WL_{eff}$	0

Diffusion Capacitance

 

$$\begin{aligned} C_{diff} &= C_{bottom} + C_{sw} = C_j \times AREA + C_{jsw} \times PERIMETER \\ &= C_j L_S W + C_{jsw} (2L_S + W) \end{aligned}$$


Linearizing the Junction Capacitance

Replace non-linear capacitance by
large-signal equivalent linear capacitance

$$C_{eq} = \frac{\Delta Q_j}{\Delta V_D} = \frac{Q_j(V_{high}) - Q_j(V_{low})}{V_{high} - V_{low}} = K_{eq} C_{j0}$$

$$K_{eq} = \frac{-\phi_0^m}{(V_{high} - V_{low})(1 - m)} [(\phi_0 - V_{high})^{1-m} - (\phi_0 - V_{low})^{1-m}]$$

Propagation Delay

 


Method 1: estimate average R_{DS}

$$t_{pHL} \approx 0.69 R_{DS} C_{out} \approx 0.69 \frac{R_{DS}(V_{DD}) + R_{DS}(V_{DD}/2)}{2} C_{out}$$

Method 2: estimate average I_D

$$t_{pHL} \approx \Delta Q / I_D \approx \frac{C_{out} V_{DD} - C_{out} V_{DD}/2}{[I_D(V_{DD}) + I_D(V_{DD}/2)]/2}$$

Power Dissipation

 

Energy and Energy-Delay

Power-Delay Product (PDP) =

$$E = \text{energy per operation} = P_{av} \times t_p$$

Energy-Delay Product (EDP) =

$$\text{quality metric of gate} = E \times t_p$$