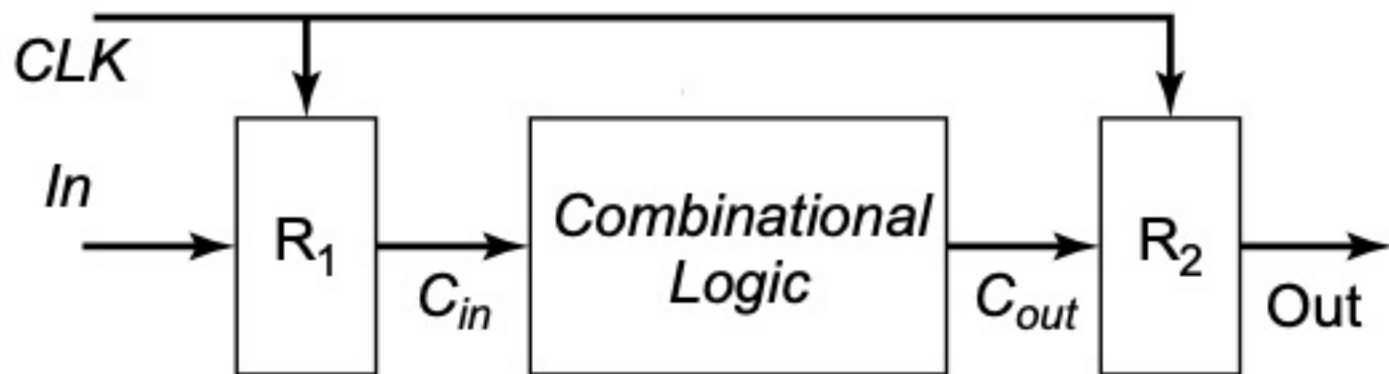


Digital ICs — Lectures

1) Introduction [Ch. 1]	TSEI03/TSTE86
2) Devices [Ch. 3, 4]	TSEI03/TSTE86
3) Interconnect [Ch. 4, 9]	TSTE86
4) Circuits [Ch. 5]	TSEI03/TSTE86
5) Combinational logic [Ch. 6]	TSEI03/TSTE86
6) Sequential circuits [Ch. 7]	TSEI03/TSTE86
7) Synchronization [Ch. 10]	TSTE86
8) Adders [Ch. 11]	TSEI03/TSTE86
9) Multipliers [Ch. 11]	TSTE86
10) Memory [Ch. 12]	TSEI03/TSTE86
11) Manufacturing [Ch. 2]	TSTE86
12) System design [Ch. 8]	TSTE86

Synchronous System




Timing parameters

$t_{c-q,cd} \dots t_{c-q}$

t_{su}, t_{hold}


$t_{logic,cd} \dots t_{logic}$

Clock Uncertainties

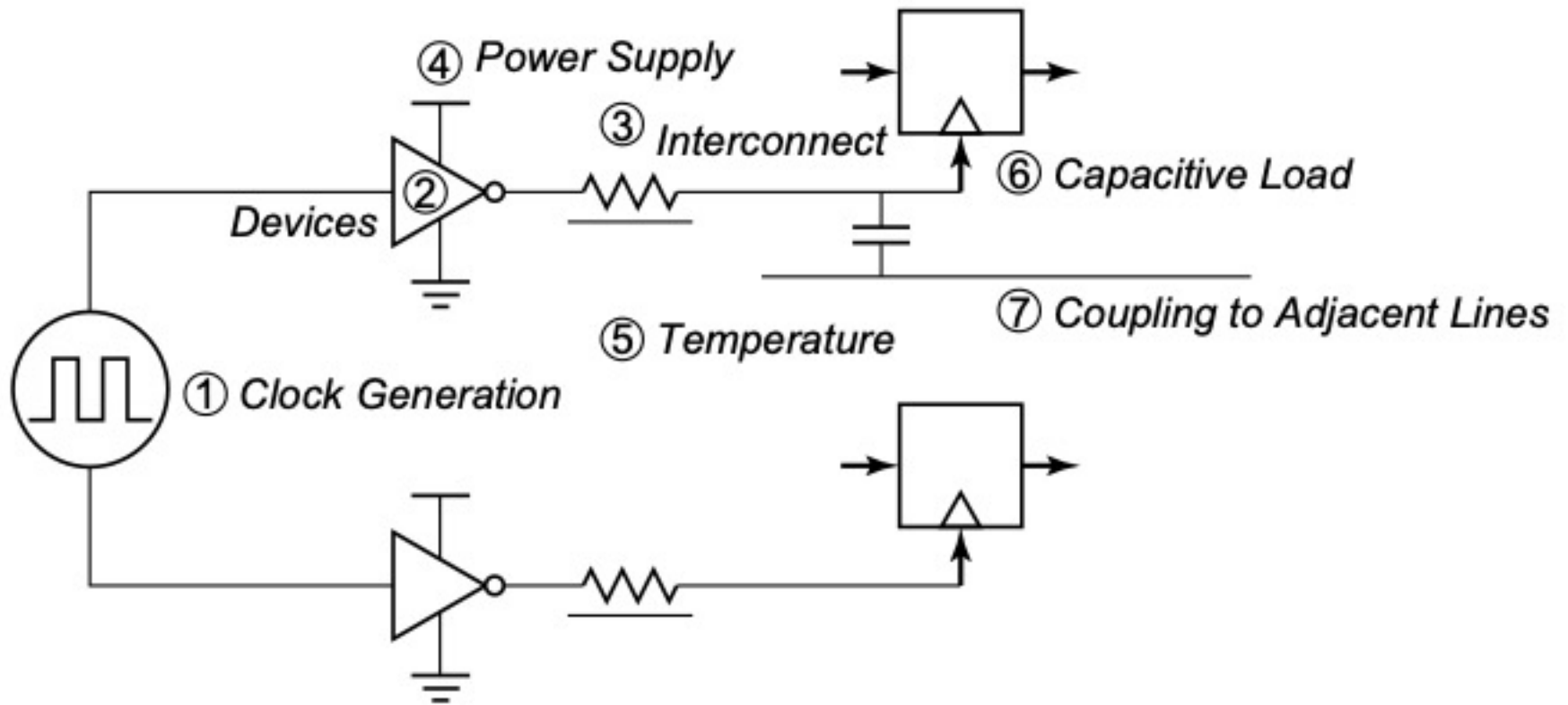


Sources of clock uncertainty


Clock Skew

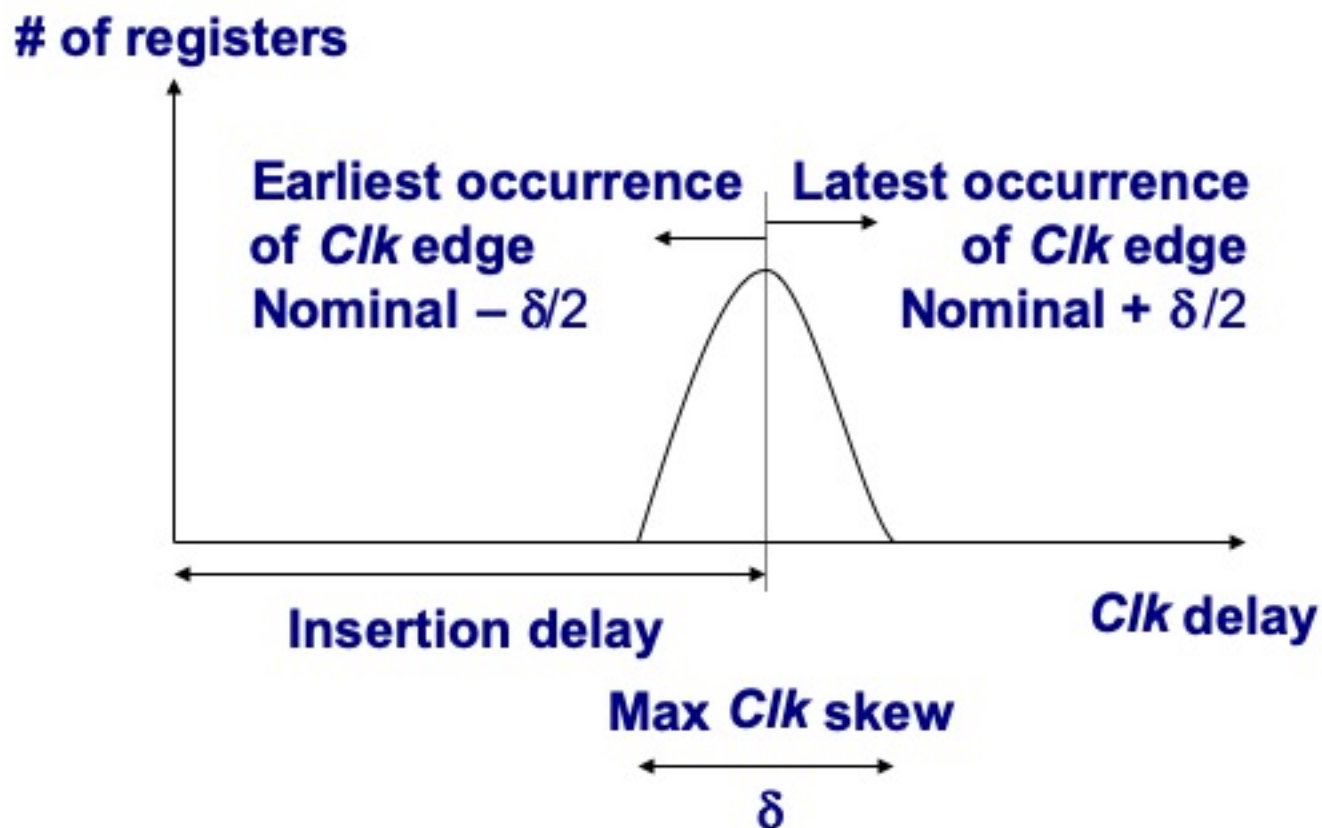

Clock Skew

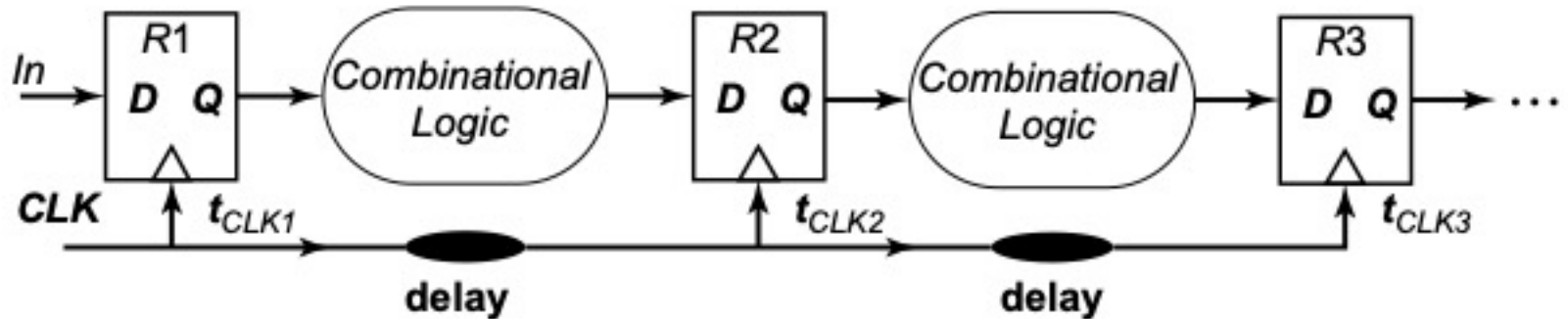


(a) Positive skew

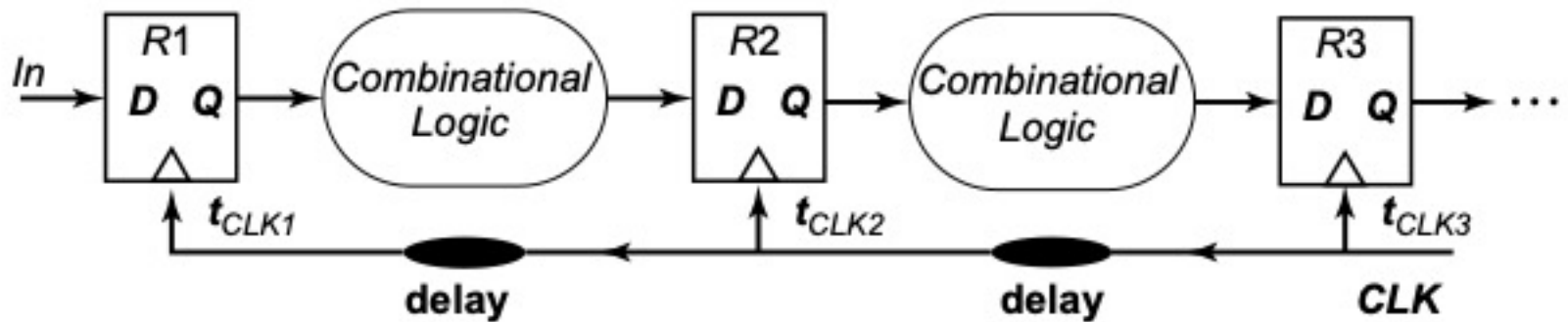



(b) Negative skew

Positive and Negative Skew

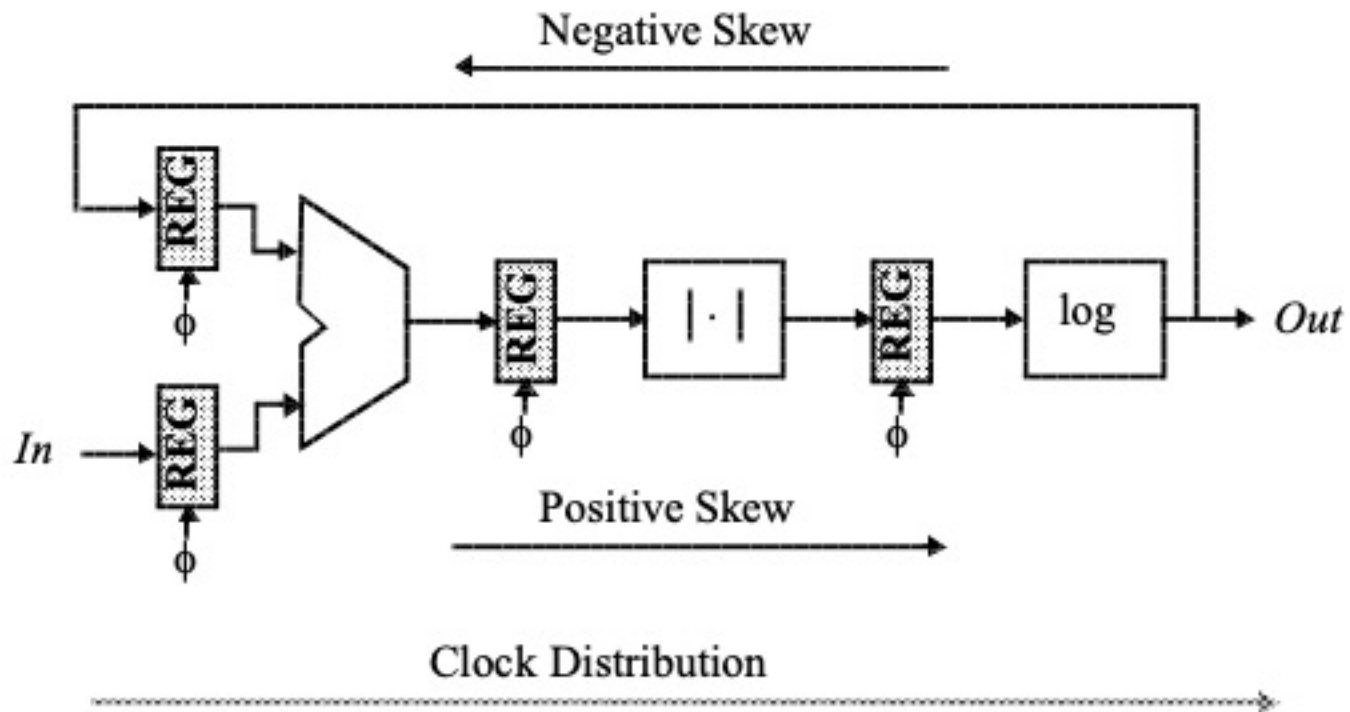


Data and Clock Routing


Register Parameters

  

Longest Path

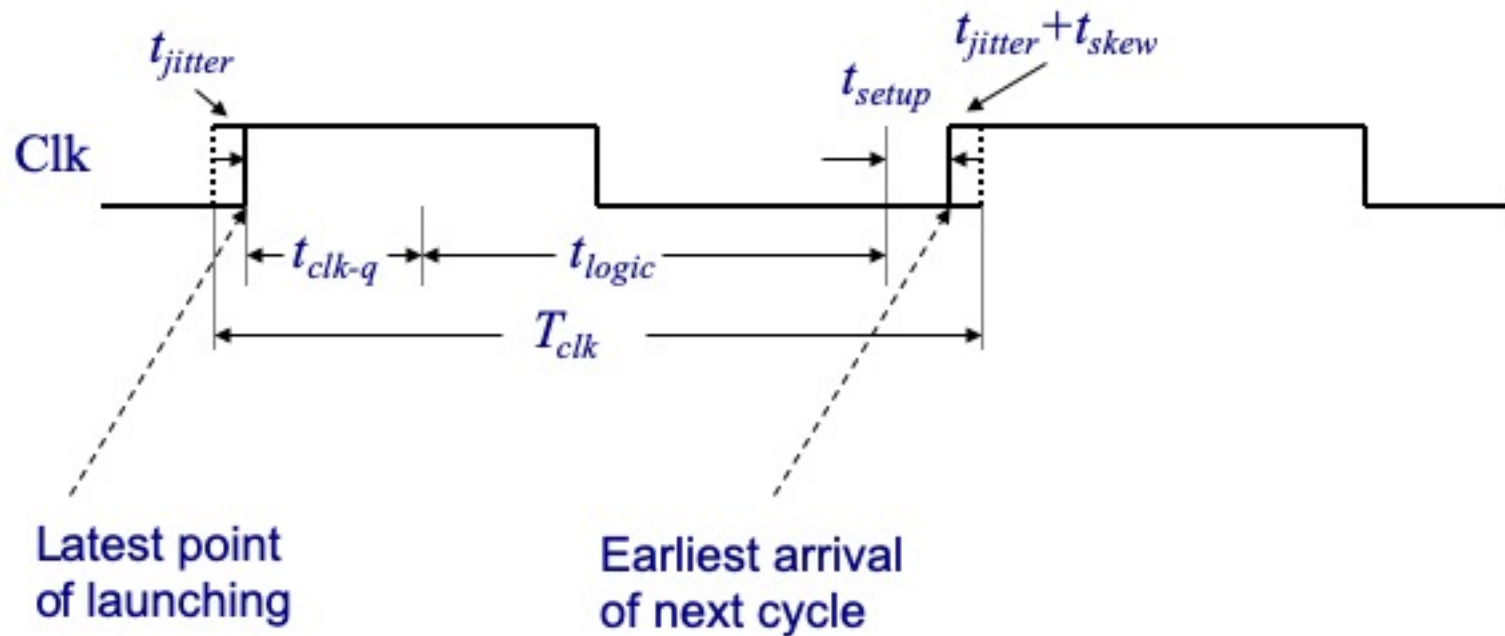


Shortest Path

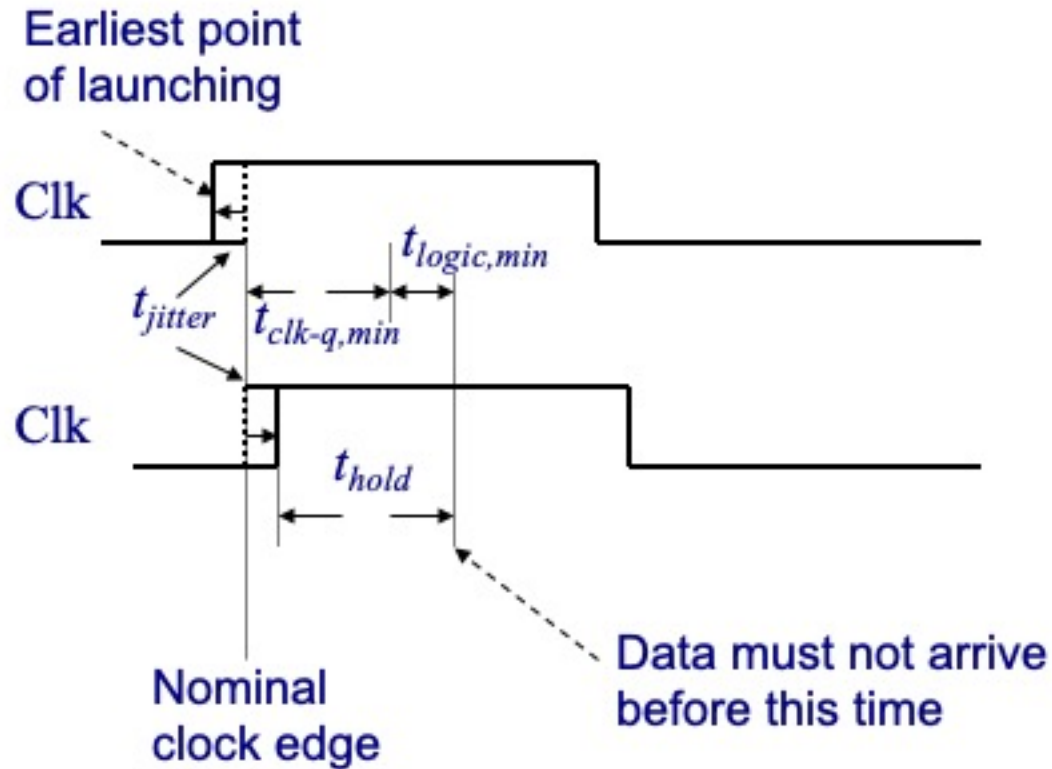


Clock Generation


Delay-Locked Loop (Delay Line Based)

 

Phase-Locked Loop (VCO-Based)

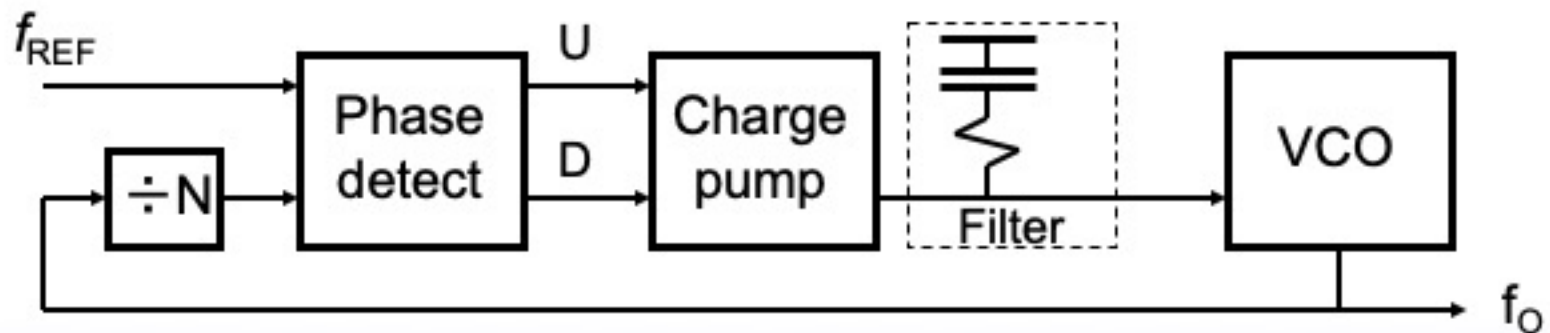


Clock Grid

 



- Low skew
- No RC matching
- Huge power

RC-matched H-tree

 

[Restle98]

Tuning Tree with Wire Width

  


[Restle01]


Example: DEC Alpha 21164




Clock waveform

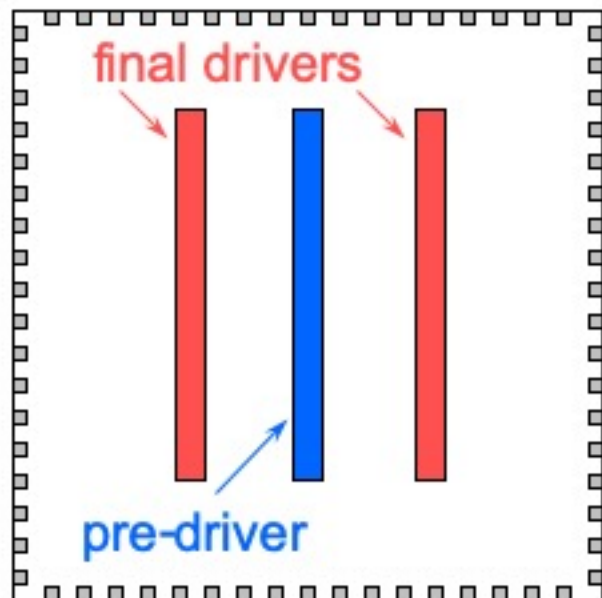




Clock driver

 


Clock Skew

 

Example: DEC Alpha 21264

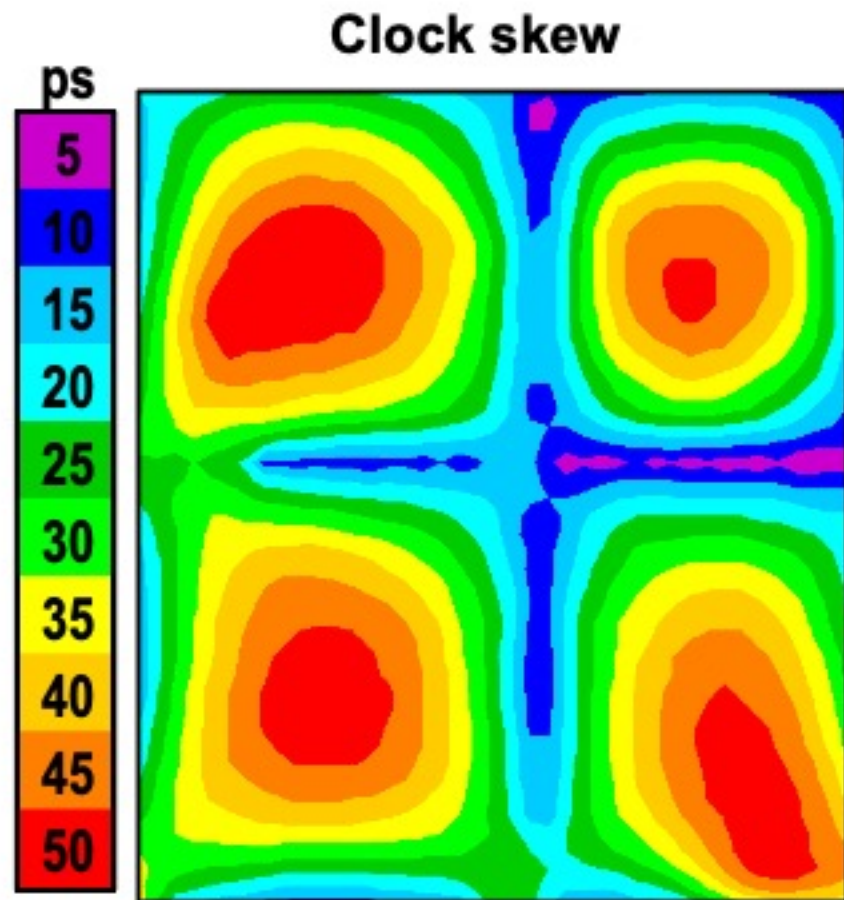  


21264 Clocking

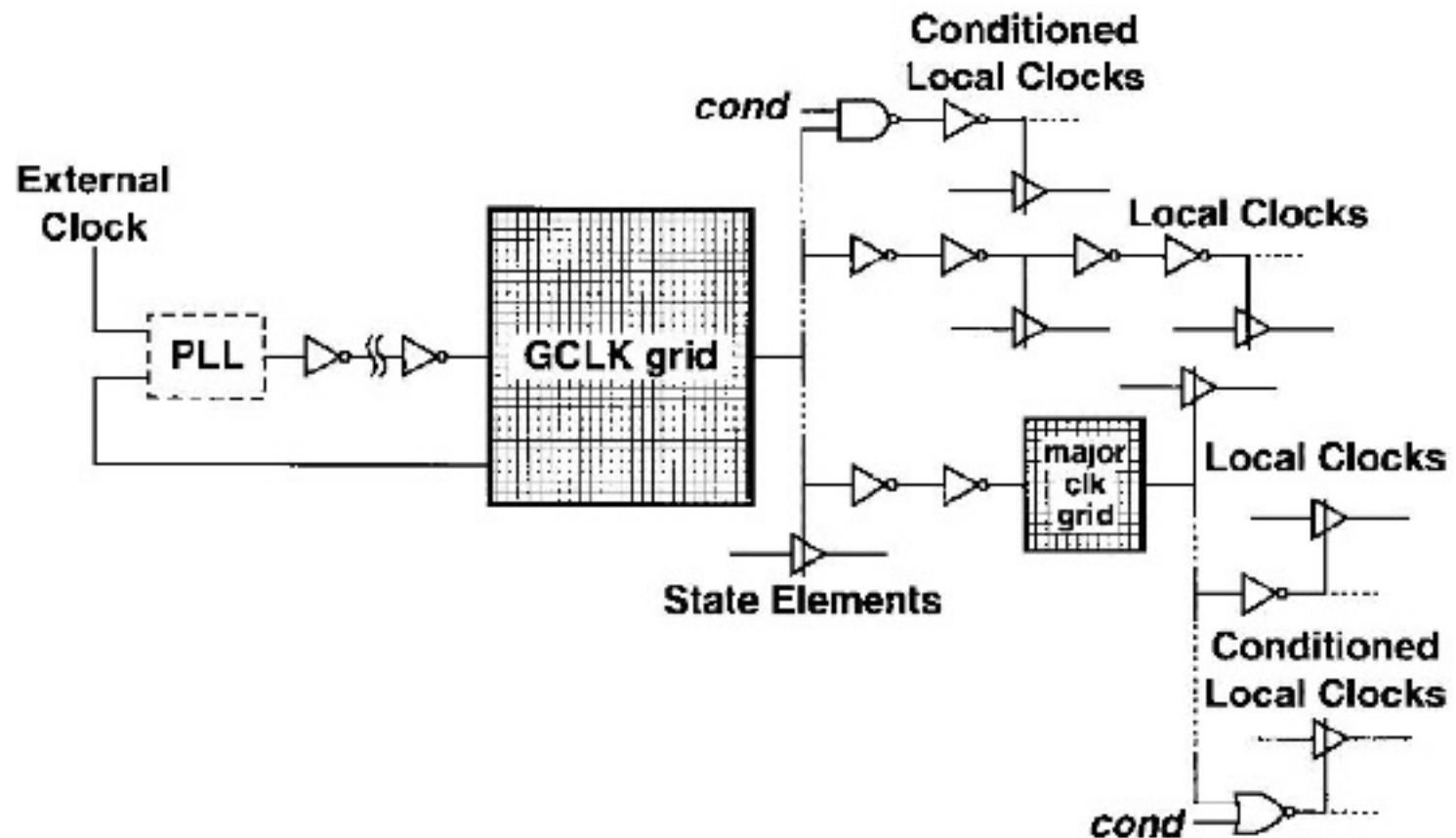





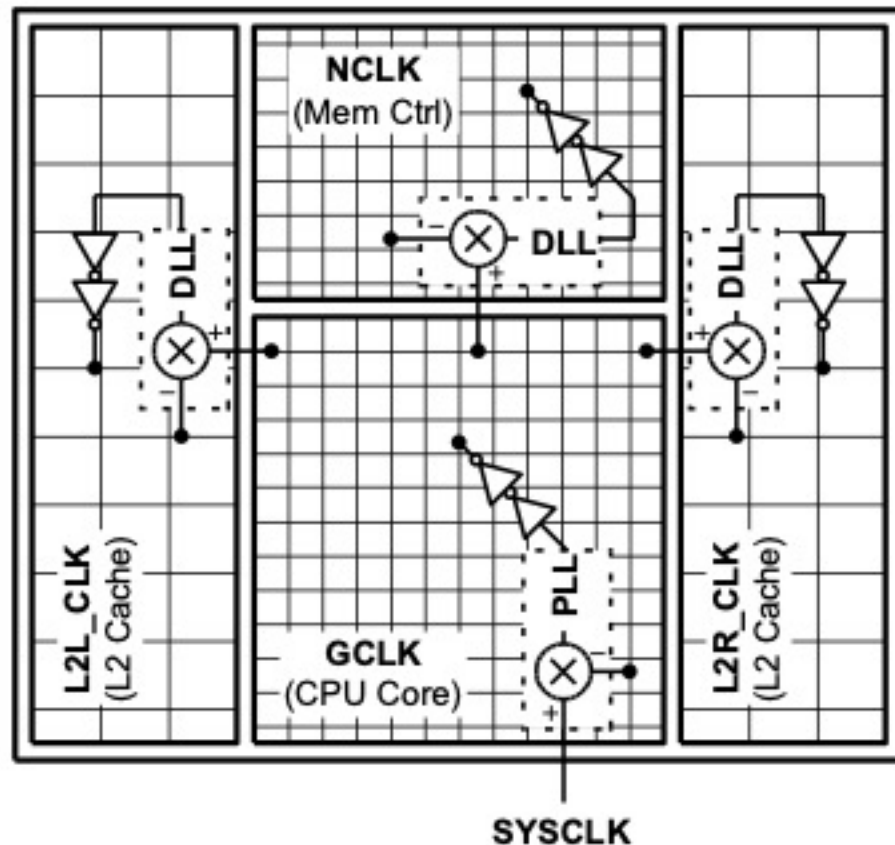




Example: DEC Alpha 21364

Active Skew Management and Multiple Clock Domains




- + widely dispersed drivers
- + DLLs compensate static and low-frequency variation
- + divides design and verification effort
- DLL design and verification is added work
- + tailored clocks


CMOS Process Layers

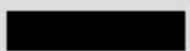Layer	Color	Representation
Well (p,n)	Yellow	
Active Area (n+,p+)	Green	
Select (p+,n+)	Green	
Polysilicon	Red	
Metal1	Blue	
Metal2	Magenta	
Contact To Poly	Black	
Contact To Diffusion	Black	
Via	Black	



Intra-Layer Design Rules

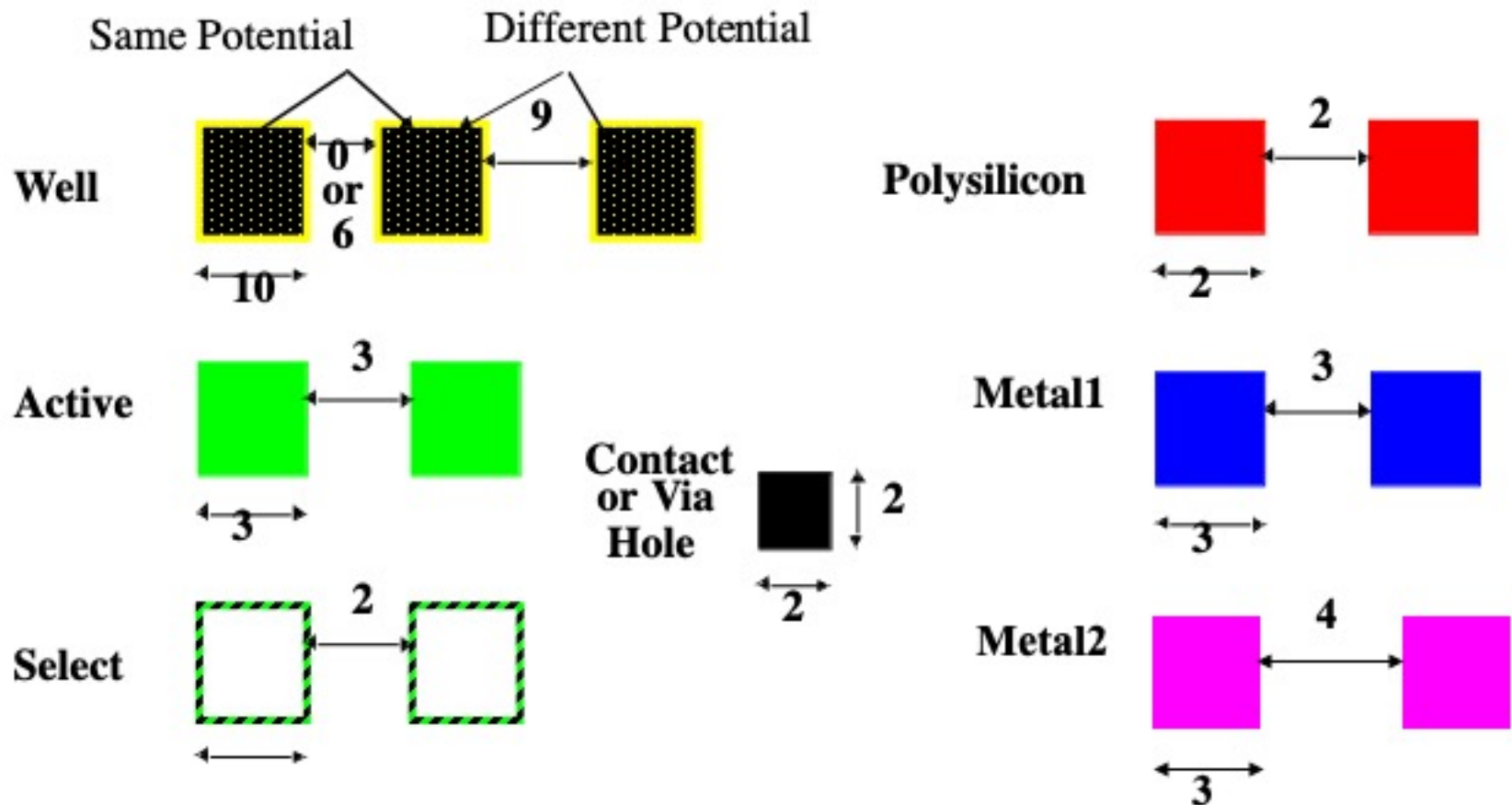

Inter-Layer Design Rules

 

Common Euler Paths

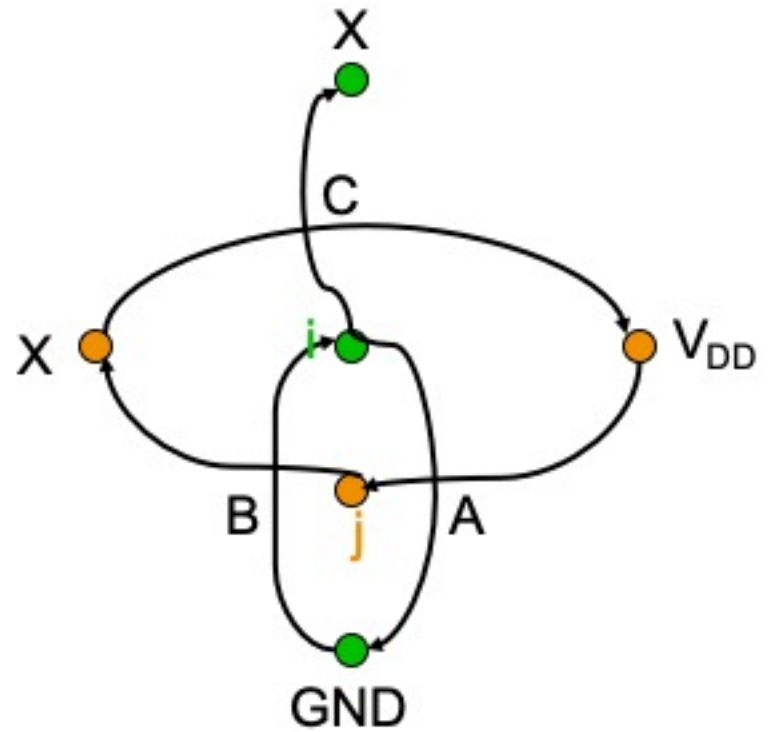 

Common Euler paths:
A-B-C

