

## TSTE86 Homework 4: Interconnection

Consider a clock driver connected with a metal wire as shown in Figure 1. The wire has width  $W = 0.5 \mu\text{m}$ , sheet resistance  $r_w = 75\text{m}\Omega/\text{sq}$ , area capacitance  $c_a = 30 \text{ aF}/(\mu\text{m})^2$ , and fringe capacitance  $c_f = 40 \text{ aF}/\mu\text{m}$ .

 


Figure 1. Clock driver loaded by metal wire.

- Model the entire circuit. The driver is modeled with a voltage source  $V_{\text{in}}$ , a series resistor  $R_S$ , and a capacitor  $C_S$  to ground. The distributed wire is modeled with a lumped RC network (e.g.  $\pi$  model).
- Use the Elmore model to find the wire length if the propagation delay in this circuit is twice the inherent propagation delay of the driver (delay without any load). Assume  $R_S = 7.25 \text{ k}\Omega$  and  $C_S = 6 \text{ fF}$ .
- What is the propagation delay of this circuit and what is the wire contribution in this case?
- Assume the propagation delay of the wire is the same as the propagation delay of the driver when loaded by such a wire. Find the wire length and the propagation delay of this circuit.