

Exam TEN1 in TSTE86 Digital Integrated Circuits

Time: Monday 22 October 2018, 14:00—18:00

Place: G32, G33, G34

Responsible teacher: Mark Vesterbacka, phone 013-281324

Allowed aid: Calculator

Max score: 60 points

Grades:
45 points for 5
35 points for 4
25 points for 3

Solutions: Posted on the course web

Results: Posted through LADOK by 7 November 2018

1. The function $F = AB + AC$ shall be implemented in static CMOS logic. The complements to A, B, C are *not* available.
 - a) Implement the function with at most eight transistors. (5 p)
 - b) Size all transistors so that the worst-case output resistance is the same as that of an inverter with an PMOS $W/L = 4$ and NMOS $W/L = 3$. (5 p)

2. A pseudo-NMOS inverter designed in $0.25 \mu\text{m}$ CMOS technology is shown in Figure 1. The supply voltage is 2.5 V and the output load is 100 fF . Channel length modulation may be neglected.

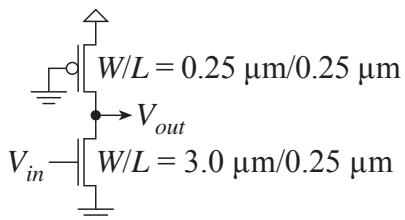


Figure 1. Pseudo-NMOS inverter.

3. The circuit in Figure 2 is supposed to realize the function $F(A, B, C) = A + BC$. However, the circuit does not work as intended.
 - a) Calculate the output voltage levels V_{OL} and V_{OH} . (5 p)
 - b) Estimate t_p . (5 p)

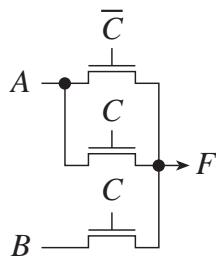


Figure 2. A faulty logic circuit.

3. The circuit in Figure 2 is supposed to realize the function $F(A, B, C) = A + BC$. However, the circuit does not work as intended.
 - a) What type of logic has been used in this realization? (2 p)
 - b) What is the problem with this circuit? (2 p)
 - c) Redesign the gate so that the wanted function $F(A, B, C)$ is realized correctly. (6 p)

4. Consider a *static random-access memory* (SRAM) with full-VDD precharge of the bit-lines and sense amplifiers connected to the bit-lines.
- Draw the transistor schematic of a six-transistor CMOS SRAM cell. (3 p)
 - Describe a write operation of the SRAM cell. (2 p)
 - Describe a read operation of the SRAM cell. (2 p)
 - Briefly discuss considerations in sizing the cell's MOSFETs. (3 p)

5. A pipelined datapath is shown in Figure 3. A register in the pipeline has the clock-to-output delay $t_{c-q} = 0.7$ ns, the set-up time $t_{su} = 0.5$ ns, and the hold time $t_{hold} = 0.4$ ns.


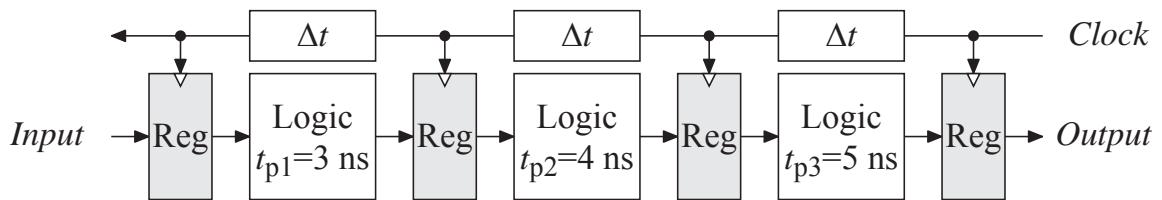


Figure 3. Pipelined datapath.

- What is the advantage of pipelining and what is the limitation of dividing a datapath into many pipelined stages? (3 p)
- What is the maximum throughput of the datapath if there is no clock skew, i.e. $\Delta t = 0$, and no clock jitter? (3 p)
- What is the minimum clock period of the datapath if there is a delay $\Delta t = 0.3$ ns between the registers and a clock jitter of at most 0.1 ns? (4 p)

6. Describe the steps of the semicustom design flow below with one or two sentences per step.
- Logic synthesis. (2 p)
 - Floor planning. (2 p)
 - Placement. (2 p)
 - Routing. (2 p)
 - Tape out. (2 p)

Equations for the MOS transistor

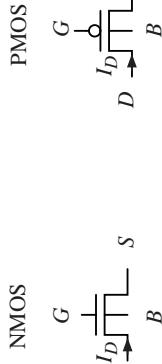

Definition of source (S) and drain (D)

NMOS: $V_S \leq V_D$
PMOS: $V_S \geq V_D$

Voltage notations

$V_{GS} = V_G - V_S$, $V_{DS} = V_D - V_S$, $V_{SB} = V_S - V_B$, $V_{GT} = V_{GS} - V_T$

Threshold voltage

$$V_T = V_{T0} + \gamma \left(\sqrt{|V_{SB} - 2\Phi_F|} - \sqrt{2|\Phi_F|} \right)$$

Unified model

NMOS: $V_{GT} \leq 0$ (PMOS: $V_{GT} \geq 0$) \Rightarrow Subthreshold region ($I_D \approx 0$)

$$\text{NMOS: } V_{GT} \geq 0 \text{ (PMOS: } V_{GT} \leq 0 \text{)} \Rightarrow I_D = k' \frac{W}{L} V_{min} \left(|V_{GT}| - \frac{V_{min}}{2} \right) (1 + \lambda V_{DS})$$

$$V_{min} = \min(|V_{GT}|, |V_{DS}|, |V_{DSAT}|)$$

$$V_{min} = |V_{GT}| \Rightarrow \text{saturation region}$$

$$V_{min} = |V_{DS}| \Rightarrow \text{resistive (linear, triode) region } (\lambda = 0)$$

$$V_{min} = |V_{DSAT}| \Rightarrow \text{velocity saturation region}$$

V_{DSAT} dependency on channel length

$$V_{DSAT} = L \xi_c$$

Subthreshold region

$$\text{NMOS: } V_{GT} \leq 0 \Rightarrow I_{Dn} = I_{D0} \frac{W}{L} e^{\frac{q(V_{GSn} - V_{Tn})}{nkT}} \left(1 - e^{-\frac{qV_{DSn}}{kT}} \right) (1 + \lambda_n V_{DSn})$$

$$\text{PMOS: } V_{GT} \geq 0 \Rightarrow I_{Dp} = I_{D0p} \frac{W}{L} e^{\frac{q(V_{SGp} - |V_{Tp}|)}{nkT}} \left(1 - e^{-\frac{qV_{DSp}}{kT}} \right) (1 + \lambda_p V_{DSp})$$

Model parameters for 0.25 μm CMOS devices

Parameters for drain current calculations

	V_{T0} [V]	γ [$\sqrt{\text{V}}$]	V_{DSAT} [V]	k' [$\mu\text{A}/\text{V}^2$]	λ	Φ_F [V]
NMOS	0.43	0.40	0.63	115	0.06	-0.30
PMOS	-0.40	-0.40	-1.00	-30	-0.10	0.30

Parameters for capacitance calculations

	C_{ox} [fF/ μm^2]	C_O [fF/ μm]	C_j [fF/ μm^2]	m_j	ϕ_b [V]	C_{jsw} [fF/ μm]	m_{jsw}	$\phi_{b_{sw}}$ [V]
NMOS	6	0.31	2.0	0.50	0.9	0.28	0.44	0.9
PMOS	6	0.27	1.9	0.48	0.9	0.22	0.32	0.9

Gate capacitance

Overlap capacitance

$$C_{GSO} = C_{GDO} = C_{ox} x_d W = C_O W$$

Channel capacitance

$$C_{GC} = C_{GCB} + C_{GCS} + C_{GCD}$$

Condition	C_{GCB}	C_{GCS}	C_{GCD}
$V_{GTn} \leq 0, V_{GTP} \geq 0$	$C_{ox} WL$	0	0
$V_{GTn} > 0, V_{GTP} < 0, V_{DS} \leq V_{GT} $	0	$C_{ox} WL/2$	$C_{ox} WL/2$
$V_{GTn} > 0, V_{GTP} < 0, V_{GT} \leq V_{DS} $	0	$2C_{ox} WL/3$	0

Junction capacitance

Average capacitance as function of voltage

$$C_j(V) = \frac{C_{j0}}{(1 - V/\phi_0)^m}$$

Average capacitance during transition from V_1 to V_2

$$C_{eq} = K_{eq} C_{j0} = \frac{-\phi_0^m}{(V_2 - V_1)(1-m)} [(\phi_0 - V_2)^{(1-m)} - (\phi_0 - V_1)^{(1-m)}] C_{j0}$$

Dynamic power consumption

$$P = df C_{tot} V_{dd}^2$$

Switch functions

$$S_N = \overline{F(A, B, \dots)}, S_P = F(\bar{A}, \bar{B}, \dots)$$

Transmission line

Characteristic impedance

$$Z_0 = \sqrt{L/c}$$

Velocity of wave

$$v = 1/\sqrt{Lc}$$

Average capacitance during transition from V_1 to V_2

$$C_{eq} = K_{eq} C_{j0} = \frac{-\phi_0^m}{(V_2 - V_1)(1-m)} [(\phi_0 - V_2)^{(1-m)} - (\phi_0 - V_1)^{(1-m)}] C_{j0}$$

Elmore delay

P_i = “the path between node 0 and i ”.

$P_{ij} = P_i \cap P_j$ = “the common part of the paths P_i and P_j ”.

R_{ij} = “the sum of all resistances in P_{ij} ”.

Time constant from node 0 to i : $\tau_{di} = \sum_{j=0}^n R_{ij} C_j$. Propagation delay: $t_{pi} \approx 0.69 \tau_{di}$.

Boolean algebra

De Morgans’ theorem

$$\overline{X + Y + Z + \dots} = \overline{XYZ\dots}, \quad \overline{XYZ\dots} = \bar{X} + \bar{Y} + \bar{Z} + \dots$$

Expansion in sum

$$f(X, Y, Z, \dots) = Xf(1, Y, Z, \dots) + \bar{X}f(0, Y, Z, \dots)$$

Expansion in product

$$f(X, Y, Z, \dots) = [X + f(0, Y, Z, \dots)][\bar{X} + f(1, Y, Z, \dots)]$$

For minimal propagation delay find the best solution to $1 = e^{(1+\gamma/k)/k}$, where k = “tapering factor”, N = “number of inverters”, $F = C_L/C_{g1} = k^N$ and $\gamma = C_{int1}/C_{g1}$.

Sizing of cascaded inverters