

Exam TEN1 in TSTE86 Digital Integrated Circuits

Time: Monday 7 January 2019, 14:00—18:00

Place: TER1

Responsible teacher: Mark Vesterbacka, phone 013-281324

Allowed aid: Calculator

Max score: 60 points

Grades: 45 points for 5
35 points for 4
25 points for 3

Solutions: Posted on the course web

Results: Posted through LADOK by 23 January 2019

1. A transistor schematic of a static CMOS gate is shown in Figure 1.

 


Figure 1. Static CMOS gate.

- a) What logic function has been implemented? (2 p)
- b) Show that the pull-up net and the pull-down net are complementary. (2 p)
- c) Size the devices so that the output resistance is the same as that of an inverter with an NMOS $W/L = 2$ and PMOS $W/L = 3$. (6 p)
- d) What input pattern(s) would give the worst and best equivalent pull-up or pull-down resistance? (4 p)

2. A precharged NOR gate shall be designed.

- a) Draw the transistor schematic of the gate. (4 p)
- b) Explain the operation of the gate. (4 p)
- c) Explain how charge leakage may impose a limitation on the operation. (2 p)

3. Figure 2 shows a clock distribution network. Each segment of the clock network is 5 mm long, 3 μm wide, and is implemented in metal. At each terminal node (such as X) resides a load capacitance of $C_L = 100$ fF. Assume a 0.25 μm process with the following metal properties: parallel plate capacitance $C_p = 0.088\text{fF}/\mu\text{m}^2$, fringing capacitance $C_f = 0.054$ fF/ μm , and sheet resistance $R_{\text{sq}} = 0.1 \Omega/\text{square}$.

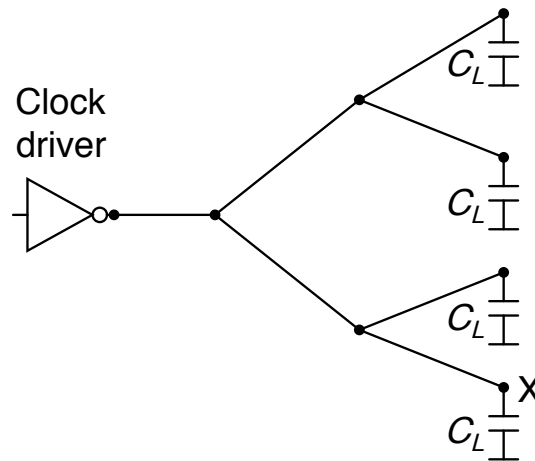


Figure 2. Clock distribution network.

- a) Determine the average current of the clock driver, given a voltage swing on the clock lines of 2.5 V and a maximum delay of 1.25 ns between clock source and node X. For this part, you may ignore the resistance and inductance of the network. (3 p)
 - b) Unfortunately, the resistance of the metal cannot be ignored. Assume that each segment of the network can be modeled with a simple π model. Draw the equivalent circuit and annotate the values of resistors and capacitors. (3 p)
 - c) Determine the dominant time-constant of the clock response at node X using the Elmore delay formula. (4 p)
4. Draw the transistor schematic of a C²MOS latch and explain its operation. (6 p)

5. Consider the signed, two's complement 4x4 bit array multiplier shown in Figure 3.

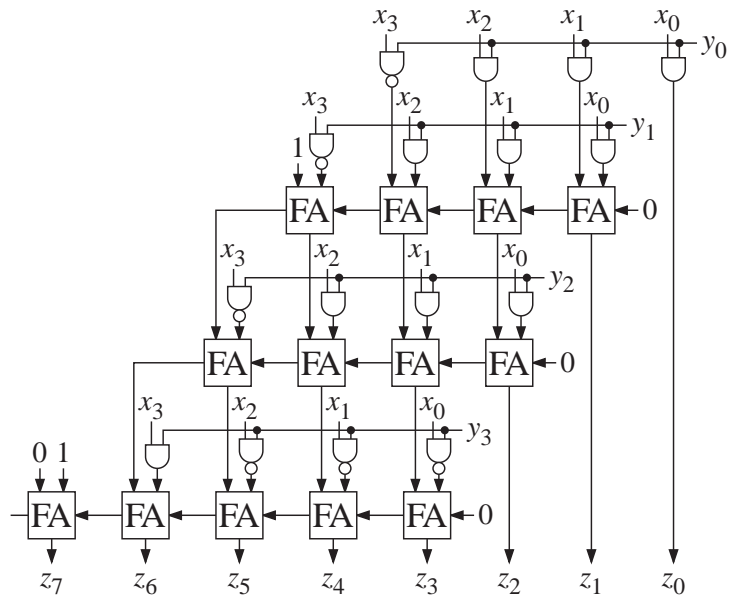


Figure 3. Two's complement multiplier.

- Calculate the partial products in squaring the two's complement number 1001_{2C} . (4 p)
- Estimate the delay of the critical path if a full adder has the propagation delay 0.7 ns, an AND gate 0.3 ns, and a NAND gate 0.2 ns. (3 p)
- What full adders can be simplified in the multiplier above and how? (3 p)

6.

- Define the terms controllability and observability. How are these properties related to an ad-hoc test? (6 p)
- For the circuit given in Figure 4, find all test patterns abc for which stuck-at-0 fault at node m can be detected from the output z . (4 p)


 



Figure 4. Combinational circuit.

Equations for the MOS transistor

NMOS

 

PMOS

 

Definition of source (S) and drain (D)

NMOS: $V_S \leq V_D$ PMOS: $V_S \geq V_D$

Voltage notations

$V_{GS} = V_G - V_S, V_{DS} = V_D - V_S, V_{SB} = V_S - V_B, V_{GT} = V_{GS} - V_T$

Threshold voltage

$V_T = V_{T0} + \gamma(\sqrt{|V_{SB} - 2\Phi_F|} - \sqrt{2|\Phi_F|})$

Unified model

NMOS: $V_{GT} \leq 0$ (PMOS: $V_{GT} \geq 0$) \Rightarrow Subthreshold region ($I_D \approx 0$)

NMOS: $V_{GT} \geq 0$ (PMOS: $V_{GT} \leq 0$) $\Rightarrow I_D = k' \frac{W}{L} V_{min} (|V_{GT}| - \frac{V_{min}}{2}) (1 + \lambda V_{DS})$

$V_{min} = \min(|V_{GT}|, |V_{DS}|, |V_{DSAT}|)$

$V_{min} = |V_{GT}| \Rightarrow$ saturation region

$V_{min} = |V_{DS}| \Rightarrow$ resistive (linear, triode) region ($\lambda = 0$)

$V_{min} = |V_{DSAT}| \Rightarrow$ velocity saturation region

V_{DSAT} dependency on channel length

$V_{DSAT} = L \tilde{E}_c$

Subthreshold region

NMOS: $V_{GT} \leq 0 \Rightarrow I_{Dn} = I_{0n} \frac{W}{L} e^{\frac{q(V_{GSn} - V_{Tn})}{nkT}} \left(1 - e^{-\frac{qV_{DSn}}{kT}} \right) (1 + \lambda_n V_{DSn})$

PMOS: $V_{GT} \geq 0 \Rightarrow I_{Dp} = I_{0p} \frac{W}{L} e^{\frac{q(V_{SGp} - |V_{Tp}|)}{nkT}} \left(1 - e^{-\frac{qV_{SDp}}{kT}} \right) (1 + \lambda_p V_{DSp})$

Model parameters for 0.25 μm CMOS devices

Parameters for drain current calculations

	V_{T0} [V]	γ [$\sqrt{\text{V}}$]	V_{DSAT} [V]	k' [$\mu\text{A}/\text{V}^2$]	λ	Φ_F [V]
NMOS	0.43	0.40	0.63	115	0.06	-0.30
PMOS	-0.40	-0.40	-1.00	-30	-0.10	0.30

Parameters for capacitance calculations

	C_{ox} [fF/ μm^2]	C_o [fF/ μm]	C_j [fF/ μm^2]	m_j	ϕ_b [V]	C_{jsw} [fF/ μm]	m_{jsw}	$\phi_{b,sw}$ [V]
NMOS	6	0.31	2.0	0.50	0.9	0.28	0.44	0.9
PMOS	6	0.27	1.9	0.48	0.9	0.22	0.32	0.9

Gate capacitance

Overlap capacitance

$C_{GSO} = C_{GDO} = C_{ox} x_d W = C_o W$

Channel capacitance

$C_{GC} = C_{GCB} + C_{GCS} + C_{GCD}$

Condition	C_{GCB}	C_{GCS}	C_{GCD}
$V_{GTn} \leq 0, V_{GTp} \geq 0$	$C_{ox} WL$	0	0
$V_{GTn} > 0, V_{GTp} < 0, V_{Ds} \leq V_{GT} $	0	$C_{ox} WL/2$	$C_{ox} WL/2$
$V_{GTn} > 0, V_{GTp} < 0, V_{GT} \leq V_{Ds} $	0	$2C_{ox} WL/3$	0

Junction capacitance

Junction capacitance as function of voltage

$$C_j(V) = \frac{C_{j0}}{(1 - V/\phi_0)^m}$$

Average capacitance during transition from V_1 to V_2

$$C_{eq} = K_{eq} C_{j0} = \frac{-\phi_0^m}{(V_2 - V_1)(1 - m)} [(\phi_0 - V_2)^{(1-m)} - (\phi_0 - V_1)^{(1-m)}] C_{j0}$$

Dynamic power consumption

$$P = \alpha f C_{tot} V_{dd}^2$$

Switch functions

$$S_N = \overline{F(A, B, \dots)}, S_P = F(\overline{A}, \overline{B}, \dots)$$

Boolean algebra

De Morgans' theorem

$$\overline{\overline{X} + Y + Z + \dots} = \overline{\overline{X}} \overline{Y} \overline{Z} \dots, \quad \overline{\overline{X} Y Z \dots} = \overline{\overline{X}} + \overline{Y} + \overline{Z} + \dots$$

Expansion in sum

$$f(X, Y, Z, \dots) = Xf(1, Y, Z, \dots) + \overline{X}f(0, Y, Z, \dots)$$

Expansion in product

$$f(X, Y, Z, \dots) = [X + f(0, Y, Z, \dots)][\overline{X} + f(1, Y, Z, \dots)]$$

Transmission line

Characteristic impedance

$$Z_0 = \sqrt{L/c}$$

Velocity of wave

$$v = 1/\sqrt{LC}$$

Reflection coefficient for a transmission line (Z_0) terminated by a load (Z_L)

$$\Gamma = (Z_L - Z_0)/(Z_L + Z_0)$$

Elmore delay

P_i = "the path between node 0 and i ".

$P_{ij} = P_i \cap P_j$ = "the common part of the paths P_i and P_j ".

R_{ij} = "the sum of all resistances in P_{ij} ".

Time constant from node 0 to i : $\tau_{di} = \sum_{j=0}^n R_{ij} C_j$. Propagation delay: $t_{pi} \approx 0.69 \tau_{di}$.

Sizing of cascaded inverters

For minimal propagation delay find the best solution to $1 = e^{(1+\gamma/k)}$, where

k = "tapering factor", N = "number of inverters", $F = C_L/C_{g1} = k^N$ and $\gamma = C_{int1}/C_{g1}$.