

- 2.5 Determine the largest current through both of the transistors during switching. We have the same current  $I_{Dn} = -I_{Dp}$  and gate-source voltage for the n-device is  $V_m$  and  $(V_m - V_{DD})$  for the p-device, respectively.  $V_m$  is the gate-source voltage when the current is maximum. Since, both devices are in the saturation region we get:

$$\frac{\mu_n C_{ox} W_n}{2 L_n} (V_m - V_{Tn})^2 = \frac{\mu_p C_{ox} W_p}{2 L_p} (V_{DD} - V_m + V_{Tp})^2$$

Solving for  $V_m$  we get  $V_m = \frac{V_{DD} + V_{Tp} + \sqrt{a} V_{Tn}}{1 + \sqrt{a}}$

where  $a = \frac{\mu_n W_n}{\mu_p W_p}$

Now, assume that  $a = 1$ , i.e., symmetric switching

$$\Rightarrow V_m = \frac{V_{DD} + V_{Tp} + V_{Tn}}{2} = \frac{V_{DD}}{2} \Rightarrow$$

$$\begin{aligned} I_{Dn} &= \frac{\mu_n C_{ox} W_n}{2 L_n} \left( \frac{V_{DD}}{2} - V_{Tn} \right)^2 = \\ &= \frac{(5.6 \cdot 10^{-2})(3.9)(8.85 \cdot 10^{-12})W_n}{(2)(100 \cdot 10^{-10}) L_n} \left( \frac{5}{2} - 0.75 \right)^2 \approx 332 \frac{W_n}{L_n} \quad [\mu A] \end{aligned}$$

where  $C_{ox} = \frac{\epsilon_r \epsilon_0}{T_{ox}}$

Rumors has it that the n- and p-transistors in the inverter that drives the global clock in the *Alpha*<sup>TM</sup> chip (Digital Equipments) has a combined widths of about 10 cm and 14 cm, respectively. The minimum feature size in the CMOS process is a 0.75  $\mu m$ , but the channel length is 0.5  $\mu m$ . The chip runs at 200 MHz and consumes about 30 W at 3.3 V. The number of devices is  $1.68 \cdot 10^6$  on a  $16.8 \times 13.9$  mm chip. Current high-performance chips consume 40 to 80 W at 1.8 V.

We guess that  $T_{ox} \approx 100 \text{ \AA}$ . We have

$$\beta = \frac{\mu_n \epsilon W}{T_{ox} L} = \frac{(5.6 \cdot 10^{-2})(3.9)(8.85 \cdot 10^{-12})W}{(100 \cdot 10^{-10})L} = 193 \cdot 10^{-6} \frac{W}{L} \quad [A]$$

The resulting drain current becomes

$$I_{Dn} \approx 193 \cdot 10^{-6} \frac{10 \cdot 10^{-2}}{0.5 \cdot 10^{-6}} = 38.6 \text{ Amperes}$$

Obviously, it is not possible to have such a large current! Special measures must be employed in order to avoid such large currents.