

Applikationsspecifika Integrerade kretsar


Tentamen TSTE81

för Y4, D4 och TE


- Tid: Onsdag 19 Mars 1997 kl. 14.00 - 18.00
- Plats: FOA1, FOA2, FOA5
- Ansvarig lärare: Kent Palmkvist, 281347
- Hjälpmedel: Räknedosa, Formelsamling i Aktiva och Tidsdiskreta filter, Formelsamling i kretsteori samt allmänna tabellverk.
- Anvisningar: För godkänd tentamen fordras ca 30 poäng
- Visning: Torsdag 3 April 1997 kl. 13.00-14.00
(Lars Wanhammars tjänsterum)
- Lösningar: Anslås på Systemtekniks anslagstavla i labkorridoren
- Betygslista: Anslås senast 1997-04-03 på anslagstavlan i labkorridoren

1.
 - a) What is an heuristic algorithm? (2)
 - b) What is the difference between multiprocessor and multicomputer systems? Describe the principal architectures. (2)
 - c) Name two different redundant number systems. (2)
 - d) Describe four approaches to partitioning of a system into a set of subsystems. (4)

 2. The filter below is to be implemented with a sample period of 5 time units. The multiplication a requires 6 time units, multiplication b requires 4 time units, and each addition requires 1 time unit.
 - a) Draw the precedence graph of the algorithm. (6)
 - b) Schedule the operations in order to reach the required sample period. (10)



 3. The filter below is to be implemented using homogenous, non-preemptive processing elements. Operation a requires 4 time units, b requires 5 time units, c requires 3 time units, d requires 7 time units, and each addition requires 1 time unit.
 - a) Determine the minimal sample period. (4)
 - b) Determine a lower limit on the number of required processing elements if the sample period is 6 time units. (4)




4. The equations below describes an algorithm that is to be implemented using distributed arithmetic.

$$y(n) = 0.101_2x(n) - 0.11_2v_2(n)$$

$$v_1(n+1) = v_2(n)$$

$$v_2(n+1) = 0.1101_2x(n) + 0.111_2v_1(n)$$

 - a) Draw the structure of the complete filter using distributed arithmetic units, shift registers etc. as building blocks. (2)
- b) Determine the contents of the ROM(s). (6)
- c) The size of the ROM(s) are reduced by utilizing the subtract/add signal in the shift accumulator. Determine the new contents of the ROM(s). (4)
3. The variables in the lifetime diagram below is to be stored using a RAM. Assign memory cells using
- a) Clique partitioning (6)
- b) Left edge algorithm (6)



5. A multiplication by the constant factor 45_{10} is to be implemented using bitserial arithmetic. The input is a bit-serial bitstream with least significant bit first. Only two adders are allowed. (Hint: $45=5*9$). (6)
6. Introduce shimming delays in the structure below which is to be implemented using bit-serial arithmetic. The multiplication has a latency of 3 clock cycles, and the additions one clock cycle. (6)

