

Applikationsspecifika Integrerade kretsar

Tentamen TSTE81


för Y4, D4 och TE

- Tid: Onsdag 1 September 1997 kl. 14.00 - 18.00
- Plats: Kårallen
- Ansvarig lärare: Kent Palmkvist, 281347
- Hjälpmedel: Räknedosa, Formelsamling i Aktiva och Tidsdiskreta filter, Formelsamling i kretsteori samt allmänna tabellverk.
- Anvisningar: För godkänd tentamen fordras ca 30 poäng
- Visning: Tisdag 16 September 1997 kl. 13.00-14.00
(Kent Palmkvists tjänsterum)
- Lösningar: Anslås på Systemtekniks anslagstavla i labkorridoren
- Betygslista: Anslås senast 1997-09-15 på anslagstavlan i labkorridoren

1. a) How fast grows the size of a distributed arithmetic unit when the number of inputs are increased? (2)
- b) How many clock cycles is needed for a multiplier implemented using Booth's algorithm compared to using an ordinary shift-accumulator? (2)
- c) What is sign-magnitude truncation? (2)
- d) What difference is there between a preemptive and non-preemptive processing element? (2)
- e) Why is it more important to generate a correct design when using ASICs compared to a standard DSP solution? (2)


2. The filter below is implemented using an isomorphic mapping to bit-serial arithmetic. The data wordlength is 14 bits. Multiplier a has a latency of 5 clock cycles, multiplier b has a latency of 7 clock cycles, and the additions has a latency of 1 clock cycle. The clock frequency is 150 MHz, and the sample rate is 5 MHz.

Introduce shimming delays. (8)

 

3. The recursive filter above is implemented using homogenous non-preemptive processing elements. Multiplication a requires 5 clock cycles, multiplication b requires 7 clock cycles, and addition requires 1 clock cycle.
 - a) What is the minimal sample period? (4)
 - b) Estimate the minimal number of resources required if the sample period is equal to the minimal sample period. (4)
 - c) Draw the precedence graph. (6)
 - d) Schedule the algorithm to reach the minimal sample period. (6)

 4. The schedule below is implemented using non-homogenous non-preemptive processing elements. Processes P1 and P7 are of the same type, and processes P2, P3, and P5 are of the same type.
- Perform processing element resource allocation and assignment using clique partitioning. (6)
 - Draw a variable lifetime diagram. (4)
 - Perform memory cell resource allocation and assignment using the left edge algorithm. Indicate the steps performed in the allocation/assignment. Variables cannot be assigned edge-to-edge, and are not allowed to overlap themselves. (6)



5. A multiplication by a constant -1.1875 is to be implemented. The input data wordlength is 15 bits.
- Draw the non-optimized logic diagram of the multiplier. Use blocks such as full adders, flip-flops etc. (4)
 - Optimize the structure. (3)
 - What is the latency measured in clock cycles for the multiplier? (2)
 - What is the throughput measured in clock cycles for the multiplier? (2)
 - Implement the multiplication using 2 or less fulladders. Hint: $-1.1875 = -1 - 0.25 + 0.0625$. (5)