

Lösningsförslag till tentamen ETE235 Digitalteknik 2012-08-21

1a)

$$\begin{array}{rclcl}
 249 / 2 & = & 124 & + 1 & \text{LSB} \\
 124 / 2 & = & 62 & + 0 & \\
 62 / 2 & = & 31 & + 0 & \\
 31 / 2 & = & 15 & + 1 & \\
 15 / 2 & = & 7 & + 1 & \\
 7 / 2 & = & 3 & + 1 & \\
 3 / 2 & = & 1 & + 1 & \uparrow \\
 1 / 2 & = & 0 & + 1 & \text{MSB}
 \end{array}$$

ALLTSÅ $249_{10} = 11111001_2$

1b)

$$\overbrace{1000}^4 \overbrace{1111}^4 = 8F_{16}$$

1c)

$$\overbrace{1000}^4 \overbrace{1111}^4 = 217_8$$

1d)

$$\begin{aligned}
 & 10001111_2 = \\
 & = 1 \cdot 2^7 + 0 \cdot 2^6 + 0 \cdot 2^5 + 0 \cdot 2^4 + 1 \cdot 2^3 + 1 \cdot 2^2 + 1 \cdot 2^1 + 1 \cdot 2^0 = \\
 & = 128 + 0 + 0 + 0 + 8 + 4 + 2 + 1 = 143
 \end{aligned}$$

1e)

$$10001111_2 = \overbrace{0001}^1 \overbrace{0100}^4 \overbrace{0011}^3_{BCD}$$

1f)

$$0,40625 \cdot 2 = 0,8125 + 0 \text{ MSB}$$

$$0,8125 \cdot 2 = 0,625 + 1 \quad \downarrow$$

$$0,625 \cdot 2 = 0,25 + 1$$

$$0,25 \cdot 2 = 0,5 + 0$$

$$0,5 \cdot 2 = 0 + 1 \text{ LSB}$$

$$\text{ALLTSA} \quad 0,40625_{10} = 0,01101_2$$

19/

$$\begin{array}{r} 11101001 \\ - 1 \\ \hline 11101000 \end{array}$$

$$00010111 = +23$$

ALLTSA $11101001 = -23$


ENLIGT TVÅKOMPLEMENTMETODEN

VÄNSTRAN BITEN " AR TECKENBIT:

0 $\rightarrow$ POSITIV TAL

1 $\rightarrow$ NEGATIVT TAL

2a)

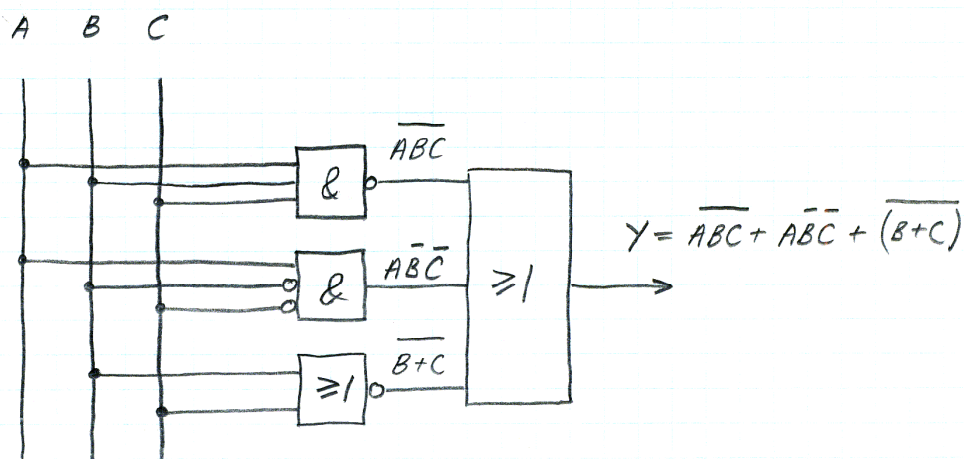

2b) $Y = \overline{ABC} + \overline{ABC} + \overline{(B+C)} =$

$$= \overline{ABC} + \overline{ABC} + \overline{BC} =$$

$$= \overline{ABC} + \overline{BC}(A+1) =$$


$$= \overline{A} + \overline{B} + \overline{C} + \overline{BC} =$$

$$= \overline{A} + \overline{B} + \overline{C} + \overline{BC} + \overline{BC} =$$

$$= \overline{A} + \overline{B}(1+\overline{C}) + \overline{C}(1+\overline{B}) =$$

$$= \overline{A} + \overline{B} + \overline{C} = \overline{ABC}$$

A B C

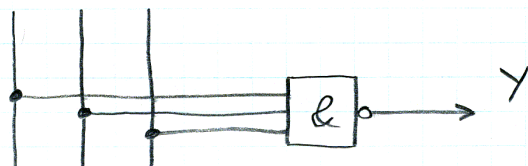


3a/

		CD			
		00	01	11	10
AB	00	1	1	0	1
	01	1	1	0	1
	11	1	1	0	0
	10	1	1	0	1

$$Y = \bar{C} + \bar{A}\bar{D} + \bar{B}\bar{D}$$


A B C D

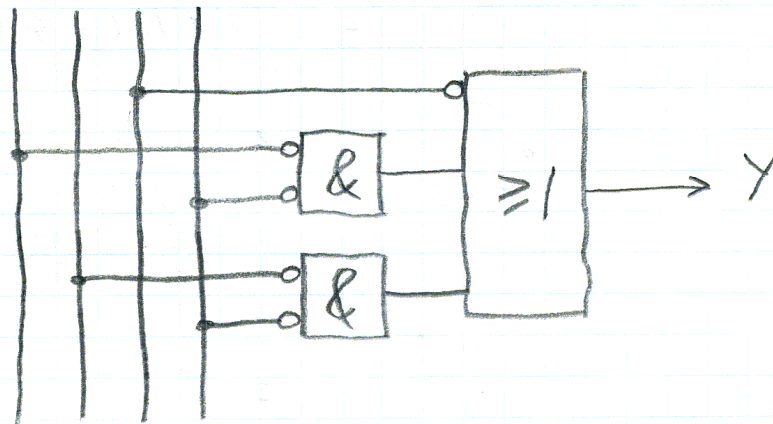

3b/

$$Y = \overline{\overline{C + \bar{A}\bar{D} + \bar{B}\bar{D}}} = \overline{C \cdot \overline{\bar{A}\bar{D}} \cdot \overline{\bar{B}\bar{D}}}$$

A B C D

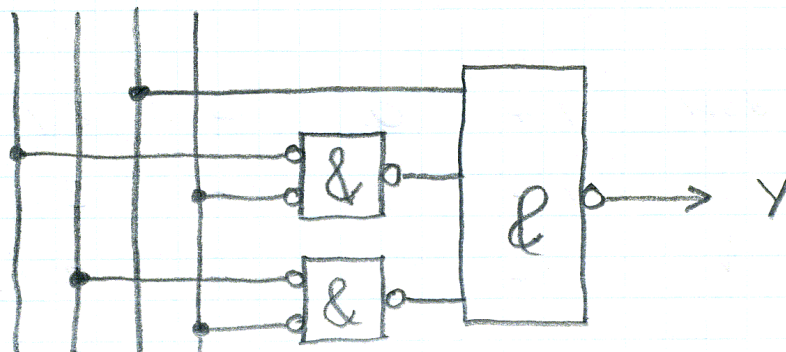

3c)

AB \ CD	CD			
	00	01	11	10
00	1	1	0	1
01	1	1	0	1
11	1	1	0	0
10	1	1	0	1

$$\bar{Y} = CD + ABC$$

$$Y = \overline{CD + ABC} =$$


$$= \overline{CD + ABC} =$$

$$= \overline{CD} \cdot \overline{ABC} =$$

$$= (\bar{C} + \bar{D}) \cdot (\bar{A} + \bar{B} + \bar{C}) =$$

$$= (\bar{C} + \bar{D}) + (\bar{A} + \bar{B} + \bar{C})$$

A B C D

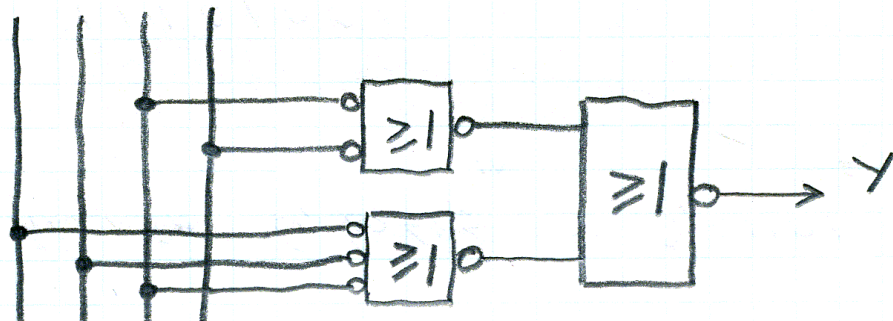

4.

$$D = Q_C + \bar{Q}_A \bar{Q}_B$$

$$S = \bar{Q}_B$$

$$R = (Q_A \oplus Q_C) + \bar{Q}_B$$


$$T = Q_C \oplus Q_B$$

FÖRE CP

EFTER CP

Q_A	Q_B	Q_C	D	S	R	T	Q_A^+	Q_B^+	Q_C^+
0	0	0	1	1	1	0	1	0	0
0	0	1	1	1	1	1	1	0	1
0	1	0	0	0	0	1	0	1	0
0	1	1	1	0	1	0	1	0	1
1	0	0	0	1	1	0	0	1	0
1	0	1	1	1	1	1	1	1	0
1	1	0	0	0	1	1	0	0	1
1	1	1	1	0	0	0	1	1	1

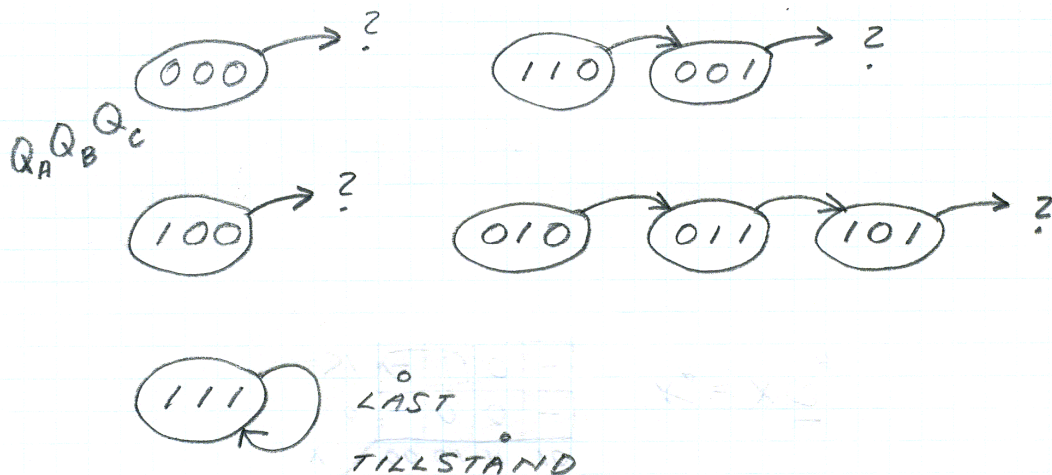*) SR-VIPPAN "ÄR FELAKTIGT ANVÄND,
S OCH R FÅR ALDRIG VARA 1
SAMTIDIGT.



5.

FÖRE CP

EFTER CP

X	Q_A	Q_B	J_A	K_A	J_B	K_B	Q_A^+	Q_B^+
0	0	0	1	-	0	-	1	0
0	0	1	0	-	-	0	0	1
0	1	0	-	0	0	-	1	0
0	1	1	-	1	-	0	0	1
1	0	0	0	-	0	-	0	0
1	0	1	0	-	-	1	0	0
1	1	0	-	0	1	-	1	1
1	1	1	-	0	-	0	1	1

X	Q_A	Q_B		
	00	01	11	10
0	1	0	-	1
1	0	0	-	-

$$J_A = \bar{X} \bar{Q}_B$$

X	Q_A	Q_B		
	00	01	11	10
0	-	1	1	0
1	-	-	0	0


$$K_A = \bar{X} Q_B$$

X	Q_A	Q_B		
	00	01	11	10
0	0	-	-	0
1	0	-	1	1


$$J_B = X Q_A$$

X	Q_A	Q_B		
	00	01	11	10
0	-	0	0	-
1	1	1	0	-

$$K_B = X \bar{Q}_A$$

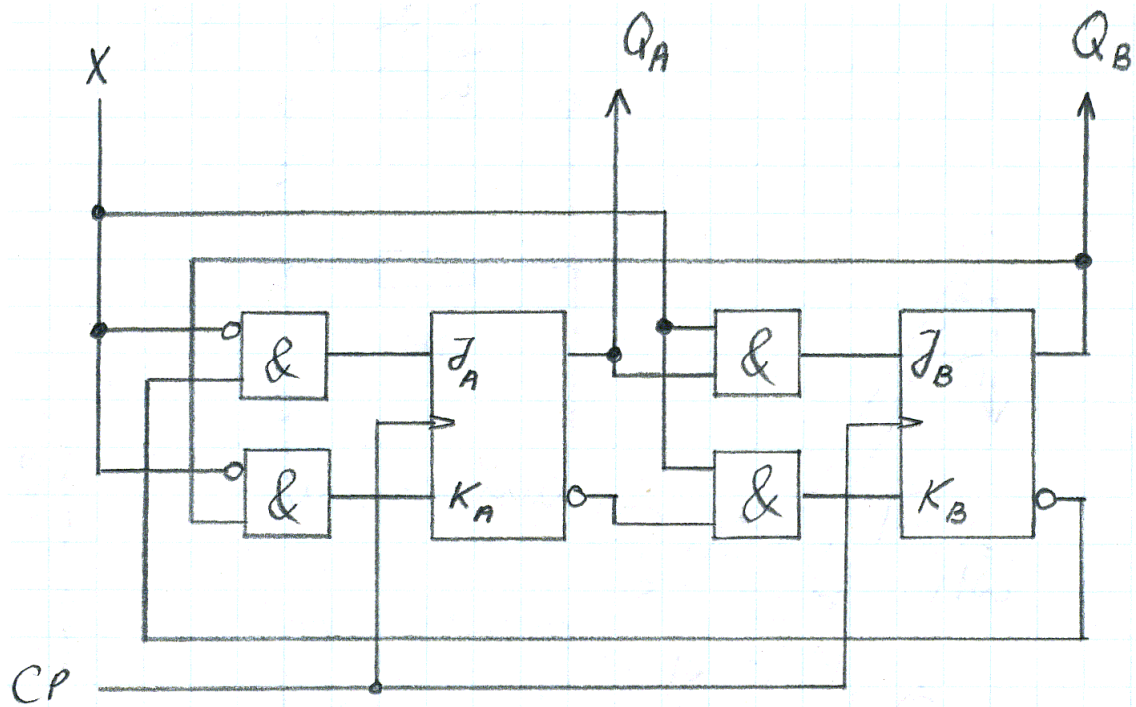

6a)

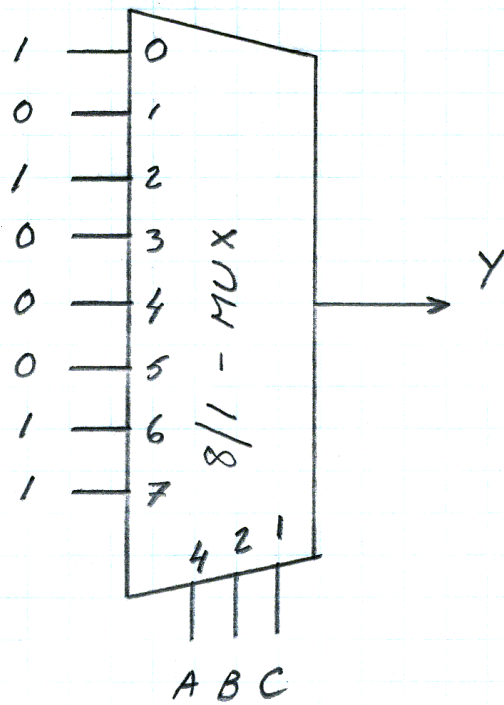

6b)


	BC			
A	00	01	11	10
0	1	0	0	1
1	0	0	1	1

$$AC = 00 \rightarrow Y = 1$$

$$AC = 01 \rightarrow Y = 0$$

$$AC = 10 \rightarrow Y = B$$

$$AC = 11 \rightarrow Y = B$$

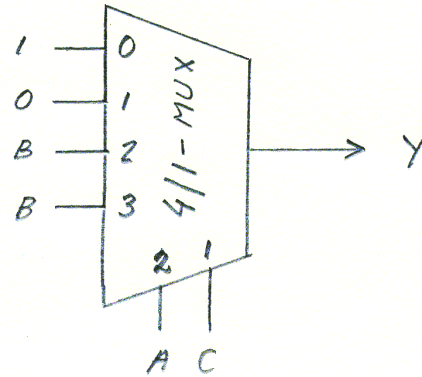

6c)

	BC			
A	00	01	11	10
0	1	0	0	1
1	0	0	1	1

$$\bar{Y} = \bar{A}C + A\bar{B}$$

$$Y = \overline{\bar{A}C + A\bar{B}} = \overline{\bar{A}C} \cdot \overline{A\bar{B}}$$

A B C

