
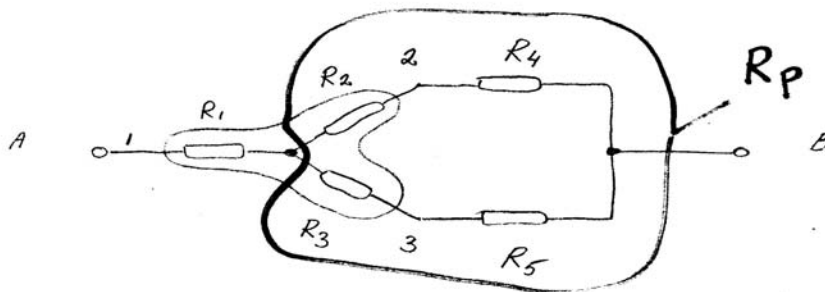


Lösning med D/Y-transformation:

A4.1

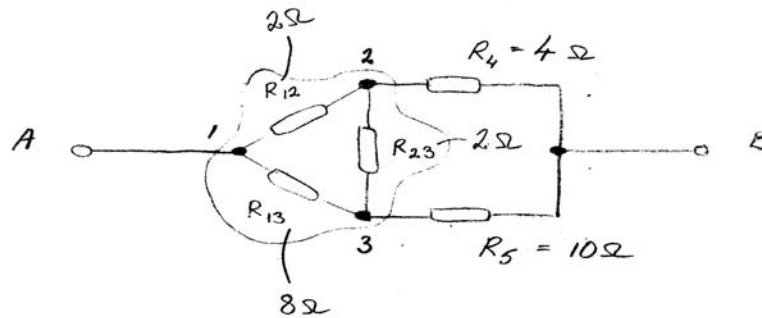

$$R_1 = \frac{R_{12} \cdot R_{13}}{R}$$

$$R = R_{12} + R_{13} + R_{23}$$

$$R_2 = \frac{R_{12} \cdot R_{23}}{R}$$

$$R = 12 \Omega$$

$$R_1 = \frac{4}{3} \Omega \approx 1,333$$

$$R_3 = \frac{R_{13} \cdot R_{23}}{R}$$

$$R_2 = \frac{1}{3} \Omega \approx 0,333$$


$$R_3 = \frac{4}{3} \Omega \approx 1,333$$

$$R_{AB} = R_1 + R_P$$

$$\frac{1}{R_P} = \frac{1}{R_2 + R_4} + \frac{1}{R_3 + R_5} \Rightarrow R_P = 3,135 \Omega$$

$$R_{AB} \approx 1,333 + 3,135 \Omega = 4,47 \Omega$$

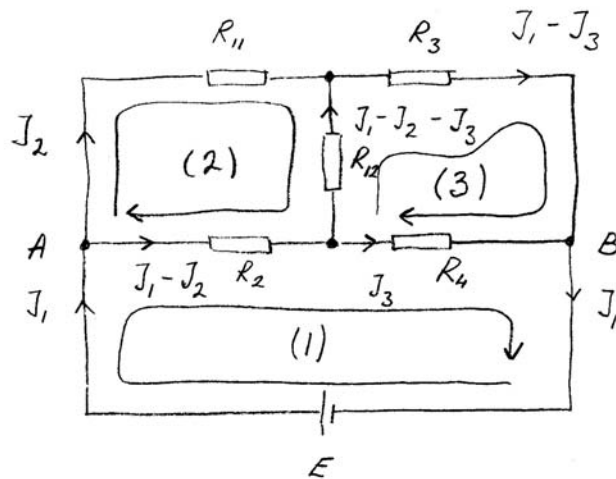Alternativ lösning med slinganalys (Kirchhoffs spänningslag):



$$R_{AB} = \frac{E}{J_1} \dots (*)$$

$$+E - R_2(J_1 - J_2) - R_4 J_3 = 0 \dots (1)$$

$$-R_{11} J_2 + R_{12}(J_1 - J_2 - J_3) + R_2(J_1 - J_2) = 0 \dots (2)$$

$$-R_{12}(J_1 - J_2 - J_3) - R_3(J_1 - J_3) + R_4 J_3 = 0 \dots (3)$$

NUMERISKT :

$$8 J_1 - 8 J_2 + 10 J_3 = E \dots (1)$$

$$10 J_1 - 12 J_2 - 2 J_3 = 0 \dots (2)$$

$$-6 J_1 + 2 J_2 + 16 J_3 = 0 \dots (3)$$

$$\begin{pmatrix} 8 & -8 & 10 \\ 10 & -12 & -2 \\ -6 & 2 & 16 \end{pmatrix} \begin{pmatrix} E \\ 0 \\ 0 \end{pmatrix} \sim \begin{pmatrix} (1) + 5 \cdot (2) \\ 8 \cdot (2) + (3) \end{pmatrix} \sim \begin{pmatrix} 58 & -68 & 0 \\ 74 & -94 & 0 \\ -6 & 2 & 16 \end{pmatrix} \begin{pmatrix} E \\ 0 \\ 0 \end{pmatrix} \sim \left\{ (1) - \frac{68}{94} \cdot (2) \right\}$$

(J_1, J_2, J_3)

$$\sim \begin{pmatrix} 4,47 & 0 & 0 \\ 74 & -94 & 0 \\ -6 & 2 & 16 \end{pmatrix} \begin{pmatrix} E \\ 0 \\ 0 \end{pmatrix} \Rightarrow J_1 \approx \frac{E}{4,47} \text{ ins } (*) \Rightarrow$$

$$\underline{\underline{R_{AB} \approx 4,47 \Omega}}$$