

F2.5

VI UTHYTTJAR RESULTATET I UPPG

F2.3

$$\frac{U_{UT}}{U_{IN}} = - \frac{-j\omega C_1 R_2}{(j\omega C_2 R_2 + 1)(j\omega C_1 R_1 + 1)} \dots (1)$$

$$C_2 R_2 = \frac{1}{2\pi \cdot 16000} \dots (2) \quad C_1 R_1 = \frac{1}{2\pi \cdot 40} \dots (3)$$

\uparrow f_0'' \uparrow f_u

$$Z_{in} \geq 20 \text{ k}\Omega \rightarrow R_1 \geq 20 \text{ k}\Omega$$

$$\underline{R_1 = 20 \text{ k}\Omega} \text{ INS I (3)} \rightarrow \underline{C_1 = 199 \text{ nF}}$$

$$F_{dB} = 20 \text{ Lg} \left| \frac{U_{UT}}{U_{IN}} \right| \quad F_{dB} = 30 \text{ dB} \rightarrow$$

$$30 = 20 \text{ Lg} \left| \frac{U_{UT}}{U_{IN}} \right| \quad \text{FÖR FREKVENSER MELLAN 40 OCH 16000 Hz}$$

$$\left| \frac{U_{UT}}{U_{IN}} \right| = 10^{\frac{30}{20}} = 31,6 \text{ GGR} \quad (\text{EX. VIS 1000 Hz})$$

Ekvation (1) ger: $31,6 \approx \frac{2\pi \cdot 1000 \cdot 199 \cdot 10^{-9} \cdot R_2}{\sqrt{\left(\frac{2\pi \cdot 1000}{2\pi \cdot 16000}\right)^2 + 1} \sqrt{\left(\frac{2\pi \cdot 1000}{2\pi \cdot 40}\right)^2 + 1}}$

Försummas

$$\Rightarrow \underline{R_2 = 632 \text{ k}\Omega} \text{ INS I (2)} \rightarrow \underline{C_2 = 15,7 \text{ pF}}$$