

BESTÄM $i(t)$, $u_R(t)$, $u_L(t)$ OCH $u_C(t)$ OM $e(t) = 5,0\sqrt{2}\sin(1000t + 0^\circ) \text{ V}$

LÖSNING:

$$\hat{J} = \frac{\hat{E}}{\hat{Z}} \quad \text{DÄR } \hat{Z} = \sqrt{R^2 + (X_L - X_C)^2}$$

IMPEDANS RESISTANS REAKTANS

$$X_L = \omega L \rightarrow X_L = 4,0 \text{ k}\Omega$$

$$X_C = \frac{1}{\omega C} \rightarrow X_C = 1,0 \text{ k}\Omega$$

$$\hat{Z} = 5,0 \text{ k}\Omega \rightarrow \hat{J} = 1,0\sqrt{2} \text{ mA}$$

$$\hat{U}_R = R \hat{J} \rightarrow \hat{U}_R = 4,0\sqrt{2} \text{ V}$$

$$\hat{U}_L = X_L \hat{J} \rightarrow \hat{U}_L = 4,0\sqrt{2} \text{ V}$$




$$\hat{U}_C = X_C \hat{J} \rightarrow \hat{U}_C = 1,0\sqrt{2} \text{ V}$$

$$u_R = R \cdot i \rightarrow u_R \text{ LIGGER I FAS MED } i$$


$$u_L = L \cdot \frac{di}{dt} \rightarrow u_L \text{ LIGGER } 90^\circ \text{ FÖRE } i$$

$$i = C \cdot \frac{du_C}{dt} \rightarrow u_C = \frac{1}{C} \int i dt$$
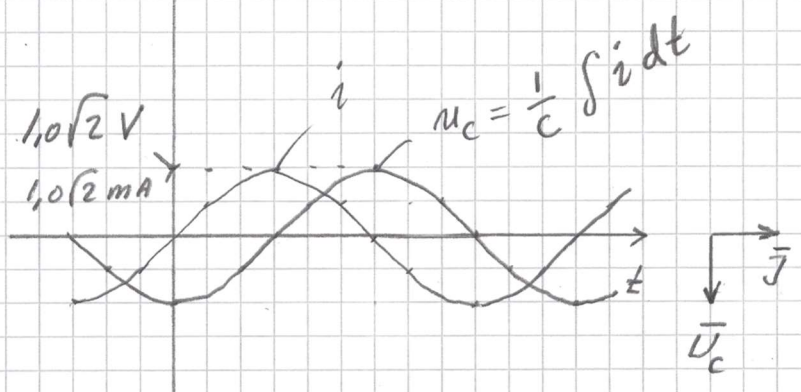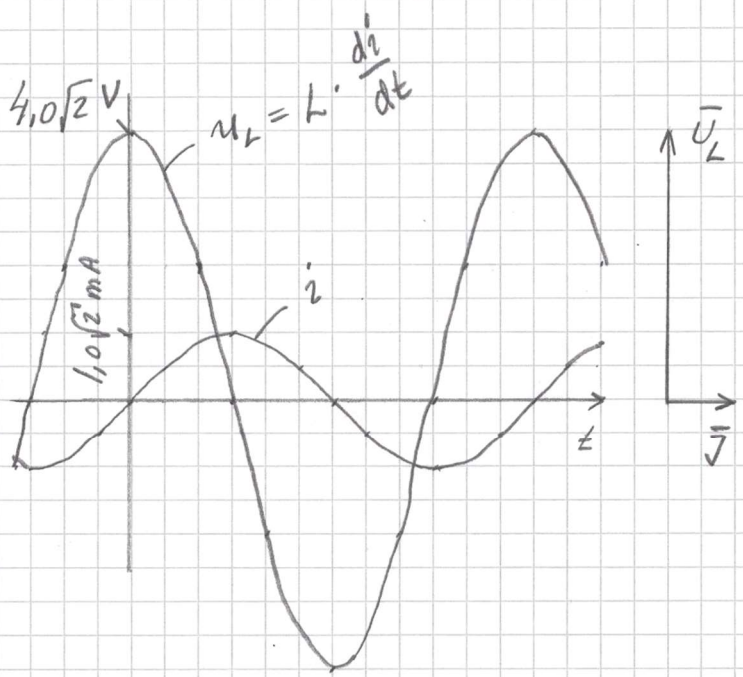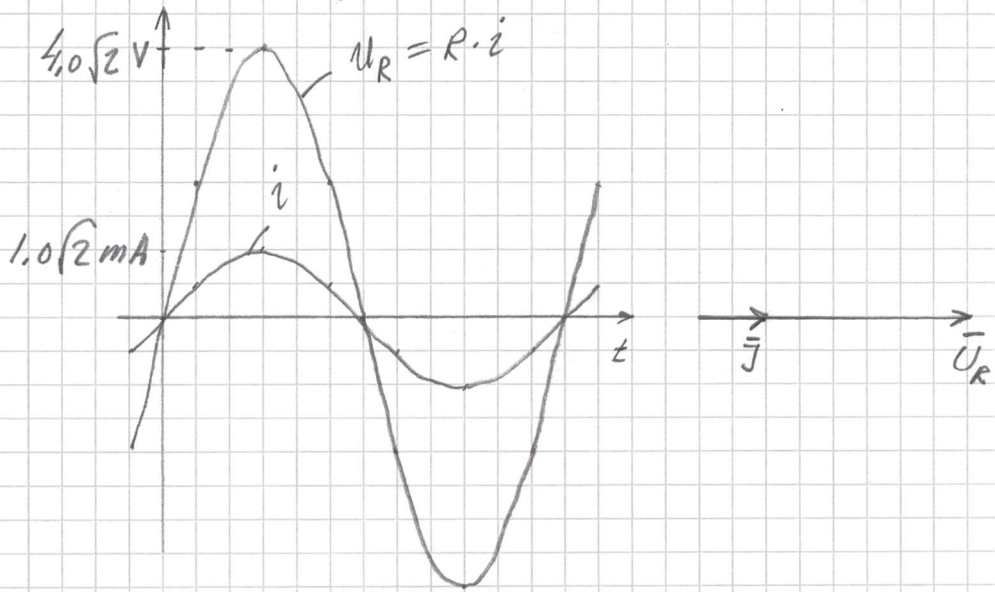
$$\rightarrow u_C \text{ LIGGER } 90^\circ \text{ EFTER } i$$



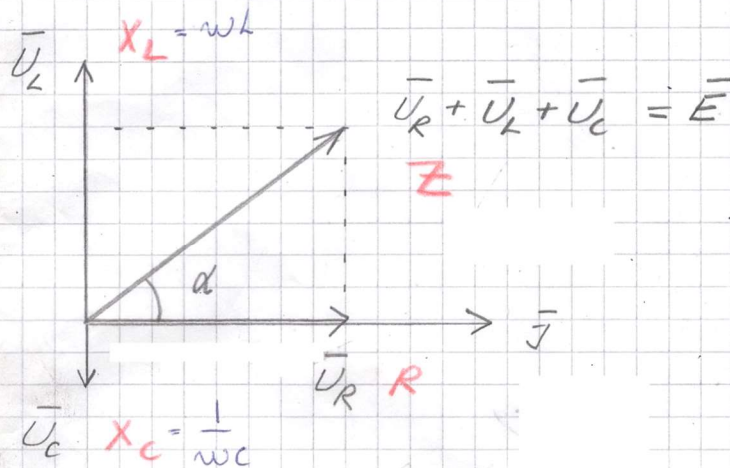*1) DIVIDERA SPÄNNINGARNA
MED STRÖMSTYRKAN
(OHMS LAG)



$$\alpha = \arctan \frac{U_L - U_C}{U_R} \rightarrow$$

$$\alpha = \arctan \frac{3,0}{4,0} \approx 37^\circ$$

$$\text{MEN } \arg \bar{E} = 0^\circ$$

⇒ VRID VISARDIAGRAMMET
37° MEDURS

$$\Rightarrow \arg \bar{J} = -37^\circ \quad \arg \bar{U}_R = -37^\circ$$

$$\arg \bar{U}_L = 90^\circ - 37^\circ = 53^\circ$$

$$\arg \bar{U}_C = -90^\circ - 37^\circ = -127^\circ$$

ALLTSA :

$$i(t) = 1,0\sqrt{2} \sin(1000t - 37^\circ) \text{ mA}$$


$$u_R(t) = 4,0\sqrt{2} \sin(1000t - 37^\circ) \text{ V}$$

$$u_L(t) = 4,0\sqrt{2} \sin(1000t + 53^\circ) \text{ V}$$

$$u_C(t) = 1,0\sqrt{2} \sin(1000t - 127^\circ) \text{ V}$$

ALTERNATIV LÖSNING MED $j\omega$ -METODEN

KOMPLEKT SCHEMA :

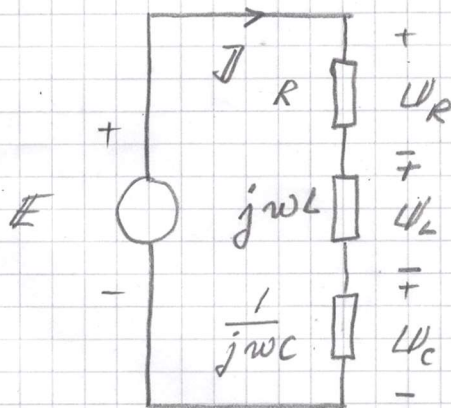

$$I = \frac{E}{R + j\omega L + \frac{1}{j\omega C}}$$

$$e(t) = 5,0\sqrt{2} \sin(1000t + 0^\circ) \text{ V}$$

$$\rightsquigarrow \underline{E} = 5,0\sqrt{2} \cdot e^{j0^\circ} \text{ V}$$

$$\frac{1}{j\omega C} = -j \cdot \frac{1}{\omega C} \Rightarrow$$

$$I = \frac{5,0\sqrt{2} \cdot e^{j0^\circ}}{4000 + j(4000 - 1000)} =$$

$$= \frac{5,0\sqrt{2} e^{j0^\circ}}{\underbrace{\sqrt{4000^2 + 3000^2}}_{5000 \Omega} \cdot e^{j \arctan \frac{3000}{4000}}}_{37^\circ} =$$

$$= 0,0010\sqrt{2} \cdot e^{-j37^\circ} \text{ A} \rightsquigarrow$$

$$i(t) = 1,0\sqrt{2} \sin(1000t - 37^\circ) \text{ mA}$$

$$U_R = R \cdot I \rightarrow U_R = 4,0\sqrt{2} \cdot e^{-j37^\circ} \text{ V}$$

$$\rightsquigarrow u_R(t) = 4,0\sqrt{2} \sin(1000t - 37^\circ) \text{ V}$$

$$U_L = j\omega L I = \underbrace{j4000 \cdot 0,0010\sqrt{2}}_{4000 \cdot e^{j90^\circ}} \cdot e^{-j37^\circ} =$$

$$= 4,0\sqrt{2} \cdot e^{j53^\circ} \text{ V} \rightsquigarrow$$

$$u_L(t) = 4,0\sqrt{2} \sin(1000t + 53^\circ) \text{ V}$$

$$U_c = -j \cdot \frac{1}{\omega C} \cdot \overset{\uparrow}{I} = -j 1000 \cdot 0,0010 \sqrt{2} \cdot e^{-j37^\circ} =$$

$$\underbrace{1000 e^{-j90^\circ}}$$

$$= 1,0 \sqrt{2} \cdot e^{-j127^\circ} \text{ V} \quad \rightsquigarrow$$

$$u_c(t) = 1,0 \sqrt{2} \sin(1000t - 127^\circ) \text{ V}$$