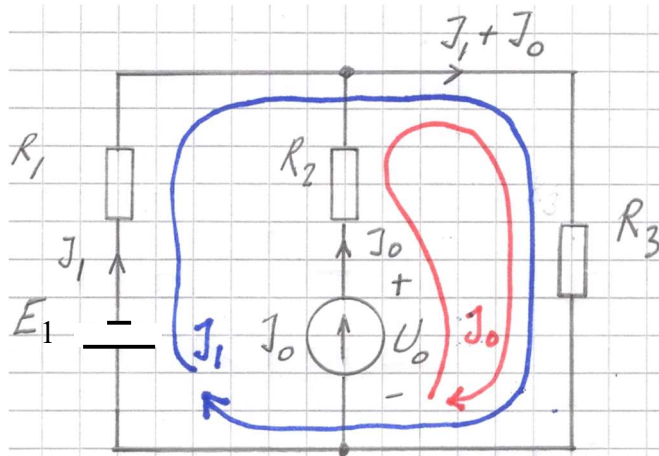


Lösningsförslag till tentamen TMEL08 Eltekniska system 2024-01-02

1.




$$-E_1 - R_1 J_1 - R_3 (J_1 + J_0) = 0 \dots (1)$$

$$+U_0 - R_2 J_0 - R_3 (J_1 + J_0) = 0 \dots (2)$$

$$(1) \rightarrow J_1 = -20 \text{ mA}$$

$$\text{INS I (2)} \rightarrow \underline{U_0 = 0 \text{ V}}$$

2. Separatmagnetiserad likströmsmotor

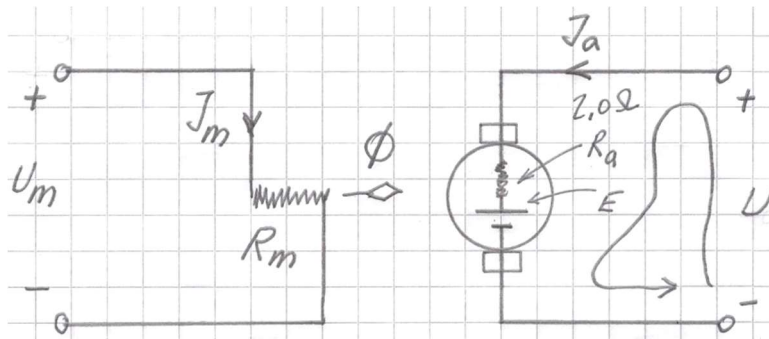

FALL I

$$U_I = 200 \text{ V}$$

$$J_{aI} = 10 \text{ A}$$

$$E_I = ?$$

$$n_I = 1000 \text{ RPM}$$

FALL II

$$U_{II} = 170 \text{ V}$$

$$J_{aII} = ?$$

$$E_{II} = ?$$

$$n_{II} = ?$$

SAMMA MOMENT OCH MAGNETISKT
" FLÖDE I DE TVÅ FALLEN.

$$\left. \begin{aligned} M &= k_2 \Phi J_{aI} \\ M &= k_2 \Phi J_{aII} \end{aligned} \right\} \Rightarrow J_{aII} = J_{aI} = \underline{10 \text{ A}}$$

b) KIRCHHOFFS SPÄNNINGSLAG \Rightarrow

$$+U_I - R_a J_{aI} - E_I = 0 \Rightarrow \underline{E_I = 180 \text{ V}}$$

$$+U_{II} - R_a J_{aII} - E_{II} = 0 \Rightarrow \underline{E_{II} = 150 \text{ V}}$$

$$\frac{E_I}{E_{II}} = \frac{k_1 \Phi n_I}{k_1 \Phi n_{II}} \Rightarrow \underline{n_{II} = 833 \text{ RPM}}$$

3a)

"ÖVRE LÄGET" →

$$U_2 = U_{ut} \cdot \frac{R_3 + R_4}{R_2 + R_3 + R_4}$$

$$5,1 = 6,6 \cdot \frac{R_3 + R_4}{30000 + R_3 + R_4} \rightarrow$$

$$R_3 + R_4 = 51000 \Omega$$

"NEDRE LÄGET" →

$$U_2 = U_{ut} \cdot \frac{R_4}{R_2 + R_3 + R_4}$$

$$5,1 = 13,2 \cdot \frac{R_4}{30000 + 51000} \rightarrow$$

$$\underline{R_4 = 25,5 \text{ k}\Omega} \quad \rightarrow \quad \underline{R_3 = 25,5 \text{ k}\Omega}$$

"SPÄNNINGEN" ÄR NOLL MELLAN
PLUS- OCH MINUSINGÅNGEN PÅ
OPERATIONSFÖRSTÄRKAREN.

3b)

$$U_{OP} - U_{BE} = U_{ut} \rightarrow U_{OP} = U_{ut} + U_{BE}$$

↑
0,70 V

$$U_{ut} = 6,6 \text{ V} \rightarrow U_{OP} = \underline{7,3 \text{ V}}$$

$$U_{ut} = 13,2 \text{ V} \rightarrow U_{OP} = \underline{13,9 \text{ V}}$$

3c)


"
 $I_{R1} = I_Z$ TY STRÖMMEN IN TILL
 OP'NS PLUSINGÅNG ÄR NOLL.

$$R_1 = \frac{U_{R1}}{I_{R1}} = \frac{U_{in} - U_Z}{I_Z}$$

$$R_1 = \frac{15 - 5,1}{0,050} = 198 \Omega$$

VÄLJ R_1 STRAX UNDER 198 Ω

4a)

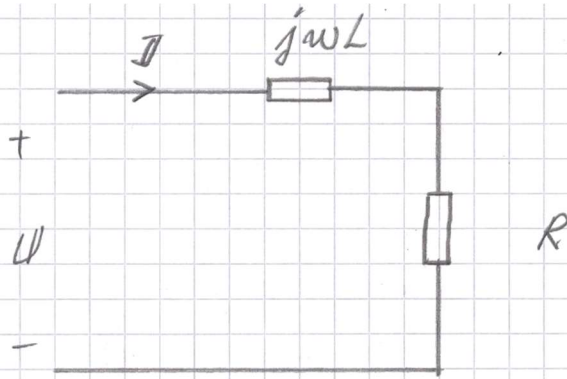

$$u(t) = 230 \sqrt{2} \sin(100\pi t + 0^\circ) \text{ V} \rightarrow U = 230 \sqrt{2} e^{j0^\circ} \text{ V}$$

$$I = \frac{U}{R + j\omega L} \Rightarrow$$

$$I = \frac{230 \sqrt{2} e^{j0^\circ}}{24,0 + j100\pi \cdot 0,0573} =$$

$$= \frac{230 \sqrt{2} e^{j0^\circ}}{\sqrt{24^2 + 18^2} \cdot e^{j \arctan \frac{18}{24}}} = 7,67 \sqrt{2} e^{-j37^\circ} \text{ A}$$

$$\rightarrow \underline{i(t) = 7,67 \sqrt{2} \sin(100\pi t - 37^\circ) \text{ A}}$$

4b)

$$I = \frac{\hat{I}}{\sqrt{2}} = 7,67 \text{ A}$$

$$P = R I^2 \Rightarrow \underline{P = 1,41 \text{ kW}}$$

(Q_L)

$$Q = X_L I^2 = |X_L| = \omega L = \underline{1,06 \text{ kVAR}}$$

$$S = \sqrt{P^2 + Q^2} \Rightarrow \underline{S = 1,76 \text{ kVA}}$$

ALTERNATIVT SÄTT ATT RÄKNA :

$$P = U \cdot I \cdot \cos \varphi$$

$$(Q_L) Q = U \cdot I \cdot \sin \varphi$$

$$S = U \cdot I$$

$$\varphi = \arg U - \arg I = 37^\circ$$

↑ ↑
0° -37°

$$U = \frac{\hat{U}}{\sqrt{2}} = 230 \text{ V}$$

4c)

$$Q = Q_L - Q_C$$

$$Q = 0 \Rightarrow Q_C = Q_L$$

$$Q_C = \frac{U^2}{X_C} = \frac{1}{X_C} = \frac{1}{\omega C} = U^2 \omega C$$

$$1,06 \cdot 10^3 = 230^2 \cdot 100\pi \cdot C \Rightarrow \underline{C = 63,7 \mu\text{F}}$$

4d)

$$Q = 0 \Rightarrow S = P \text{ och } \cos \varphi = 1 \Rightarrow \varphi = 0^\circ$$


$$S = U \cdot I \Rightarrow 1,41 \cdot 10^3 = 230 \cdot I$$

$$\Rightarrow I = 6,13 \text{ A} \quad \hat{I} = 6,13 \sqrt{2} \text{ A}$$

$$\Rightarrow \underline{i(t) = 6,13 \sqrt{2} \sin(100\pi t) \text{ A}}$$

($\varphi = 0^\circ$ INNEBÄR ATT $\arg I = \arg U$)

5.

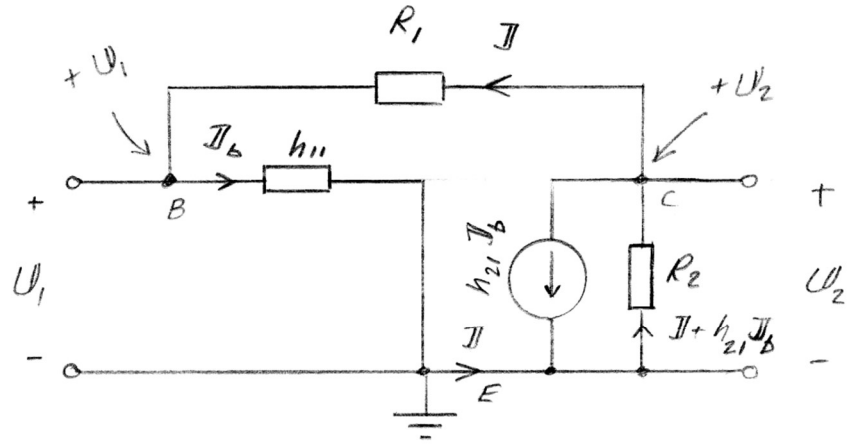

$$F = \frac{U_2}{U_1} \dots (3)$$

$$U_2 = -R_2 (I + h_{21} I_b) \dots (4)$$

$$I = \frac{U_2 - U_1}{R_1}$$

$$U_1 = h_{11} I_b \Rightarrow I_b = \frac{U_1}{h_{11}}$$

INS , (4) \rightarrow


$$U_2 = -R_2 \left(\frac{U_2 - U_1}{R_1} + \frac{h_{21}}{h_{11}} \cdot U_1 \right)$$

$$U_2 + \frac{R_2}{R_1} U_2 = \frac{R_2}{R_1} U_1 - R_2 \cdot \frac{h_{21}}{h_{11}} \cdot U_1$$

$$\frac{U_2}{U_1} = \frac{\frac{R_2}{R_1} - R_2 \cdot \frac{h_{21}}{h_{11}}}{1 + \frac{R_2}{R_1}} \rightarrow F \approx -135$$

$$\underline{\underline{|F| \approx 135}}$$

6a)

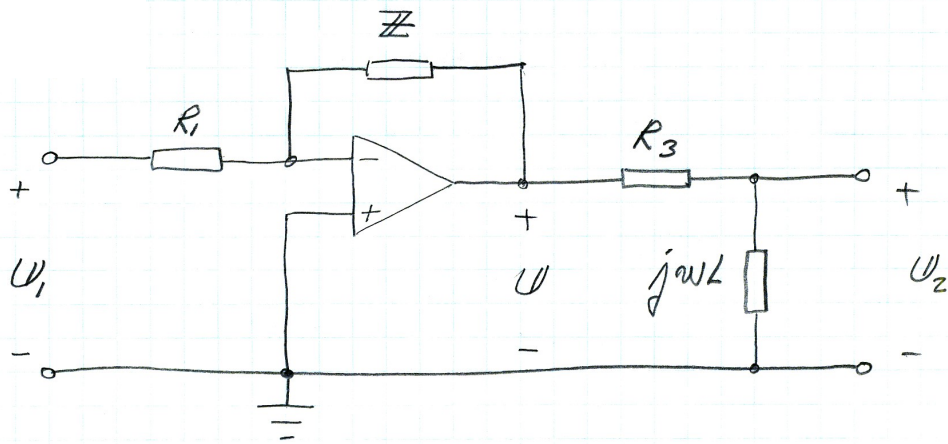

$$\frac{U_2}{U_1} = \frac{U_2}{U} \cdot \frac{U}{U_1} \dots (1)$$

$$U_2 = U \cdot \frac{j\omega L}{R_3 + j\omega L} \Rightarrow \frac{U_2}{U} = \frac{j\omega \cdot \frac{L}{R_3}}{1 + j\omega \cdot \frac{L}{R_3}}$$

$$\Rightarrow \frac{U_2}{U} = \frac{j \frac{\omega}{1587}}{1 + j \frac{\omega}{1587}}$$

$$\frac{U}{U_1} = - \frac{Z}{R_1} \quad \text{DAR} \quad Z = \frac{\frac{1}{j\omega C} \cdot R_2}{\frac{1}{j\omega C} + R_2} =$$

$$= - \frac{R_2}{1 + j\omega C R_2} \Rightarrow \frac{U}{U_1} = - \frac{R_2}{R_1} \cdot \frac{1}{1 + j\omega C R_2}$$

$$\Rightarrow \frac{U}{U_1} = -10 \cdot \frac{1}{1 + j \frac{\omega}{62500}}$$

$$(1) \Rightarrow \frac{U_2}{U_1} = -10 \cdot \frac{1}{1 + j \frac{\omega}{62500}} \cdot \frac{j \frac{\omega}{1587}}{1 + j \frac{\omega}{1587}}$$

6b)


$$\left| \frac{U_2}{U_1} \right| = 10 \cdot \frac{1}{\sqrt{1 + \left(\frac{\omega}{62500}\right)^2}} \cdot \frac{\omega}{1587 \sqrt{1 + \left(\frac{\omega}{1587}\right)^2}}$$

$$\text{OM } \omega \ll 1587 \frac{\text{RAD}}{\text{s}} \Rightarrow \left| \frac{U_2}{U_1} \right| \approx \frac{10}{1587} \cdot \omega$$

$$\text{OM } 1587 \frac{\text{RAD}}{\text{s}} < \omega < 62500 \frac{\text{RAD}}{\text{s}} \Rightarrow \left| \frac{U_2}{U_1} \right| = 10$$

$$\text{OM } \omega \gg 62500 \frac{\text{RAD}}{\text{s}} \Rightarrow \left| \frac{U_2}{U_1} \right| = \frac{625000}{\omega}$$

BODEDIAGRAM (AMPLITUDKURVA)

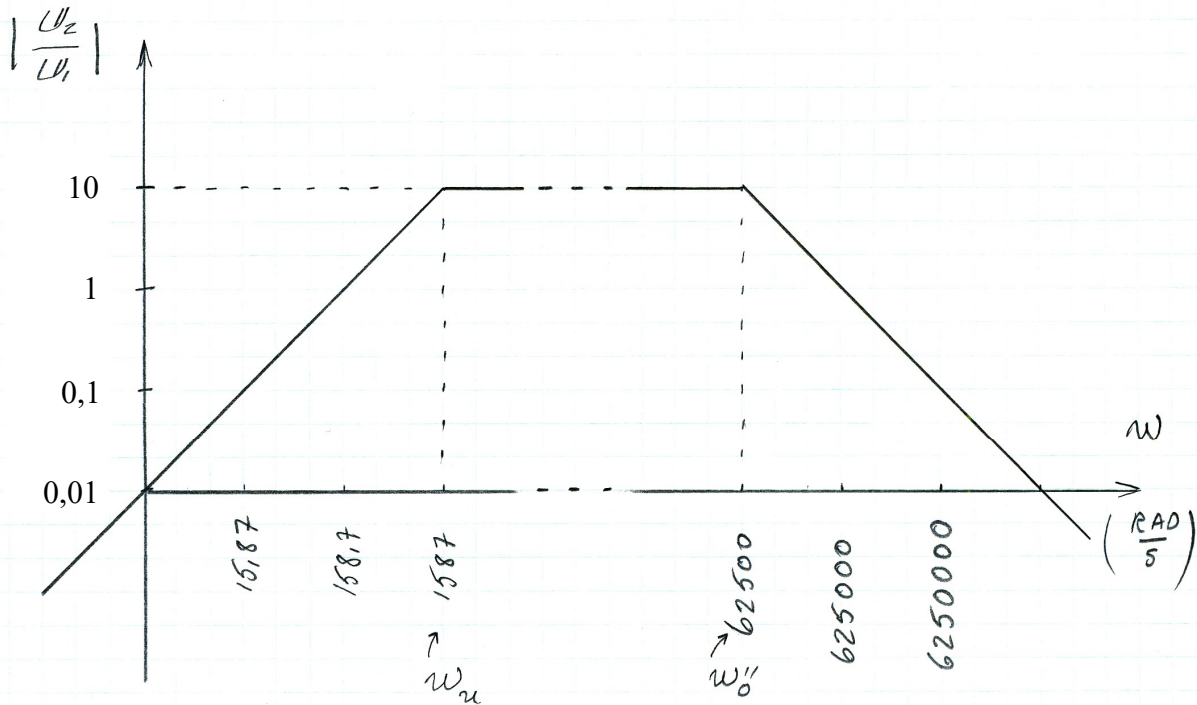

$$\omega_u = 2\pi f_u \Rightarrow \underline{f_u \approx 0,25 \text{ KHz}}$$

$$\omega_o = 2\pi f_o \Rightarrow \underline{f_o \approx 9,9 \text{ KHz}}$$