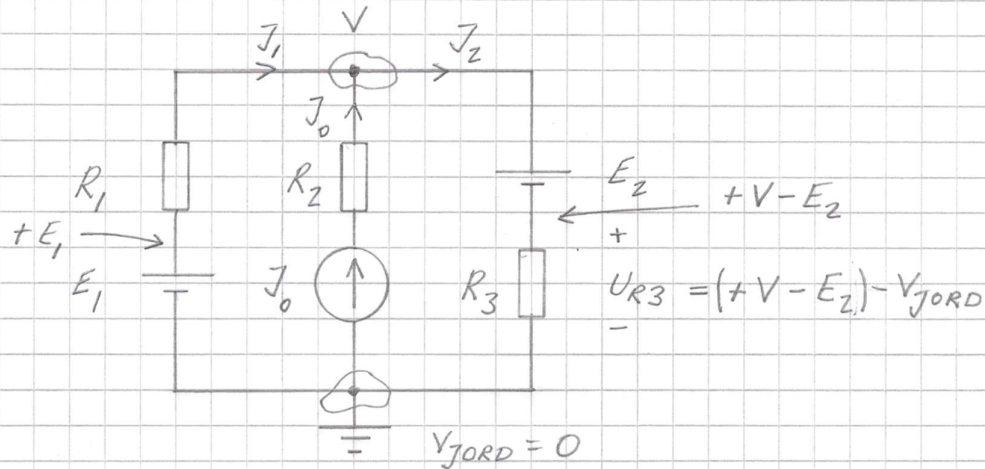


Lösningsförslag till tentamen TMEL08 Eltekniska system 2024-03-15

1. ANVÄND EXEMPELVIS MODANALYS



$$J_1 + J_0 - J_2 = 0 \Rightarrow$$

$$\frac{E_1 - V}{R_1} + J_0 - \frac{(V - E_2) - 0}{R_3} = 0$$


$$\frac{25 - V}{1000} + 0,005 - \frac{V - 10}{1000} = 0$$

$$25 - V + 5 - V + 10 = 0$$

$$V = +20 \text{ V}$$

$$\text{ALLTSA } U_{R3} = (+20 - 10) - 0 = \underline{\underline{10 \text{ V}}}$$

2. Separatmagnetiserad likströmsmotor

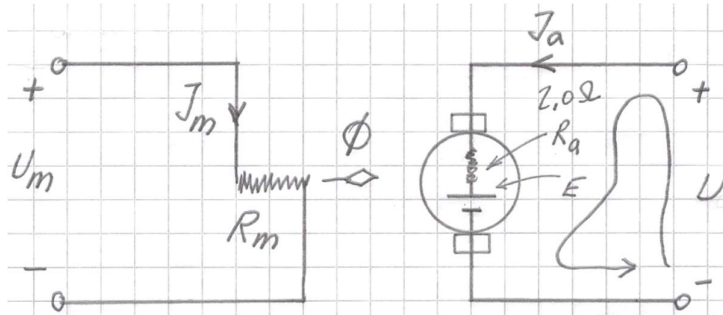

FALL I

$$U_I = 200 \text{ V}$$

$$J_{aI} = 10 \text{ A}$$

$$E_I = ?$$

$$n_I = 1000 \text{ RPM}$$

FALL II

$$U_{II} = 170 \text{ V}$$

$$J_{aII} = ?$$

$$E_{II} = ?$$

$$n_{II} = ?$$

SAMMA MOMENT OCH MAGNETISKT
"FLÖDE" I DE TVÅ FALLEN.

$$\begin{aligned} a) \quad M &= k_2 \Phi J_{aI} \\ M &= k_2 \Phi J_{aII} \end{aligned} \quad \Rightarrow \quad J_{aII} = J_{aI} = \underline{10 \text{ A}}$$


b) KIRCHHOFFS SPÄNNINGSLAG \Rightarrow

$$+U_I - R_a J_{aI} - E_I = 0 \quad \Rightarrow \quad \underline{E_I = 180 \text{ V}}$$

$$+U_{II} - R_a J_{aII} - E_{II} = 0 \quad \Rightarrow \quad \underline{E_{II} = 150 \text{ V}}$$

$$c) \quad \frac{E_I}{E_{II}} = \frac{k_1 \Phi n_I}{k_1 \Phi n_{II}} \quad \Rightarrow \quad \underline{n_{II} = 833 \text{ RPM}}$$

3a)

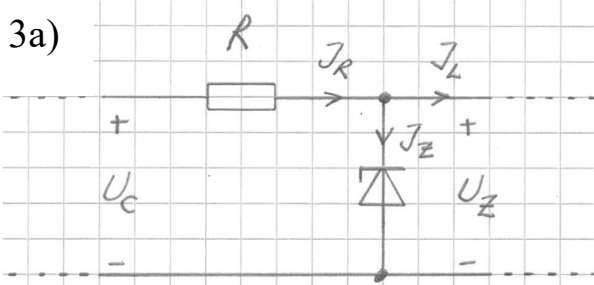

$$R = \frac{U_C - U_Z}{J_R} \quad \text{"DAR"} \quad J_R = J_Z + J_L$$

$$R_{\text{MIN}} = \frac{U_C - U_Z}{J_{R\text{MAX}}} \quad J_{R\text{MAX}} = J_{Z\text{MAX}} \quad \text{DÄ } J_L = 0 \quad (R_L \text{ BORTKOPPLAD})$$

$$P_{Z\text{MAX}} = U_Z J_{Z\text{MAX}} \Rightarrow J_{Z\text{MAX}} = 0,833 \text{ A}$$

\uparrow \uparrow
 10W 12V

$$\Rightarrow R_{\text{MIN}} = \frac{32 - 12}{0,833} = 24 \Omega$$

$$R_{\text{MAX}} = \frac{U_C - U_Z}{J_{R\text{MIN}}} \quad J_{R\text{MIN}} = J_{Z\text{MIN}} + J_{L\text{MAX}}$$


\uparrow \uparrow
 100mA 500mA

$$\Rightarrow R_{\text{MAX}} = \frac{32 - 12}{0,600} = 33 \Omega$$

ALLTSA " VÄLT $24 \Omega < R < 33 \Omega$

3b)

" LIKSTROMSCHEMA

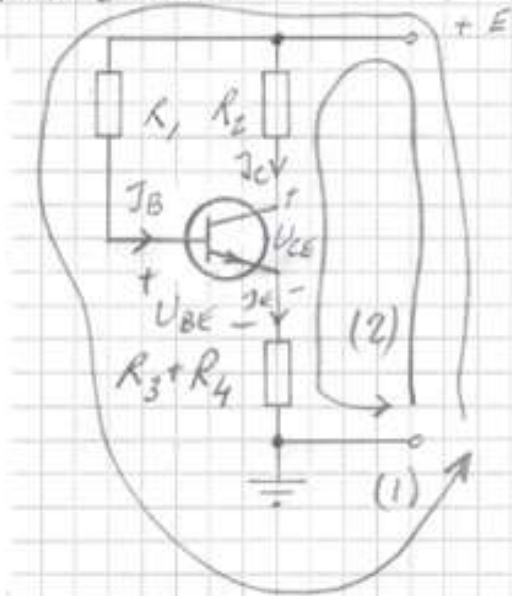

$$h_{FE} = \frac{I_C}{I_B} \Rightarrow I_B = 20 \mu A$$

$$I_E = I_B + I_C \Rightarrow I_E = 4020 \mu A$$

$$+E - R_1 I_B - U_{BE} - (R_3 + R_4) I_E = 0 \dots (1)$$

$$(1) \rightarrow R_1 \approx 0,49 \text{ M}\Omega$$

$$+E - R_2 I_C - U_{CE} - (R_3 + R_4) I_E = 0 \dots (2)$$

$$(2) \rightarrow U_{CE} = 6,4 \text{ V}$$

4a)

$$\frac{N_1}{N_2} = \frac{\hat{U}_1}{\hat{U}_2}$$


$$\hat{U}_2 = U_C + 2 \cdot U_{D100} = 33,4 \text{ V}$$

\uparrow \uparrow
 32V 0,70V

$$\hat{U}_1 = 230\sqrt{2} \text{ V} \Rightarrow$$

$$\frac{N_1}{N_2} = \frac{230\sqrt{2}}{33,4} \approx 9,7$$


4b)

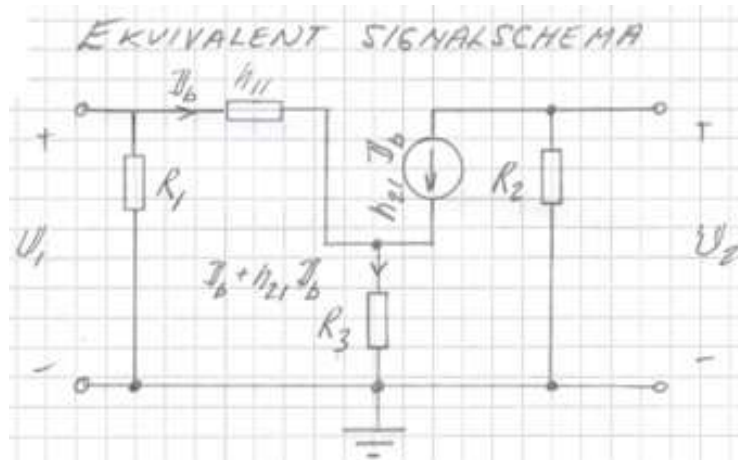

$$F = \frac{U_2}{U_1} = \frac{-h_{21} I_b R_2}{R_3 (I_b + h_{21} I_b) + h_{11} I_b}$$

$$|F| = 50 \Rightarrow R_3 = 10 \Omega \Rightarrow R_4 = 380 \Omega$$

5.

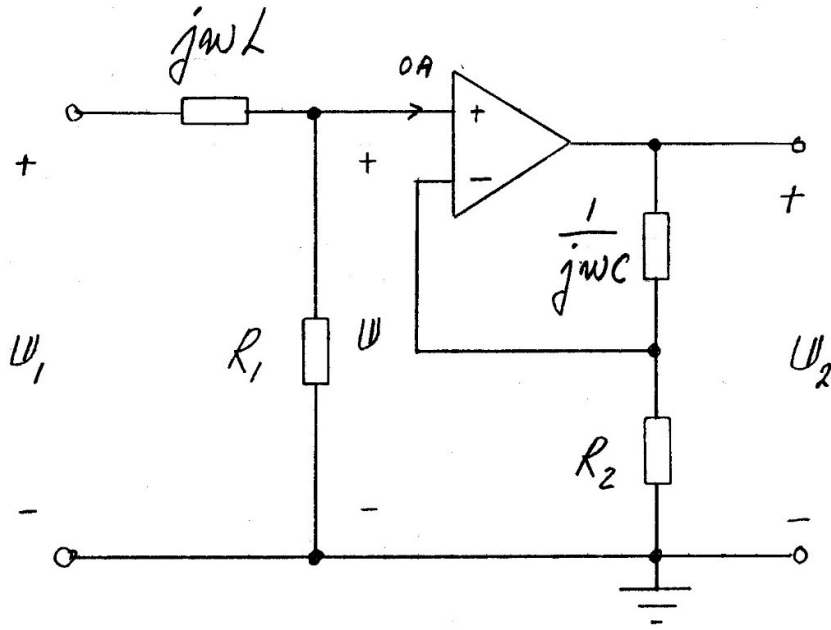

$$U = U_1 \cdot \frac{R_1}{R_1 + j\omega L} = U_1 \cdot \frac{1}{1 + j\omega \frac{L}{R_1}} \dots (1)$$

$$U_2 = U \cdot \frac{\frac{1}{j\omega C} + R_2}{R_2} = U \cdot \frac{1 + j\omega C R_2}{j\omega C R_2} \dots (2)$$

(1) ins , (2) \Rightarrow

$$\frac{U_2}{U_1} = \frac{1 + j\omega C R_2}{(1 + j\omega \frac{L}{R_1}) j\omega C R_2} \Rightarrow$$

$$\left| \frac{U_2}{U_1} \right| = \frac{\sqrt{1^2 + (\omega C R_2)^2}}{\sqrt{1^2 + \left(\omega \cdot \frac{L}{R_1}\right)^2} \cdot \omega C R_2} \Rightarrow$$


$$\left| \frac{U_2}{U_1} \right| = \frac{\sqrt{1^2 + \left(\frac{\omega}{10000} \right)^2}}{\sqrt{1^2 + \left(\frac{\omega}{1000000} \right)^2} \cdot \frac{\omega}{10000}}$$

$$\omega \ll 10000 \rightarrow \left| \frac{U_2}{U_1} \right| \approx \frac{10000}{\omega}$$

$$10000 < \omega < 1000000 \rightarrow \left| \frac{U_2}{U_1} \right| \approx 1$$

$$\omega \gg 1000000 \rightarrow \left| \frac{U_2}{U_1} \right| \approx \frac{1000000}{\omega}$$

AMPLITUD KURVAN :

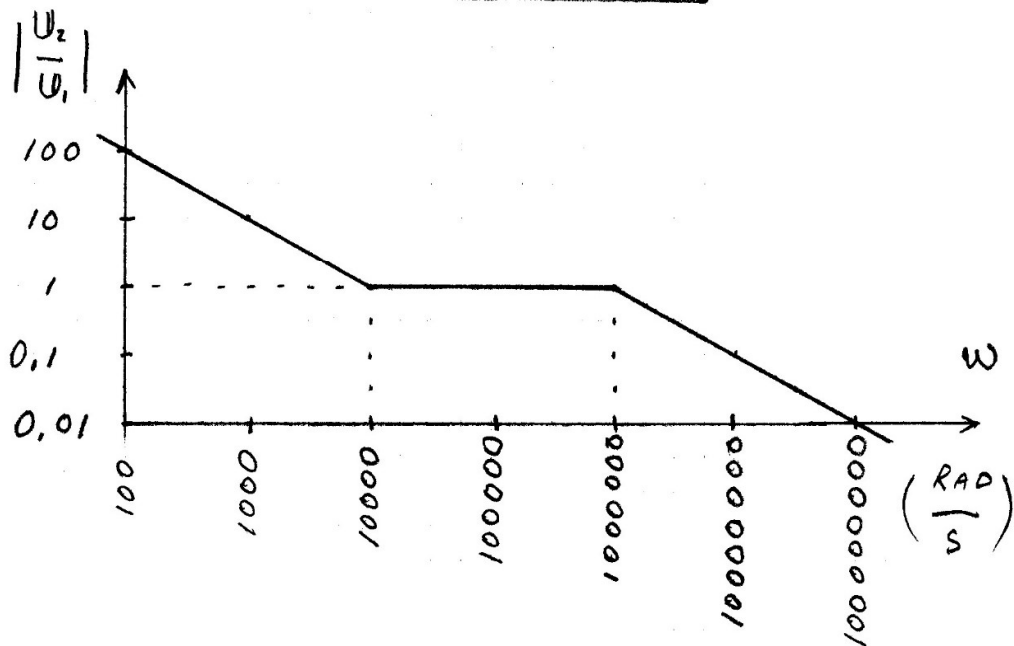



$$\arg U_2 - \arg U_1 = \arg \left(\frac{U_2}{U_1} \right) =$$

$$= \arg \left(\frac{1 + j\omega CR_2}{(1 + j\omega \frac{L}{R_1}) j\omega CR_2} \right) =$$

$$= \underbrace{\arg(1 + j\omega CR_2)}_{\arctan(\omega CR_2)} - \underbrace{\arg(1 + j\omega \frac{L}{R_1})}_{\arctan(\frac{\omega L}{R_1})} - \underbrace{\arg(j\omega CR_2)}_{90^\circ}$$

ω (RAD/s)	$\arg U_2 - \arg U_1$
100	- 89°
1000	- 84°
10000	- 46°
100000	- 11°
1000000	- 46°
10000000	- 84°
100000000	- 89°

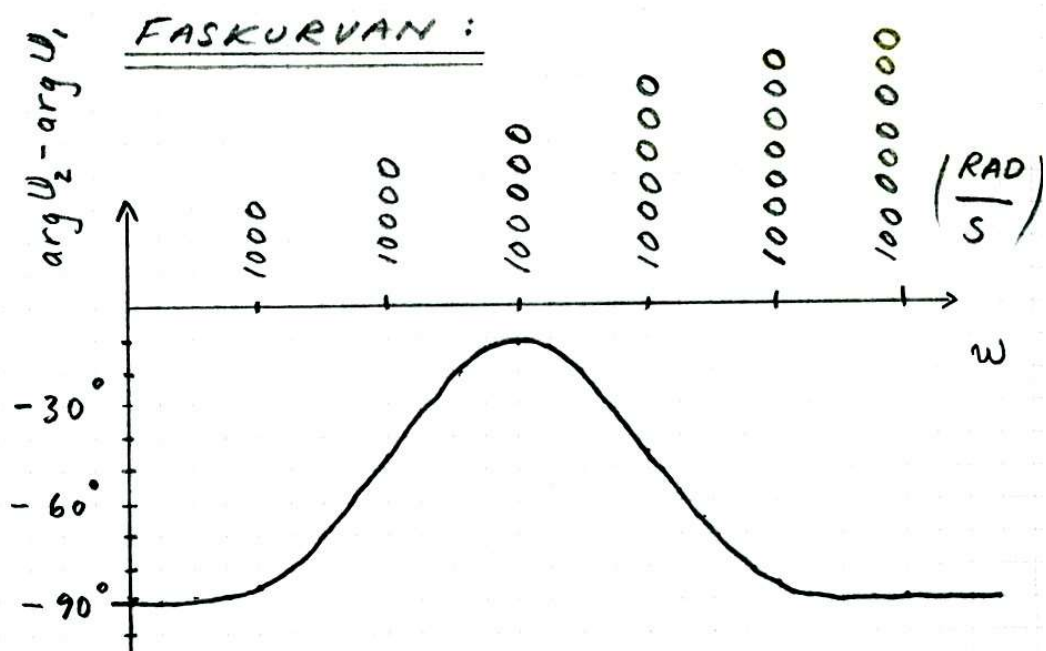

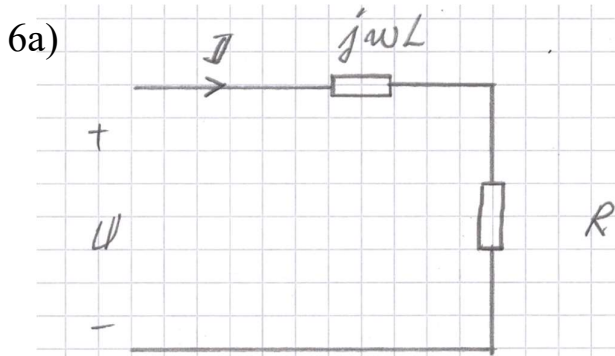

$$u(t) = 230\sqrt{2} \sin(100\pi t + 0^\circ) \text{ V} \rightarrow U = 230\sqrt{2} e^{j0^\circ} \text{ V}$$

$$I = \frac{U}{R + j\omega L} \Rightarrow$$

$$I = \frac{230\sqrt{2} e^{j0^\circ}}{24,0 + j100\pi \cdot 0,0573} =$$

$$= \frac{230\sqrt{2} e^{j0^\circ}}{\sqrt{24^2 + 18^2} \cdot e^{j \arctan \frac{18}{24}}} = 7,67\sqrt{2} e^{-j37^\circ} \text{ A}$$

$$\rightarrow i(t) = 7,67\sqrt{2} \sin(100\pi t - 37^\circ) \text{ A}$$

6b)

$$I = \frac{\hat{I}}{\sqrt{2}} = 7,67 \text{ A}$$

$$P = R I^2 \Rightarrow \underline{P = 1,41 \text{ kW}}$$

(Q_L)

$$Q = X_L I^2 = |X_L = \omega L| = \underline{1,06 \text{ kVAR}}$$

$$S = \sqrt{P^2 + Q^2} \Rightarrow \underline{S = 1,76 \text{ kVA}}$$

ALTERNATIVT SÄTT ATT RÄKNA :

$$P = U \cdot I \cdot \cos \varphi$$

$$(Q_L) Q = U \cdot I \cdot \sin \varphi$$

$$S = U \cdot I$$

$$\varphi = \arg U - \arg I = 37^\circ$$

↑ ↑
0° -37°

$$U = \frac{\hat{U}}{\sqrt{2}} = 230 \text{ V}$$

6c) $Q = Q_L - Q_C$

$$Q = 0 \Rightarrow Q_C = Q_L$$

$$Q_C = \frac{U^2}{X_C} = |X_C| = \frac{1}{\omega C} \Rightarrow U^2 \omega C$$

$$1,06 \cdot 10^3 = 230^2 \cdot 100\pi \cdot C \Rightarrow \underline{C = 63,7 \mu\text{F}}$$

6d) $Q = 0 \Rightarrow S = P$ och $\cos \varphi = 1 \Rightarrow \varphi = 0^\circ$

$$S = U \cdot I \Rightarrow 1,41 \cdot 10^3 = 230 \cdot I$$

$$\Rightarrow I = 6,13 \text{ A} \quad \hat{I} = 6,13 \sqrt{2} \text{ A}$$

$$\Rightarrow \underline{i(t) = 6,13 \sqrt{2} \sin(100\pi t) \text{ A}}$$

($\varphi = 0^\circ$ INNEBÄR ATT $\arg I = \arg U$)