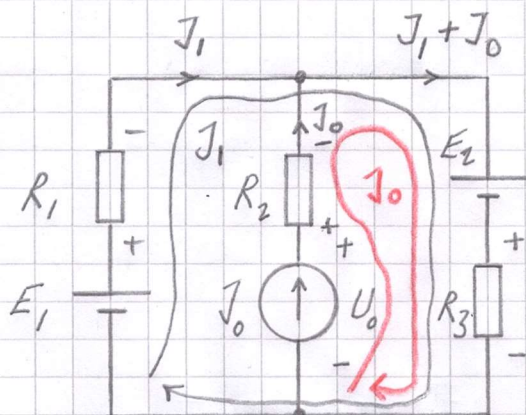


Lösningsförslag till tentamen TMEL08 Eltekniska system 2024-10-28

1.

ANVÄND EXEMPELVIS SLINGANALYS:



$$+ E_1 - R_1 J_1 - E_2 - R_3 (J_1 + J_0) = 0 \quad \dots (1)$$

$$+ U_0 - R_2 J_0 - E_2 - R_3 (J_1 + J_0) = 0 \quad \dots (2)$$


$$+ 25 - 1000 J_1 - 10 - 1000 (J_1 + 0,005) = 0 \quad \dots (1)$$

$$+ U_0 - 1000 \cdot 0,005 - 10 - 1000 (J_1 + 0,005) = 0 \quad \dots (2)$$

$$(1) \Rightarrow J_1 = 0,005 \text{ A}$$

$$(2) \Rightarrow \underline{U_0 = 25 \text{ V}}$$

2.

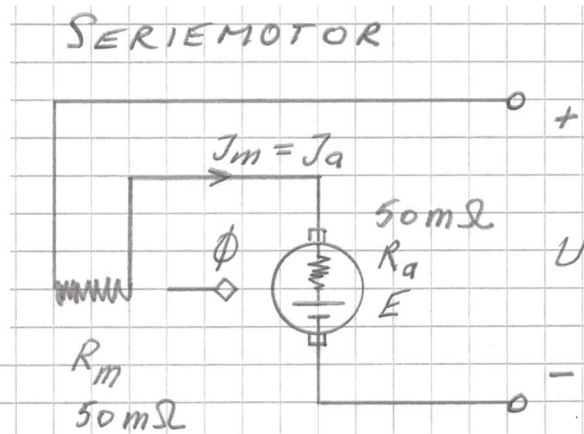

MAGNETISKT OMÄTTAD

$$\Rightarrow \Phi = k J_m = k J_a$$

FALL I

$$U_I = 220 \text{ V}$$

$$n_I = 1000 \text{ RPM}$$

$$M_I = M$$

$$J_{aI} = 100 \text{ A}$$

FALL II

$$U_{II} = 220 \text{ V}$$

$$n_{II} = ?$$

$$M_{II} = 4M$$

$$J_{aII} = ?$$

$$\frac{M_I}{M_{II}} = \frac{k_2 \Phi_I J_{aI}}{k_2 \Phi_{II} \cdot J_{aII}}$$

$$\frac{M}{4M} = \frac{k_2 \cdot k J_{aI} \cdot J_{aI}}{k_2 \cdot k J_{aII} \cdot J_{aII}}$$

$$\frac{1}{4} = \frac{J_{aI}^2}{J_{aII}^2} \Rightarrow \underline{\underline{J_{aII} = 200 \text{ A}}}$$

KIRCHHOFFS SPANNUNGSZUG

$$\text{FALL I} \Rightarrow +U_I - R_m J_{aI} - R_a J_{aI} - E_I = 0$$

$$\text{FALL II} \Rightarrow +U_{II} - R_m J_{aII} - R_a J_{aII} - E_{II} = 0$$


$$\Rightarrow E_I = 210 \text{ V} \quad E_{II} = 200 \text{ V}$$

$$\frac{E_I}{E_{II}} = \frac{k_1 \Phi_I n_I}{k_1 \Phi_{II} n_{II}}$$

$$\frac{E_I}{E_{II}} = \frac{k_1 k J_{aI} n_I}{k_1 k J_{aII} n_{II}}$$

$$\frac{E_I}{E_{II}} = \frac{J_{aI} n_I}{J_{aII} n_{II}} \Rightarrow \underline{n_{II} = 476 \text{ RPM}}$$

3a)

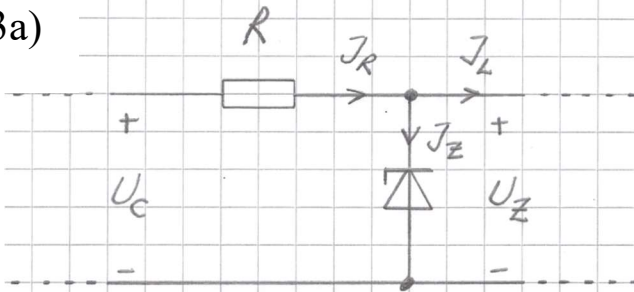

$$R = \frac{U_C - U_Z}{I_R} \quad \text{"DAR"} \quad I_R = I_Z + I_L$$

$$R_{\min} = \frac{U_C - U_Z}{I_{R\max}} \quad I_{R\max} = I_{Z\max} \quad \text{DÄ } I_L = 0 \quad (R_L \text{ BORTKOPPLAD})$$

$$P_{Z\max} = U_Z I_{Z\max} \Rightarrow I_{Z\max} = 0,833 \text{ A}$$

$\uparrow$ $\uparrow$
 10W 12V

$$\Rightarrow R_{\min} = \frac{32 - 12}{0,833} = 24 \Omega$$

$$R_{\max} = \frac{U_C - U_Z}{I_{R\min}} \quad I_{R\min} = I_{Z\min} + I_{L\max}$$


$\uparrow$ $\uparrow$
 100mA 500mA

$$\Rightarrow R_{\max} = \frac{32 - 12}{0,600} = 33 \Omega$$

ALLTSA " VÄLT $24 \Omega < R < 33 \Omega$

3b)

LIKSTROMSSHEMA

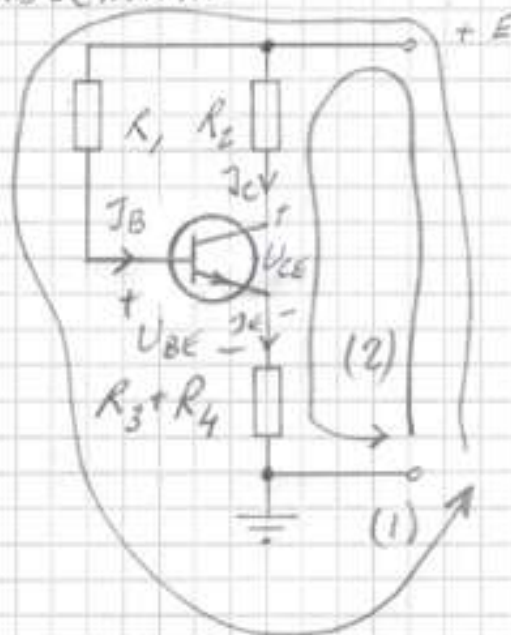

$$h_{FE} = \frac{I_C}{I_B} \Rightarrow I_B = 20 \mu A$$

$$I_E = I_B + I_C \Rightarrow I_E = 4020 \mu A$$

$$+E - R_1 I_B - U_{BE} - (R_3 + R_4) I_E = 0 \dots (1)$$

$$(1) \rightarrow R_1 \approx 0,49 M\Omega$$

$$+E - R_2 I_C - U_{CE} - (R_3 + R_4) I_E = 0 \dots (2)$$

$$(2) \rightarrow U_{CE} = 6,4 V$$

4a)

$$\frac{N_1}{N_2} = \frac{\hat{U}_1}{\hat{U}_2}$$


$$\hat{U}_2 = U_c + 2 \cdot U_{D100} = 33,4 \text{ V}$$

$\uparrow \quad \quad \quad \uparrow$
 $32 \text{ V} \quad 0,70 \text{ V}$

$$\hat{U}_1 = 230 \sqrt{2} \text{ V} \Rightarrow$$

$$\frac{N_1}{N_2} = \frac{230 \sqrt{2}}{33,4} \approx 9,7$$


4b)

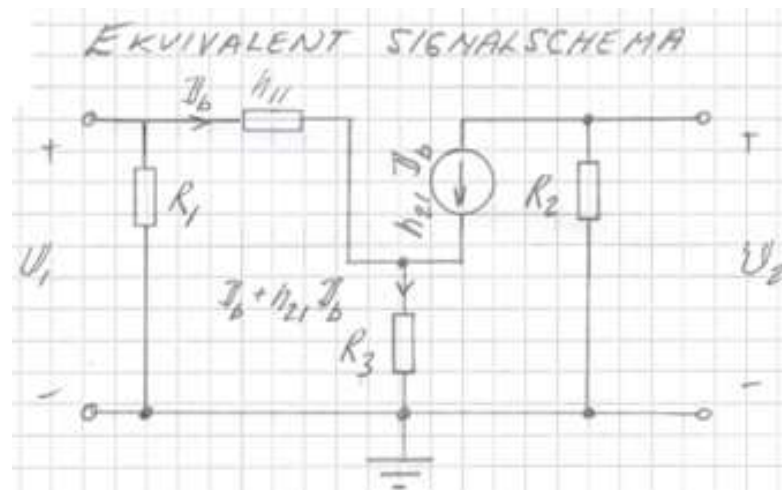

$$F = \frac{U_2}{U_1} = \frac{-h_{21} I_b R_2}{R_3 (I_b + h_{21} I_b) + h_{11} I_b}$$

$$|F| = 50 \Rightarrow \underline{R_3 = 10 \Omega} \Rightarrow \underline{R_4 = 380 \Omega}$$

5a)

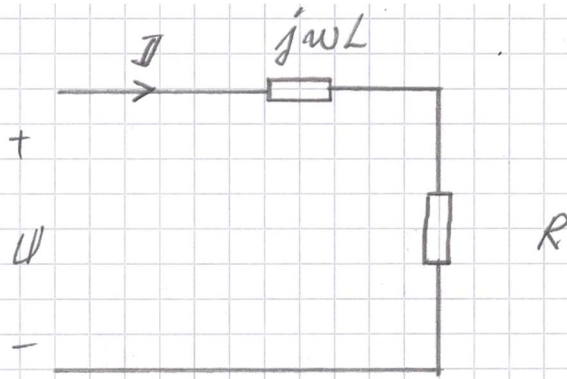

$$u(t) = 230\sqrt{2} \sin(100\pi t + 0^\circ) \text{ V} \rightarrow U = 230\sqrt{2} e^{j0^\circ} \text{ V}$$

$$I = \frac{U}{R + j\omega L} \Rightarrow$$

$$I = \frac{230\sqrt{2} e^{j0^\circ}}{24,0 + j100\pi \cdot 0,0593} =$$

$$= \frac{230\sqrt{2} e^{j0^\circ}}{\sqrt{24^2 + 18^2} \cdot e^{j \arctan \frac{18}{24}}} = 7,67\sqrt{2} e^{-j37^\circ} \text{ A}$$

$$\rightarrow i(t) = 7,67\sqrt{2} \sin(100\pi t - 37^\circ) \text{ A}$$

5b)

$$I = \frac{\hat{I}}{\sqrt{2}} = 7,67 \text{ A}$$

$$P = R I^2 \Rightarrow \underline{P = 1,41 \text{ kW}}$$

(Q_L)

$$Q = X_L I^2 = |X_L| = \omega L = \underline{1,06 \text{ kVAR}}$$

$$S = \sqrt{P^2 + Q^2} \Rightarrow \underline{S = 1,76 \text{ kVA}}$$

ALTERNATIVT SÄTT ATT RÄKNA :

$$P = U \cdot I \cdot \cos \varphi$$

$$(Q_L) Q = U \cdot I \cdot \sin \varphi$$

$$S = U \cdot I$$

$$\varphi = \arg U - \arg I = 37^\circ$$

$\uparrow \quad \quad \uparrow$
 $0^\circ \quad -37^\circ$

$$U = \frac{\hat{U}}{\sqrt{2}} = 230 \text{ V}$$

5c)

$$Q = Q_L - Q_C$$

$$Q = 0 \Rightarrow Q_C = Q_L$$

$$Q_C = \frac{U^2}{X_C} = \frac{1}{\omega C} = U^2 \omega C$$

$$1,06 \cdot 10^3 = 230^2 \cdot 100\pi \cdot C \Rightarrow \underline{C = 63,7 \mu\text{F}}$$

5d)

$$Q = 0 \Rightarrow S = P \text{ och } \cos \varphi = 1 \Rightarrow \varphi = 0^\circ$$


$$S = U \cdot I \Rightarrow 1,41 \cdot 10^3 = 230 \cdot I$$

$$\Rightarrow I = 6,13 \text{ A} \quad \hat{I} = 6,13 \sqrt{2} \text{ A}$$

$$\Rightarrow \underline{i(t) = 6,13 \sqrt{2} \sin(100\pi t) \text{ A}}$$

$$(\varphi = 0^\circ \text{ INNEBÄR ATT } \arg I = \arg U)$$

6.

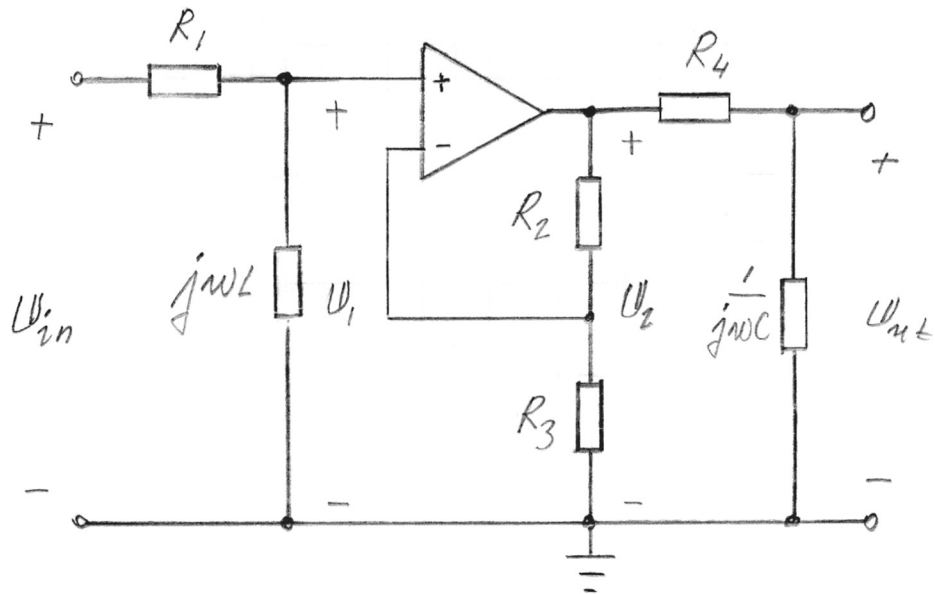

$$\frac{U_{ut}}{U_{in}} = \frac{U_{ut}}{U_2} \cdot \frac{U_2}{U_1} \cdot \frac{U_1}{U_{in}}$$

$$\frac{U_{ut}}{U_2} = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R_4} = \frac{1}{1 + j\omega C R_4}$$

$$\frac{U_2}{U_1} = \frac{R_2 + R_3}{R_3}$$

$$\frac{U_1}{U_{in}} = \frac{j\omega L}{R_1 + j\omega L} = \frac{j\omega \cdot \frac{L}{R_1}}{1 + j\omega \cdot \frac{L}{R_1}}$$

$$\Rightarrow \frac{U_{ut}}{U_{in}} = \frac{j \frac{\omega}{100}}{1 + j \frac{\omega}{100}} \cdot 2,5 \cdot \frac{1}{1 + j \frac{\omega}{10000}}$$

$$\left| \frac{U_{ut}}{U_{in}} \right| = 2,5 \cdot \frac{\frac{\omega}{100}}{\sqrt{1 + \left(\frac{\omega}{100}\right)^2} \sqrt{1 + \left(\frac{\omega}{10000}\right)^2}}$$

$$\omega \ll 100 \frac{\text{RAD}}{\text{s}} \Rightarrow \left| \frac{U_{ut}}{U_{in}} \right| \approx 2,5 \cdot \frac{\omega}{100}$$

$$100 \frac{\text{RAD}}{\text{s}} < \omega < 10000 \frac{\text{RAD}}{\text{s}} \Rightarrow \left| \frac{U_{ut}}{U_{in}} \right| \approx 2,5$$

$$\omega \gg 10000 \frac{\text{RAD}}{\text{s}} \Rightarrow \left| \frac{U_{ut}}{U_{in}} \right| \approx 2,5 \cdot \frac{10000}{\omega}$$

BODEDIAGRAM (AMPLITUDKURVA)

