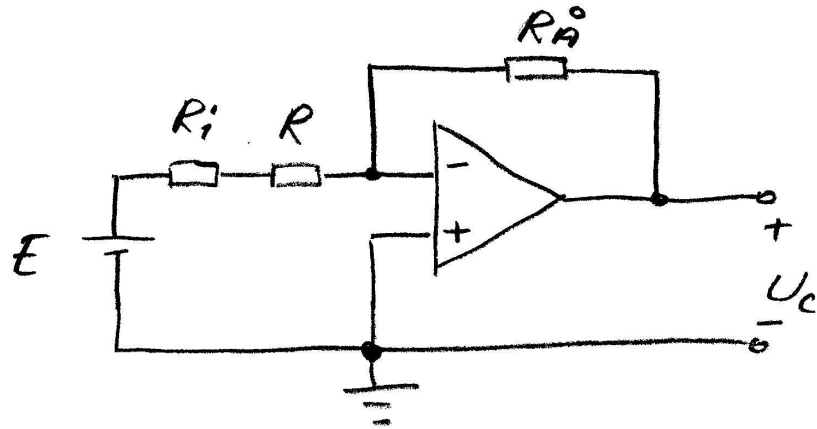


F1.3



$$\frac{U_c}{E} = - \frac{R_A}{R_i + R}$$

$$E = 12,5 \text{ mV}$$

$$R_i = 600 \Omega$$

$$R = 2,4 \text{ k}\Omega$$

$$R_A = 240 \text{ k}\Omega$$

$$\Rightarrow U_c = \underline{\underline{-1,0 \text{ V}}}$$