

TSEA26 Tutorial 4. Design of Program Control Flow Units


Frans Skarman ¹

November 29, 2021

¹based on material by Oscar Gustafsson, Dake Liu, Olle Seger, Andreas Ehliar, and Jian Wang


Program Flow Control Unit

 - ▶ Choose which instruction to execute next
- ▶ Easy in theory, harder in practice
 - ▶ Hardware repeat
 - ▶ Conditional jumps
 - ▶ Call/return
 - ▶ ...
- ▶ PFC needs to
 - ▶ Flush pipeline
 - ▶ Insert nops
 - ▶ Handle delay slots
 - ▶ ...



A pipelined CPU

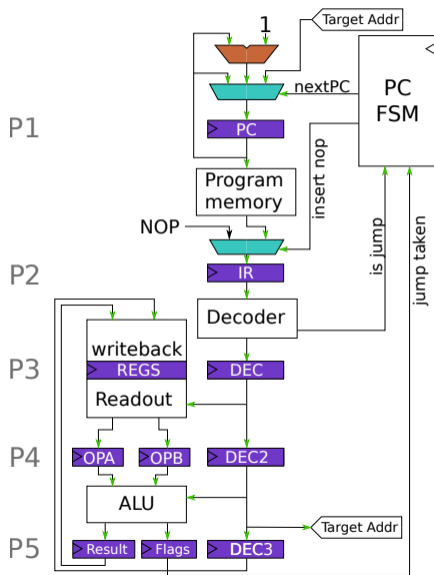
- ▶ Similar to senior
- ▶ PC FSM controls behaviour during jumps
 - ▶ When to insert NOPs
 - ▶ When to Stall
- ▶ Inputs:
 - ▶ **is jump** is next insn. a jump? If so which kind?
 - ▶ **jump taken** should this conditional jump be executed?
- ▶ Outputs:
 - ▶ **insert nop** replace current insn. with nop?
 - ▶ **nextPC** next PC = target address, ++ or stall



PC fsm example

Try running through the following program

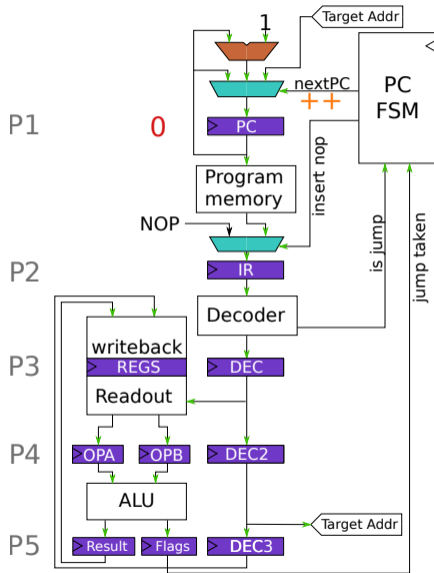
```
pc  
0:  add r0, r1, r2  
1:  jump.eq 9  
2:  xxx
```



PC fsm example

Try running through the following program

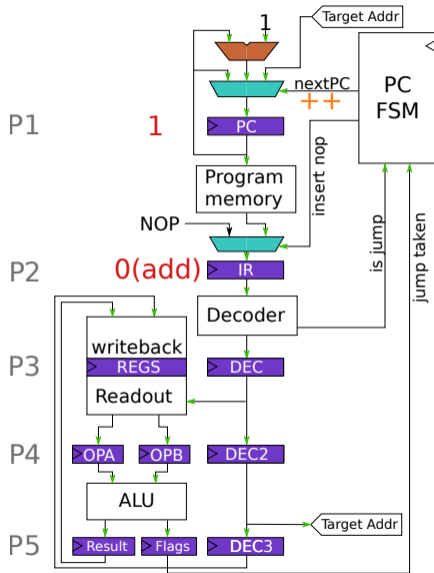
```
pc  
0:  add r0, r1, r2  
1:  jump.eq 9  
2:  xxx
```



PC fsm example

Try running through the following program

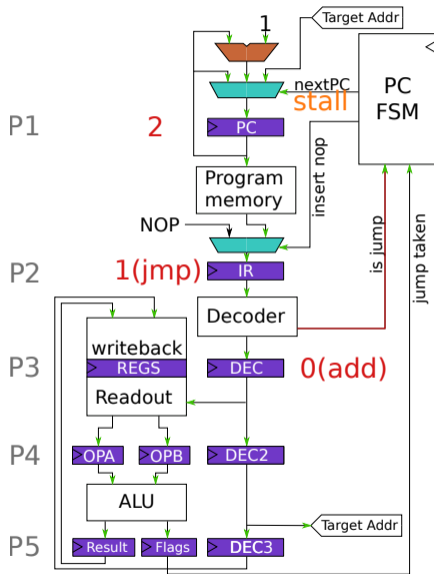
```
pc  
0:  add r0, r1, r2  
1:  jump.eq 9  
2:  xxx
```



PC fsm example

Try running through the following program

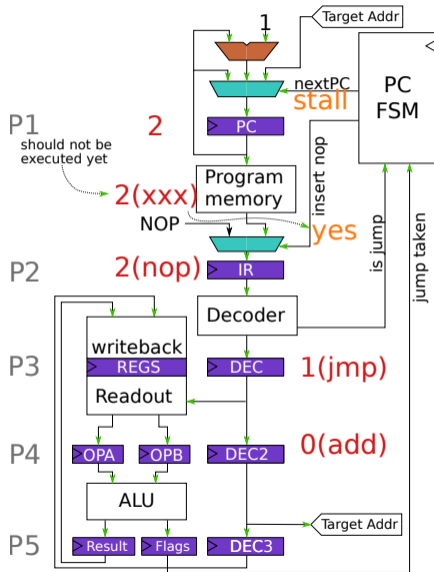
```
pc  
0:  add r0, r1, r2  
1:  jump.eq 9  
2:  xxx
```



PC fsm example

Try running through the following program

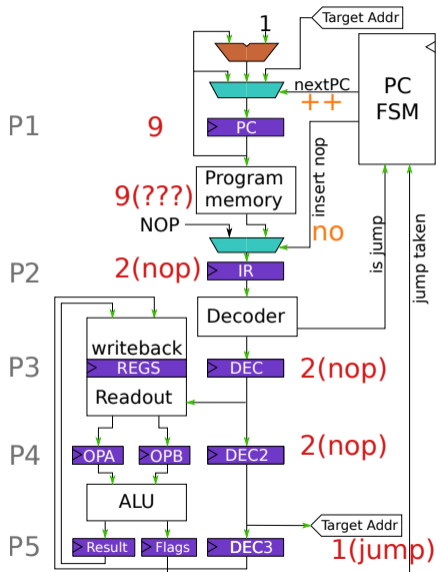
```
pc  
0:  add r0, r1, r2  
1:  jump.eq 9  
2:  xxx
```



PC fsm example

Try running through the following program
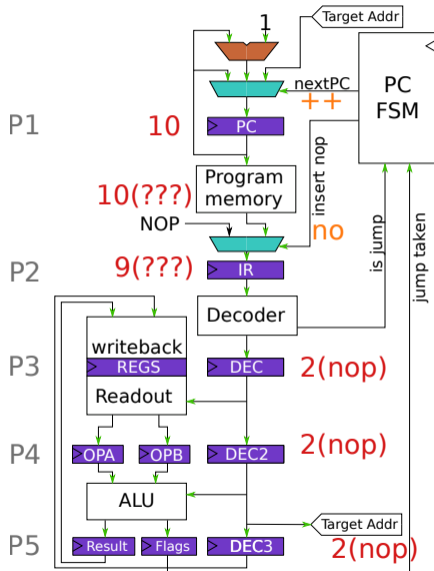
```
pc
0:  add r0, r1, r2
1:  jump.eq 9
2:  xxx
```




Pipeline table

- ▶ Helpful tool to figure out when and where to set PFC signals
- ▶ Each column represents a pipeline stage or a signal


<i>nextPC</i>	P1	<i>PM</i>	<i>nop?</i>	P2	P3	P4	P5
++	0	add	no				
++	1	jmp		0(add)			
	2	xxx		1(jmp)	0(add)		
	2	xxx		nop	1(jmp)	0(add)	
	2	xxx		nop	nop	1(jmp)	0(add)
++	9	9(aaa)	no	nop	nop	nop	1(jmp)
++	10	10(bbb)	no	9(bbb)	nop	nop	nop

Pipeline table

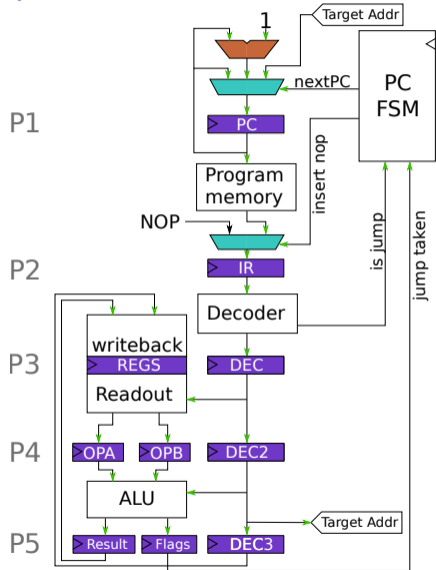


<i>nextPC</i>	P1	PM	<i>nop?</i>	P2	P3	P4	P5
++	0	add	no				

Pipeline table

 


<i>nextPC</i>	P1	PM	<i>nop?</i>	P2	P3	P4	P5
++	0	add	no				
++	1	jmp	no	0(add)			

Pipeline table

 


<i>nextPC</i>	P1	<i>PM</i>	<i>nop?</i>	P2	P3	P4	P5
++	0	add	no				
++	1	jmp	no	0(add)			

Pipeline table

 


<i>nextPC</i>	P1	PM	<i>nop?</i>	P2	P3	P4	P5
++	0	add	no				
++	1	jmp	no	0(add)			
	2	xxx		1(jmp)	0(add)		

Pipeline table

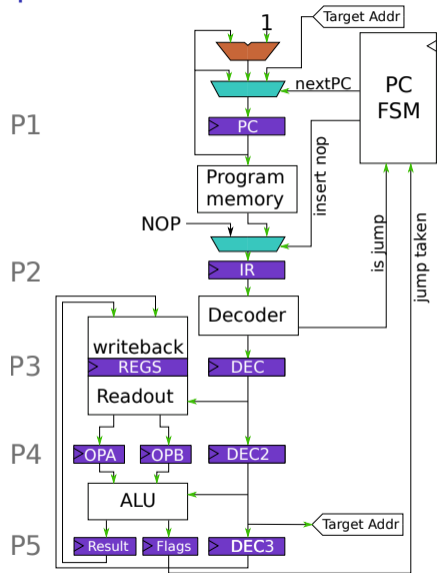


<i>nextPC</i>	P1	PM	<i>nop?</i>	P2	P3	P4	P5
++	0	add	no				
++	1	jmp	no	0(add)			
stall	2	xxx		1(jmp)	0(add)		

Pipeline table

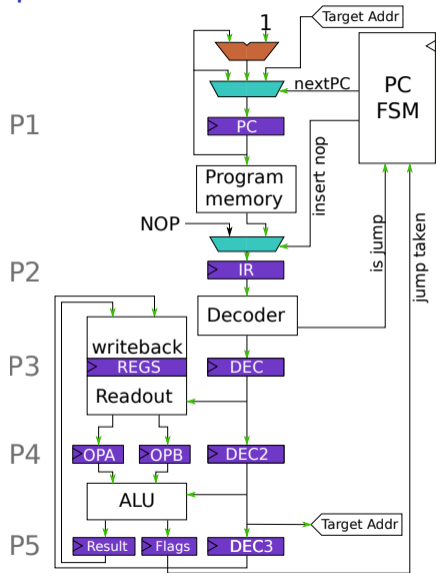


<i>nextPC</i>	P1	PM	<i>nop?</i>	P2	P3	P4	P5
++	0	add	no				
++	1	jmp	no	0(add)			
stall	2	xxx	yes	1(jmp)	0(add)		

Pipeline table

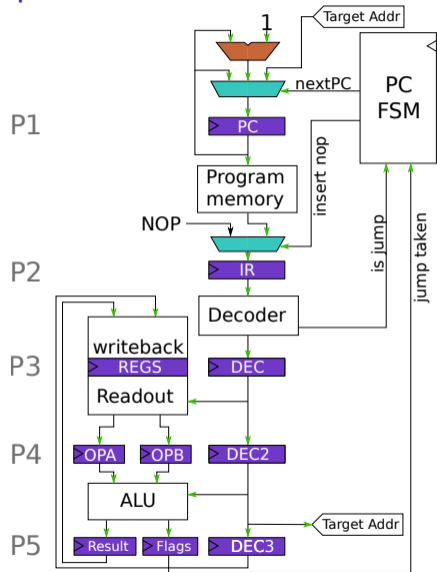


<i>nextPC</i>	P1	PM	<i>nop?</i>	P2	P3	P4	P5
++	0	add	no				
++	1	jmp	no	0(add)			
stall	2	xxx	yes	1(jmp)	0(add)		
	2	xxx		nop	1(jmp)	0(add)	

Pipeline table

 


<i>nextPC</i>	P1	PM	<i>nop?</i>	P2	P3	P4	P5
++	0	add	no				
++	1	jmp	no	0(add)			
stall	2	xxx	yes	1(jmp)	0(add)		
stall	2	xxx		nop	1(jmp)	0(add)	

Pipeline table

 


<i>nextPC</i>	P1	PM	<i>nop?</i>	P2	P3	P4	P5
++	0	add	no				
++	1	jmp	no	0(add)			
stall	2	xxx	yes	1(jmp)	0(add)		
stall	2	xxx	yes	nop	1(jmp)	0(add)	

Pipeline table

 


<i>nextPC</i>	P1	PM	<i>nop?</i>	P2	P3	P4	P5
++	0	add	no				
++	1	jmp	no	0(add)			
stall	2	xxx	yes	1(jmp)	0(add)		
stall	2	xxx	yes	nop	1(jmp)	0(add)	
	2	xxx		nop	nop	1(jmp)	0(add)

Pipeline table

 


<i>nextPC</i>	P1	PM	<i>nop?</i>	P2	P3	P4	P5
++	0	add	no				
++	1	jmp	no	0(add)			
stall	2	xxx	yes	1(jmp)	0(add)		
stall	2	xxx	yes	nop	1(jmp)	0(add)	
TA	2	xxx		nop	nop	1(jmp)	0(add)

Pipeline table

 


<i>nextPC</i>	P1	PM	<i>nop?</i>	P2	P3	P4	P5
++	0	add	no				
++	1	jmp	no	0(add)			
stall	2	xxx	yes	1(jmp)	0(add)		
stall	2	xxx	yes	nop	1(jmp)	0(add)	
TA	2	xxx	yes	nop	nop	1(jmp)	0(add)

Pipeline table

 

<i>nextPC</i>	P1	PM	<i>nop?</i>	P2	P3	P4	P5
++	0	add	no				
++	1	jmp	no	0(add)			
stall	2	xxx	yes	1(jmp)	0(add)		
stall	2	xxx	yes	nop	1(jmp)	0(add)	
TA	2	xxx	yes	nop	nop	1(jmp)	0(add)
++	9	9(aaa)	no	nop	nop	nop	1(jmp)

Pipeline table

 


<i>nextPC</i>	P1	<i>PM</i>	<i>nop?</i>	P2	P3	P4	P5
++	0	add	no				
++	1	jmp	no	0(add)			
stall	2	xxx	yes	1(jmp)	0(add)		
stall	2	xxx	yes	nop	1(jmp)	0(add)	
TA	2	xxx	yes	nop	nop	1(jmp)	0(add)
++	9	9(aaa)	no	nop	nop	nop	1(jmp)
++	10	10(bbb)	no	9(bbb)	nop	nop	nop

Finite state machines


Used in the PCF unit to set the appropriate control signals. State depends on where jump is in pipeline and delay slots

- ▶ Can be Moore
 - ▶ Output only depends on current state
 - ▶ Output is delayed 1 cycle
- ▶ Or Mealy
 - ▶ Output is function of state and input
 - ▶ Can react instantly
 - ▶ But you can create combinatorial loops
- ▶ We want quick reaction to jump instructions
- ▶ \Rightarrow Mealy

PC FSM State graph

 

With delay slots

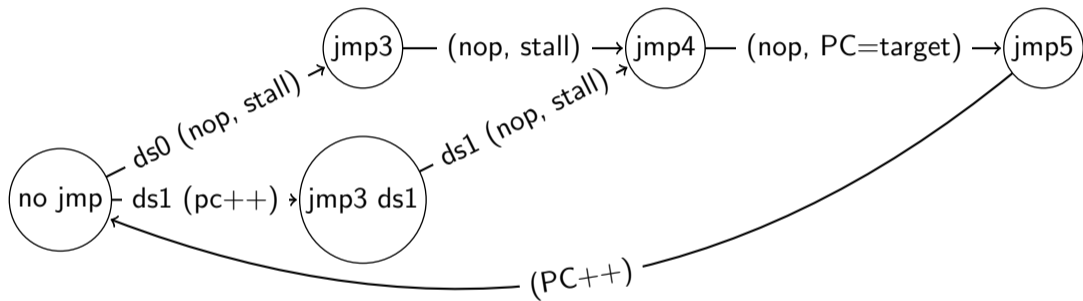

Speculative execution

- ▶ Jumps have a lot of overhead, 3 cycles from start to finish
- ▶ Speculative execution can help
- ▶ Branch prediction
 - ▶ "Guess" the outcome of a branch
 - ▶ Statically try to predict result based on heuristics
 - ▶ Dynamically try to predict result based on history
 - ▶ ...
- ▶ Branch target prediction
 - ▶ Guess the branch of the target before it's known/calculated
- ▶ Return address buffering
 - ▶ Keep a small stack of return addresses in registers
 - ▶ And the rest in main memory
- ▶ Be weary of security issues (spectre, meltdown)
- ▶ Not part of the course

Exercises

- ▶ Exercise 4.1 and 4.3