

A short introduction to SystemVerilog

- For those who know VHDL
- We aim for synthesis

Verilog & SystemVerilog

- 1984 – Verilog invented, C-like syntax
 - First standard – Verilog 95
 - Extra features – Verilog 2001
 - A super set - SystemVerilog
- ← VHDL


www.vhdl.org/sv/SystemVerilog_3.1a.pdf




**SystemVerilog 3.1a
Language Reference Manual**

Accellera's Extensions to Verilog®

Verilog vs VHDL

 

SystemVerilog

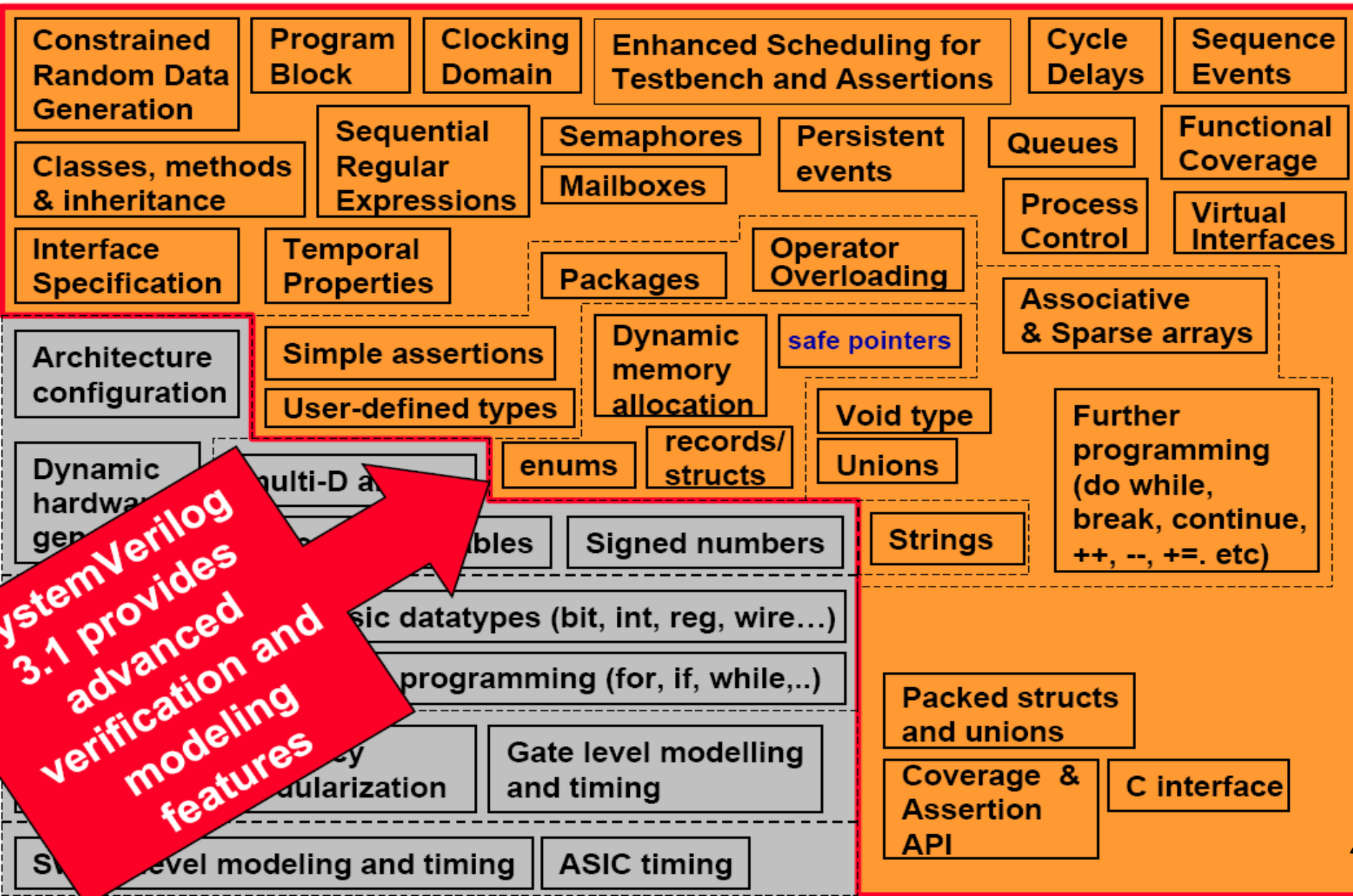


An example: PN check digit

A **PN** consists of 10 digits

$$\textcircled{d_1 d_2 d_3 d_4 d_5 d_6 d_7 d_8 d_9} \rightarrow d_{10}$$

d_{10} is a check digit computed by the algorithm

$$d_{10} = (10 - (d_1 + [2d_2] + d_3 + \dots + d_9)) \bmod 10$$

 
 digit sum

$$S^{(0)} = 0$$

$$S^{(k)} = S^{(k-1)} \oplus_{10} X 2(d_k) \quad k = 1 \dots 9$$

$$d_{10} = 10 - S_9$$


We want to design the block PNR

 

Top module

```
`include "timescale.v"

 module pnr(input clk, rst, stb,
           input [3:0] kb,
           output [3:0] u);
```




``timescale 1ns / 1ps`

time unit precision

```
// our design
```

```
endmodule
```

 * No entity/architecture distinction => just module



schematics

- Green boxes: synch FSM
- White boxes: Comb
- button is singlepulsed

Synch and Single Pulse

```
reg x,y;          // variable type  (0,1,Z,X)
wire button;      // net type  (0,1,Z,X)
```

```
// SSP
```


```
always @(posedge clk)          // procedural block
begin
```

```
    x <= stb;
```

```
    y <= x;
```

```
end
```
 
```
assign button = x & ~y;        //continuous assignment
```



Is this the same thing?

```
reg x,y;      // variable type  (0,1,Z,X)
wire button;  // net type  (0,1,Z,X)
```

```
// SSP
```


```
always @(posedge clk)
begin
    x <= stb;
end
```

```
// procedural block
```

```
always @(posedge clk)
begin
    y <= x;
end
```

```
// procedural block
```

```
assign button = x & ~y;
```

 

One more thing


```
// This is OK
always @(posedge clk)
begin
    x <= stb;
    if (rst)
        x <= 0;
end

// same as
always @(posedge clk)
begin
    if (rst)
        x <= 0;
    else
        x <= stb;
end
```

```
// This is not OK
// multiple assignment
always @(posedge clk)
begin
    x <= stb;
end

always @(posedge clk)
begin
    if (rst)
        x <= 0;
end
```

SV: ~~always_{comb, ff, latch}~~

 

```
// forgot else branch
// a synthesis warning
```

```
always @(a or b)
    if (b) c = a;
```

```
// compilation error
```

```
always_comb
```

```
    if (b)
        c = a;
```

```
// yes
```

```
always_comb
```

```
    if (b)
        c = a;
    else
        c = d;
```

- **always** blocks do not guarantee capture of intent
- If not edge-sensitive then only a warning if latch inferred
- **always_comb**, **always_latch** and **always_ff** are explicit
- Compiler Now Knows User Intent and can flag errors accordingly


decade counter

```
reg [3:0]    p;
wire         odd,last;

// 10 counter
always_ff @(posedge clk) begin
    if (rst)
        p <= 4'd0;
    else begin
        if (button)
            if (p<9)
                p <= p+1;
            else
                p <= 4'd0;
    end
end

assign odd = ~p[0];
assign last = (p==4'h9) ? 1'b1 : 1'b0;
```


X2

 

```
always_comb begin
    if (odd)
        case (d)
            4'h0:
                d2 = 4'h0;
            4'h1:
                d2 = 4'h2;
            4'h3:
                d2 = 4'h6;
            4'h4:
                d2 = 4'h8;
            4'h5:
                d2 = 4'h1;
            4'h6:
                d2 = 4'h3;
            4'h7:
                d2 = 4'h5;
            4'h8:
                d2 = 4'h7;
            4'h9:
                d2 = 4'h9;
            default:
                d2 = 4'h0;
        endcase
    else
        d2 = d;
    end
end
```

ADD

REG2,MOD10 K

 

```
// ADD
```

```
assign d3 = {1'b0,s} + {1'b0,d2};
```

```
// REG2 and MOD10
```

```
always_ff @(posedge clk) begin
```

```
  if (rst)
```

```
    s <= 4'h0;
```

```
  else if (button)
```

```
    if (d3 < 10)
```

```
      s <= d3[3:0];
```

```
    else
```

```
      s <= d3[3:0] + 4'd6;
```

```
end
```


```
// K
```

```
assign u = (last == 1'b0) ? d :  
           (s == 4'd0) ? 4'd0 :  
           4'd10 - s;
```

reg or wire in Verilog

1) **always** ...
 a <= **b** & **c**;
 reg **both**

 2) **wire** **both**
assign **a** = **b** & **c**;



SV relaxes variable use

A variable can receive a value from one of these :

- any number of `always/initial`-blocks
- one `always_ff/always_comb`-block
- one continuous assignment
- one module instance

We can skip `wire`

If you don't like `reg`, use `logic` instead

Signed/unsigned

Numbers in verilog (95) are unsigned. If you write

```
assign d3 = s + d2;
```

s and **d2** get zero-extended

```
wire signed [4:0] d3;  
reg signed [3:0] s;  
wire signed [3:0] d2;
```

```
assign d3 = s + d2;
```

s and **d2** get sign-extended

Test bench part 1

```
`include "timescale.v"
```

```
module testbench();
```

```
// Inputs
```

```
    reg clk;
```

```
    reg rst;
```

```
    reg [3:0] kb;
```


```
    reg stb;
```

```
// Outputs
```

```
    wire [3:0] u;
```

```
// Instantiate the UUT
```
 
```
    pnr uut (
        .clk(clk),
        .rst(rst),
        .kb(kb),
        .stb(stb),
        .u(u) );
```



```
SV: pnr uut(.*);
```

Test bench part 2

```
// Initialize Inputs
```

```
initial begin
```

```
    clk = 1'b0;
```

```
    rst = 1'b1;
```

```
    kb = 4'd0;
```

```
    stb = 1'b0;
```

```
    #70 rst = 1'b0;
```

```
    //
```

```
    #30 kb = 4'd8;
```

```
    #40 stb = 1'b1;
```

```
    #30 stb = 1'b0;
```

```
    //
```

```
    #30 kb = 4'd0;
```

```
    #40 stb = 1'b1;
```

```
    #30 stb = 1'b0;
```

```
end
```

```
always #12.5 clk = ~clk; // 40 MHz
```

```
endmodule
```

Blocking vs Non-Blocking

- Blocking assignment (=)
 - Assignments are blocked when executing
 - The statements will be executed in sequence, one after one

```
always_ff @(posedge clk) begin
    B = A;
    C = B;
end
```

- Non-blocking assignment (<=)
 - Assignments are not blocked
 - The statements will be executed concurrently

```
always_ff @(posedge clk) begin
    B <= A;
    C <= B;
end
```

Use <= for sequential logic


Blocking vs Non-Blocking

```
always_comb begin  
    C = A & B;  
    E = C | D;  
end
```

```
always_comb begin  
    C <= A & B;  
    E <= C | D;  
end
```

Same result

Use = for combinatorial logic

 

Verilog constructs for synthesis

Construct type	Keyword	Notes
ports	input, inout, output	
parameters	parameter	
module definition	module	
signals and variables	wire, reg	Vectors are allowed
instantiation	module instances	E.g., mymux m1(out, iO, il, s);
Functions and tasks	function, task	Timing constructs ignored
procedural	always, if, then, else, case	initial is not supported
data flow	assign	Delay information is ignored
loops	for, while, forever	
procedural blocks	begin, end, named blocks, disable	Disabling of named blocks allowed

Operators

Operator Type	Operator Symbol	Operation Performed
Arithmetic	*	Multiply
	/	Division
	+	Add
	-	Subtract
	%	Modulus
	+	Unary plus
	-	Unary minus
Logical	!	Logical negation
	&&	Logical and
		Logical or
Relational	>	Greater than
	<	Less than
	>=	Greater than or equal
	<=	Less than or equal
Equality	==	Equality
	!=	inequality
Reduction	~	Bitwise negation
	~&	nand
		or
	~	nor
	^	xor
	^~	xnor
	~^	xnor
Shift	>>	Right shift
	<<	Left shift
Concatenation	{ }	Concatenation
Conditional	?	conditional

Replication
 {3{a}}
 same as
 {a,a,a}

Parameters

```
module w(x,y);  
input x;  
output y;  
parameter z=16;  
localparam s=3'h1;  
...  
  
endmodule
```

```
w w0(a,b);  
  
w #(8) w1(a,b);  
  
w #(.z(32)) w2(.x(a),.y(b));
```

Constants ...

```
`include "myconstants.v"
```

```
`define PKMC
```

```
`define S0 1'b0
```

```
`define S1 1'b1
```

```
`ifdef PKMC
```



```
...
```

```
`else
```

```
...
```


```
`endif
```

Comment: FSM1

  

```
//NEXT
always_ff @(posedge clk) begin
    if (rst)
        s <= `S0;
    else
        case (s)
            `S0:
                if (x)
                    s <= `S1;
                default:
                    if (x)
                        s <= `S0;
        end
end
```
 
```
//OUT
always_comb begin
    case (s)
        `S0: if (x)
                u = 1'b1;
            else
                u = 1'b0;
        default: if (x)
                u = 1'b0;
            else
                u = 1'b1;
    end
end
```




```

// COMB ☺
always_comb begin
    ns = `S0;    // defaults
    u = 1'b0;
    case (s)
        `S0: if (x) begin
                ns = `S1;
                u = 1'b1;
            end
        default:
            if (~x) begin
                u = 1'b1;
                ns = `S1;
            end
    end
end

```

Comment: FSM2

 

```

// state register
always_ff @(posedge clk) begin
    if (rst)
        s <= `S0;
    else
        s <= ns;
    end
end

```

Good to have

```
typedef logic [3:0] nibble;  
nibble  nibbleA, nibbleB;
```

```
typedef enum {WAIT, LOAD, STORE} state_t;  
state_t state, next_state;
```

```
typedef struct {  
    logic [4:0] alu_ctrl;  
    logic stb,ack;  
    state_t state } control_t;  
control_t control;
```

```
assign control.ack = 1'b0;
```

System tasks

Initialize memory from file

```
module test;
reg [31:0] mem[0:511]; // 512x32 memory
integer i;

initial begin
    $readmemh("init.dat", mem);
    for (i=0; i<512; i=i+1)
        $display("mem %0d: %h", i, mem[i]); // with CR
end

...


endmodule
```

Do you want a nicer test bench?

=> Try a task or two!

my_test_bench
 
```
initial begin  
  uart1.putstr("s 0");  
end
```



Tasks

```
module uart_tasks(input clk, uart_tx,
                  output logic uart_rx);

    initial begin
        uart_rx = 1'b1;
    end

    task getch();
        reg [7:0] char;

        begin
            @(negedge uart_tx);
            #4340;
            #8680;
            for (int i=0; i<8; i++) begin
                char[i] = uart_tx;
                #8680;
            end
            $fwrite(32'h1, "%c", char);
        end
    endtask // getch
```

```
    task putch(input byte char);
        begin
            uart_rx = 1'b0;
            for (int i=0; i<8; i++)
                #8680 uart_rx = char[i];
            #8680 uart_rx = 1'b1;
            #8680;
        end
    endtask // putch


    task putstr(input string str);
        byte ch;
        begin
            for (int i=0; i<str.len; i++)
                begin
                    ch = str[i];
                    if (ch)
                        putch(ch);
                end
            putch(8'h0d);
        end
    endtask // putstr

endmodule // uart_tb
```

In the testbench

```
wire tx,rx;  
...  
// send a command  
initial begin  
    #100000 // wait 100 us  
    uart1.putstr("s 0");  
end  
  
// instantiate the test UART  
uart_tasks uart1(.*);  
  
// instantiate the computer  
computer computer1(.*);
```


Lab 0 : Build a UART in Verilog

 

clk = 40 MHz

baud rate = 115200

full duplex

 

UCF = User constraint file

```
CONFIG PART = XC2V4000-FF1152-4 ;
```

```
NET "clk" LOC = "AK19";
```

```
# SWx buttons
```

```
NET "stb" LOC = "B3" ;
```

```
NET "rst" LOC = "C2" ;
```

```
# LEDs
```

```
NET "u<0>" LOC = "N9"; //leftmost
```

```
NET "u<1>" LOC = "P8";
```

```
NET "u<2>" LOC = "N8";
```

```
NET "u<3>" LOC = "N7";
```

```
...
```

```
# DIP switches
```

```
NET "kb<0>" LOC = "AL3"; //leftmost
```

```
NET "kb<1>" LOC = "AK3";
```

```
NET "kb<2>" LOC = "AJ5";
```

```
NET "kb<3>" LOC = "AH6";
```

```
...
```

Lab0: Testbench


 
 


Figure 2.1: The letter A (0x41). Time per bit is $8.68 \mu\text{s}$.

Arrays-packed/unpacked

```
wire [31:0] bus;           // a packed array
reg [3:0][7:0] mem;        // so is this
                           // both are contiguous
```
 
```
assign bus = mem;
assign bus[31:16] = mem[3:2];
```



Arrays-packed/unpacked

```
wire [31:0] bus;  
reg [7:0] mem [0:3];  // 4 bytes  
...  
assign bus[31:24] = mem[3];
```

