

Lecture 8


- A memory controller
- Lab4 – a special instruction

PKMC

Wishbone bus

Memory bus



 

AVNET
electronics marketing
DESIGN SERVICES

VE1428C4
DP83861VOM-3
5

Pulse
H5007
0323-J CHINA

SDRAM

U3
49LC16M82
TC
75 C

EM34A8
LP3966ES
-1.8

Intel
E28F640
13A120
A2467320C
©1999

Intel
E28F640
13A120
A2467320C
©1999


FLASH

SRAM

SDRAM

13445-0148


305 3303
94V-8
2 ET

 



SRAM

Static RAM

 
- Asynchronous device
- Memory element: Latch
- $2 \times (256k \times 16) = 1MB$




SRAM - Cell

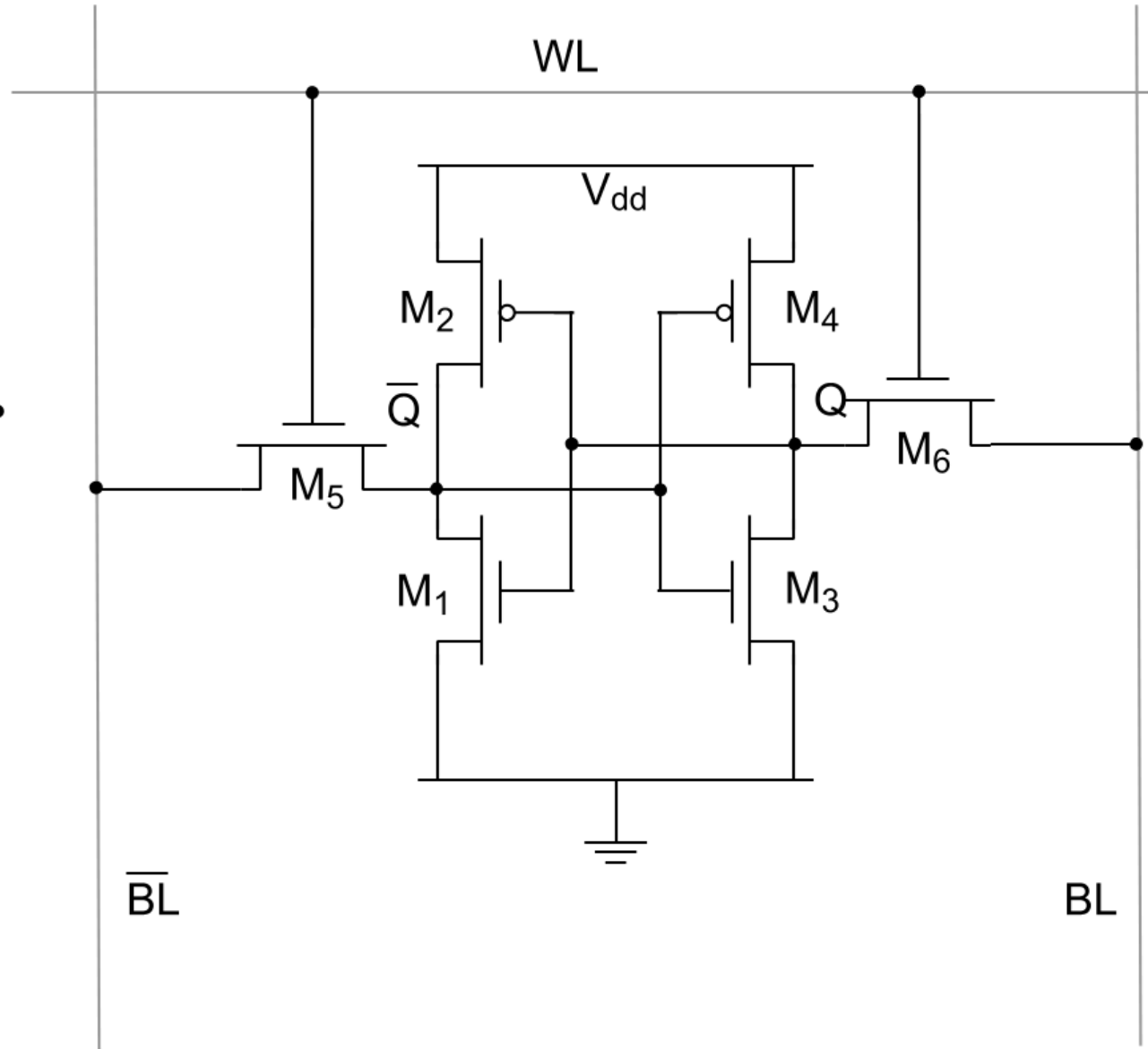 


SRAM - Read

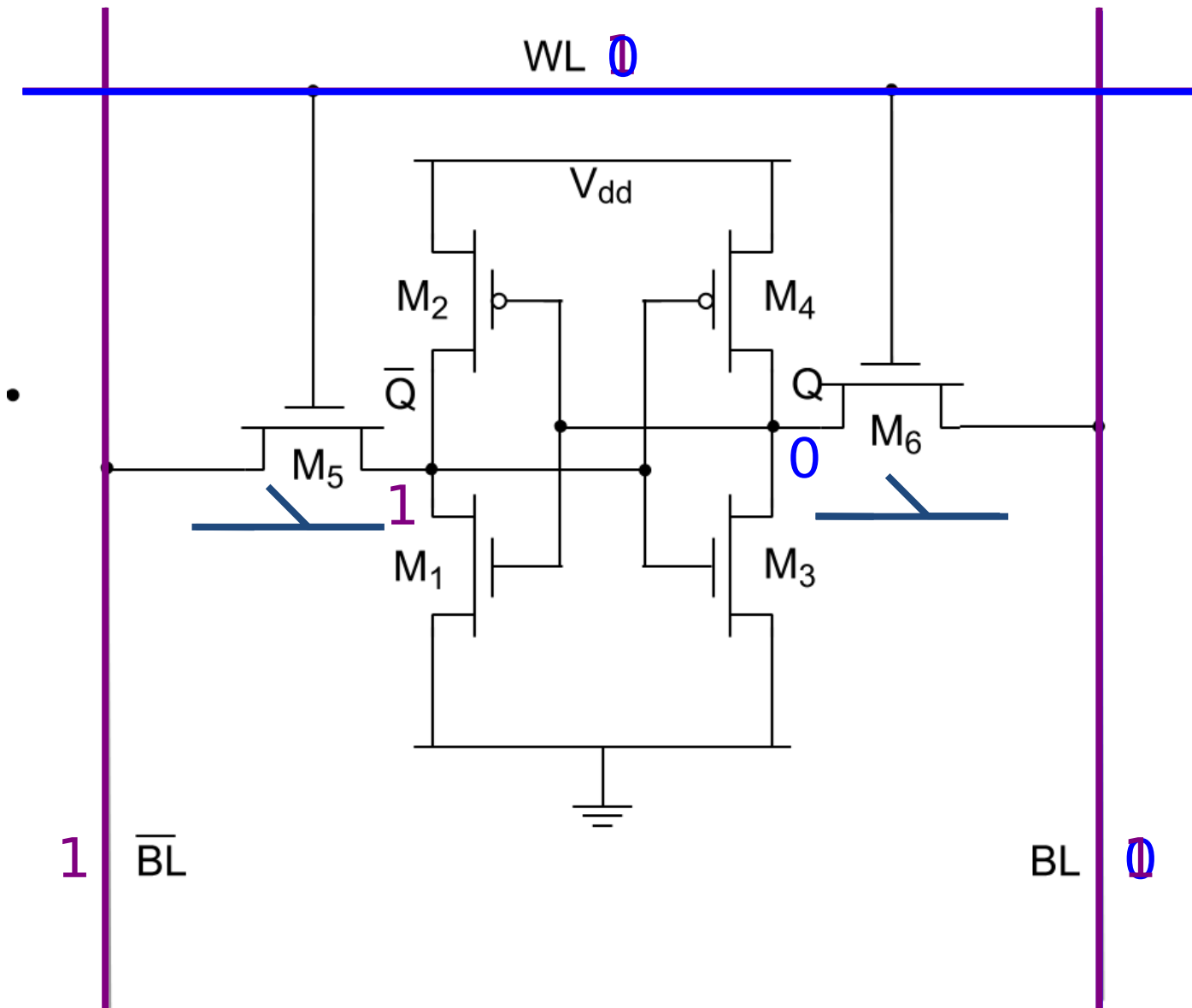


SRAM - Read

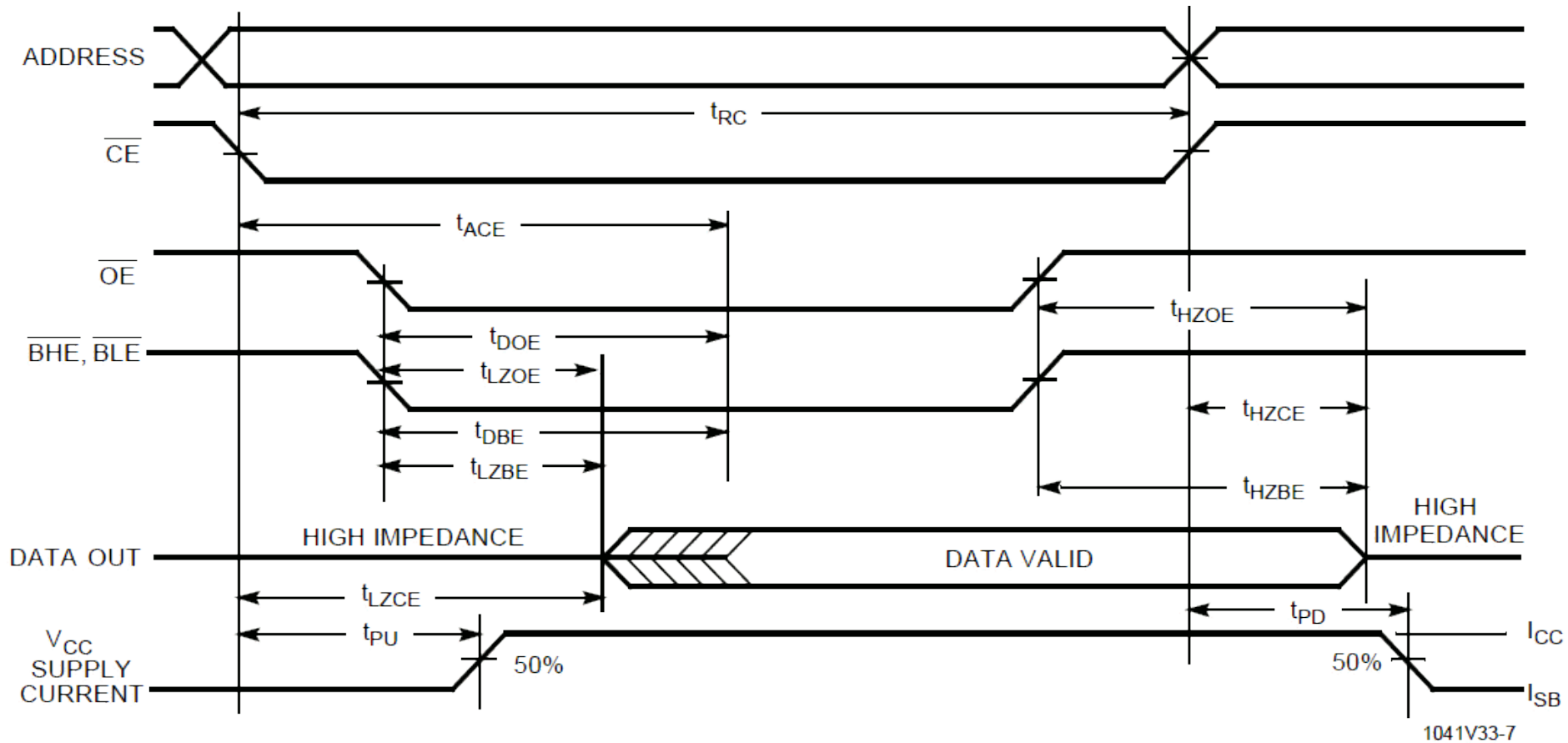

SRAM - Write

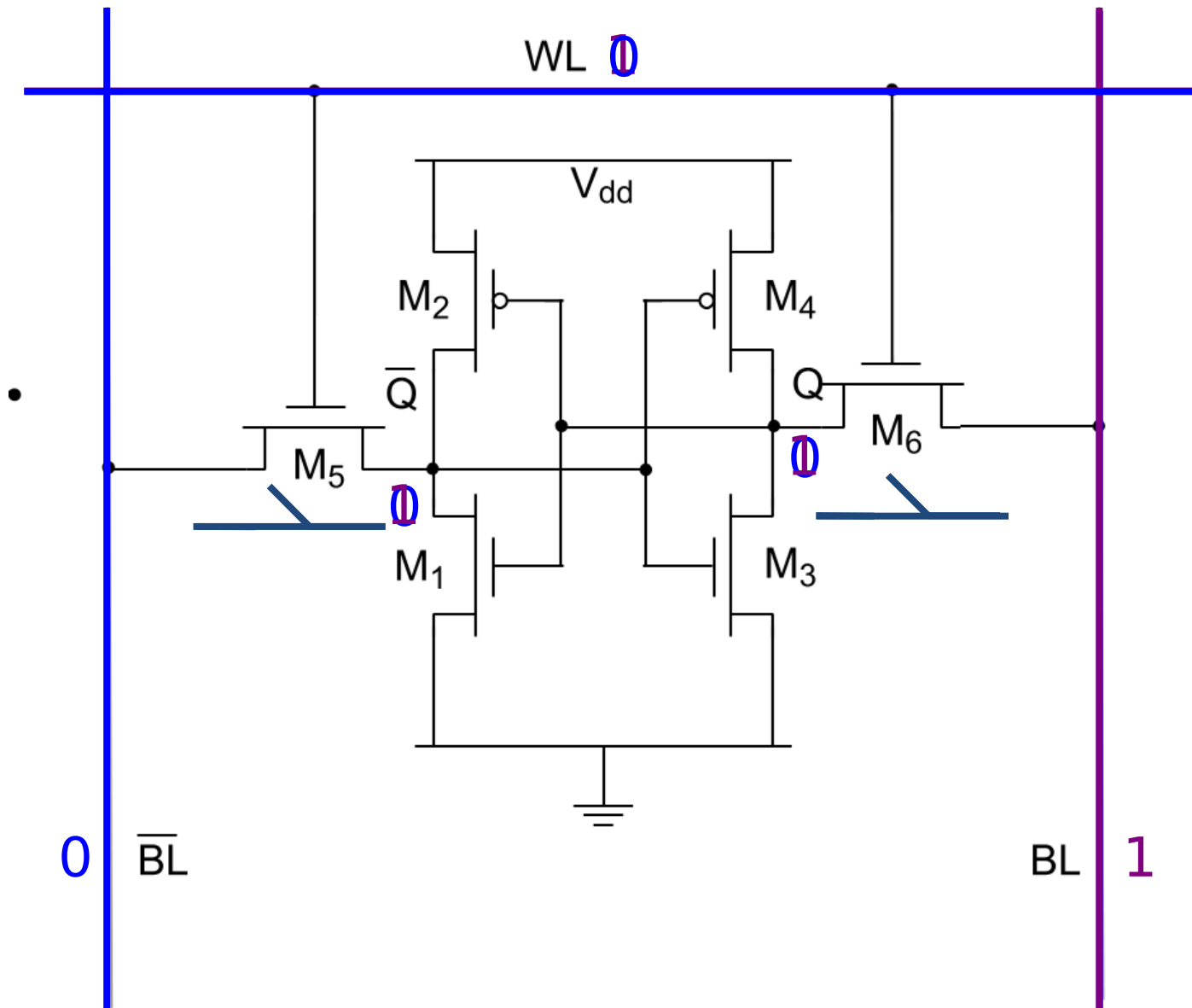

SRAM - Write

 


1041

SDRAM

Synchronous Dynamic RAM

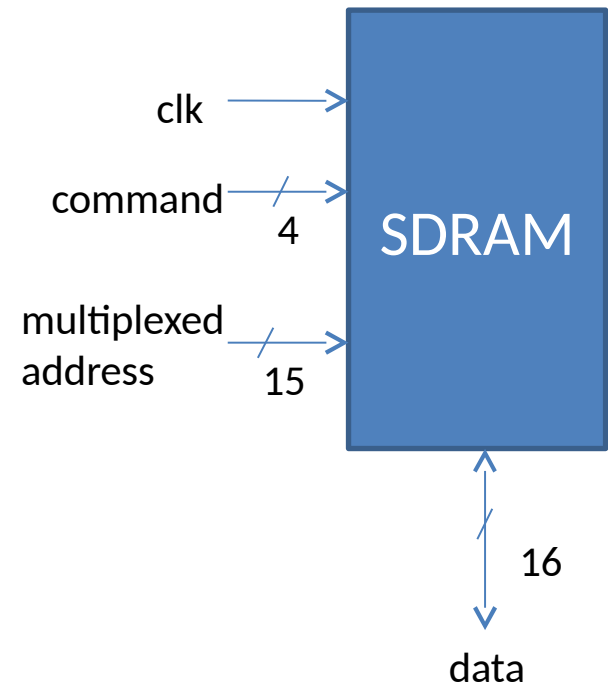- Clocked device
- Memory element: Capacitance
- Needs periodic refreshing
- Pipelined operation
- Burst oriented
 - Single burst in our design
- $2 \times (16\text{M} \times 16) = 64\text{MB}$




SDRAM

Sketchy read cycle

1. Precharge bit line to $V/2$
2. Let bit line float
3. Connect sense amp to bit line
4. Connect C to bit line
5. Hold value in latch
6. Write value back to C

Refresh cycle

Dummy read cycle

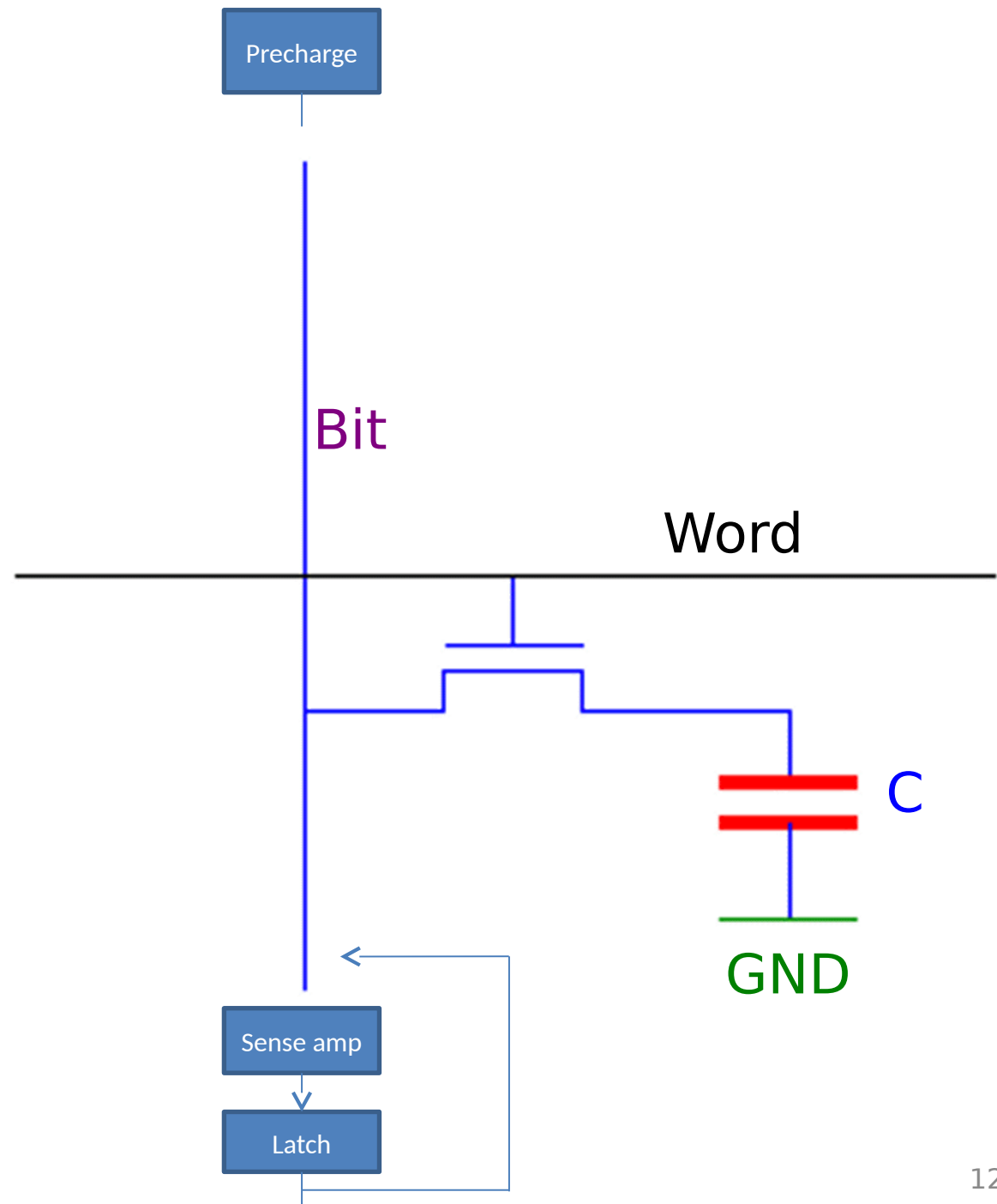


SDRAM Architecture


32 MB = 16 MW per chip, address bits = 24 =

13+11


burst oriented

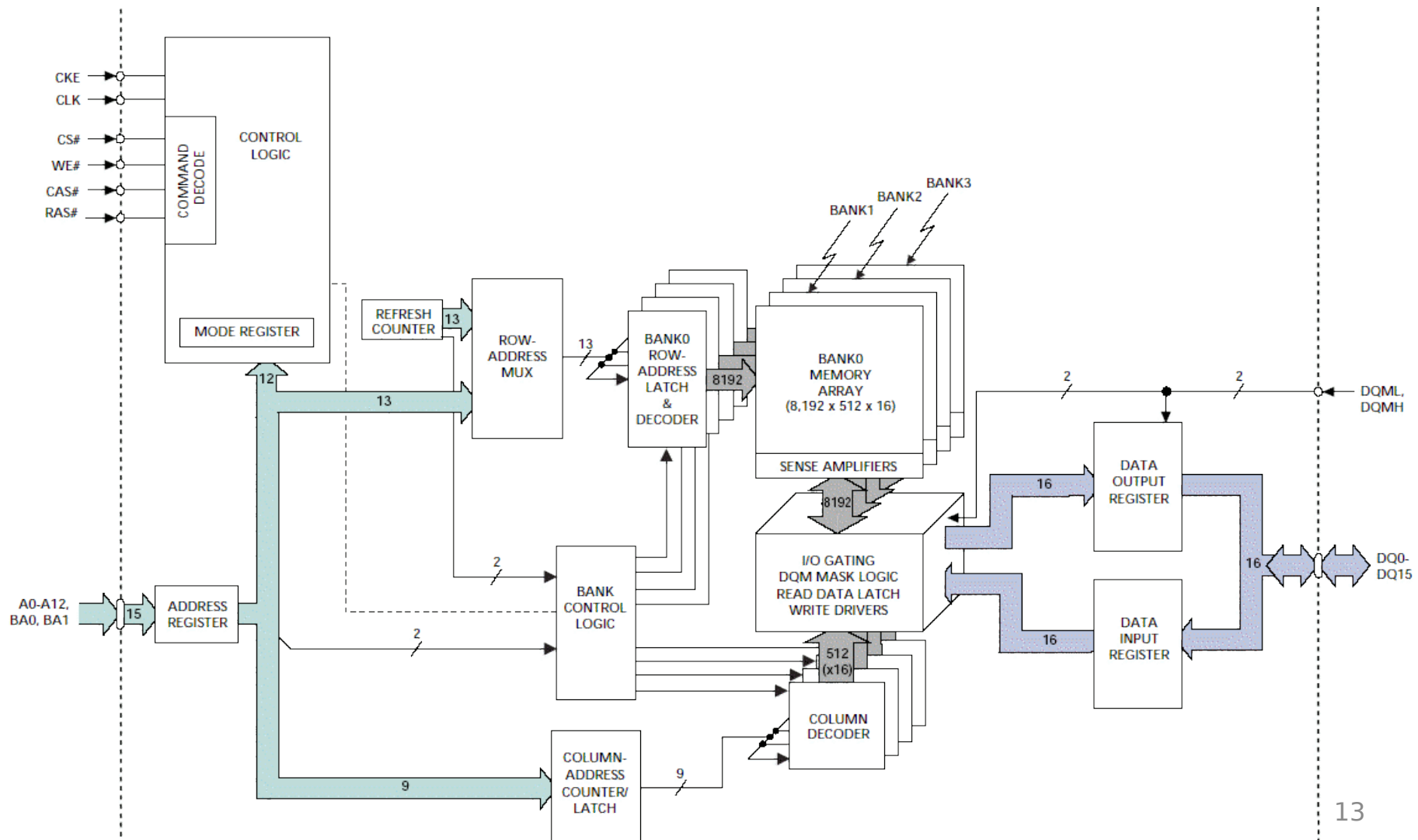

SDRAM Read

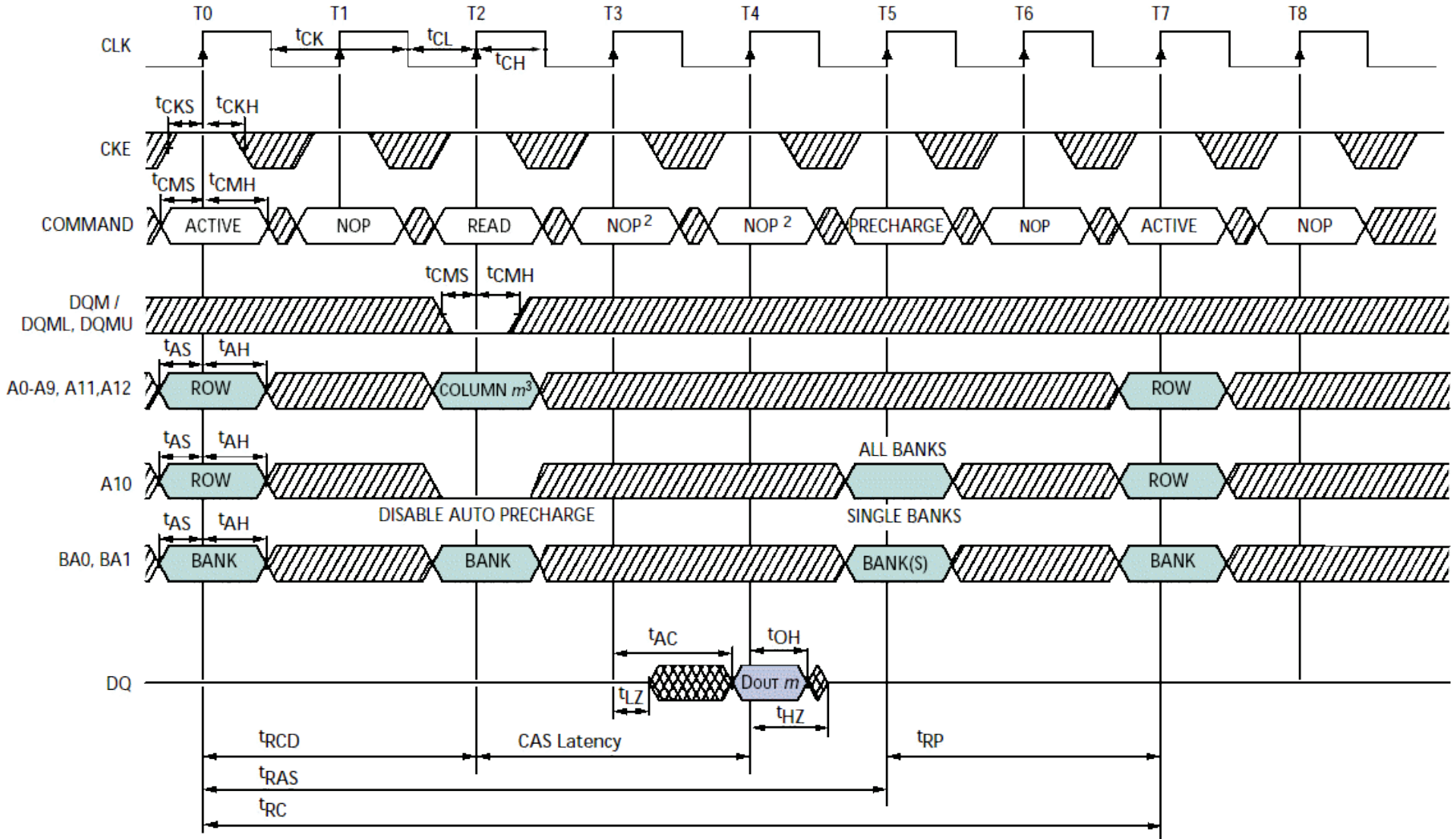


SDRAM Write

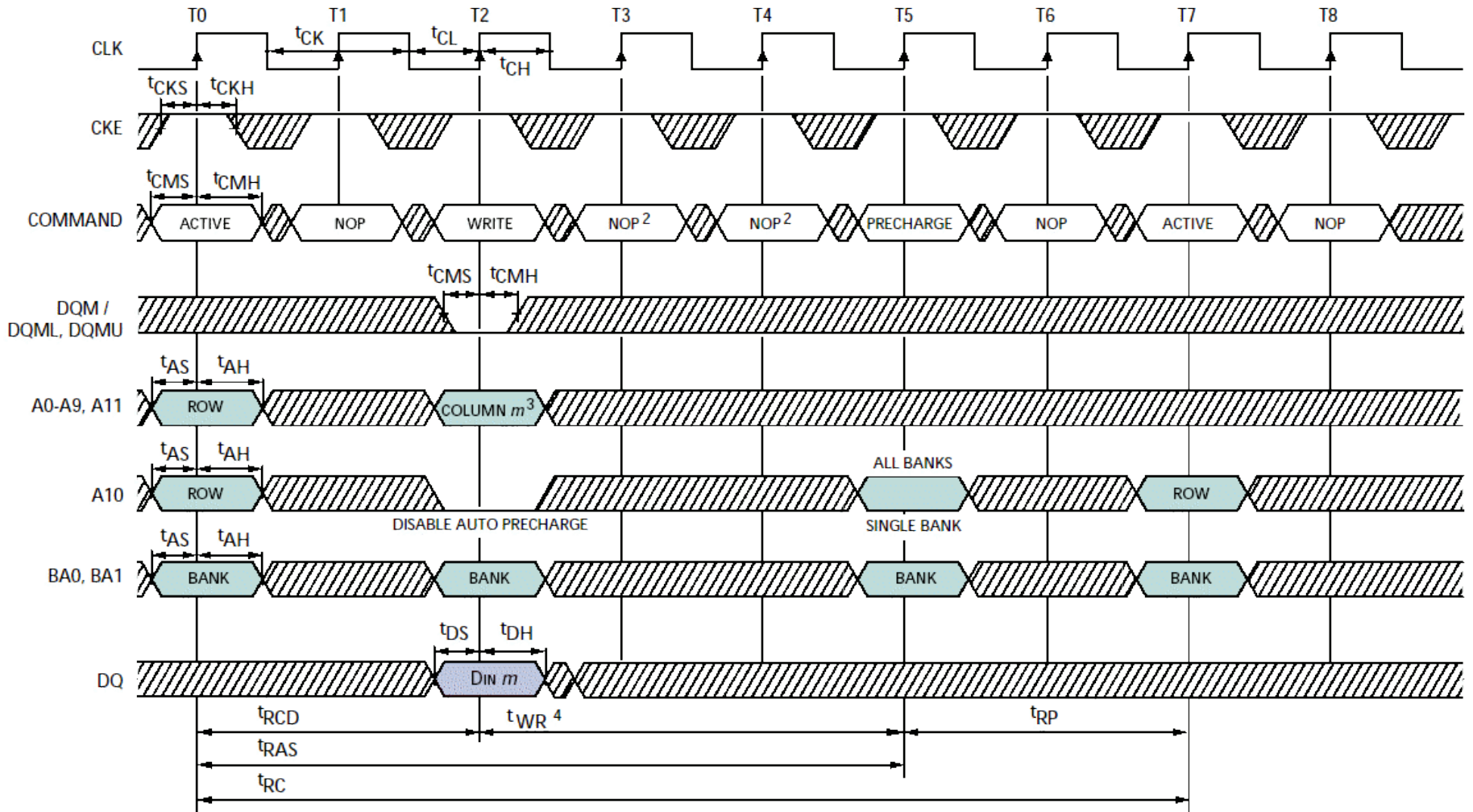

Consecutive read bursts


Mode register must be programmed

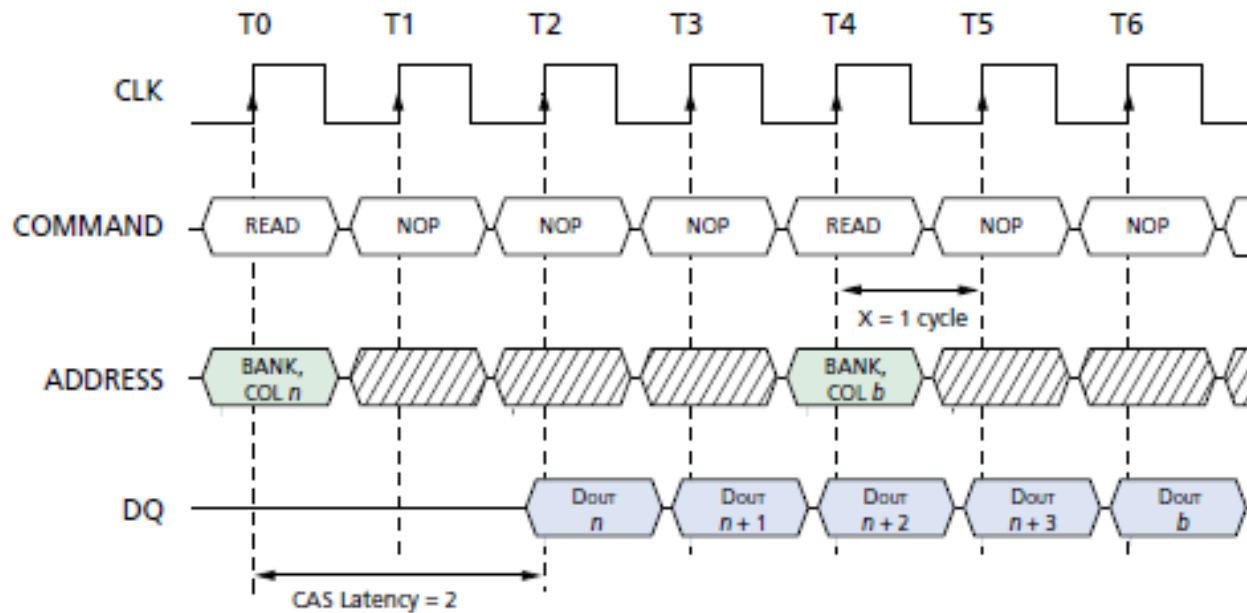

FLASH - Interface



- Looks like SRAM
 - Read
 - Write commands
- Erase is done in blocks
- Contains uCLinux kernel +file system

FLASH - Cell

 


FLASH - Read (NOR)


1

 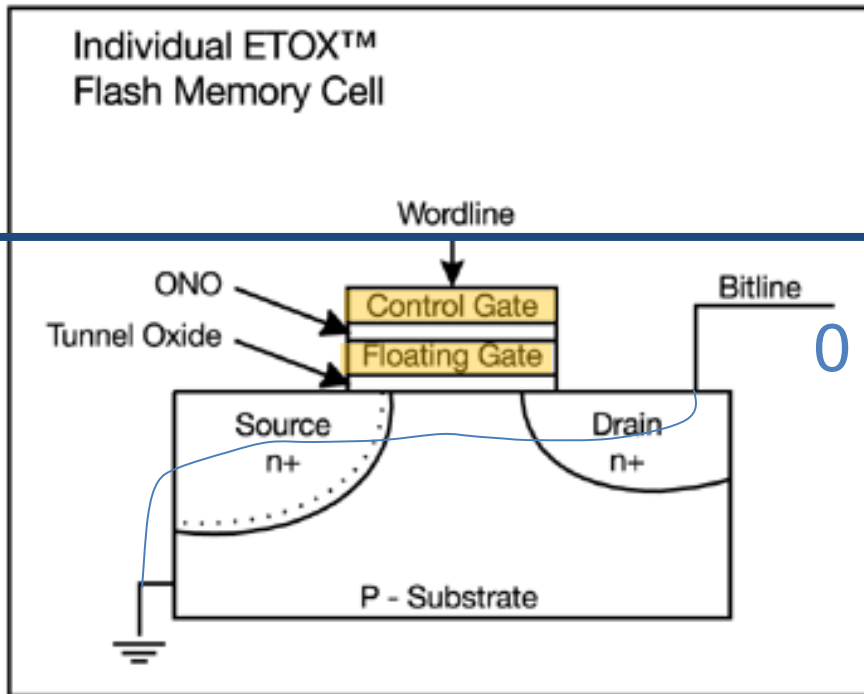


FLASH – Program (to 0)

 


FLASH - Erase (to 1) only blockwise

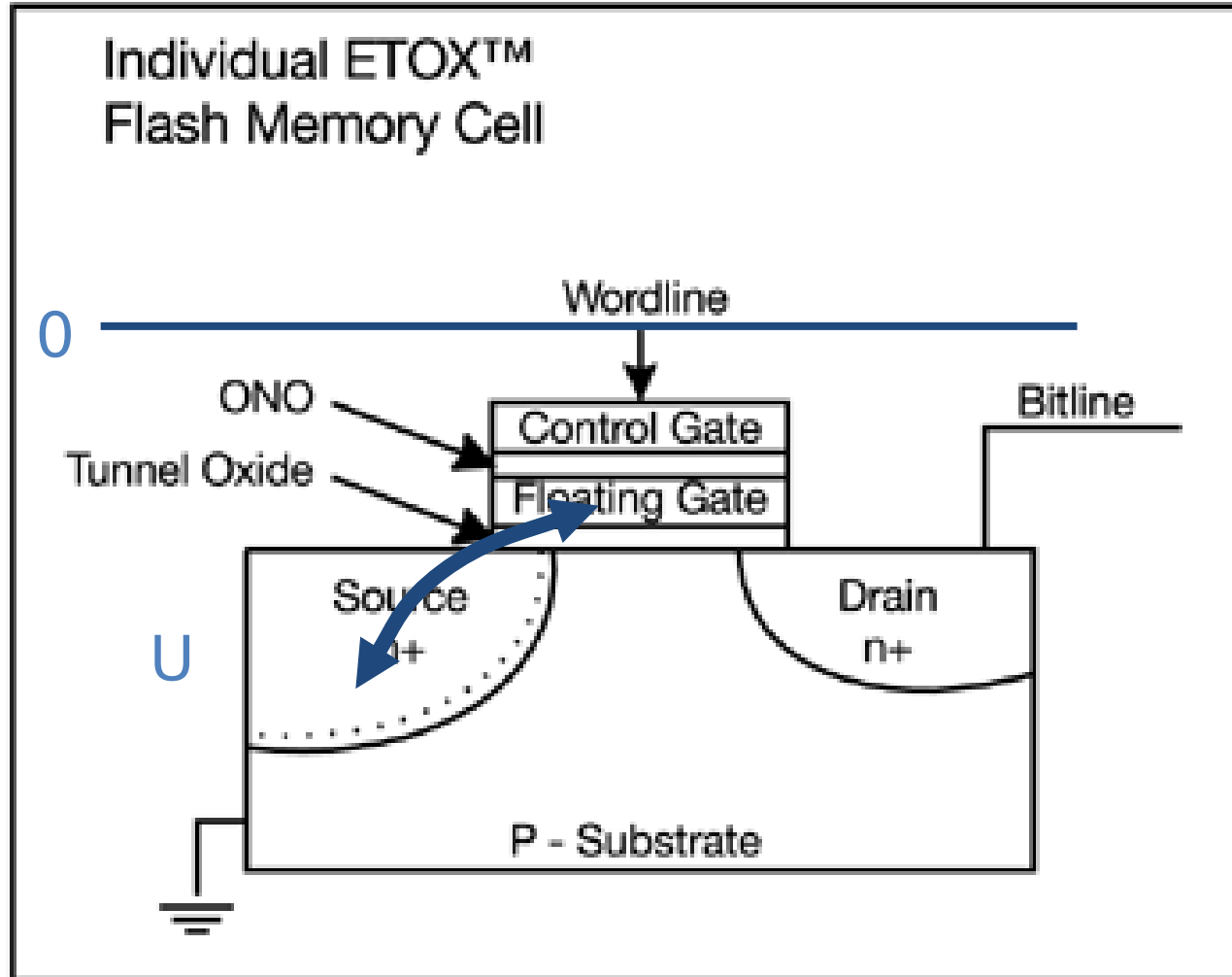


System Overview

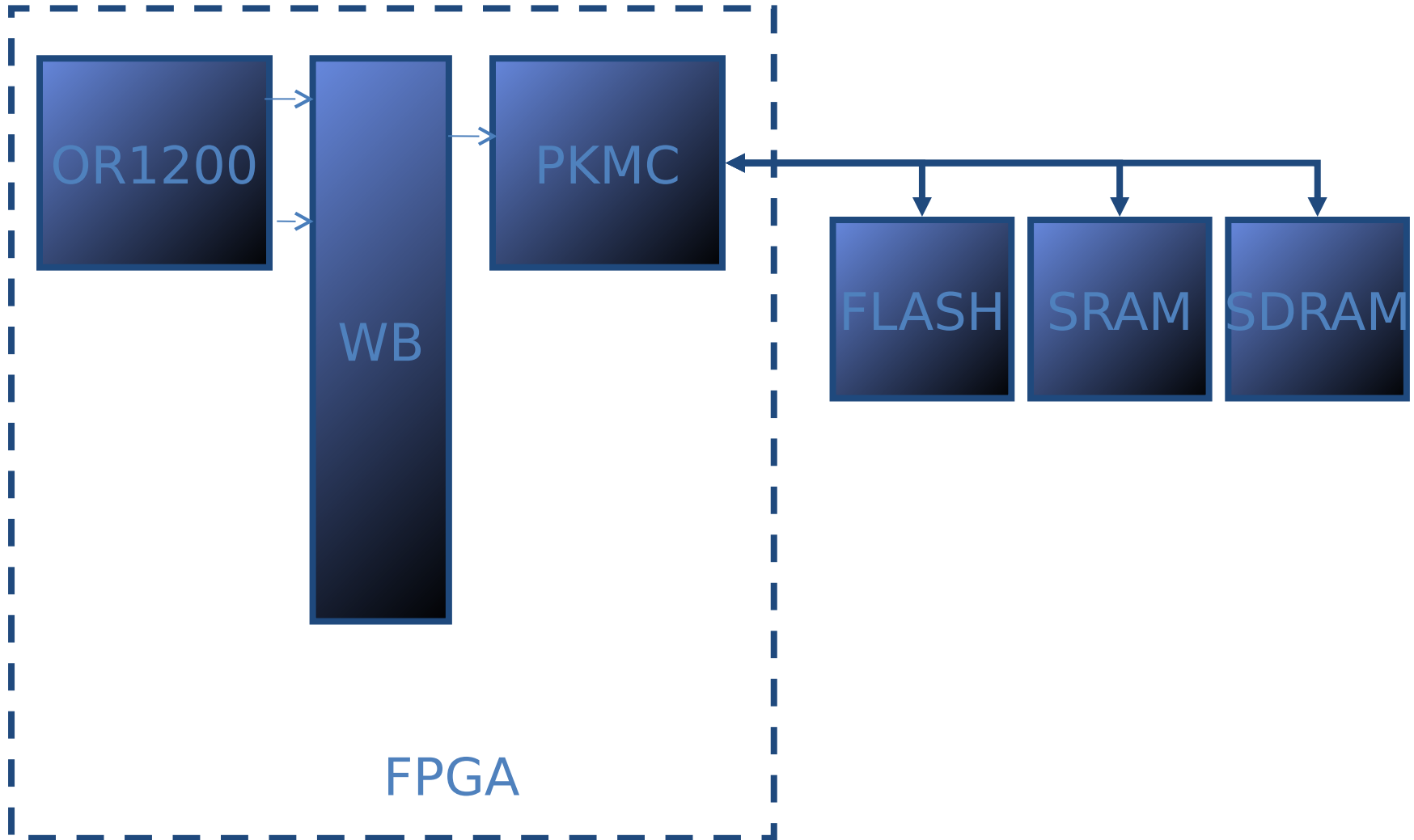

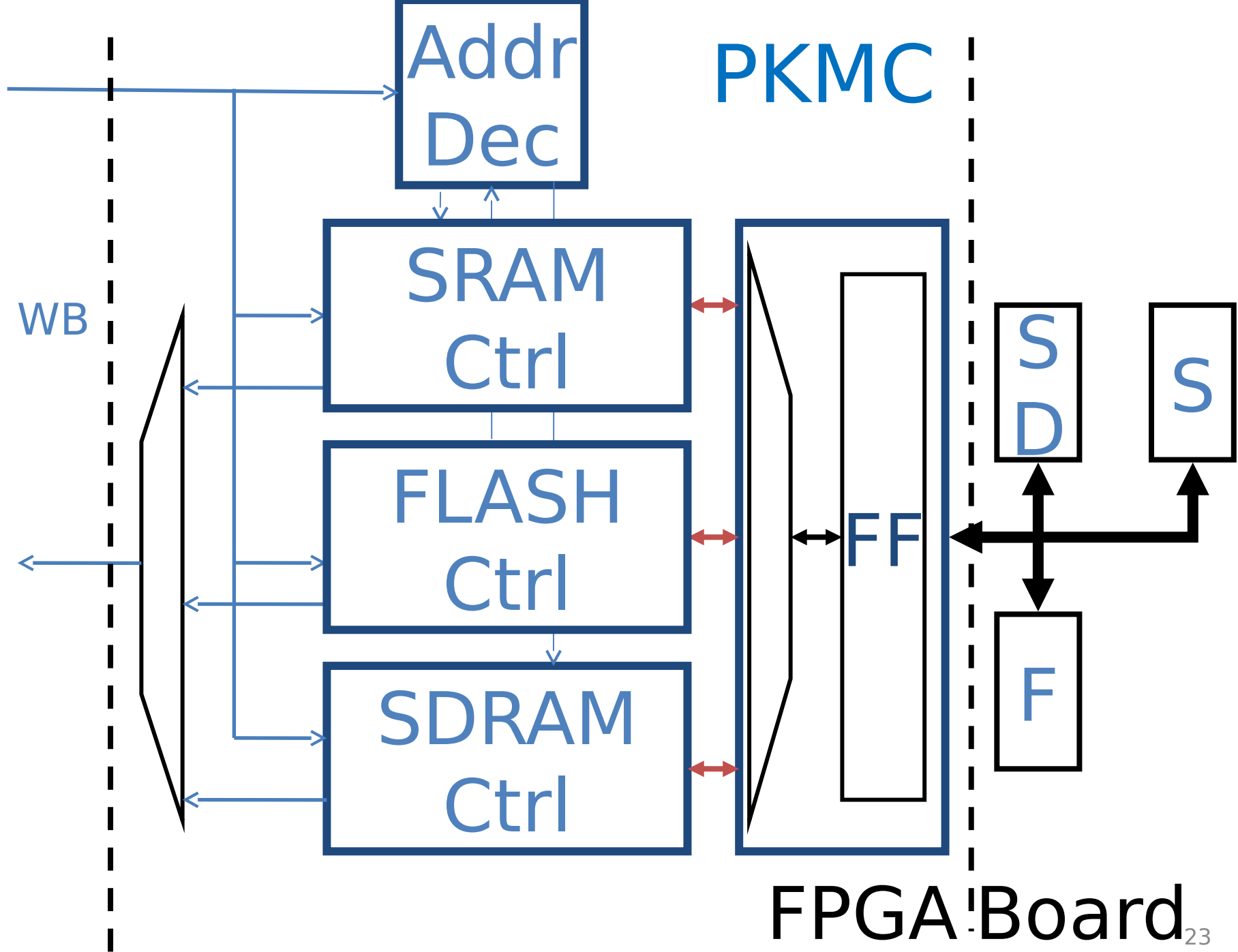


SDRAM Controller Internals

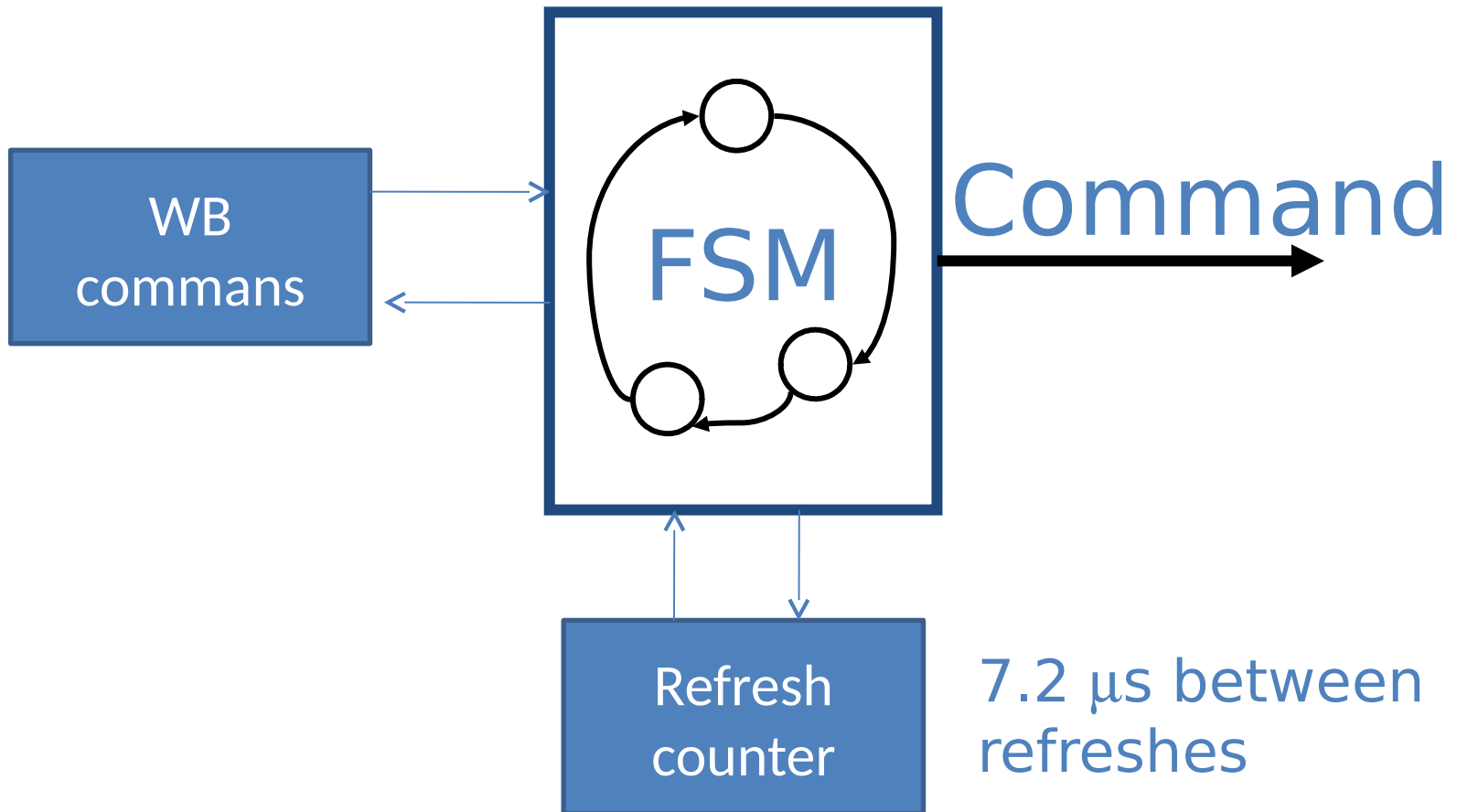

Refresh cycle

Start of refresh cycle

 

Start of WB cycle

Lab 4

Custom Instruction

Huffman Encoding/Decoding

1) After Q

$$\begin{bmatrix} 22 & 12 & 0 & -12 & 0 & 0 & 0 & 0 \\ 0 & 0 & -8 & 0 & 0 & 0 & 0 & 0 \\ 4 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix}$$

2) After zig-zag

```

22
12
0 4
0 0 -12
-8
00000000000000000000
00000000000000000000
000000000000000001
    
```

3) After RLE

value raw bits

```

05 10110
04 1100
13 100
24 0011
04 0111
F0
F0
D1 1
00
    
```



4) After Huffman


The values (bytes) are encoded by table lookup

Huffman in JFIF

- Output: 1 – 16 bits
- Encodes bytes
- 2 tables used
 - Y DC
 - Y AC

jpegfiles

jpegtest.c, jcdctmgr.c, jdct.c, jchuff.c

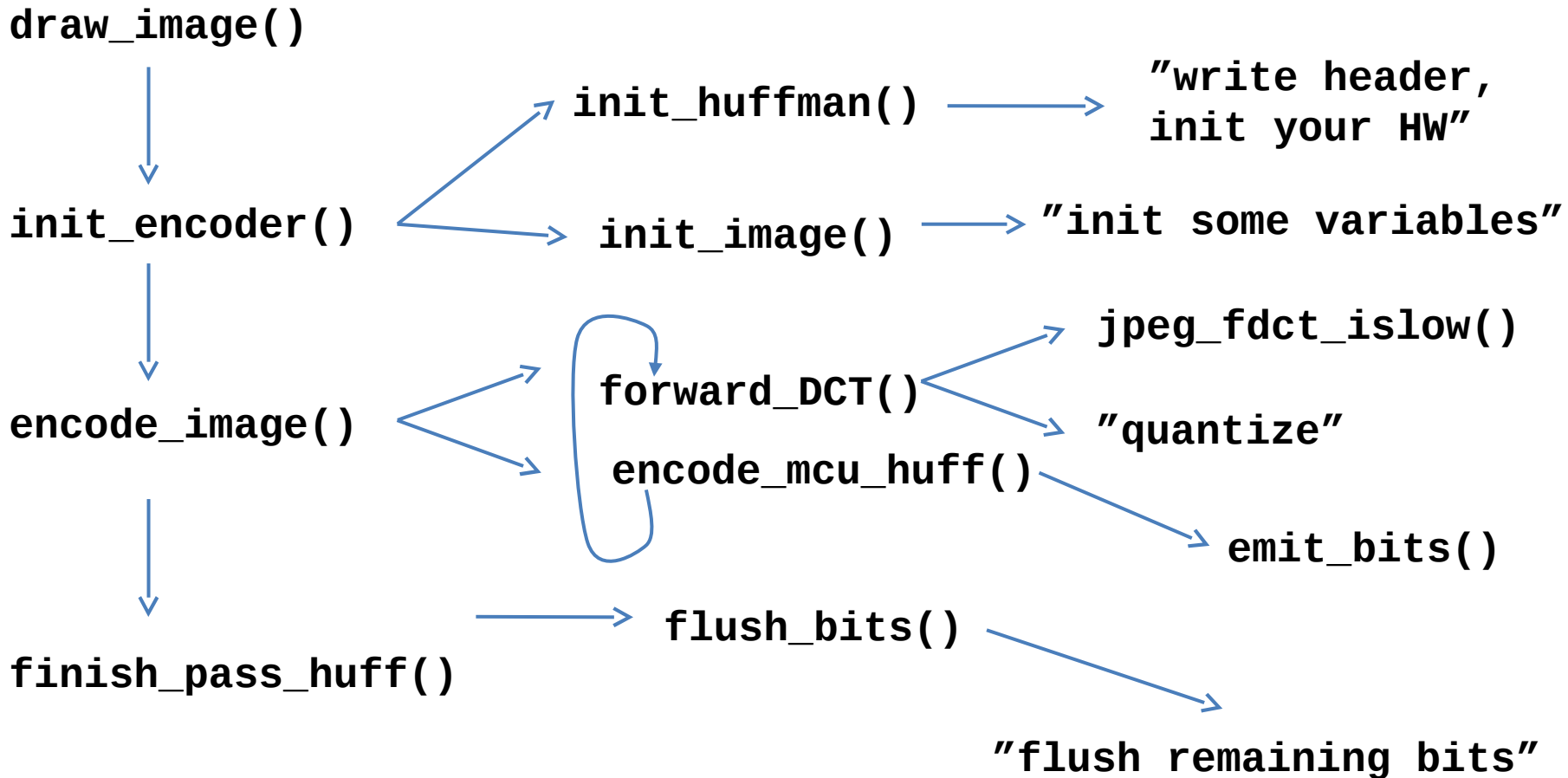

Emit_bits()

```
/* Only the right 24 bits of put_buffer are used; the valid bits are
 * left-justified in this part. At most 16 bits can be passed to emit_bits
 * in one call, and we never retain more than 7 bits in put_buffer
 * between calls, so 24 bits are sufficient.
 */
static void emit_bits (unsigned int code, int size)
{
    unsigned int startcycle;

    new_put_buffer = (int) code;

    // Add new bits to old bits. If at least 8 bits then write a char to buffer,
    // save the rest until we get more bits.


    new_put_buffer &= (1<<size) - 1;          /* mask off any extra bits in code */
    current_buffer_bit += size;              /* new number of bits in buffer */
    new_put_buffer = new_put_buffer << (24 - current_buffer_bit); /* align incoming bits */
    new_put_buffer = new_put_buffer | old_put_buffer; /* and merge with old buffer contents */

    while (current_buffer_bit >= 8) {
        int c = ((new_put_buffer >> 16) & 0xFF); // Mask out the 8 bits we want
        buffer[next_buffer] = (char) c;
        next_buffer++;
        if (c == 0xFF) { // 0xFF is a reserved code for tags, if we get image data
            buffer[next_buffer] = 0x00; // with an FF value it has to be followed by 0x00.
            next_buffer++;
        }
        new_put_buffer <<= 8;
        current_buffer_bit -= 8;
    }
    old_put_buffer = new_put_buffer; /* update state variables */
}
```

Emit_bits()

old_put_buffer

current_buffer_bit=7

 

code



size=16

new_put_buffer

current_buffer_bit=23



Write bytes to mem

old_put_buffer

current_buffer_bit=7



Adding an Instruction

1. Instruction Selection
2. Hardware modification
3. Assembler modification
4. Compiler modification


Instruction Selection

- **l.custx**
 - No operands
- Instructions for 64 bit
 - Not used
 - Assembler can understand
 - **l.sd I(rA), rB**

Hardware Modifications

- Instruction decoder modifications
 - Legal instruction
 - or1200_ctrl.v
- Special purpose register
 - New group
 - or1200_sprs.v
- Data path
 - New hardware
 - or1200_lsu.v
 - or1200_vlx_top.v

or1200 Pipeline

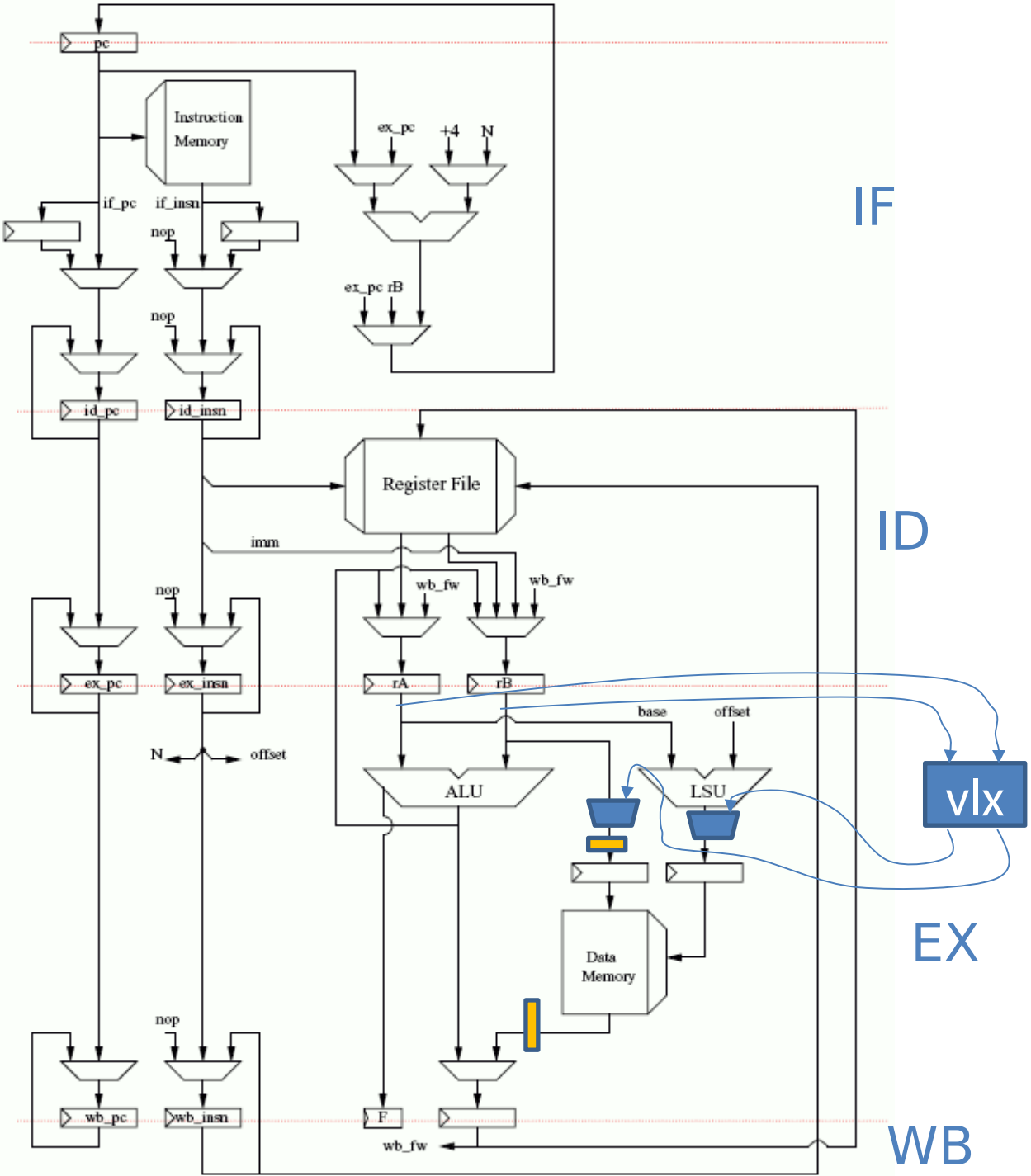

code size
 ↓
 1.sd (rA), rB

vlx


align

or1200 Pipeline

- Remember stall


	1	2	3	4	5	6	7
IF	ld	add	sub	-			
ID/RR		ld	add	-	sub		
EX/M			ld	ld	add	sub	
W				-	ld	add	sub

Align reg2mem

 

Proposed Architecture

 internal regs
(mapped as SPR)
bit_reg
bit_reg_wr_pos
vix_addr_o



Inline asm


In jpegfiles insert:

template
↓
`asm volatile("l.sd 0x0(%0),%1" : : "r"(code), "r"(size));`
↓ ↓
input input

=> code and size will show up at your vlx

Data Path

 - Fill buffer
 - One bit / clock cycle
 - All bits at once
- Write to mem
 - One byte
 - One 32 bit word, must be on word boundaries



Control

- May not be needed
- May be an FSM

Store Unit

- Stores the data
- 0xFF stored as 0xFF00
 - Jpeg markers
- Only byte alignment!
 - Parallel stores faster

Software

- New Assembler
 - Easy
- New Compiler
 - Hard problem for complex instructions
 - Compiler knows functions
- C
 - Inline Assembler

Instruction Usage

```
unsigned char* sb_get_buff_pos(void)
{
    unsigned char* pos;
    asm volatile("l.mfspr %0,%1,0x2" : "=r"(pos) : "r"(0xc000));
    return pos;
}
```

output

00000250 <_sb_get_buff_pos>:

```
250: 9c 21 ff fc  l.addi r1,r1,0xfffffffffc
254: d4 01 10 00  l.sw 0x0(r1),r2
258: 9c 41 00 04  l.addi r2,r1,0x4
25c: a9 60 c0 00  l.ori r11,r0,0xc000
260: b5 6b 00 02  l.mfspr r11,r11,0x2
264: 84 41 00 00  l.lwz r2,0x0(r1)
268: 44 00 48 00  l.jr r9
26c: 9c 21 00 04  l.addi r1,r1,0x4
```